



SOLUTION

Exercise for Chapter 4_1

- 1) $C_0 = 2 \text{ pF}$
- 2) The simplest configuration is a bridge using the cap inside the equipment and two other similar resistors.
- 3) $S = 25 \text{ mV}/\mu\text{m}$
- 4) The required gain is $G = 20$

$$V_0 = \left(1 + \frac{R_1}{R_2} + 2 \frac{R_1}{R_g} \right) (V_2 - V_1) + V_{ref}$$

$$R_1 = R_2 = 9 \text{ k}\Omega$$

$$R_g = 1 \text{ k}\Omega$$

$$V_{ref} = V_g$$