



SOLUTION

Exercise for Chapter 4_2

- 1) $V_m = \pm 40 \text{ mV}$
- 2) Circuit analysis using superposition
- 3)

$$V_0 = -\frac{R_{12}}{R_{11}} \left(1 + 2 \frac{R_5}{R_3} \right) \left(1 + \frac{2R_6}{R_7} \right) \frac{V_m}{2}$$

$$R_{12} = 69.1 \text{ k}\Omega$$