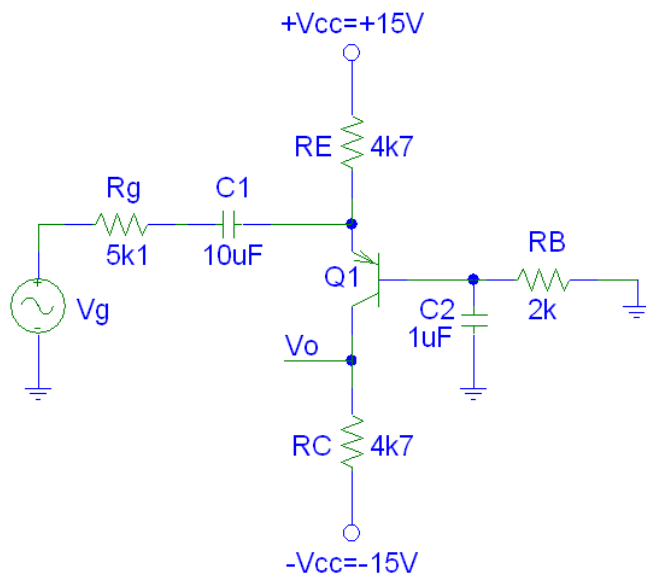




Time: 1 hour and 30 minutes

EXERCISE 1

Figure 1 shows a bias circuit of a BJT transistor used as a common base amplifier.



DATA:

$|V_{BE}| = 0.7 \text{ V}$
 $|V_{CE-sat}| = 0.2 \text{ V}$
 $\beta_F = \beta_0 = 300$
 $r_0 \rightarrow \infty$
 $V_T = 25 \text{ mV}$

$R_B = 2 \text{ K}\Omega$
 $R_E = R_C = 4.7 \text{ K}\Omega$
 $R_g = 5.1 \text{ K}\Omega$
 $C_1 = 10 \text{ }\mu\text{F}$
 $C_2 = 1 \text{ }\mu\text{F}$

Figure 1

a) Obtain V_B , V_E e I_E (consider negligible I_B). Show that the approximation is right.



b) Calculate the bias point (I_{CQ} , V_{ECQ}). Which is the operating region? Justify the answer.

c) Draw the small-signal equivalent circuit valid for midrange frequency and calculate the small signal parameters of the BJT (g_m and r_π).

d) Draw the small-signal equivalent circuit valid for the low-frequency range.

EXERCISE 2

Figure 2 shows a transconductance amplifier with an accumulation N-channel MOSFET transistor (NMOS).

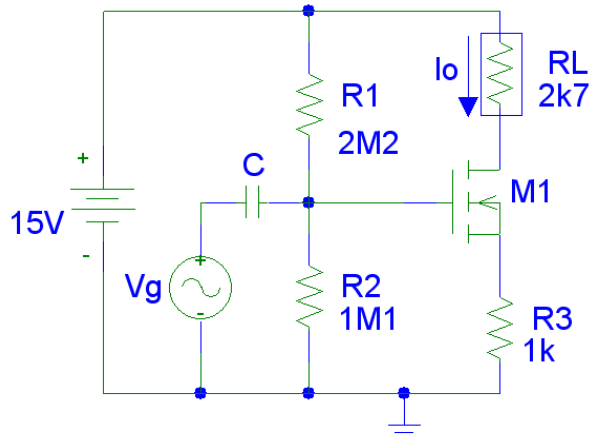


Figure 2

DATA:

MOSFET Transistor

$$V_t = 1 \text{ V}$$

$$K = 0.5 \text{ mA/V}^2$$

NOTA: $I_D = K \cdot (V_{GS} - V_t)^2$

$$V_A = 100 \text{ V}$$

$$C \rightarrow \infty$$

a) Calculate the DC load current (I_D).

b) Which is the operating region? Justify the answer. Plot the output characteristic of the transistor and the load line.



- c) Calculate the small-signal parameters, draw the small signal equivalent circuit for midrange frequency and obtain the transconductance gain i_o/v_g .

- d) Draw the small-signal equivalent circuit valid for the high-frequency range



EXERCISE 3

The circuit of Figure 3 is an AC coupled amplifier based on a JFET transistor.

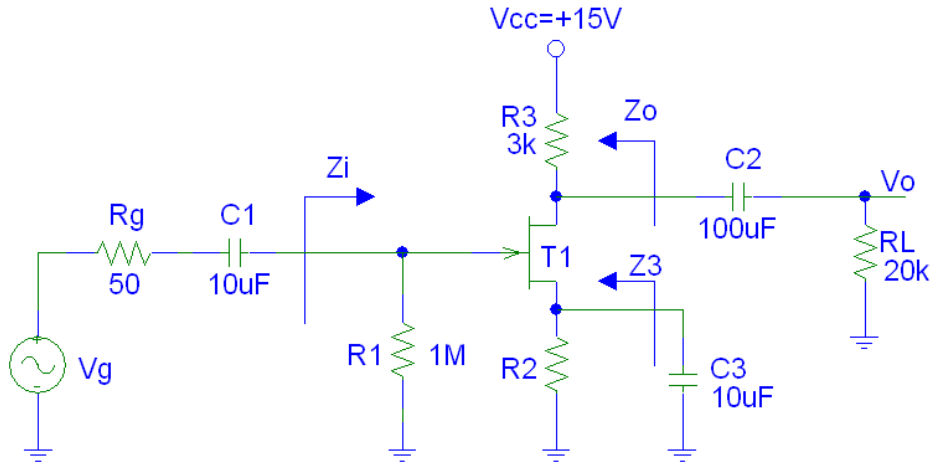


Figure 3

DATA:

| | | | | |
|---------------------------|---------------------------|-----------------------------|--|----------------------------|
| $I_{DQ} = 2.5 \text{ mA}$ | $R_g = 50 \ \Omega$ | $R_1 = 1 \text{ M}\Omega$ | $R_3 = 3 \text{ K}\Omega$ | $R_L = 20 \text{ K}\Omega$ |
| $I_{DSS} = 10 \text{ mA}$ | $V_p = -3 \text{ V}$ | $r_{ds} \rightarrow \infty$ | $I_D = I_{DSS} \cdot (1 - V_{GS}/V_p)^2$ | |
| $C_1 = 10 \ \mu\text{F}$ | $C_2 = 100 \ \mu\text{F}$ | $C_3 = 10 \ \mu\text{F}$ | $C_{gs} = 2 \text{ pF}$ | $C_{gd} = 1 \text{ pF}$ |

- a) Calculate R_2 for a bias current $I_{DQ} = 2.5 \text{ mA}$. Calculate the small-signal parameter g_m .



b) Draw the small-signal equivalent circuit valid for midrange.

c) Obtain the gain V_o/V_g and the impedances Z_i and Z_o .

d) Calculate the impedance Z_3 that is in parallel with C_3 .



EXERCISE 4

The circuit of Figure 4 is a DC coupled multi-stage amplifier.

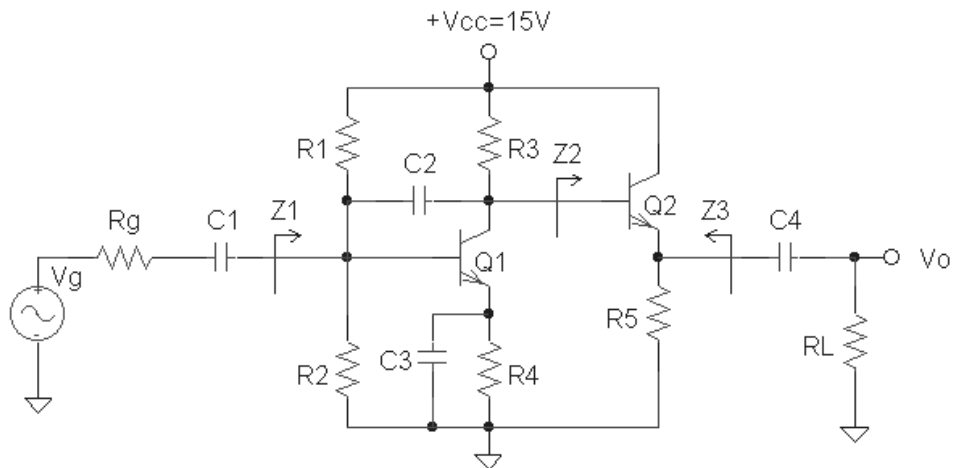


Figure 4

DATA:

$R_g = 5 \text{ K}\Omega$ $C_1, C_3 \rightarrow \infty$ $C_2 = 2.5 \text{ pF}$ $C_4 = 20 \text{ }\mu\text{F}$
 $R_1 = 30 \text{ K}\Omega$ $R_2 = 15 \text{ K}\Omega$ $R_3 = 10 \text{ K}\Omega$ $R_4 = 8.8 \text{ K}\Omega$ $R_5 = R_L = 4.7 \text{ K}\Omega$
 $V_{BE} = 0.6 \text{ V}$ $V_T = 25 \text{ mV}$ $\beta = 200$ $C_{\mu_1} = 0.5 \text{ pF}$ $C_{\pi_1} = C_{\pi_2} = C_{\mu_2} = 0 \text{ pF}$

a) Obtain the bias point of both transistors (I_{C1} , I_{C2} , V_{CE1} , V_{CE2}) and V_o DC value.



b) Draw the small-signal equivalent circuit for midrange frequency. Obtain the impedances Z_1 , Z_2 and Z_3 .

c) Calculate the low cut-off frequency. Use the time constants method.



d) Calculate the high cut-off frequency. Explain each and any approximation.

e) Obtain the Bode plot approximately (amplitude and phase).
Midrange frequency gain (40 dB, -180°).