
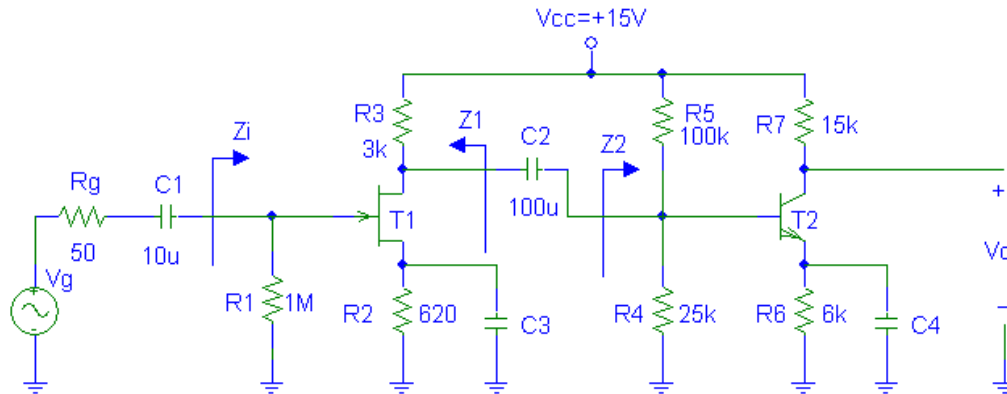


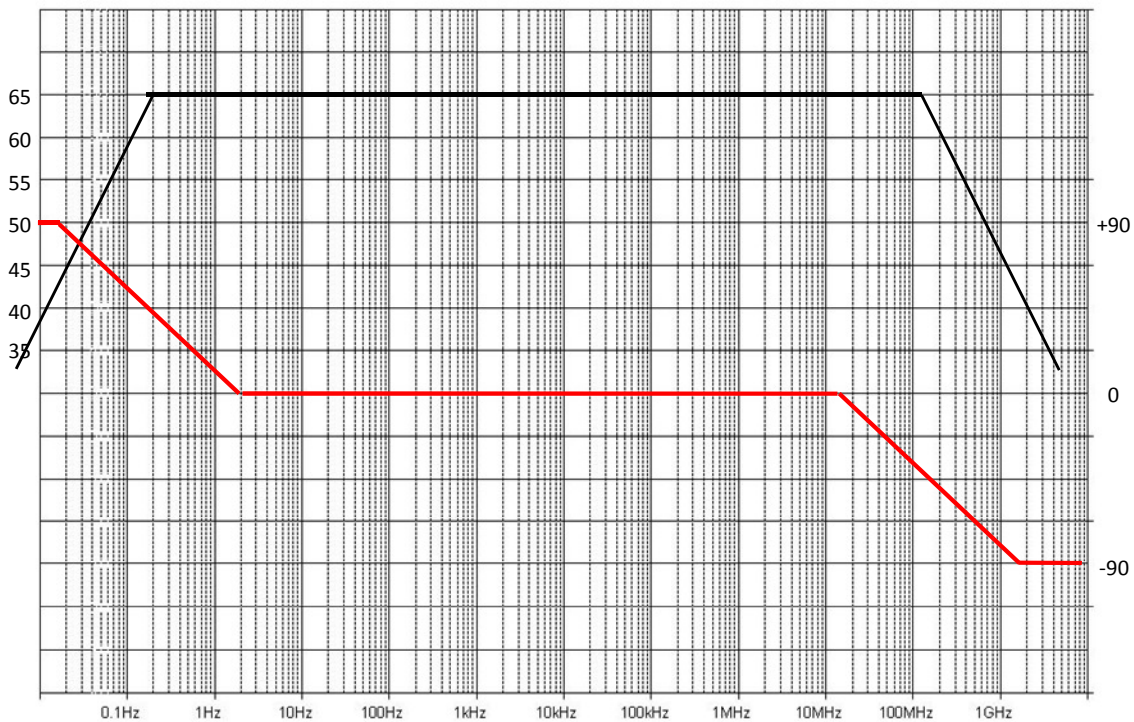

PROBLEM - SOLUTION




- a) $V_{GS1} = -1.5\text{ V}$ $I_{D1} = 2.4\text{ mA}$ $V_{DS1} = 6.3\text{ V}$
b) $I_{C2} = 0.4\text{ mA}$ $V_{CE2} = 6.6\text{ V}$ $I_{B2} = 2\text{ }\mu\text{A} \ll I_{R4,R5} = 120\text{ mA}$
c) $Z1 = R3 = 3\text{ K}\Omega$ $Z2 = R4 // R5 // r_{\pi} = 7.7\text{ K}\Omega$ $Zi = R1 = 1\text{ M}\Omega$
 $V_o/V_g = [-g_{m2}R7] \cdot [-g_{m1}(R3 // R4 // R5 // r_{\pi})] = 1742.4\text{ V/V}$ 64.8 dB
d) $\tau_1 = 50\text{ ps}$ $\tau_2 = 1.1\text{ ns}$ $f_H = 138\text{ MHz}$
e) $\tau_1 = 10\text{ s}$ $\tau_2 = 1.07\text{ s}$ $f_L = 0.16\text{ Hz}$
f) Asymptotic Bode plot (amplitude and phase)






QUESTION 1 - SOLUTION

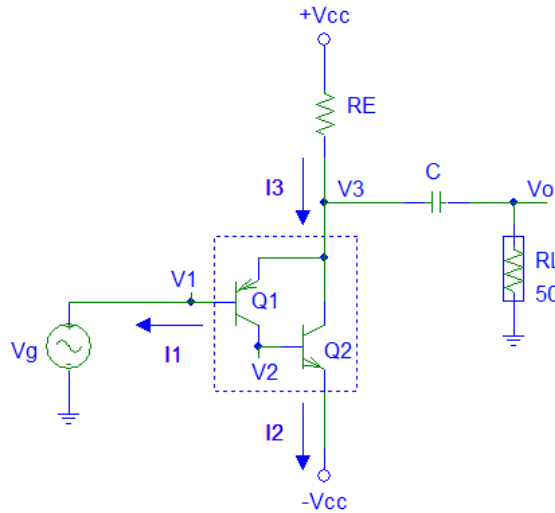

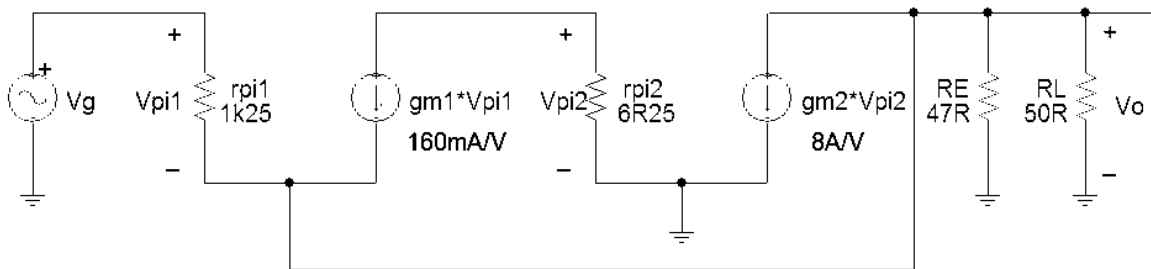- a) $V_1 = 0 \text{ V}$ $V_2 = -9.3 \text{ V}$ $V_3 = 0.6 \text{ V}$ $V_o = 0 \text{ V}$
b) $R_E = 47 \Omega$
c) $I_2 = \beta_{F1} \cdot (1 + \beta_{F2}) \cdot I_1$ $I_1 = 19.6 \mu\text{A}$ $I_2 \approx I_3 = 200 \text{ mA}$
d) $V_{EC1} = 9,9 \text{ V} > V_{EC-SAT}$ $V_{CE2} = 10,6 \text{ V} > V_{CE-SAT}$
e) $I_{C1} \approx 4 \text{ mA}$ $g_{m1} = 160 \text{ mA/V}$ $r_{\pi 1} = 1.025 \text{ k}\Omega$
 $I_{C2} \approx 200 \text{ mA}$ $g_{m2} = 8 \Omega^{-1}$ $r_{\pi 2} = 6.25 \Omega$




- f) $V_g = V_{\pi 1} + V_o$

$$V_o = \frac{V_{\pi 1}}{r_{\pi 1}} (1 + \beta_{01} + \beta_{01} \cdot \beta_{02}) (R_E // R_L) = (1 + 200 + 50 \cdot 200) \frac{50 // 47 \Omega}{1,25 \text{ k}\Omega} V_{\pi 1}$$

$$V_o \gg V_{\pi 1} \Rightarrow V_o / V_g \approx 1 \Rightarrow \text{Exactly: } V_o = 0.995 \cdot V_g$$




QUESTION 2 - SOLUTION

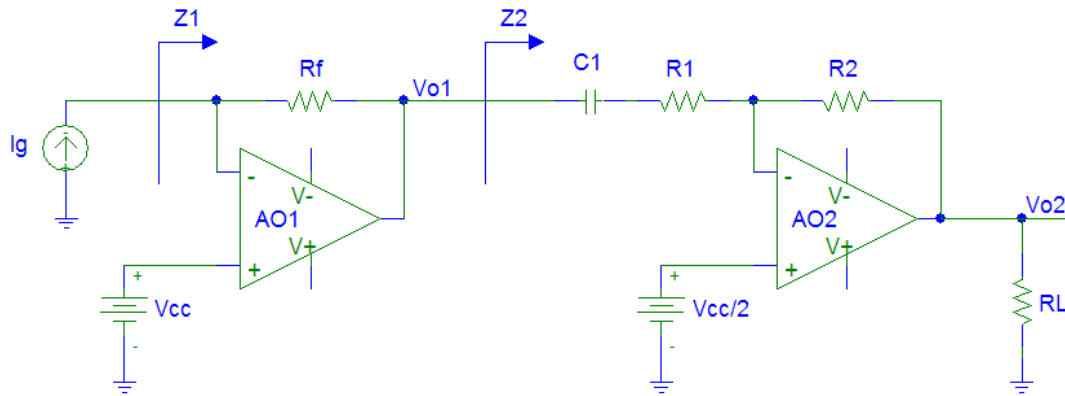


- a) $V_{o1} = V_{cc} \Rightarrow V_{o1} = 5V$ $V_{o2} = V_{cc}/2 \Rightarrow V_{o2} = 2,5V$
- b) $V_{o1} = -R_f \cdot I_g \Rightarrow V_{o1}/I_g = -R_f = -50K\Omega$ $Z1 = 0 \Omega$
- c) $V_{o2}/V_{o1} = -R_2/R_1 = -4,7 V/V$ $Z2 = R_1 = 10 K\Omega$

d) I_g :

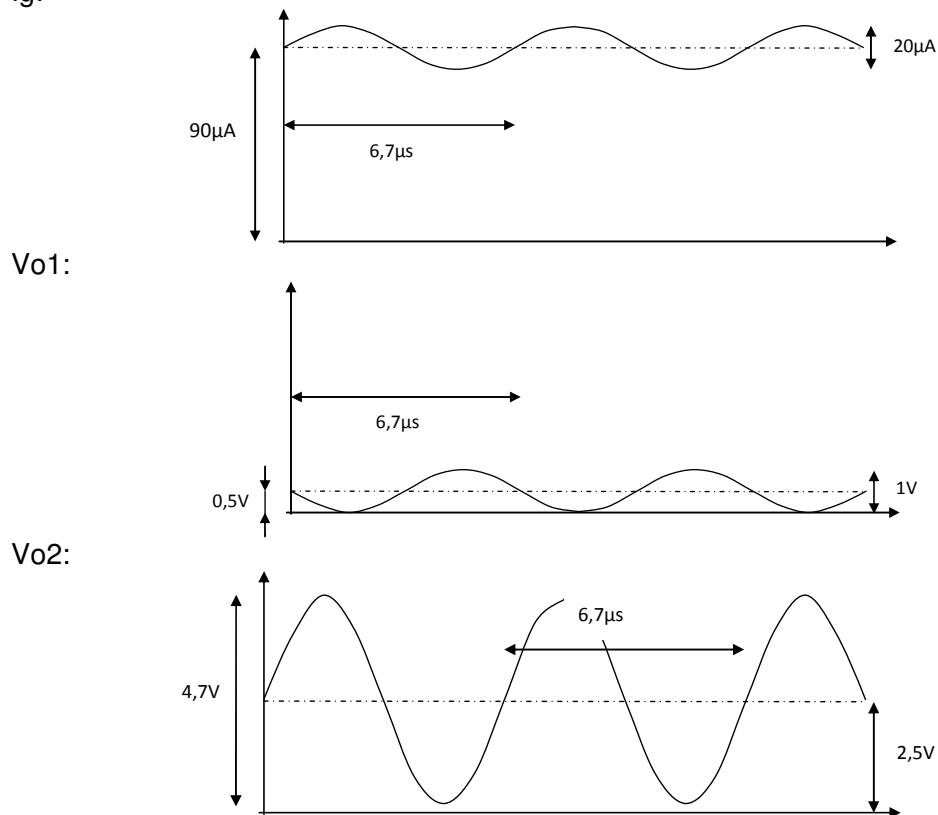




QUESTION 3 - SOLUTION

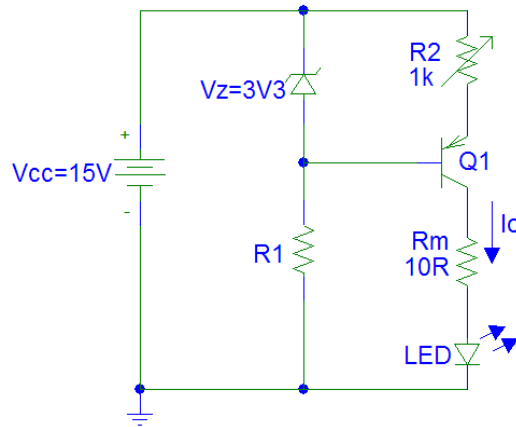

- a) $R1 = 585 \Omega$
- b) $I_o = 2.6 \text{ mA}$ $I_B = 17.3 \mu\text{A} \ll I_o < I_Z$
- c) $I_{CQ} = 2.6 \text{ mA}$ $V_{ECQ} = 10.77 \text{ V}$ $V_{EC} = V_{CC} - V_{LED-ON} - V_Z + V_{EB-ON} - I_C \cdot R_m$
- d) $I_{o_{max}} = 48.5 \text{ mA} < 62.5 \text{ A} < 100 \text{ mA}$
- e) $R2_{min} = 53.6 \Omega$ $V_{EC} = 10.32 \text{ V} > V_{EC-SAT}$


QUESTION 4 - SOLUTION

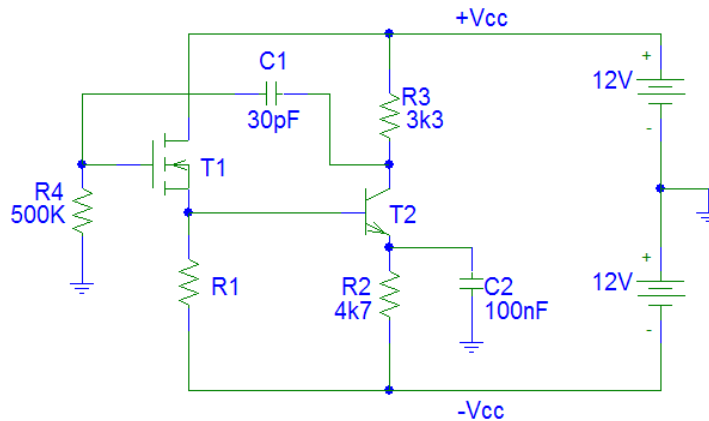

- a) C1 and C2 open-circuit
- b) $R1 = 10 \text{ K}\Omega$ $V_{DS} = 14 \text{ V} > V_{DS-SAT} = (2\text{V} - 1\text{V})$
- c) $I_C = 2 \text{ mA}$ $V_{CE} = 8\text{V}$
- d) $V_G = 0 \text{ V}$ $V_C = 5.4 \text{ V}$
- e) Common drain - common emitter
 $Z_o = R3 = 3.3 \text{ K}\Omega$



QUESTION 5 - SOLUTION

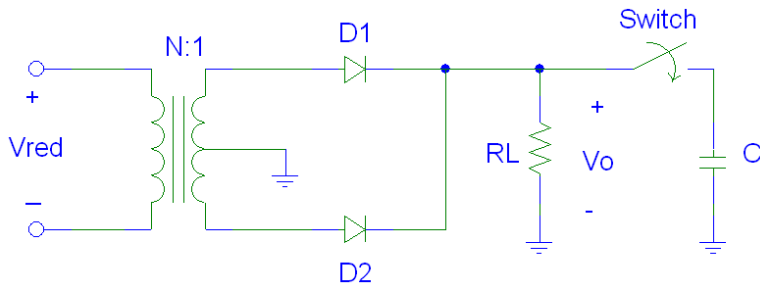

DATA:

$V_{red} = 220 \text{ V}_{rms}; 50 \text{ Hz}$
Ideal diodes ($V_{D-ON} = 0V$)
 $R_L = 300 \Omega$

Figure 6.1

- Rectifier – full wave – double wave. AC to DC conversion. DC voltage supply.
- V_{a1} and V_{a2} are out of phase (180° phase shift), 12V peak and period 20 ms.
 V_o is positive, amplitude 12V, period of the ripple 10 ms.
- $PIV = 2 \cdot V_p = 24 \text{ V}$
- $I_m = V_p / (\pi \cdot R_L) = 12.73 \text{ mA}$.
- Ripple V_r : 1V peak-peak and period 10 ms.
- $C = (T/2R_L) \cdot (V_p/V_r) = 400 \mu\text{F}$
- $V_{om}(\text{without } C) = 2 \cdot V_p / \pi = 7.64 \text{ V}$
 $V_{om}(\text{with } C) = V_p - V_r/2 = 11.5 \text{ V}$

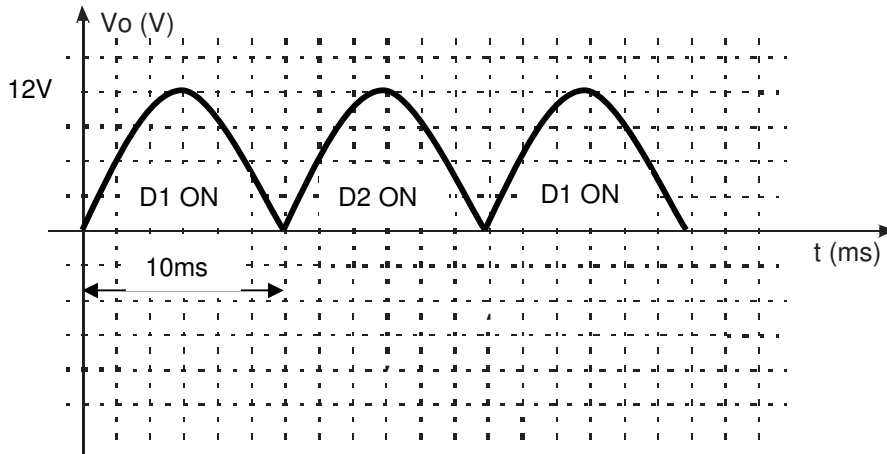
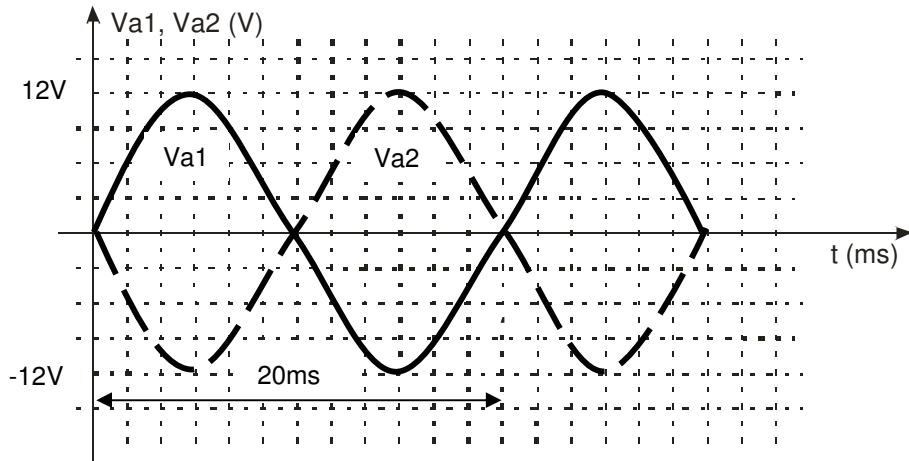


Figure 6.2

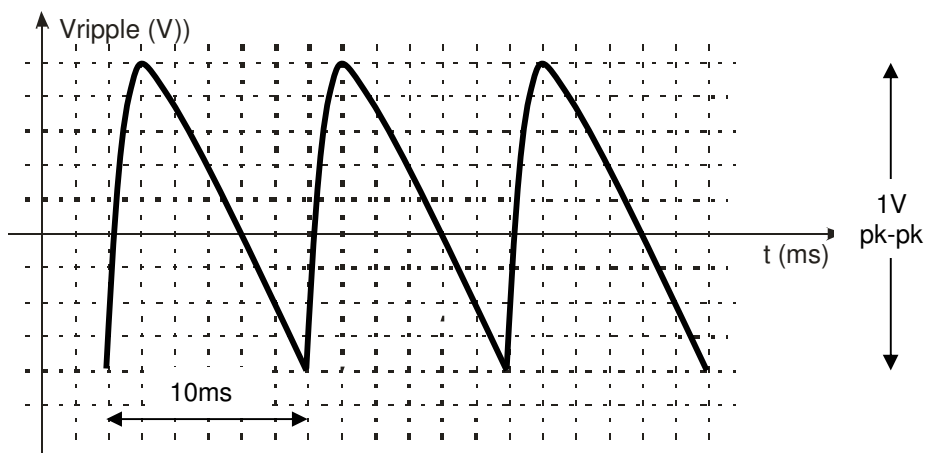


Figure 6.3