



Universidad  
Carlos III de Madrid  
[www.uc3m.es](http://www.uc3m.es)

# Session 17

## Amplifiers with BJT transistors - Exercises

Electronic Components and Circuits  
José A. Garcia Souto

[www.uc3m.es/portal/page/portal/dpto\\_tecnologia\\_electronica/Personal/JoseAntonioGarcia](http://www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia)

# Amplifiers with BJT transistors

## OBJECTIVES


- To analyze small-signal equivalent circuits and interpret the characteristics of the amplifier
- To obtain gains: voltage gain, current gain, transconductance.
- To obtain input impedances.
- To obtain output impedances.

# Small signal analysis of amplifier circuits

## METHODOLOGY

1. Analyze / design the bias circuit (DC).
2. Represent the small signal equivalent circuit of the devices with external signal sources.
3. Obtain the most important gain characteristics of the amplifier.
4. Replace the signal generator with an ideal test generator to calculate the input impedance.
5. Cancel independent signal sources and connect an ideal test generator to calculate the output impedance.

# Exercise: Practical circuit

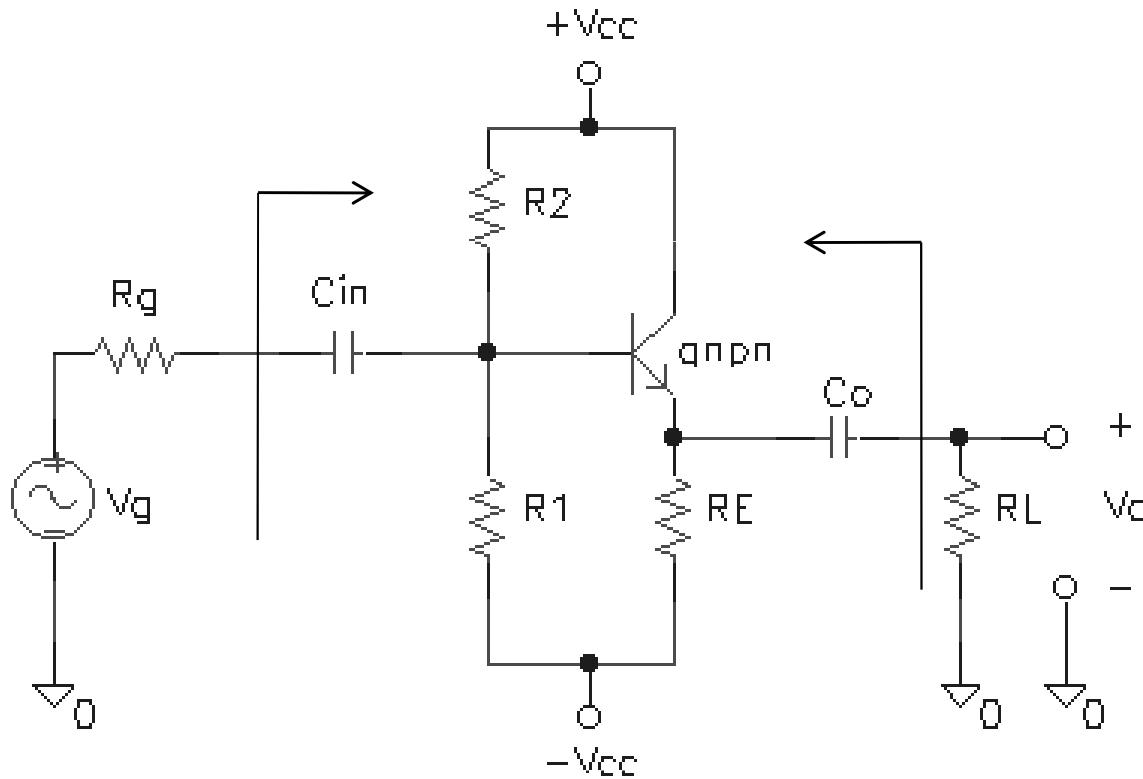


- What kind of amplifier is?
- Obtain the gain  $V_o/V_g$
- Obtain the input impedance
- Obtain the output impedance

## EXAMPLE

- $V_{CC} = 12 \text{ V}$
- $I_C \approx 1 \text{ mA}$
- $V_E \approx 0 \text{ V} (\text{DC})$
- $R_1 = R_2 = 180\text{K}\Omega$
- $R_E = ?$
- $R_L \approx 1\text{K}\Omega$
- $R_g = 50\Omega$
- $C_{in} = 10\mu\text{F}$
- $C_o = 100\mu\text{F}$
- $Q_1 = \text{BC547B}$   
 $(\beta_F \approx \beta_O \approx 300)$   
 $(V_{BE-ON} = 0,7 \text{ V})$   
 $(V_{CE-sat} = 0,2 \text{ V})$

# Exercise: Two DC coupled transistors

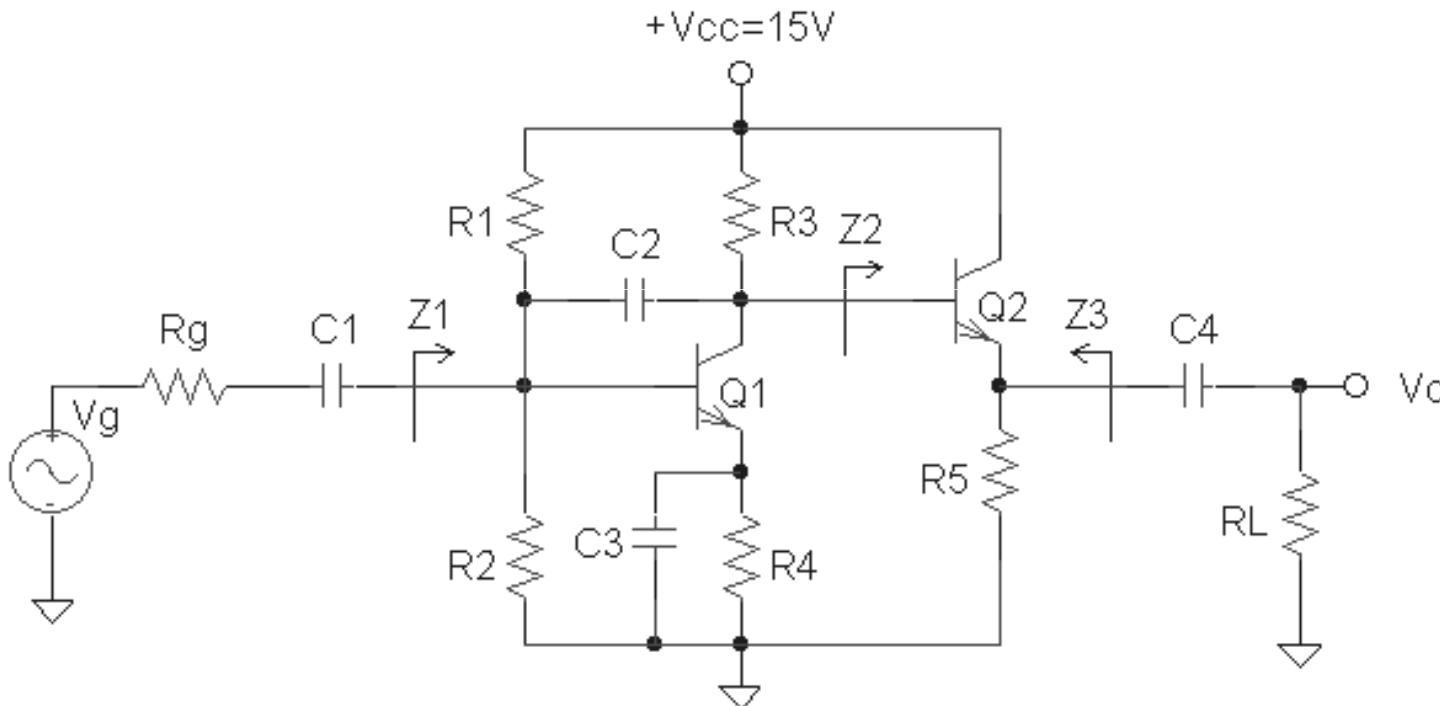

$$R_g = 5 \text{ k}\Omega; R_1 = 30 \text{ k}\Omega; R_2 = 15 \text{ k}\Omega; R_3 = 10 \text{ k}\Omega; R_4 = 8,8 \text{ k}\Omega; R_5 = R_L = 4,7 \text{ k}\Omega$$

$$C_1, C_3 \rightarrow \infty;$$

$$C_2 = 2,5 \text{ pF};$$

$$C_4 = 20 \mu\text{F}$$

$$V_T = 25 \text{ mV}$$

$$\beta_F = \beta_0 = 200;$$

$$r_o \rightarrow \infty;$$

$$C_{\mu_1} = 0,5 \text{ pF};$$

$$C_{\pi 1} = C_{\pi 2} = C_{\mu 2} = 0 \text{ pF}$$

- Draw the equivalent circuit for midrange frequency.
- Calculate the impedances  $Z_1$ ,  $Z_2$  and  $Z_3$ .
- Replace  $Q_2$  by the impedance  $Z_2$  and calculate the gain of  $Q_1$ .
- Calculate the total gain  $V_o/V_g$ .