



Universidad
Carlos III de Madrid
www.uc3m.es

Session 20

Frequency Response of Transistor Amplifiers : Exercises

Electronic Components and Circuits

Pablo Acedo


www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/PabloAcedo

Frequency response analysis of transistor amplifiers

INDEX

- Numerical resolution of an example, including the obtaining of the midband gain, the high cut-off frequency and the low cut-off frequency.
- Use of the former example to illustrate the methodology to obtain the bode plot.

Proposed Exercise

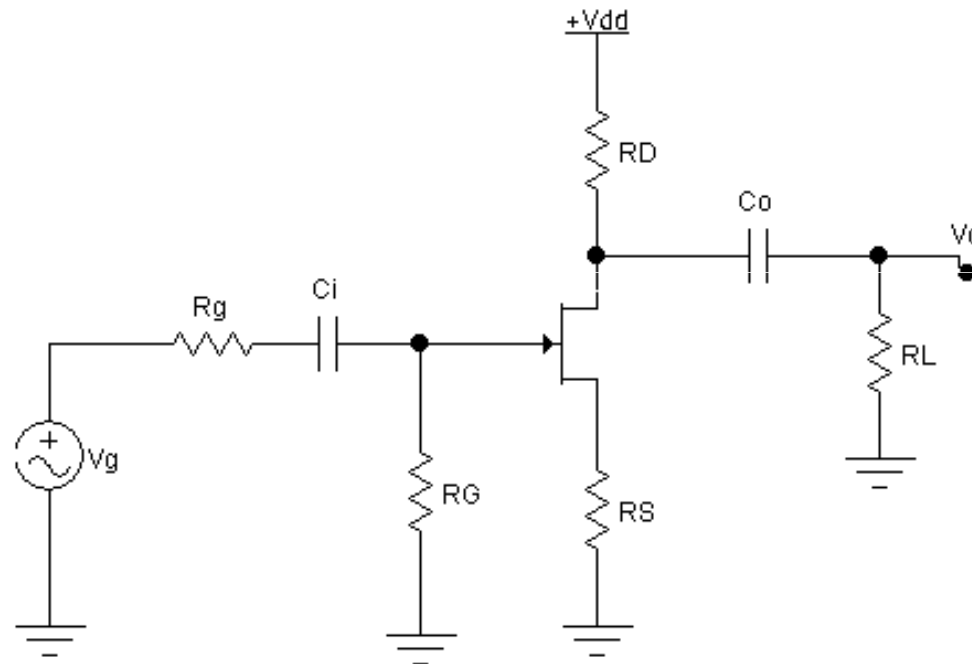

$$+V_{dd} = 15 \text{ V}$$

$$R_S = 560 \Omega$$

$$R_G = 1 \text{ M}\Omega$$

$$R_g = 50 \Omega$$

$$R_D = 5,6 \text{ K}\Omega$$

$$R_L = 10 \text{ K}\Omega$$

$$C_i = 10 \mu\text{F}$$

$$C_o = 10 \mu\text{F}$$

Transistor:

$$I_{DSS} = 10 \text{ mA}$$

$$V_P = -2 \text{ V}$$

$$C_{gd} = 0.36 \text{ pF}$$


$$C_{gs} = 1 \text{ pF}$$

$$I_D = I_{DSS} \cdot (1 - V_{GS}/V_P)^2$$

Proposed Exercise

1. Determination of the dc operating point of the BJT and the small-signal model parameters
2. Determination of the midband gain.
3. Determination of the high cut-off frequency using the open-circuit time constants method
4. Determination of the low cut-off frequency using the short-circuit time constants method
5. Drawing of the Bode Plot.

Bode Plot

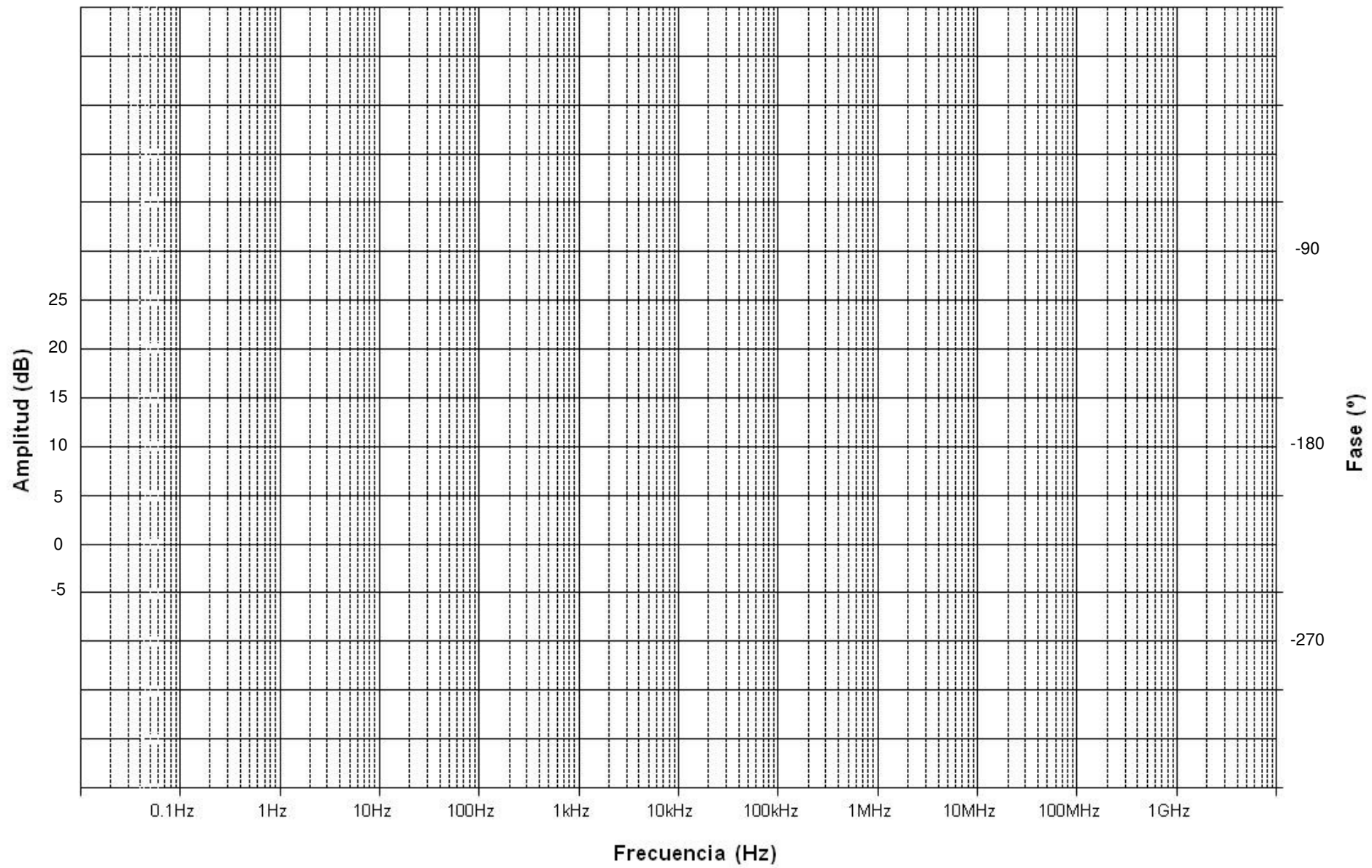

Bode Plot

