



Universidad
Carlos III de Madrid
www.uc3m.es

Session 8

Diodes and Applications

Electronic Components and Circuits

Isabel Pérez

www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/IsabelPerez


Diode Applications

SKILLS

- To obtain and to interpret the signals and parameters (ripple voltage, PIV, dissipated power) in rectifiers circuits
- To know the parameters (Zener voltage, minimum current, maximum power...) and applications of Zener diodes
- To know the basics parameters of light-emitting (LED y LASER) and light-detecting (photodiodes) diodes




Applications

Power Supply (AC-DC Converter)

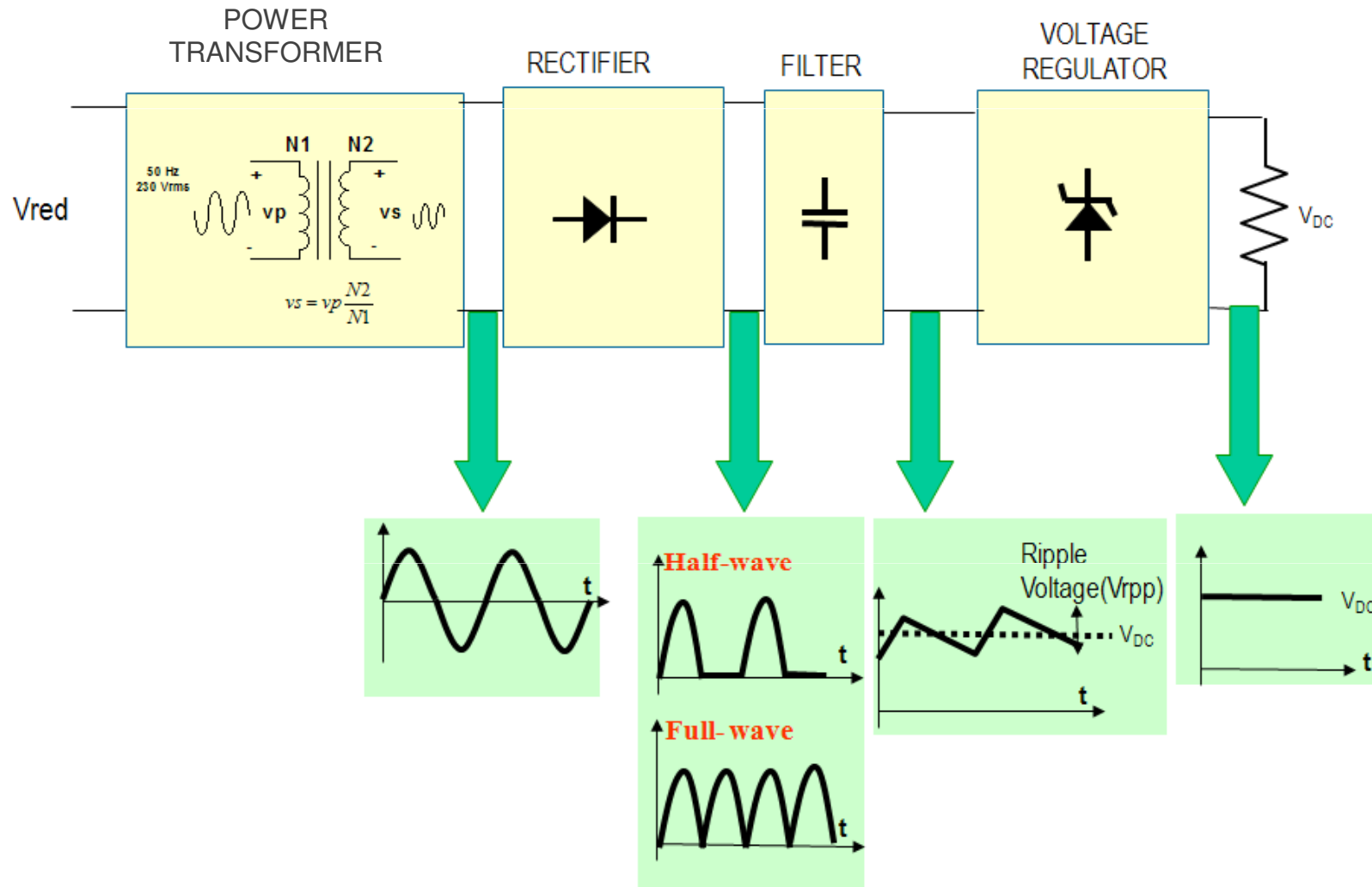


Rectifiers

Half-Wave Rectifier

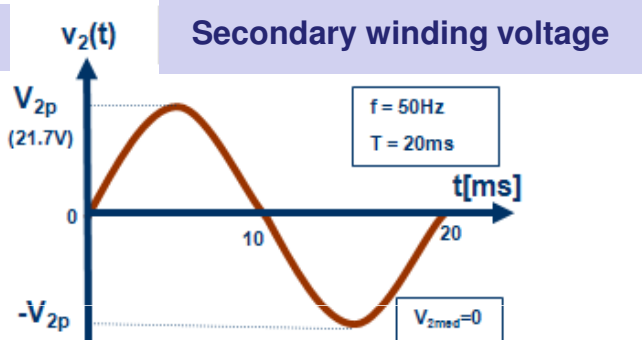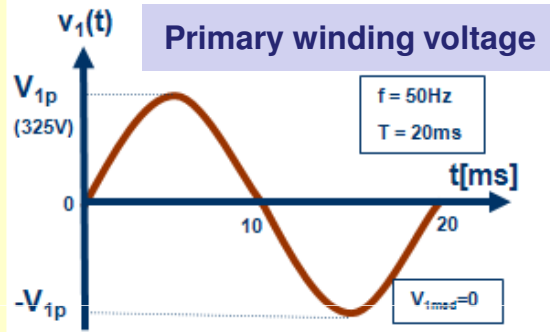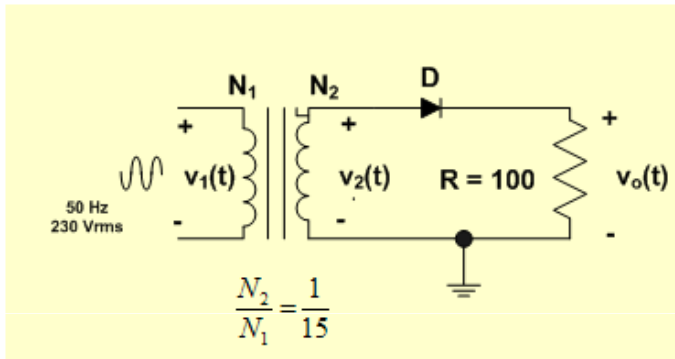


Ideal Diode

Output voltage

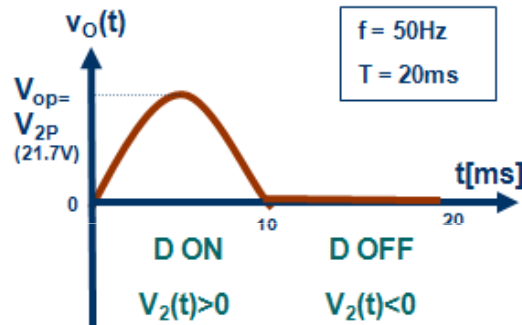


$$\overline{v_o} = \frac{V_{op}}{\pi}$$

Diode current



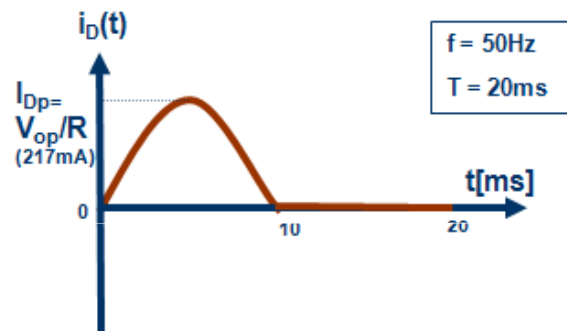


Diode voltage

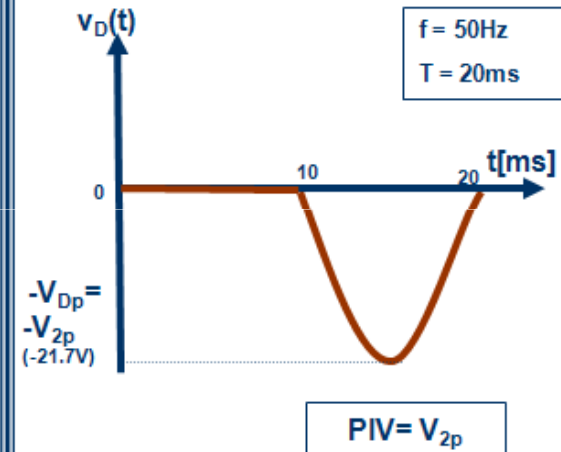


Rectifiers

Half-Wave Rectifier

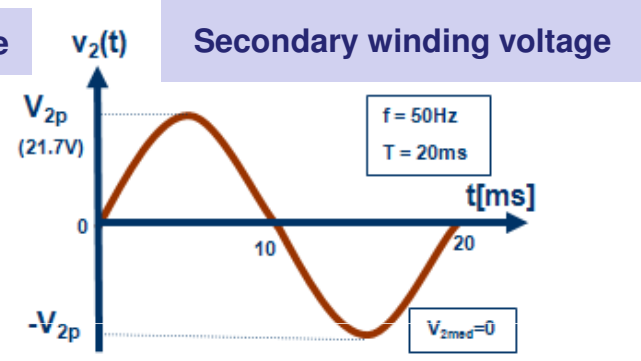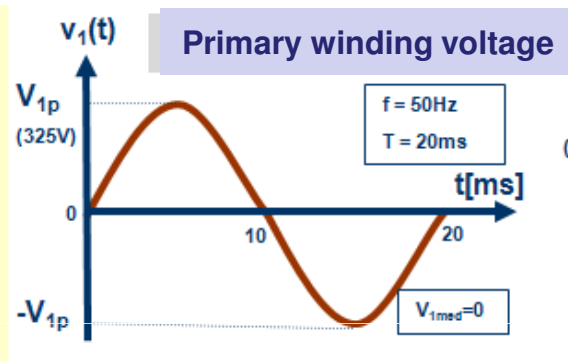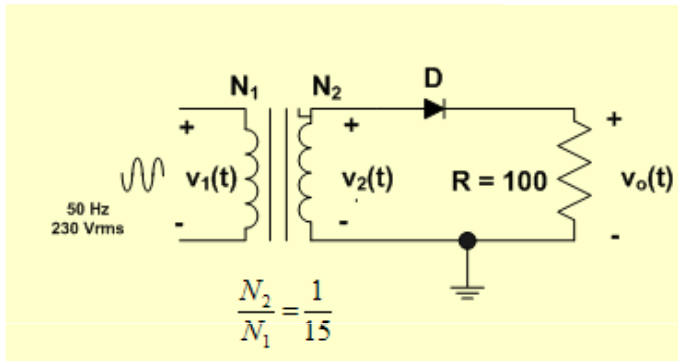


Diode 2^o approximation (V_γ ON)

Output voltage

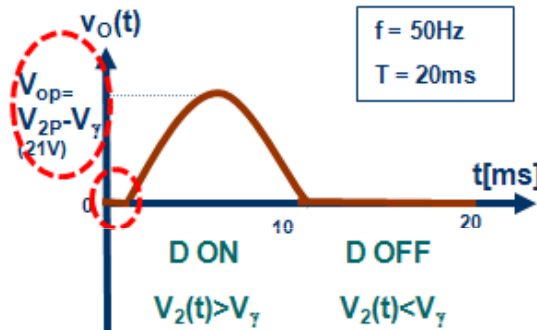


$$\bar{v}_o \approx \frac{V_{op}}{\pi}$$

Diode current


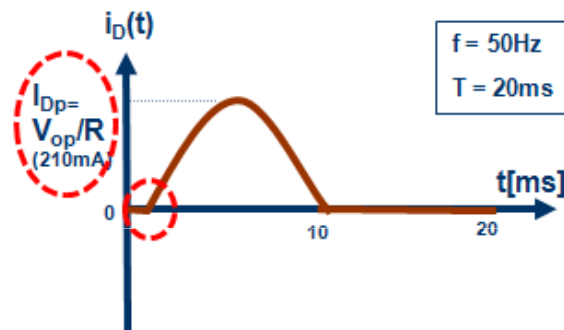


Diode voltage


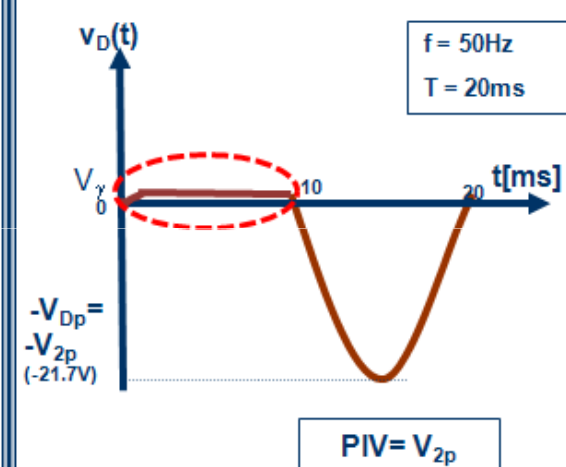


Rectifiers

Half-Wave Rectifier + Filter


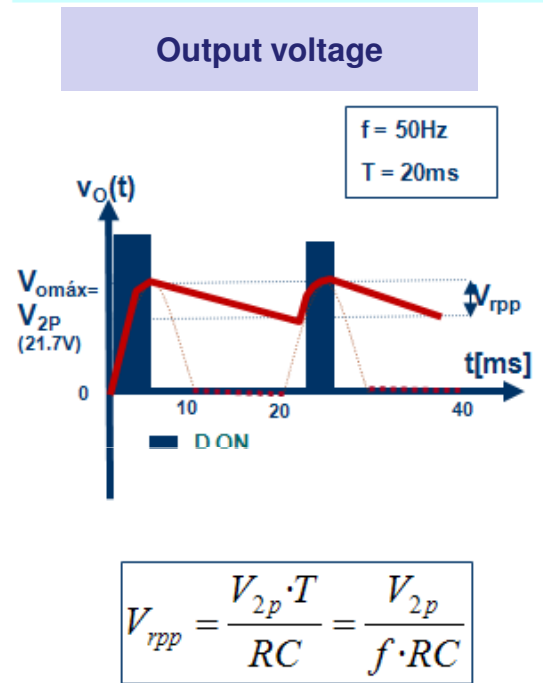
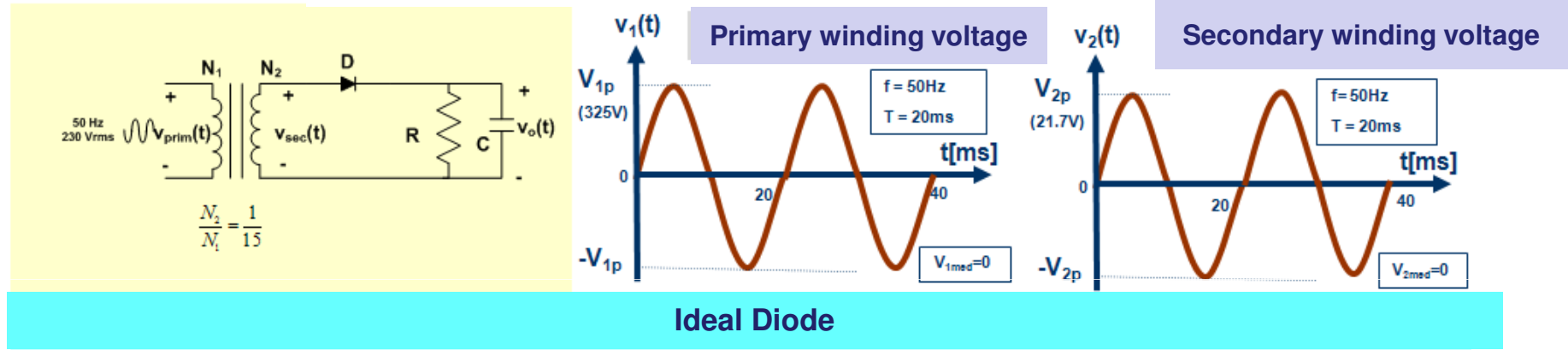


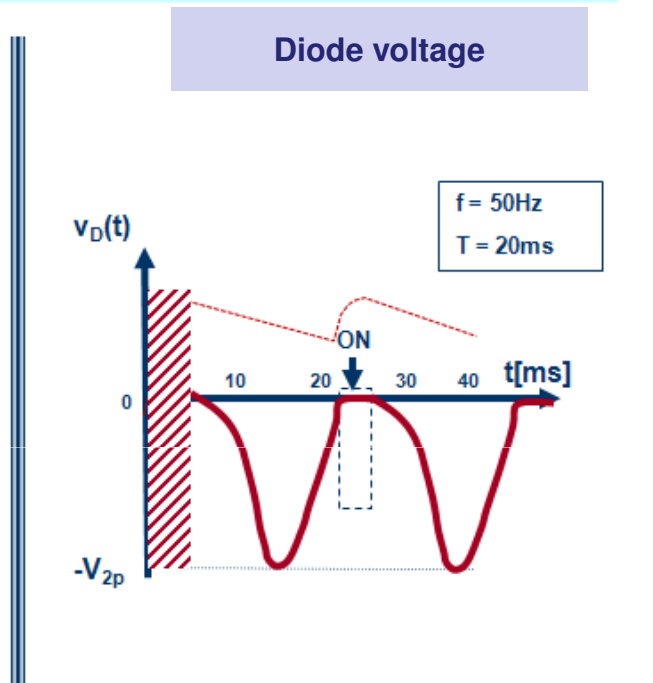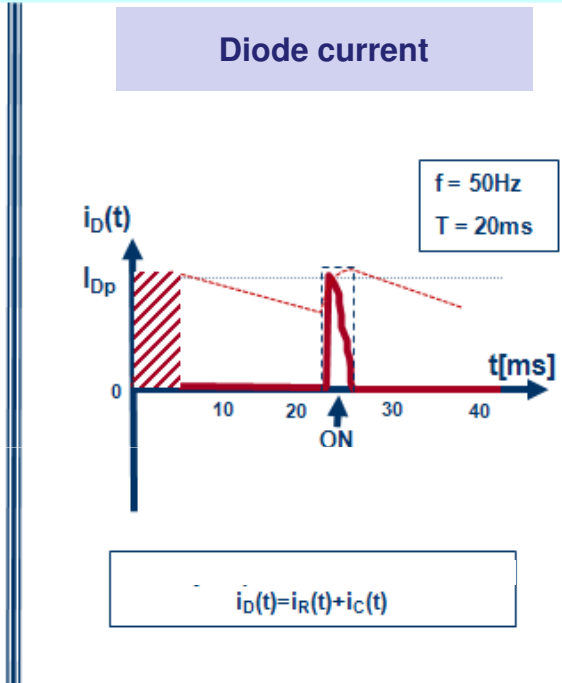T: Secondary winding voltage period
f: Secondary winding voltage frequency




Rectifiers

Full-Wave Rectifier (Bridge rectifier)

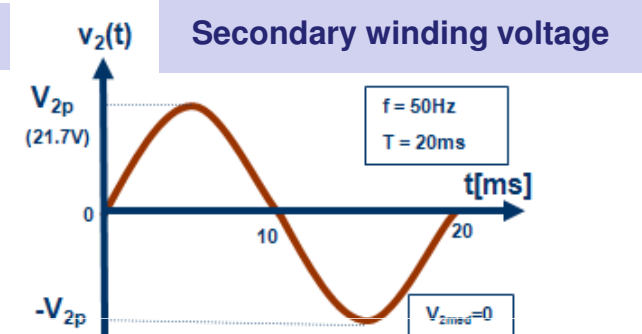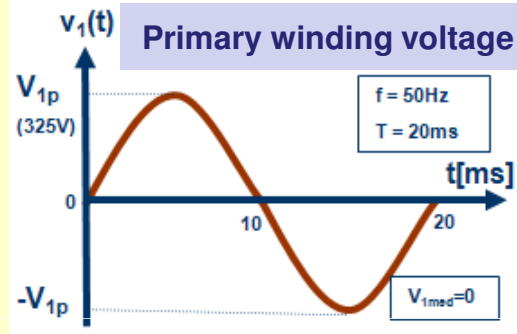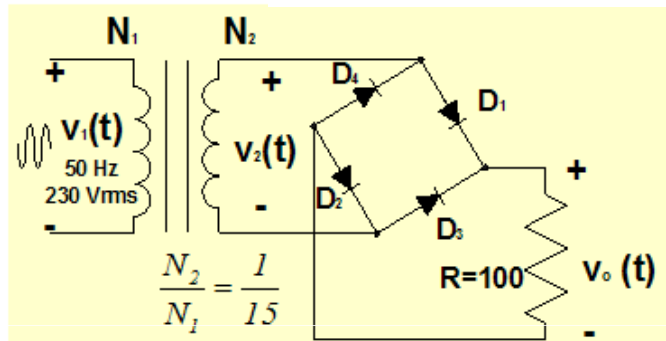


Ideal Diode

Output voltage

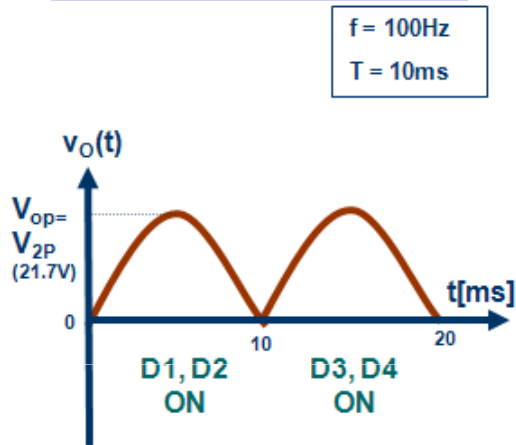


$$V_o = \frac{2V_{op}}{\pi}$$

Diode current



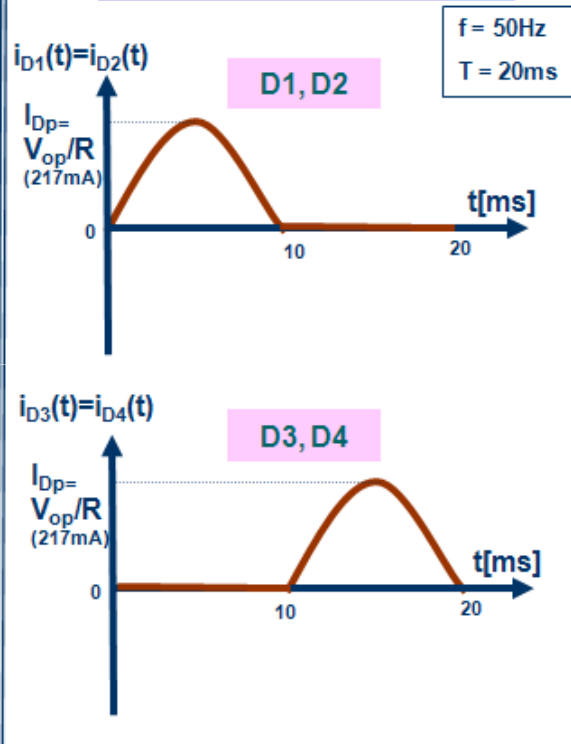


Diodes voltage



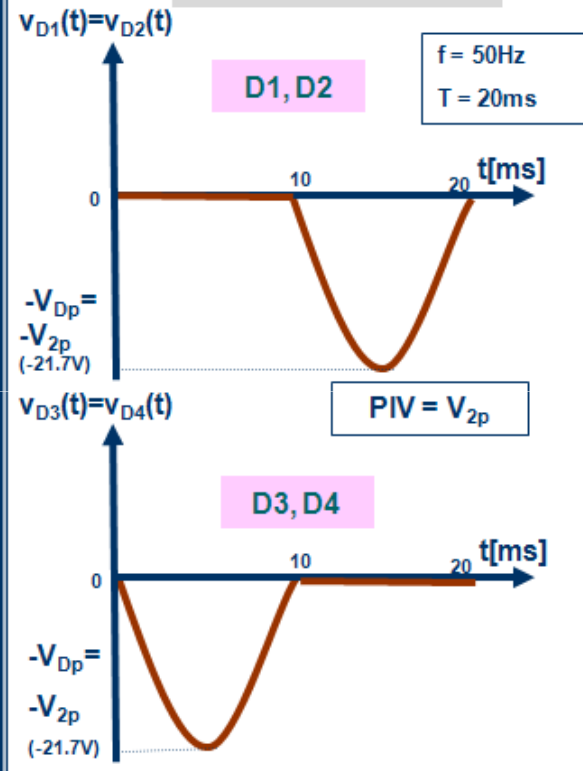


Rectifiers

Full-Wave Rectifier (Bridge rectifier)

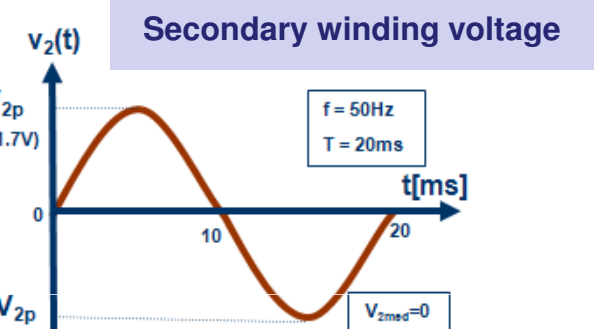
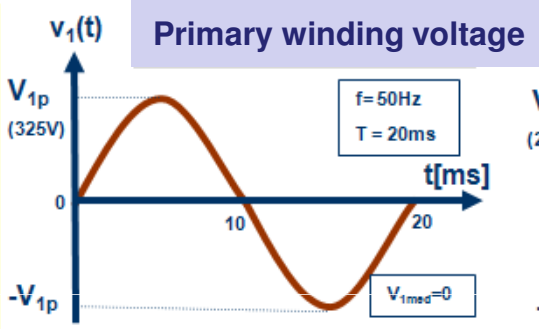
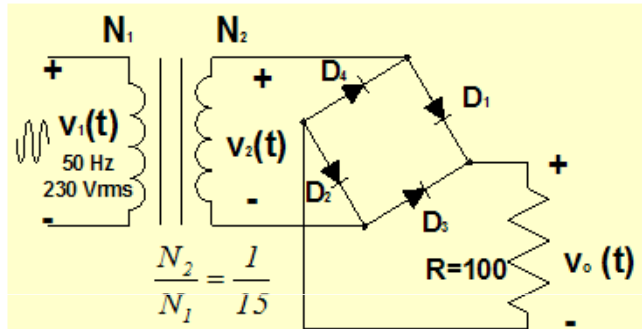


Diode 2^o approximation (V_γ ON)

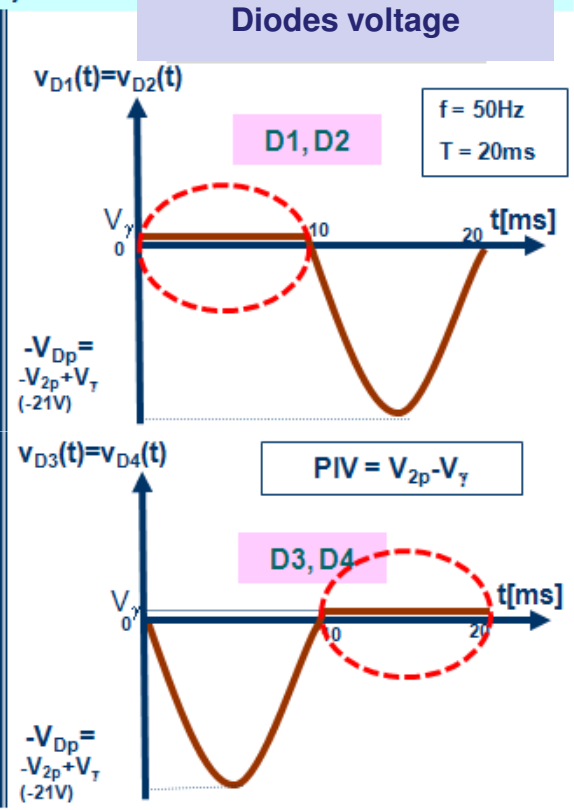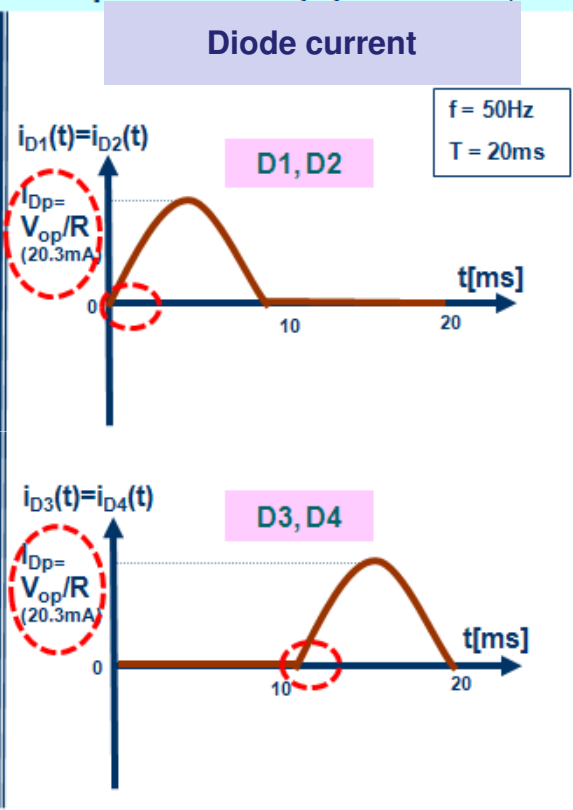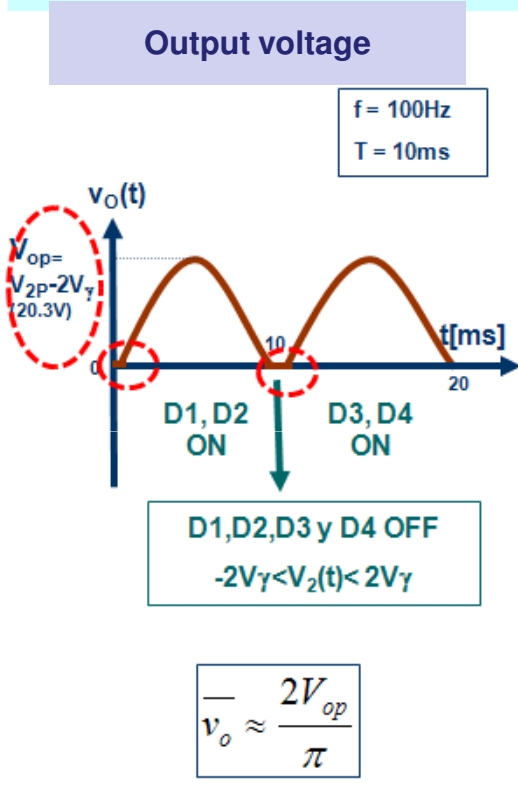


Rectifiers

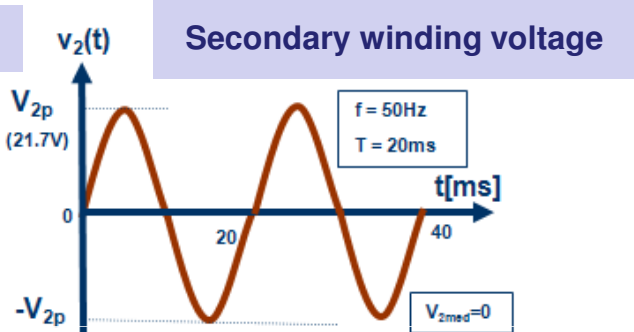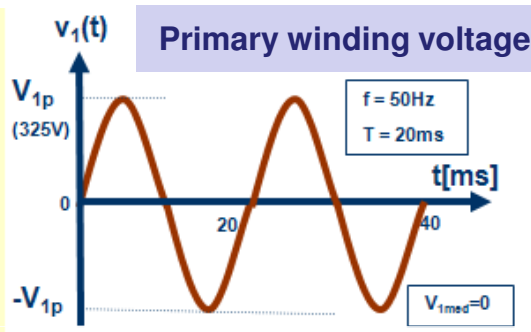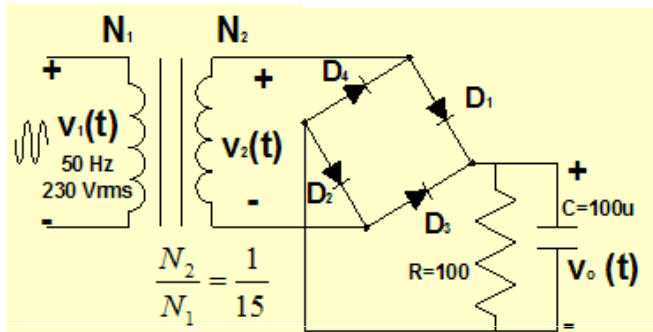Full-Wave Rectifier (Bridge rectifier) + Filter



Ideal Diode



Output voltage

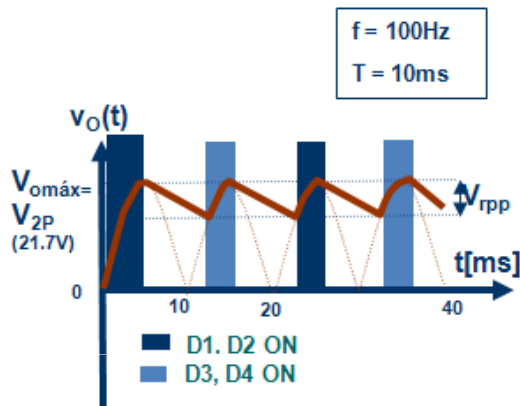

$$V_{ripp} = \frac{V_{2p} \cdot T}{2 \cdot RC} = \frac{V_{2p}}{2 \cdot f \cdot RC}$$



T: Secondary winding voltage period
 f: Secondary winding voltage frequency

Diode current

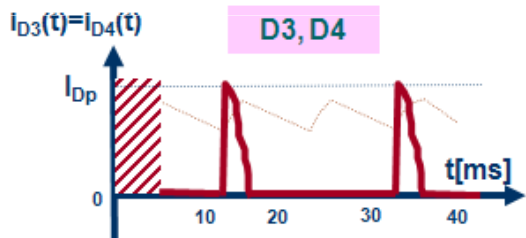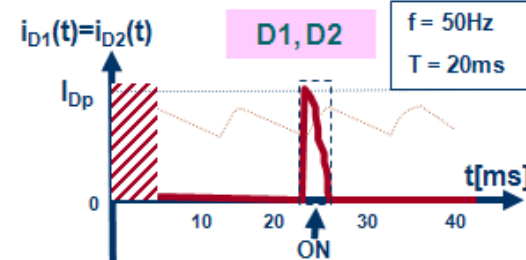


$$i_D(t) = i_R(t) + i_C(t)$$


Diodes voltage

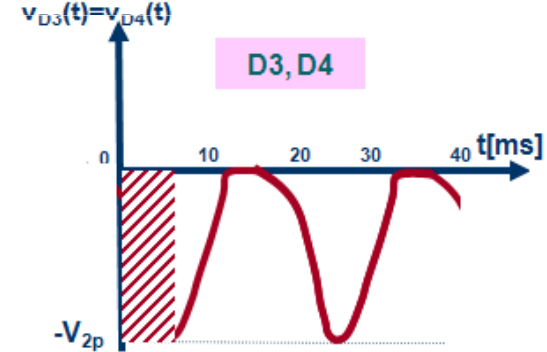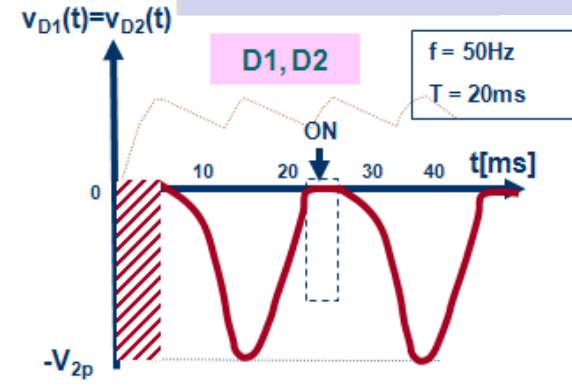


Zener Diodes

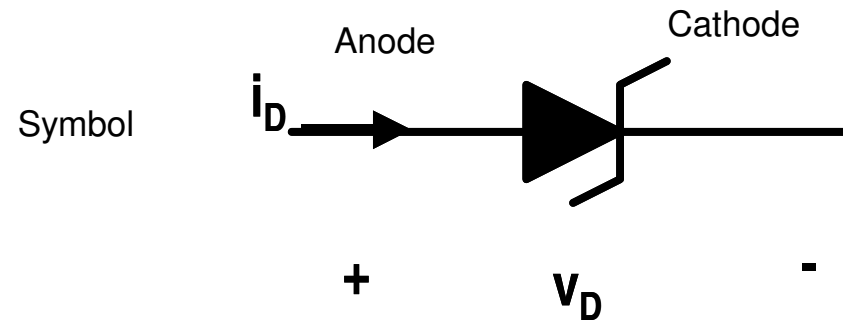

I-V characteristic

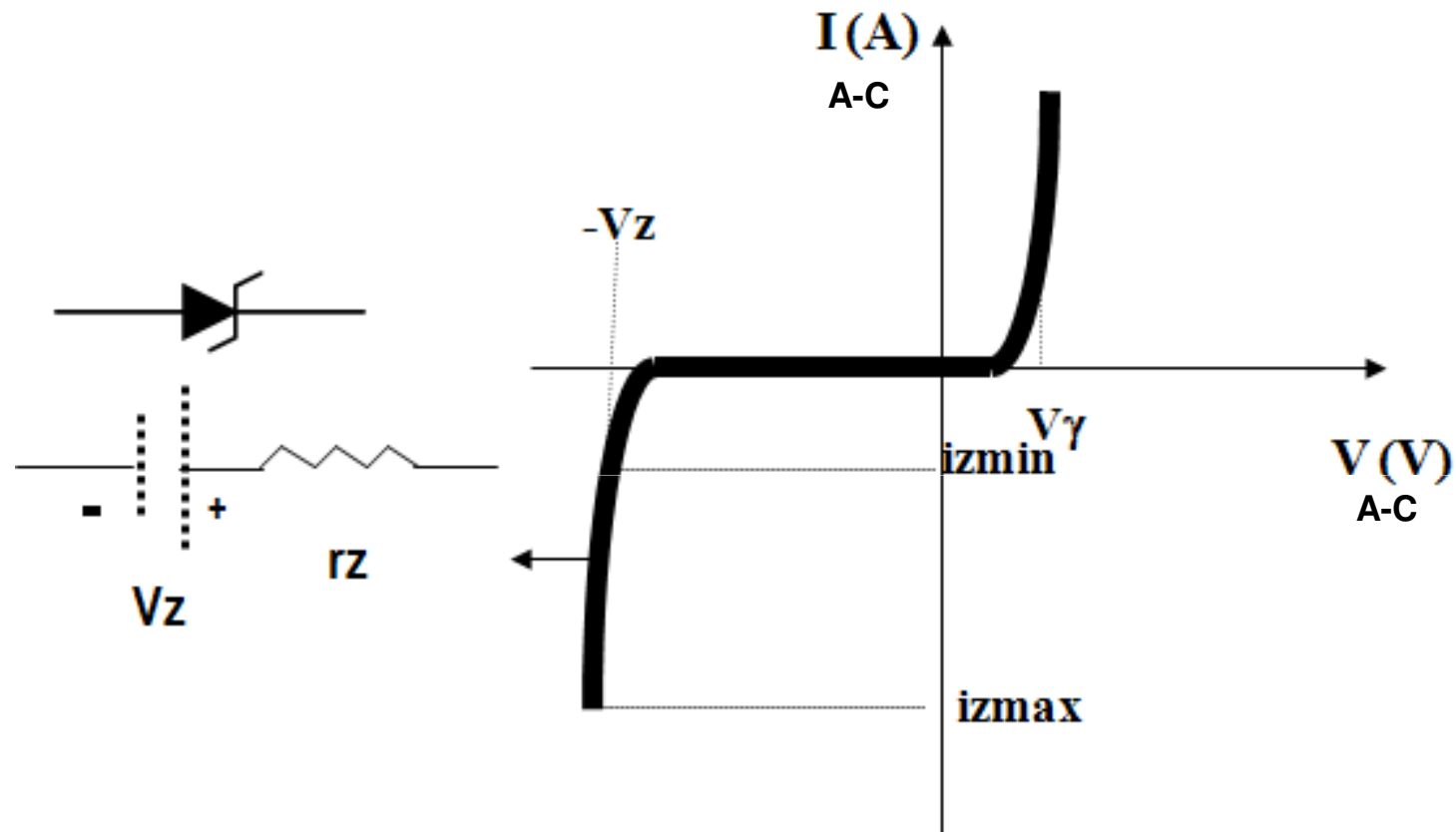


Zener Diodes

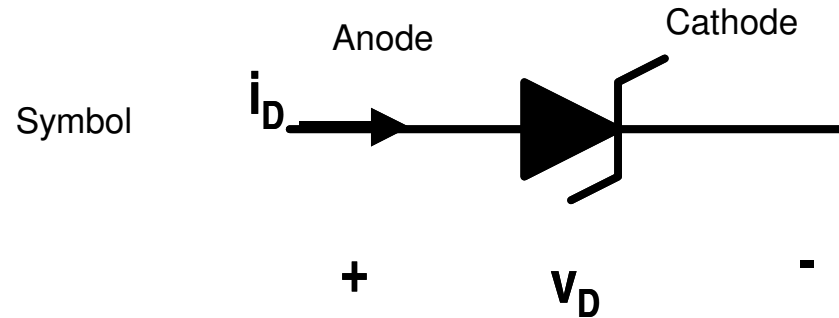

I-V characteristic approximations

Ideal Zener

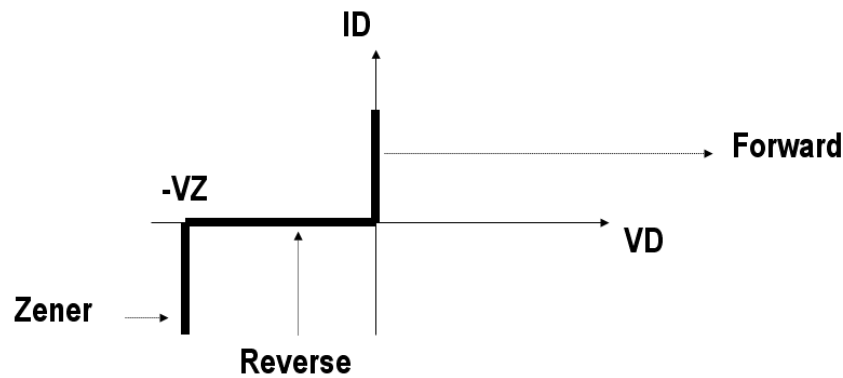


Forward: Short circuit: $V_D=0, I_D>0$

Reverse: Open circuit: $I_D=0, V_D<0$

Zener: $V_A-C=-V_Z, I_D<0$

2^o approximation

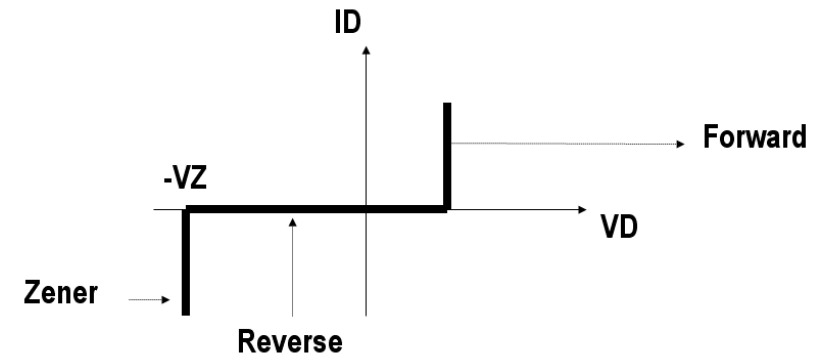


Forward: $V_A-C=V_\gamma, I_D>0$

Reverse: Open circuit: $I_D=0, V_D<0$


Zener: $V_A-C=-V_Z, I_D<0$

Zener Diodes

Applications : Voltage stabilizer

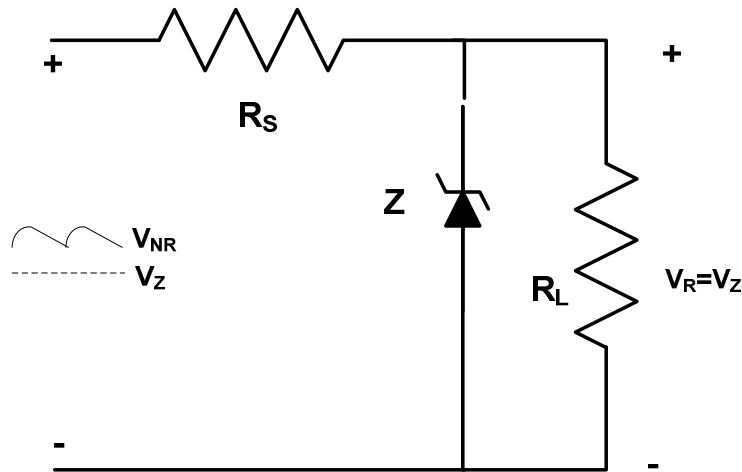

Working in Zener region

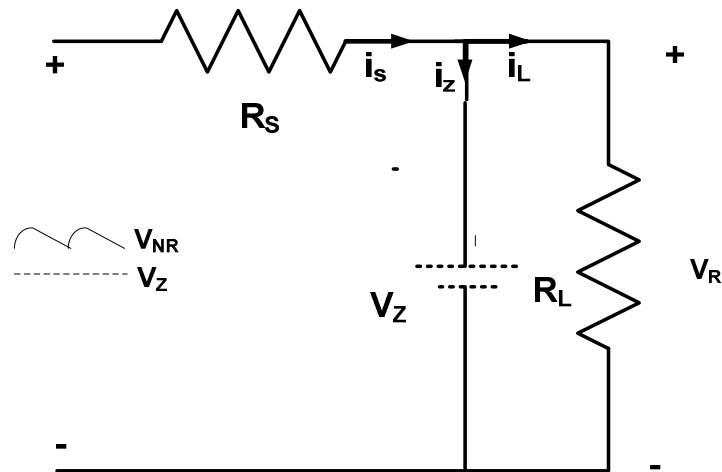

$$i_Z = i_S - i_L = \frac{V_{NR} - V_Z}{R_S} - \frac{V_Z}{R_L}$$

Design

$$i_Z > i_{Z\min} \Rightarrow R_{S\max} = \frac{V_{NR(\min)} - V_Z}{i_{L\max} + i_{Z\min}}$$

$$i_Z < i_{Z\max} \Rightarrow R_{S\min} = \frac{V_{NR(\max)} - V_Z}{i_{S\max}}$$


$$P_{RS} = i_{S\max}^2 \cdot R_S$$

$$P_Z = V_Z \cdot (i_{S\max} - i_{L\min})$$


Zener Diodes

Applications : Limiters (using i-v characteristic approximations)

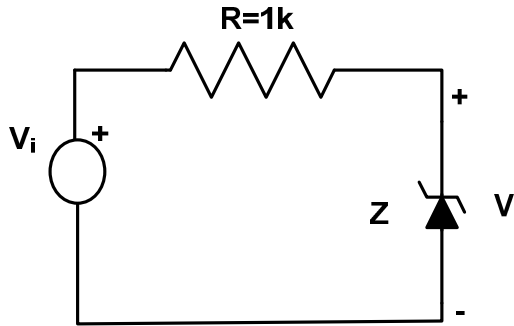Calculate and draw the transfer function, V_o as a function of V_i , with $V_\gamma=0.7V$, $V_Z=5V$.




•Zener : Forward region

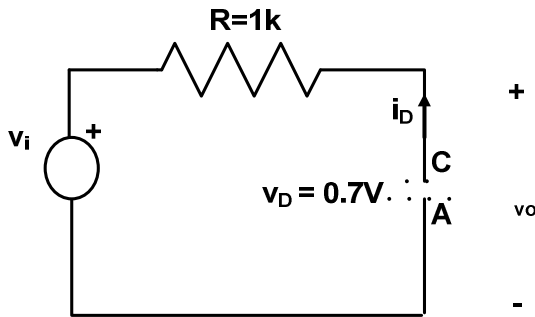

$$v_o = -v_D = -0.7V$$

$$v_i < -0.7V$$


•Zener : Reverse region

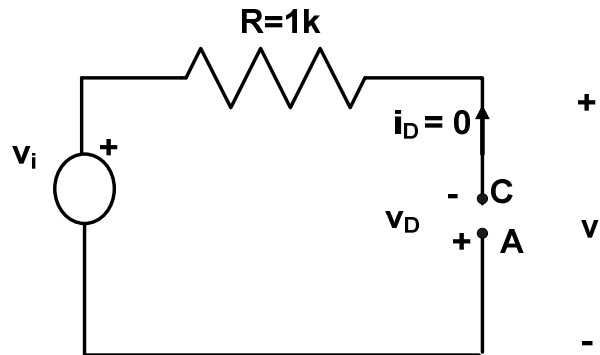

$$v_o = v_i$$

$$-0.7 < v_i < 5V$$


•Zener : Zener region

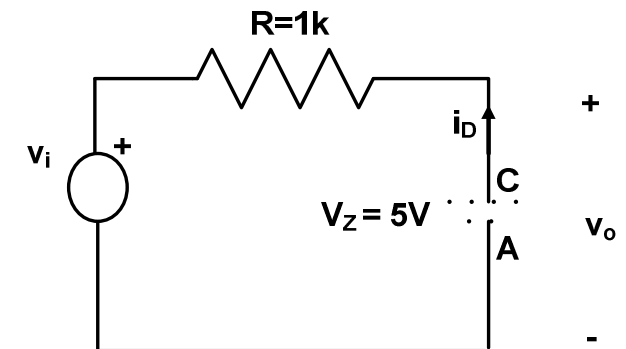

$$v_o = V_Z$$

$$v_i > 5V$$

LEDs y LASER Diodes

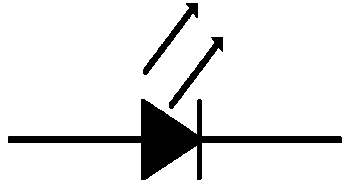

- Forward region: Current to light conversion
- Emission wavelengths, λ , (different colors).


LED (Light Emitting Diode)




- Wide emission spectrum (several λ)
- Conduction threshold voltage (Blue LED: $V_{\gamma} \approx 3V$; Green LED: $V_{\gamma} \approx 2.5V$; Yellow LED: $V_{\gamma} \approx 1V$)

Diodo LASER

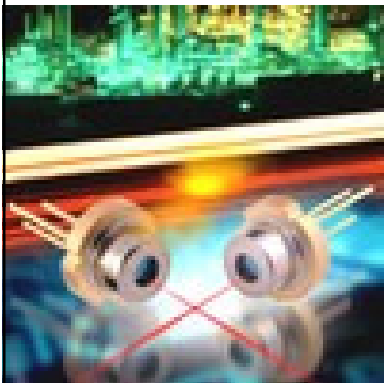
(Light Amplification by Stimulated Emission of Radiation)



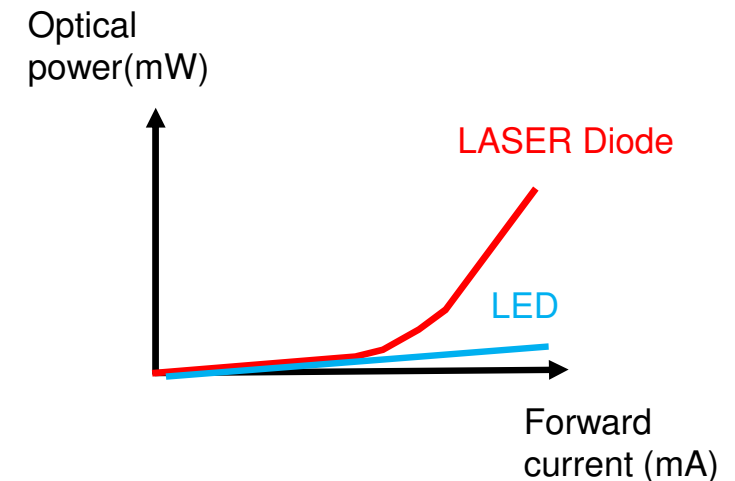
- Narrow emission spectrum (\cong only one λ)
- Coherent light



Photodiodes

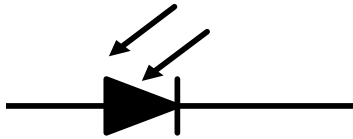

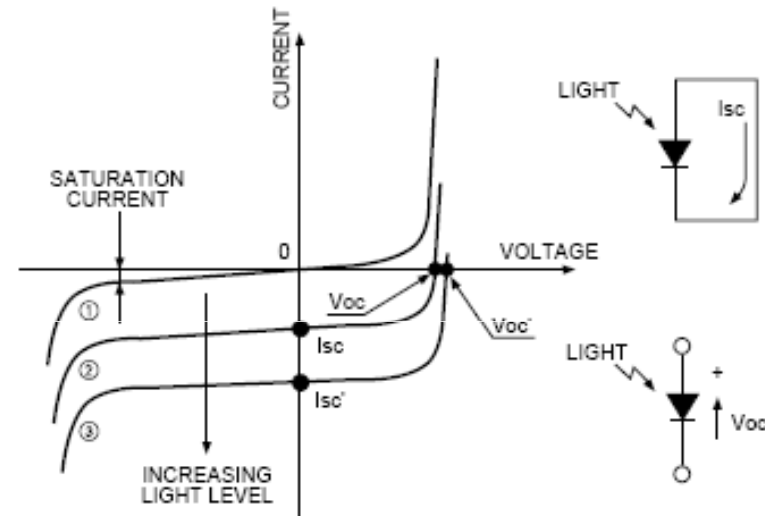- Reverse region: Light to current conversion
- Wavelength range



KPDC0005EA

www.hamamatsu.com

Conditioner circuit (Current- Voltage converter)

