



Universidad  
Carlos III de Madrid  
[www.uc3m.es](http://www.uc3m.es)

# Session 14

## Introduction to electronic amplifiers

Electronic Components and Circuits

José A. Garcia-Souto

[www.uc3m.es/portal/page/portal/dpto\\_tecnologia\\_electronica/Personal/JoseAntonioGarcia](http://www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia)


# Introduction to electronic amplifiers

## OBJECTIVES


- To know the basic parameters of an amplifier
- To understand the process of analyzing the characteristic parameters of amplifiers: gain, input impedance and output impedance
- To understand and use the loading effect
- To generalize the amplifiers frequency response: bandwidth
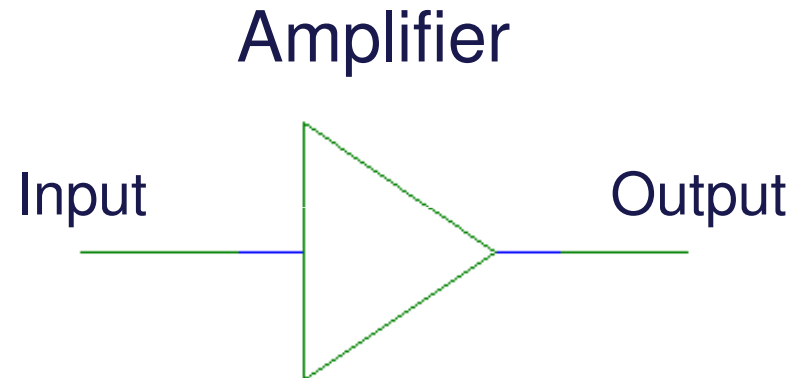
# Amplification concept



- Amplification  
Output > Input  
 $P_i$ ,  $P_o$



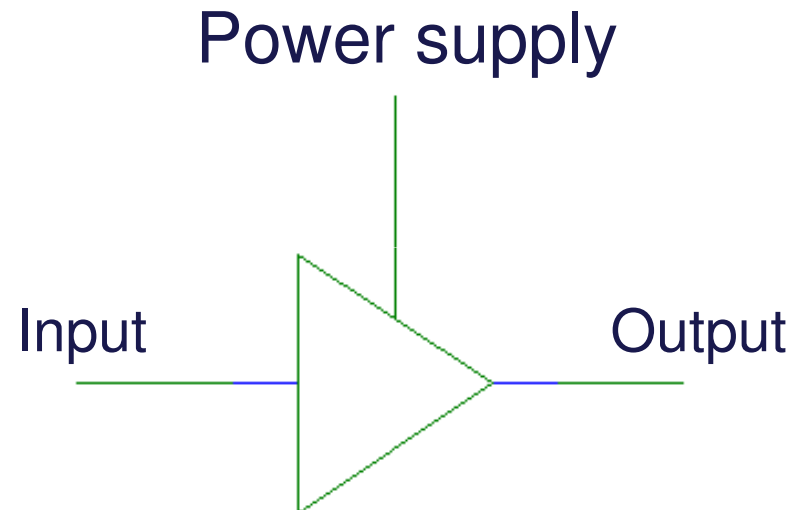- Power supply  
Continuous sources  
 $P_{cc}$







# Gain and Dynamic Range

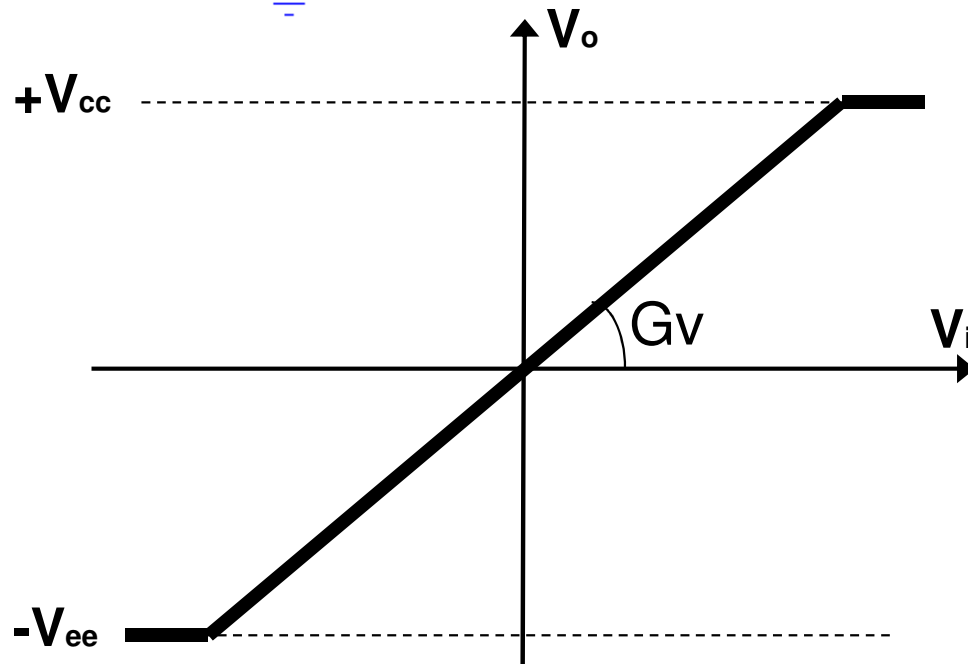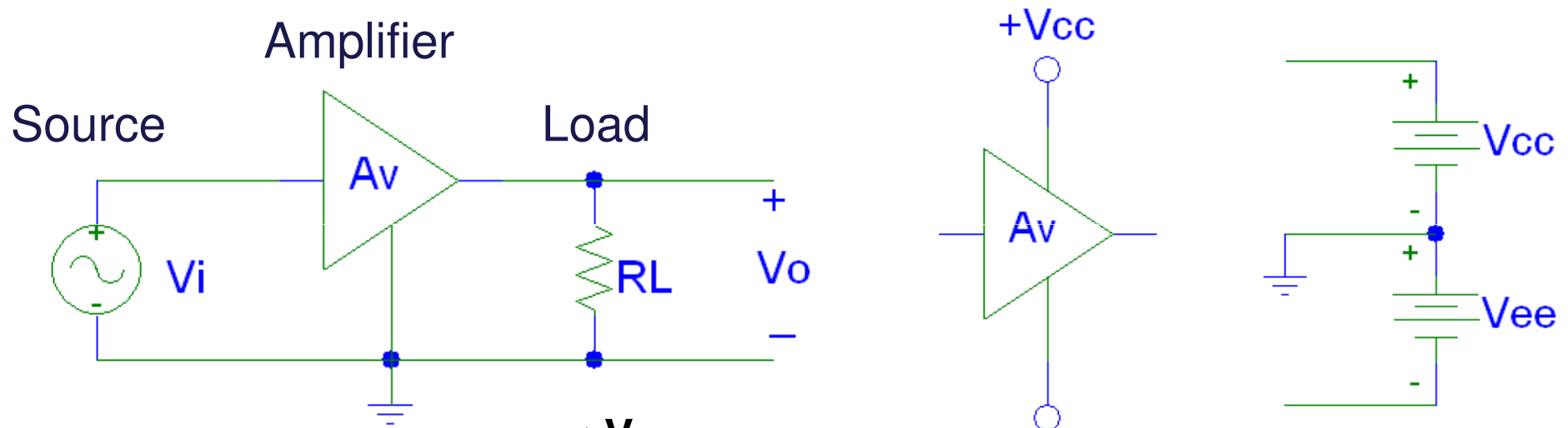

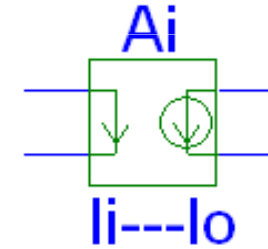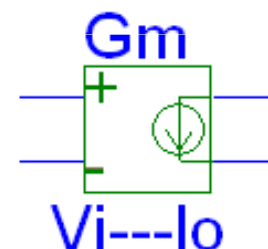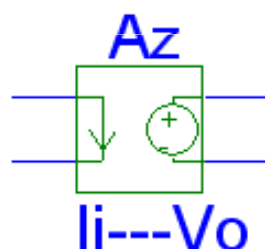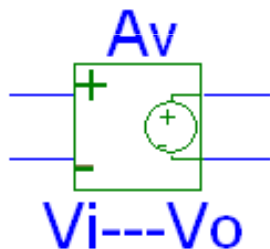
# Amplification (gain)

- Idea of dependent sources
  - V controlled V generators ( $A_v$ )
  - V controlled V generators ( $A_z$ )
  - V controlled I generators ( $G_m$ )
  - I controlled I generators ( $A_i$ )




# Ideal amplifiers


Voltage amplifier

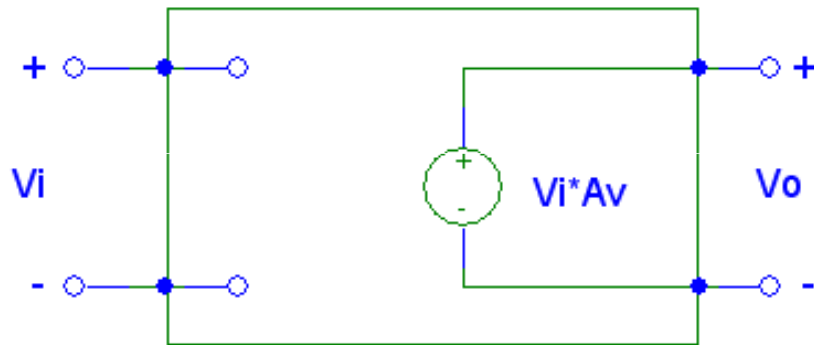


Transimpedance amplifier

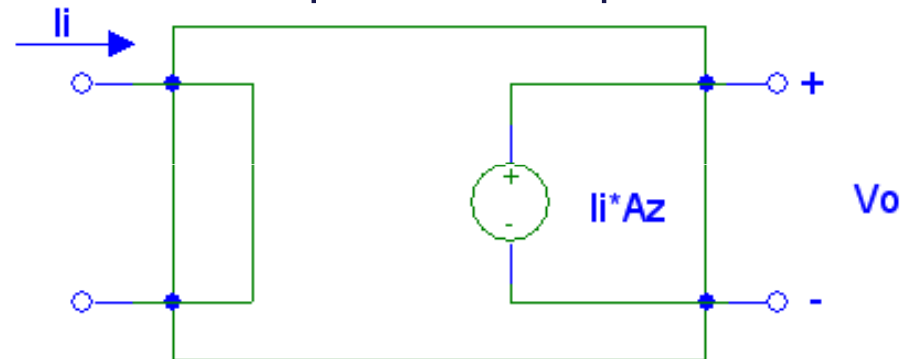

Transconductance amplifier

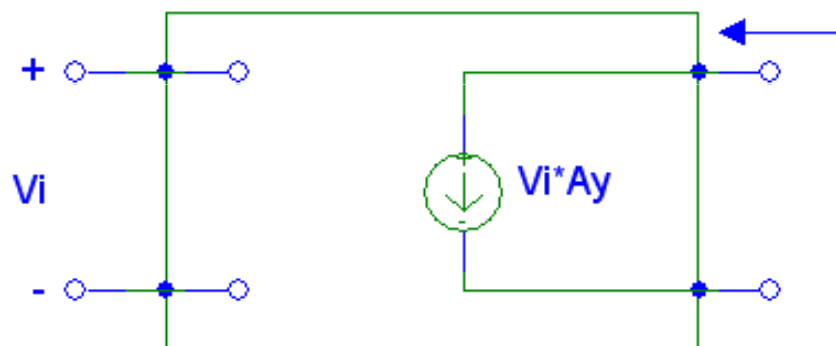


Current amplifier

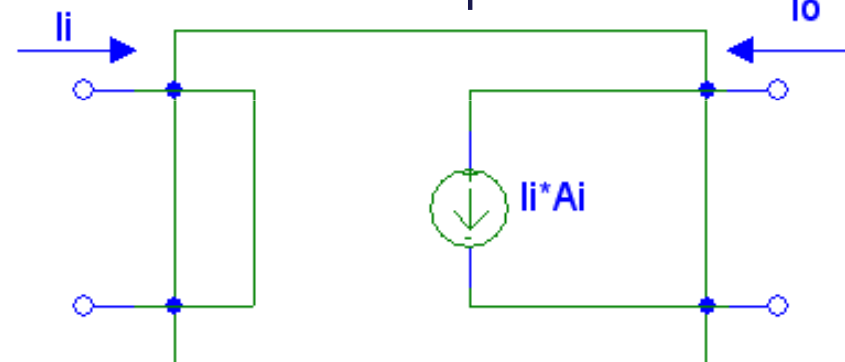


# Real Amplifiers

Voltage amplifier

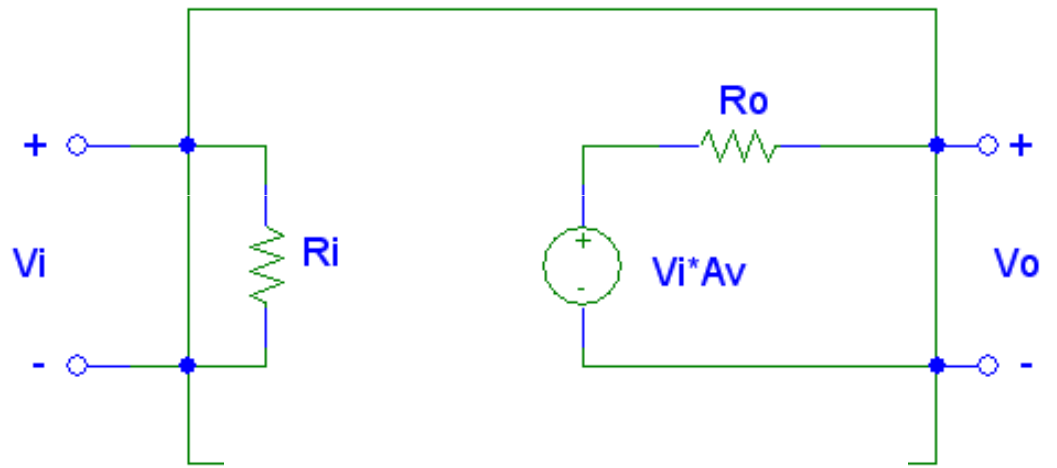


Transimpedance amplifier

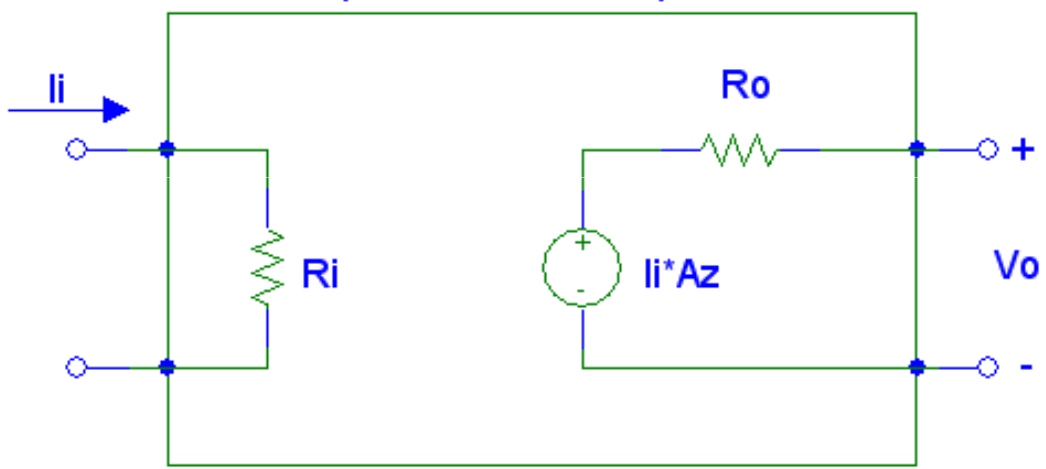


# Real Amplifiers

Transconductance amplifier

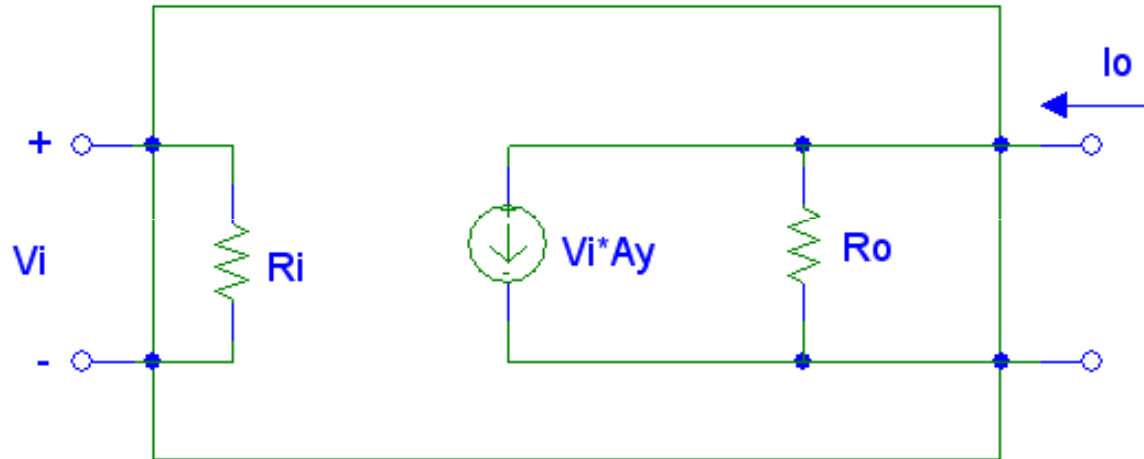


Current amplifier

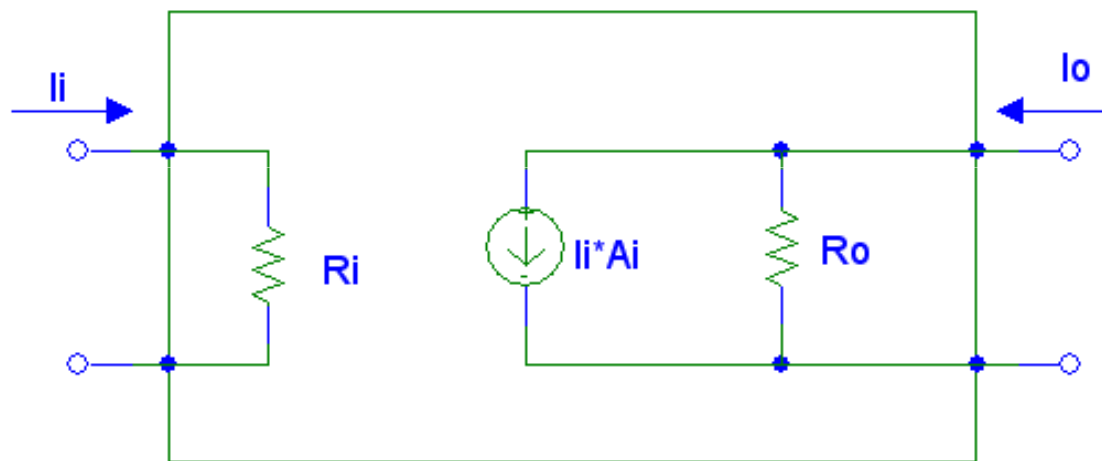



# Loading Effects

Voltage amplifier

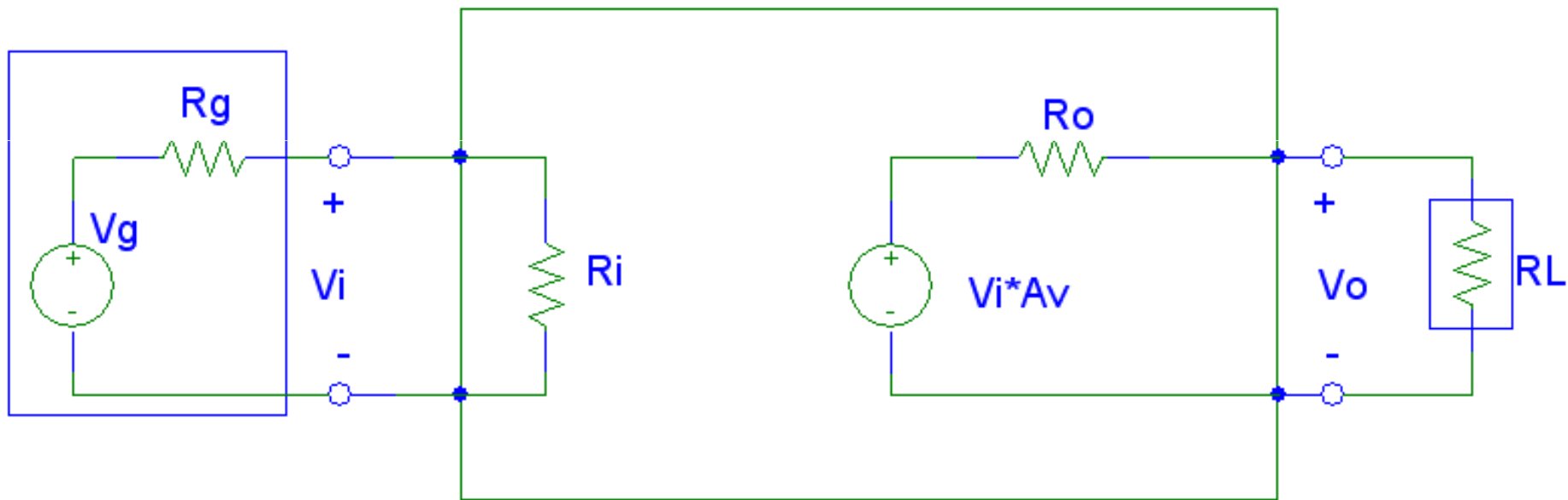


Input Divider  $R_g - R_i$  ( $R_i$  input impedance)

Divisor de salida  $R_L - R_o$  ( $R_o$  impedancia de salida)

$$V_o = A_v \cdot \frac{R_i}{R_i + R_g} \cdot \frac{R_L}{R_o + R_L} \cdot V_g$$
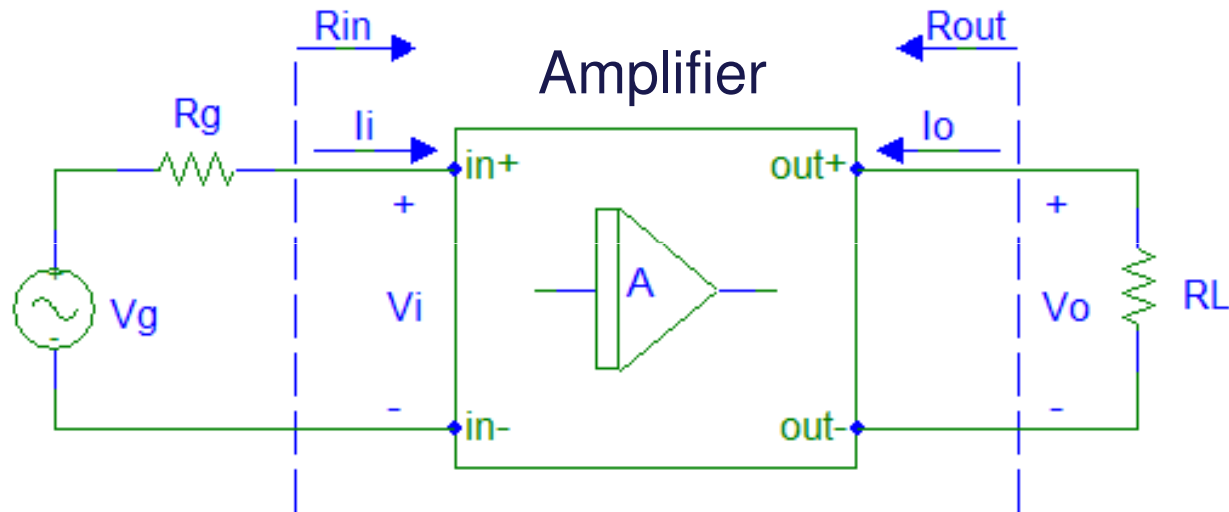
# Characteristic parameters of amplifiers



- Voltage Gain,  $A_v$  y  $G_v$

$$A_v = \frac{V_o}{V_i} \quad G_v = \frac{V_o}{V_g} \quad A_i = \frac{i_o}{i_i}$$

- Current Gain,  $A_i$

- Input resistance,  $R_{in}$


(generalizing: impedance  $Z_{in}$ )

- Output Resistance,  $R_{out}$

(generalizing: impedance  $Z_{out}$ )

$$R_{in} = \frac{V_i}{i_i} \quad R_{out} = \frac{V_o}{i_o}$$

# Open circuit characteristic parameters

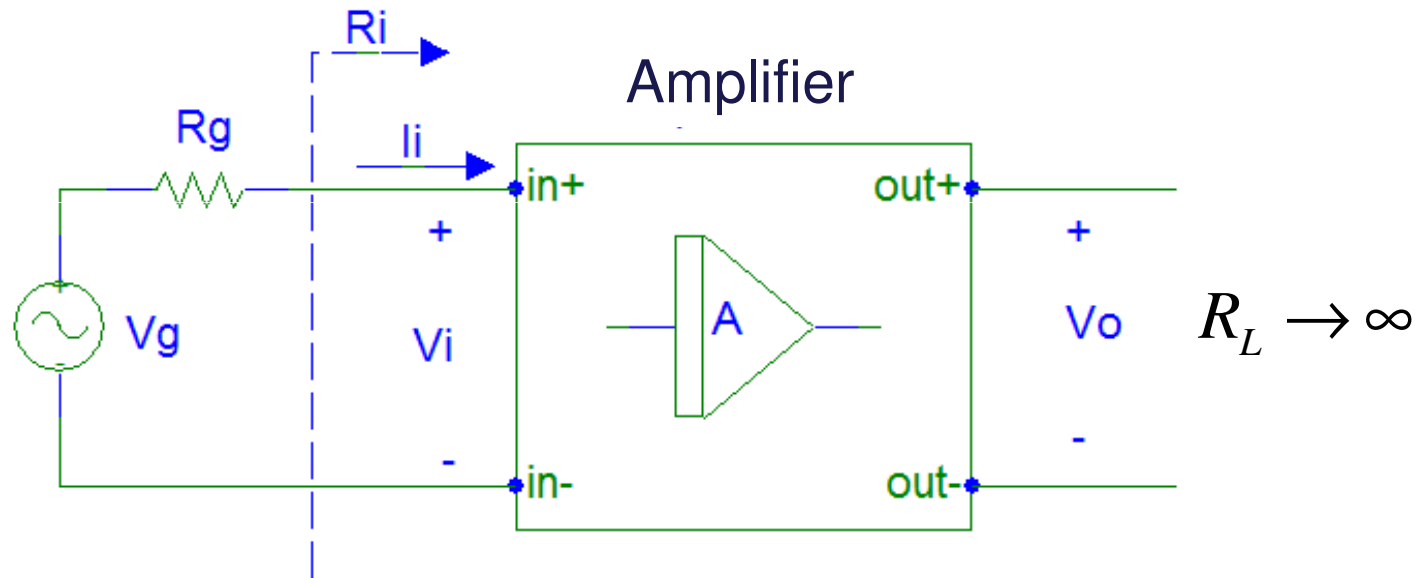


- No-load voltage gain,  $A_{vo}$

$$A_{vo} = \left. \frac{V_o}{V_i} \right|_{R_L \rightarrow \infty}$$

- No-load input resistance,  $R_i$

$$R_i = \left. \frac{V_i}{i_i} \right|_{R_L \rightarrow \infty}$$
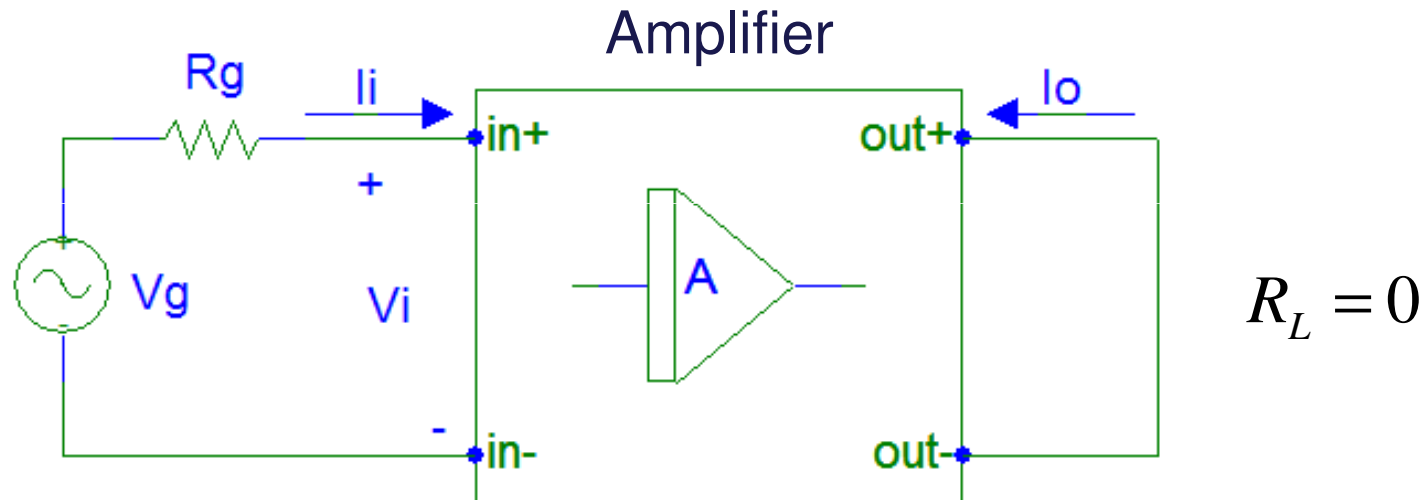
# Short circuit characteristic parameters




- Short circuit current gain,  $A_{i(sc)}$

$$A_{i(sc)} = \left. \frac{i_o}{i_i} \right|_{R_L=0}$$


- Short-circuit transconductance,  $G_m$

$$G_m = \left. \frac{i_o}{V_i} \right|_{R_L=0}$$

# Input Impedance Analysis

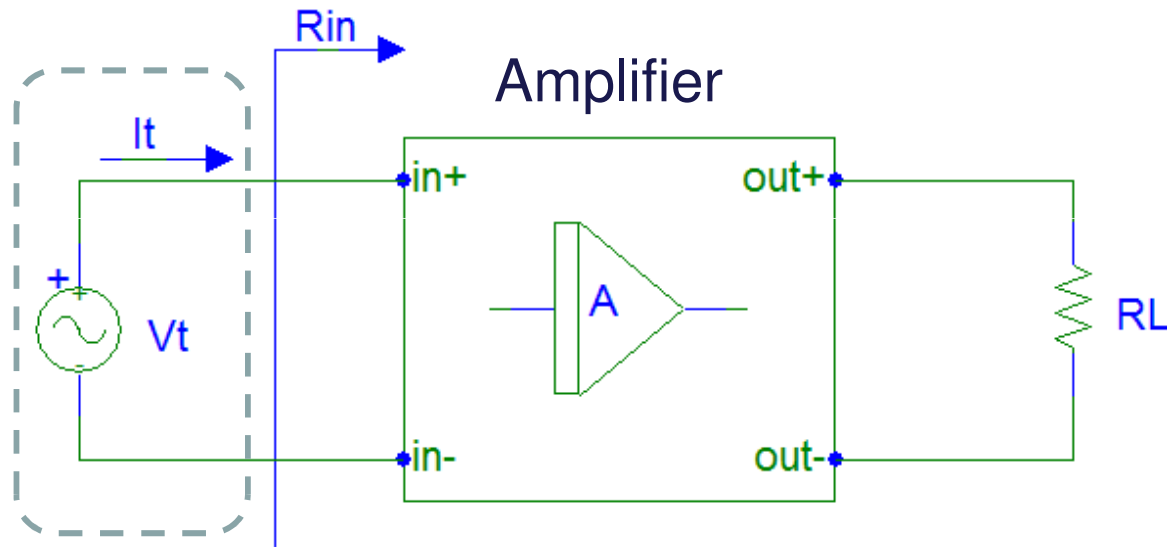


$$R_{in} = \frac{V_t}{i_t}$$

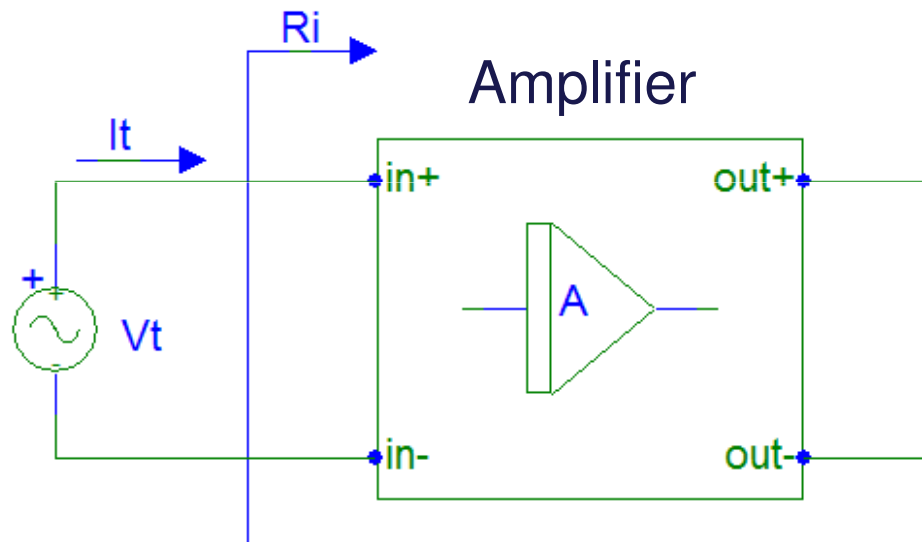


$$R_i = \left. \frac{V_t}{i_t} \right|_{R_L \rightarrow \infty}$$

# Output Impedance Analysis

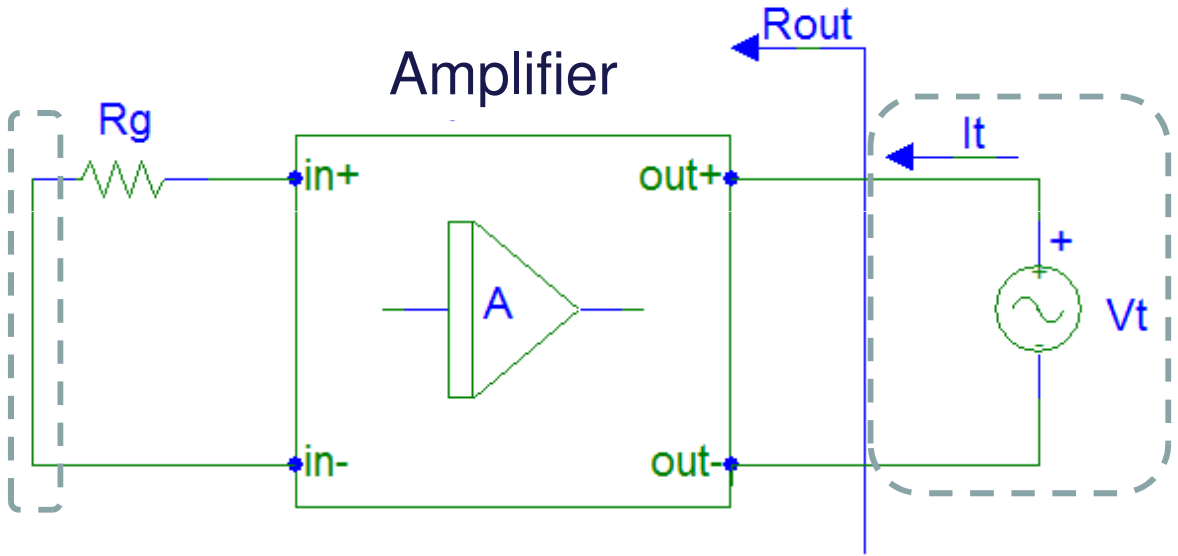



$$R_{out} = \left. \frac{V_t}{i_t} \right|_{V_g=0}$$

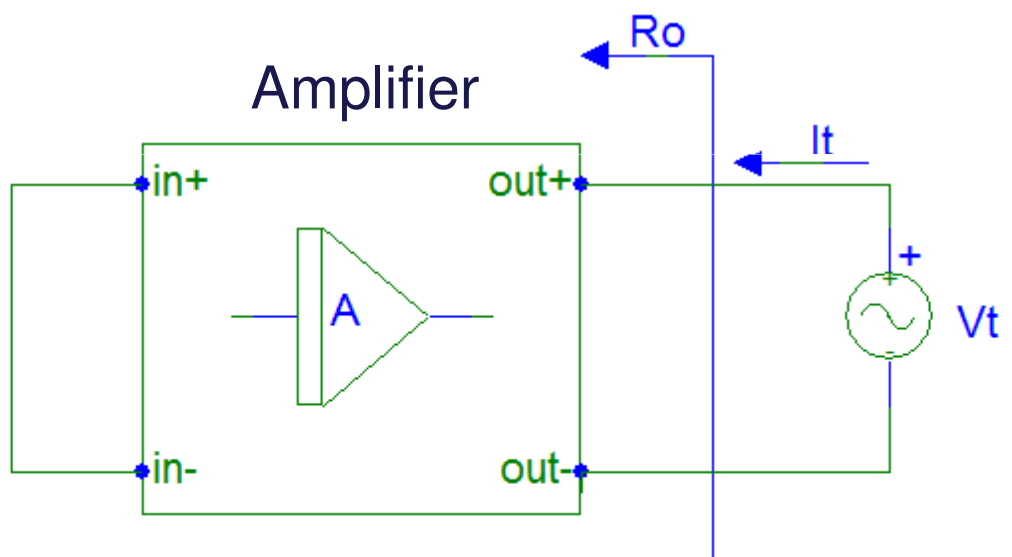



$$R_o = \left. \frac{V_t}{i_t} \right|_{V_i=0}$$

# Generalization of frequency response



## Lowpass RC

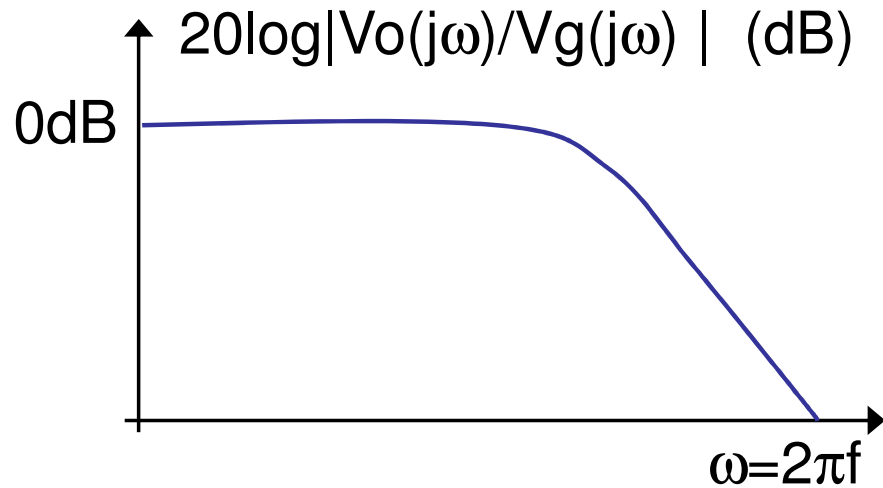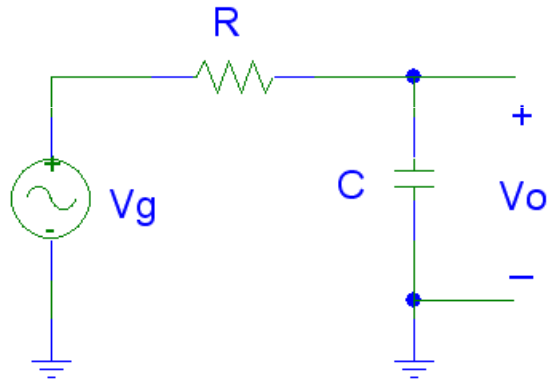

## High-pass RC

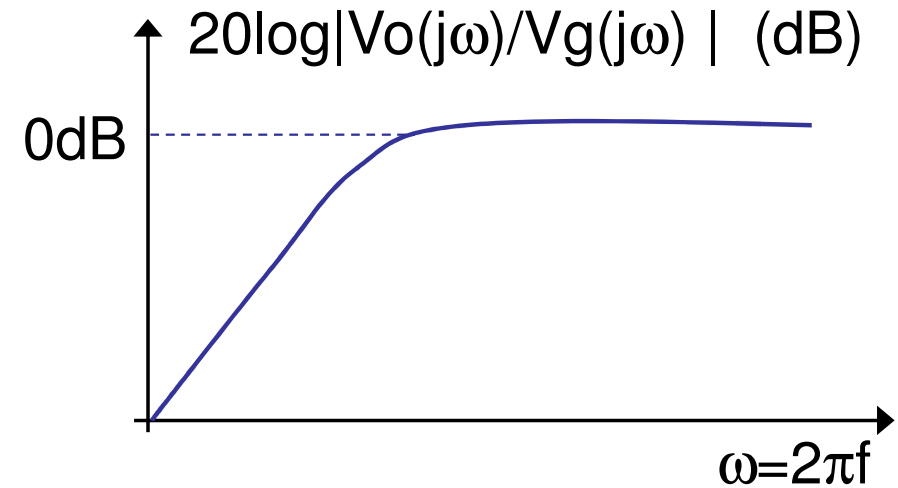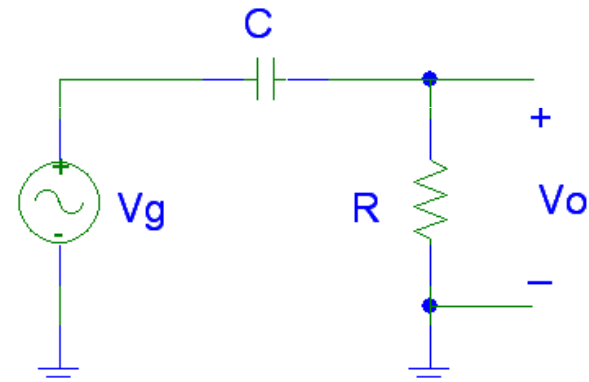

# Amplifier frequency response

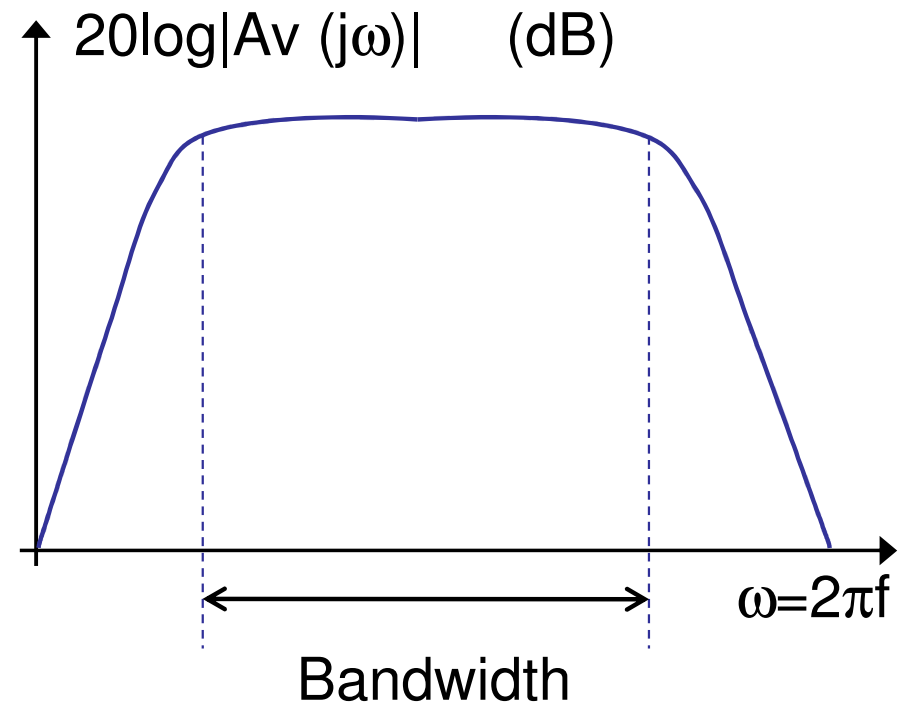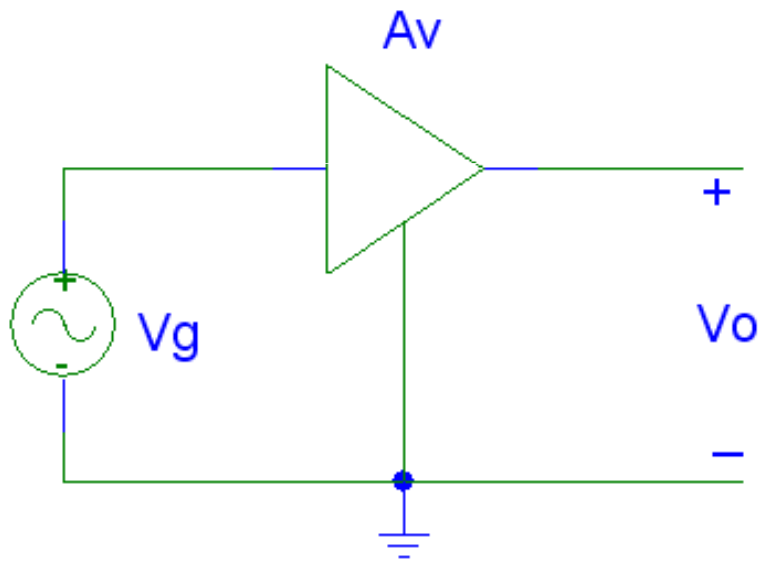

$$V_g = V_{go} \cdot \sin(\omega t)$$

$$V_o = V_{go} \cdot |A_v(j\omega)| \cdot \sin(\omega t + \phi)$$

$$A_v(j\omega) = \frac{V_o(j\omega)}{V_g(j\omega)}$$