



Universidad
Carlos III de Madrid
www.uc3m.es

Session 16

Single-stage amplification circuits (BJT)

Electronic Components and Circuits

José A. Garcia-Souto / Pablo Acedo

www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia


Single-stage amplification circuits

Transistor configurations as an amplification device

OBJECTIVES

- To review the process of analyzing the characteristic parameters of amplifiers.
- Analyze small-signal circuits for single-stage BJT amplifiers :
 - Common emitter.
 - Common-emitter with RE (emitter degeneration).
 - Common-Colector.
 - Common-Base.
- Compare the features of these configurations.

Characteristic parameters of amplifiers

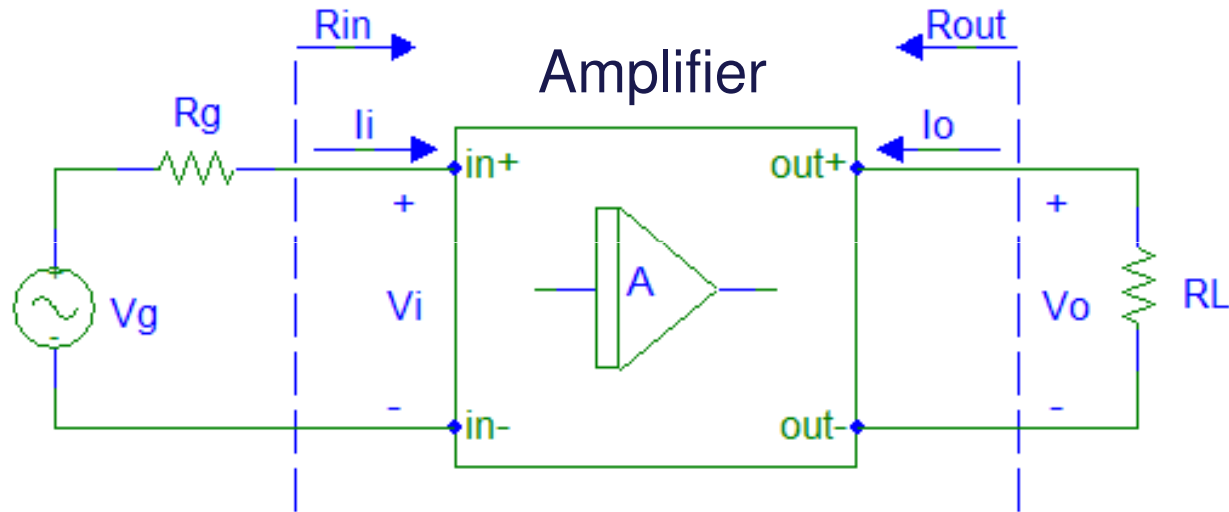

- Voltage Gain, A_v y G_v

$$A_v = \frac{V_o}{V_i} \quad G_v = \frac{V_o}{V_g} \quad A_i = \frac{i_o}{i_i}$$


- Current Gain, A_i

- Input resistance, R_{in}


$$R_{in} = \frac{V_i}{i_i} \quad R_{out} = \frac{V_o}{i_o}$$

- Output Resistance, R_{out}

Input Impedance Analysis

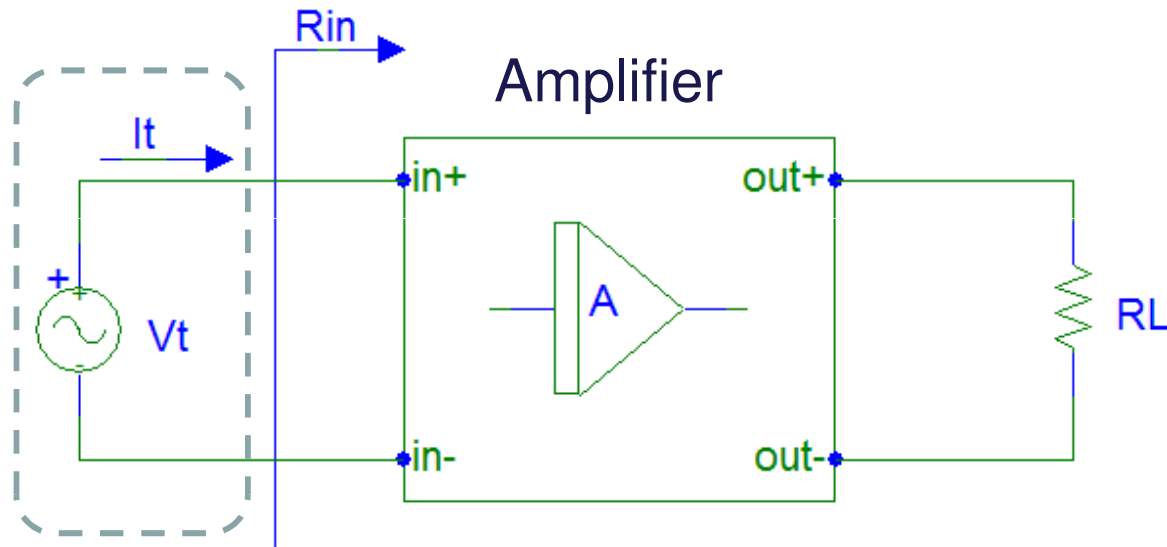


$$R_{in} = \frac{V_t}{i_t}$$

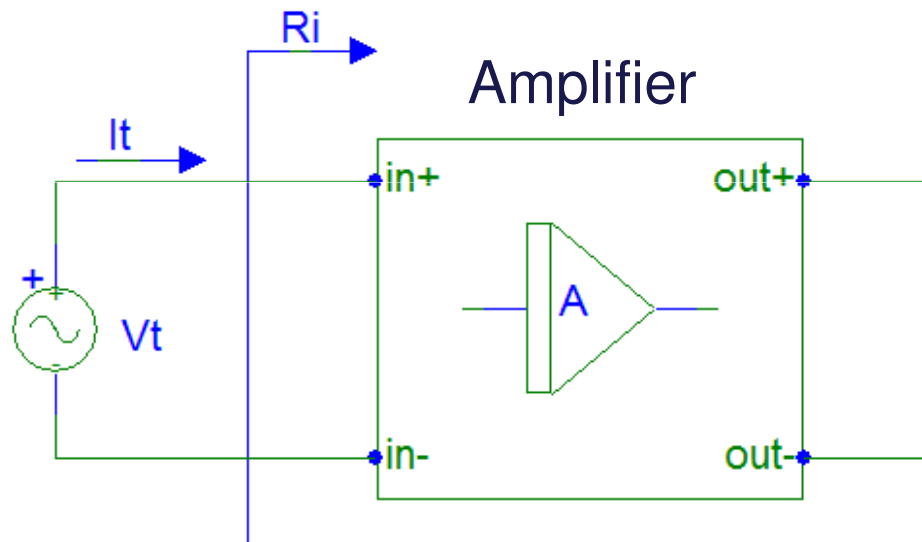


$$R_i = \left. \frac{V_t}{i_t} \right|_{R_L \rightarrow \infty}$$

Output Impedance Analysis

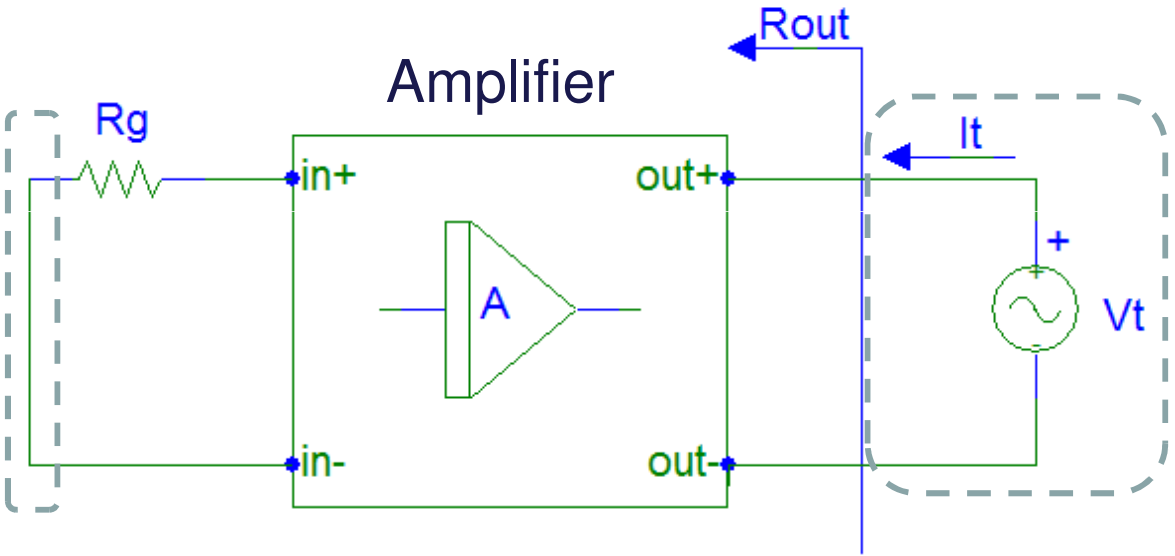





$$R_{out} = \left. \frac{V_t}{i_t} \right|_{V_g=0}$$

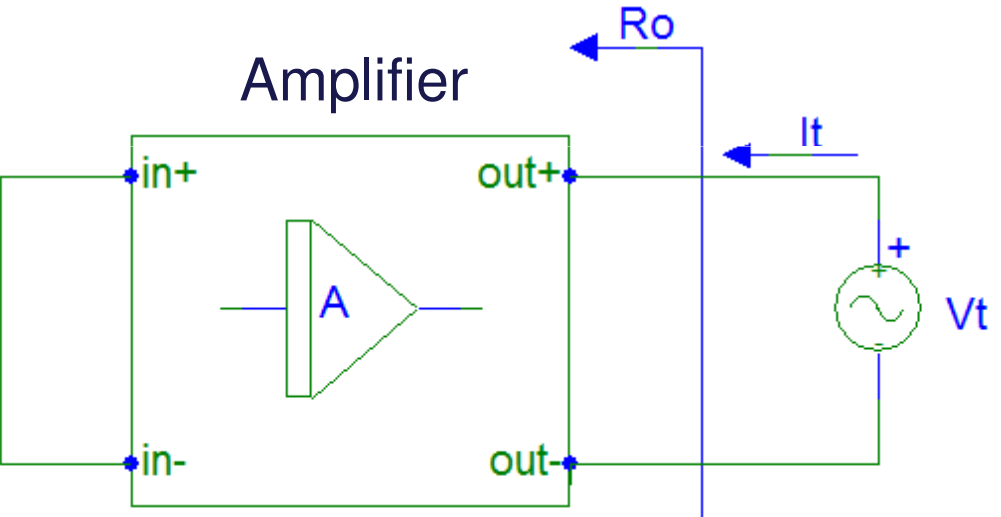


$$R_o = \left. \frac{V_t}{i_t} \right|_{V_i=0}$$

Single stage amplifiers

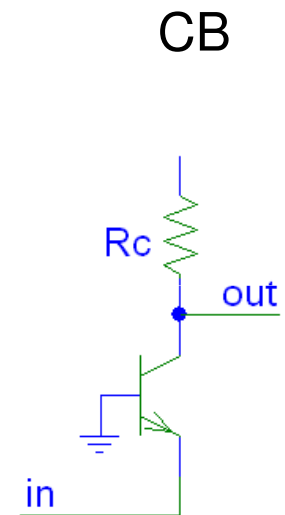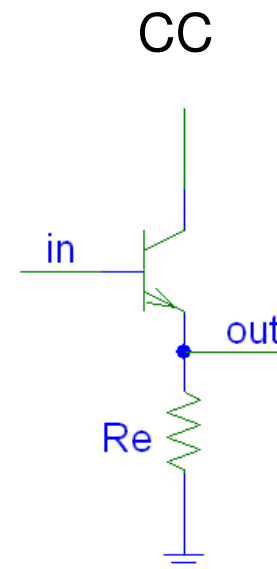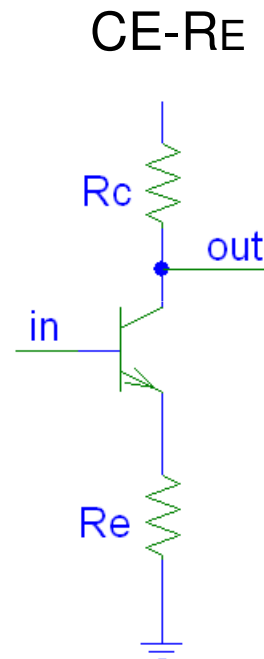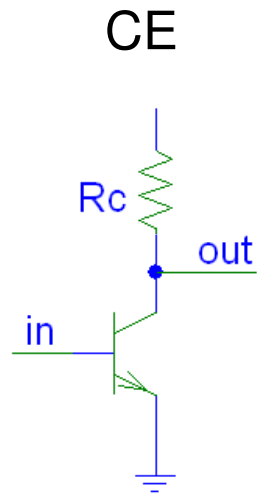- Common-emitter amplifier (CE)
- Common-emitter amplifier with R_E and emitter degeneration
- Common-collector amplifier (CC) or emitter-follower
- Common-base amplifier (CB)



Common-emitter amplifier (CE)

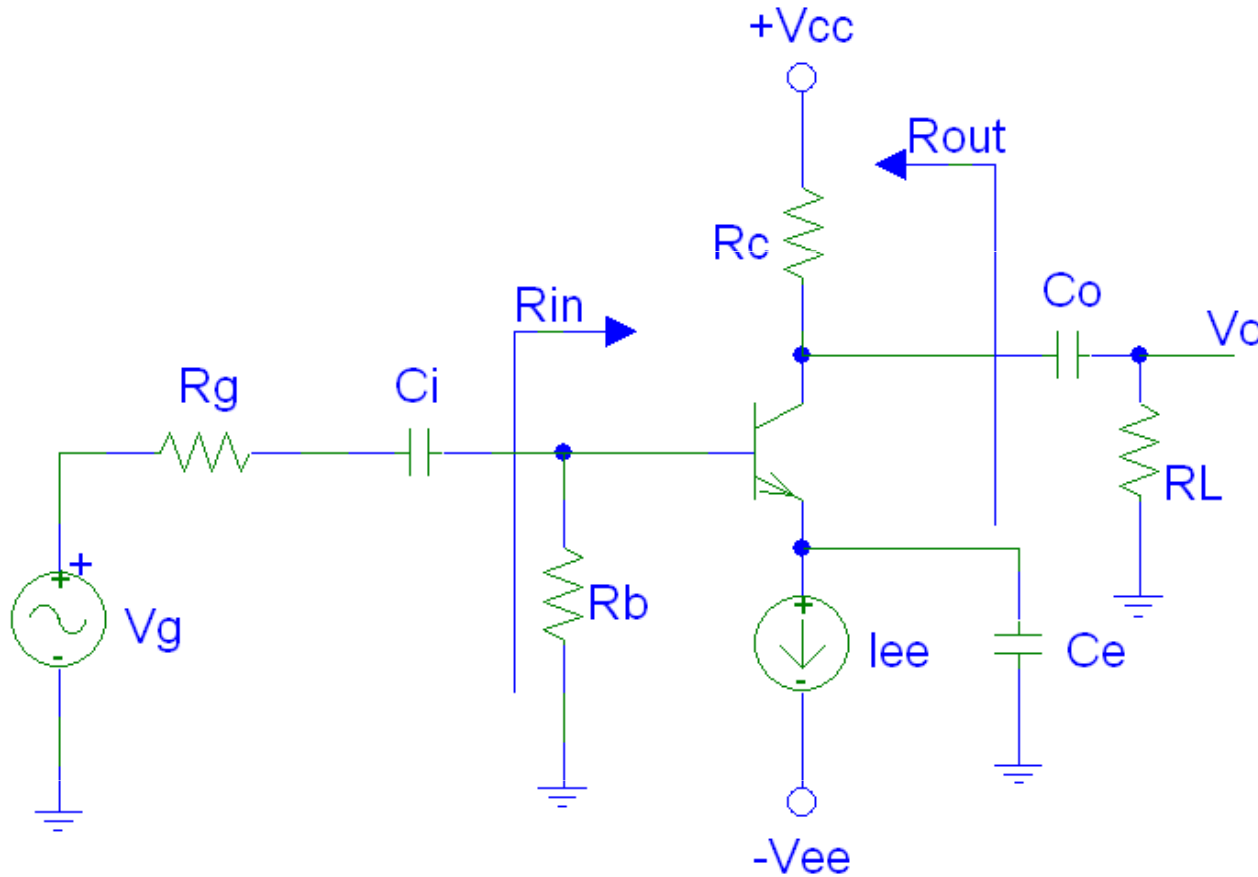

(1) BIAS ANALYSIS

$C_i, C_o, C_e \rightarrow \infty$
(Open Circuit)

$$I_E = I_{ee}$$

$$I_{CQ} \approx I_{ee}$$

EXAMPLE

- $\beta_o = 100$
- $V_A = 100 \text{ V}$
- $R_b = 100 \text{ k}\Omega$
- $R_c = 8 \text{ k}\Omega$
- $R_L = 100 \text{ k}\Omega$
- $V_{cc} = V_{ee} = 10 \text{ V}$
- $I_{ee} = 1 \text{ mA}$


$$I_{CQ} \approx 1 \text{ mA}$$

$$g_m = 40 \text{ mA/V}$$

$$r_\pi = 2,5 \text{ k}\Omega$$

$$r_o = 100 \text{ k}\Omega$$


Common-emitter (Impedances)

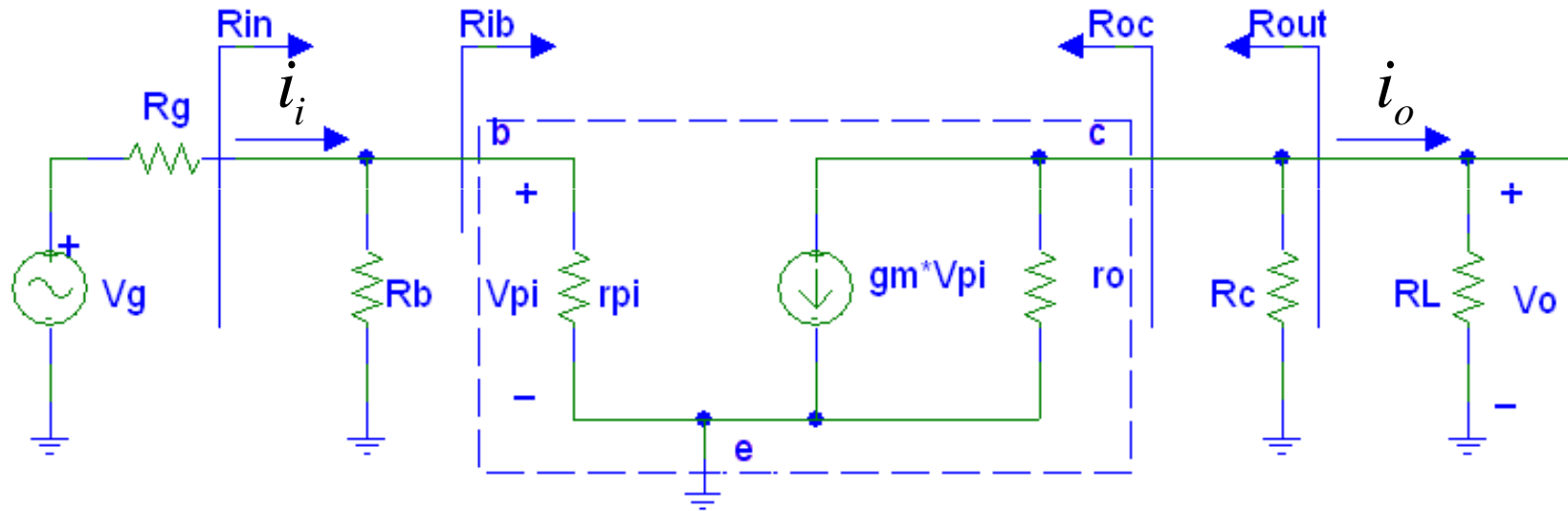

(2) SMALL SIGNAL ANALYSIS

$$\begin{aligned}
 R_{ib} &= r_{\pi} & R_{in} &= R_b // r_{\pi} & R_{in} \Big|_{R_b \gg r_{\pi}} &\approx r_{\pi} \\
 R_{oc} &= r_o & R_{out} &= R_c // r_o & R_{out} \Big|_{r_o \gg R_c} &\approx R_c
 \end{aligned}$$

Common-emitter (Small Signal)

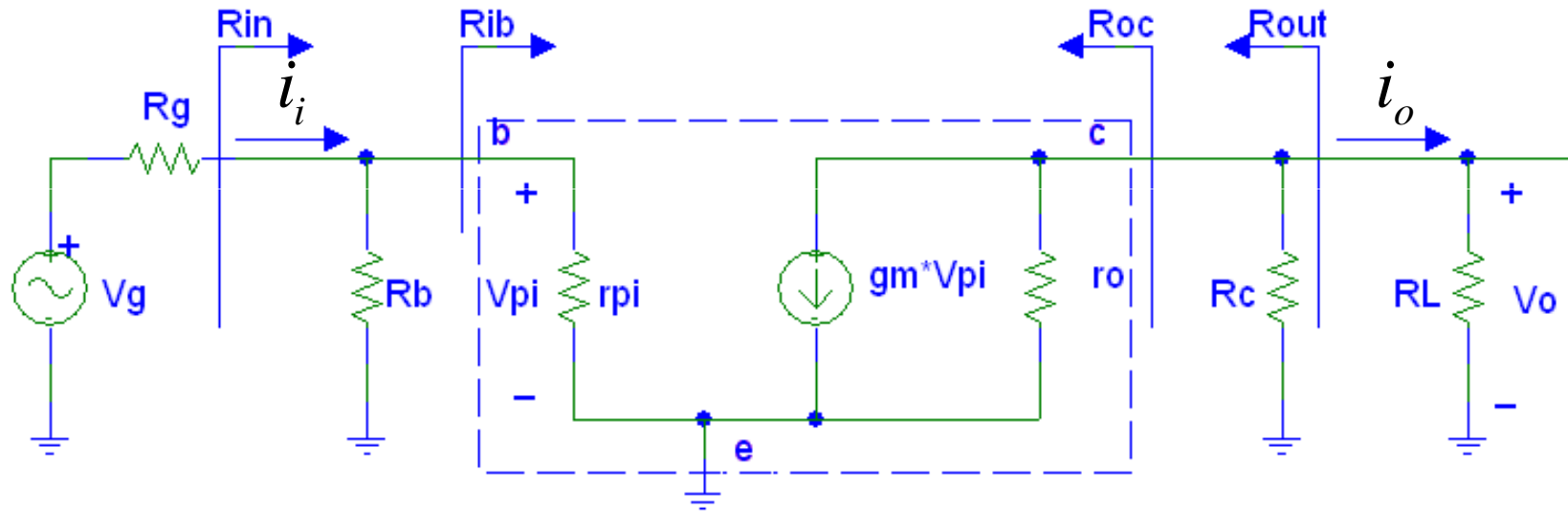

(2) SMALL SIGNAL ANALYSIS


$$i_i = \frac{V_g}{R_g + R_{in}}$$

$$V_\pi = V_g \frac{R_{in}}{R_g + R_{in}}$$

$$i_o = -g_m V_\pi \frac{R_{out}}{R_L + R_{out}}$$

$$V_o = -g_m V_\pi (r_o \parallel R_c \parallel R_L)$$

Common-emitter (Gain)

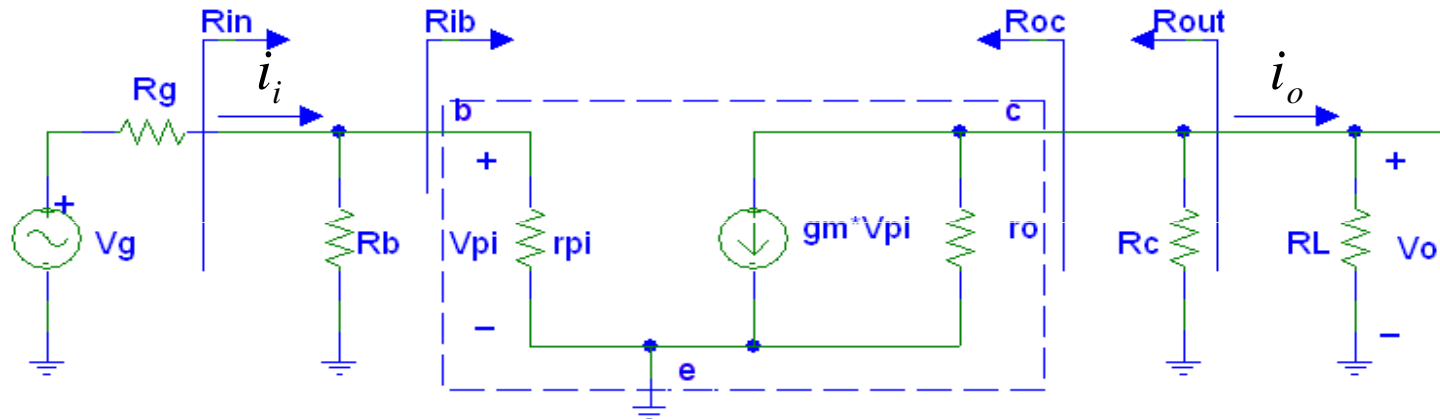

$$A_v = \frac{V_o}{V_\pi} = -g_m (r_o \parallel R_c \parallel R_L)$$

$$G_v = \frac{V_o}{V_g} = -g_m (r_o \parallel R_c \parallel R_L) \frac{R_{in}}{R_g + R_{in}}$$


$$A_i = \frac{i_o}{i_i} = -g_m \frac{R_{out}}{R_L + R_{out}} R_{in}$$

$$A_{vo} \Big|_{r_o \gg R_c} \approx -g_m R_c$$

$$G_v \Big|_{R_b \gg r_\pi} \approx -\frac{\beta_o}{R_g + r_\pi} (r_o \parallel R_c \parallel R_L)$$

$$A_{i(sc)} \Big|_{R_b \gg r_\pi} = -\beta_o$$


Common-emitter amplifier with RE

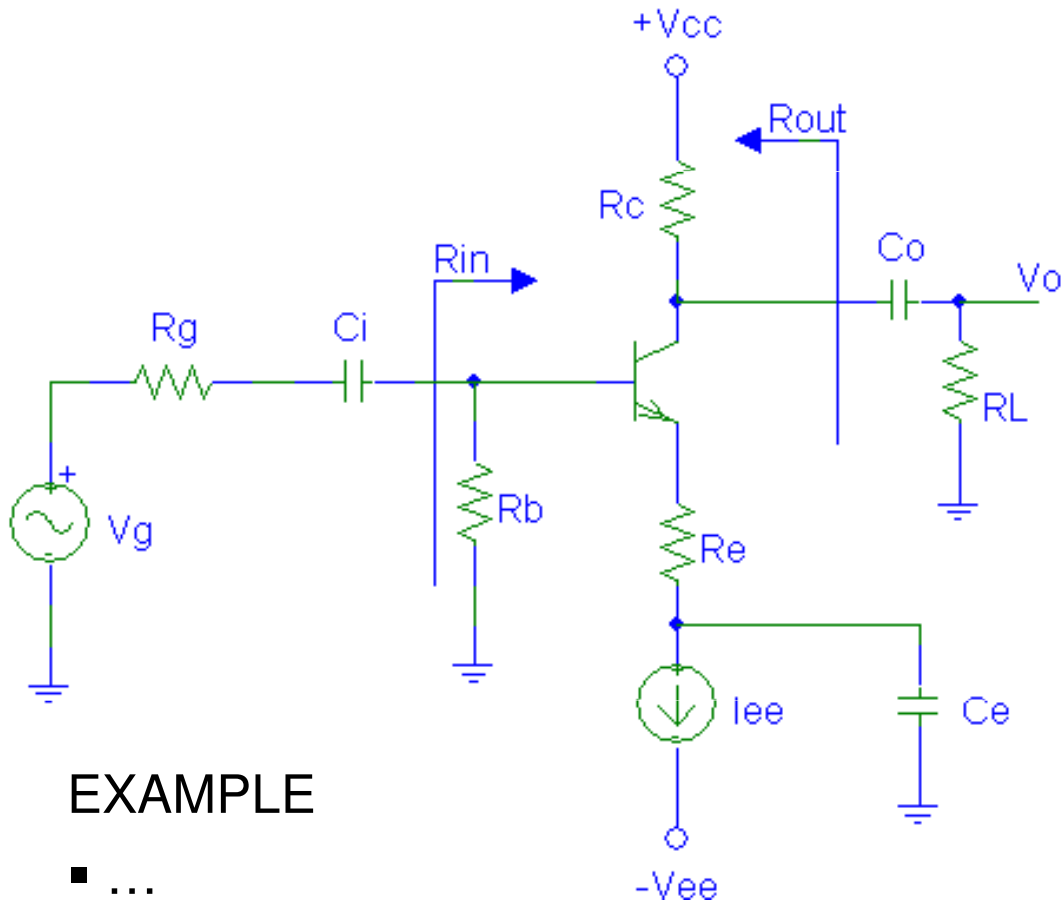

EXAMPLE


- ...
- $R_e = 1 \text{ k}\Omega$

$$I_{CQ} \approx 1 \text{ mA}$$

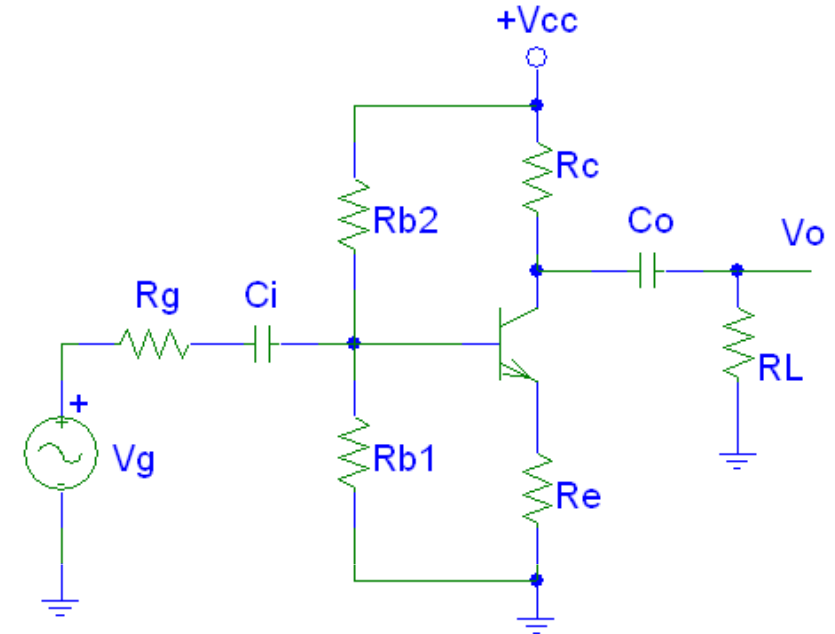

$$R_b = R_{b1} // R_{b2}$$

Common-emitter with R_E (Impedance)

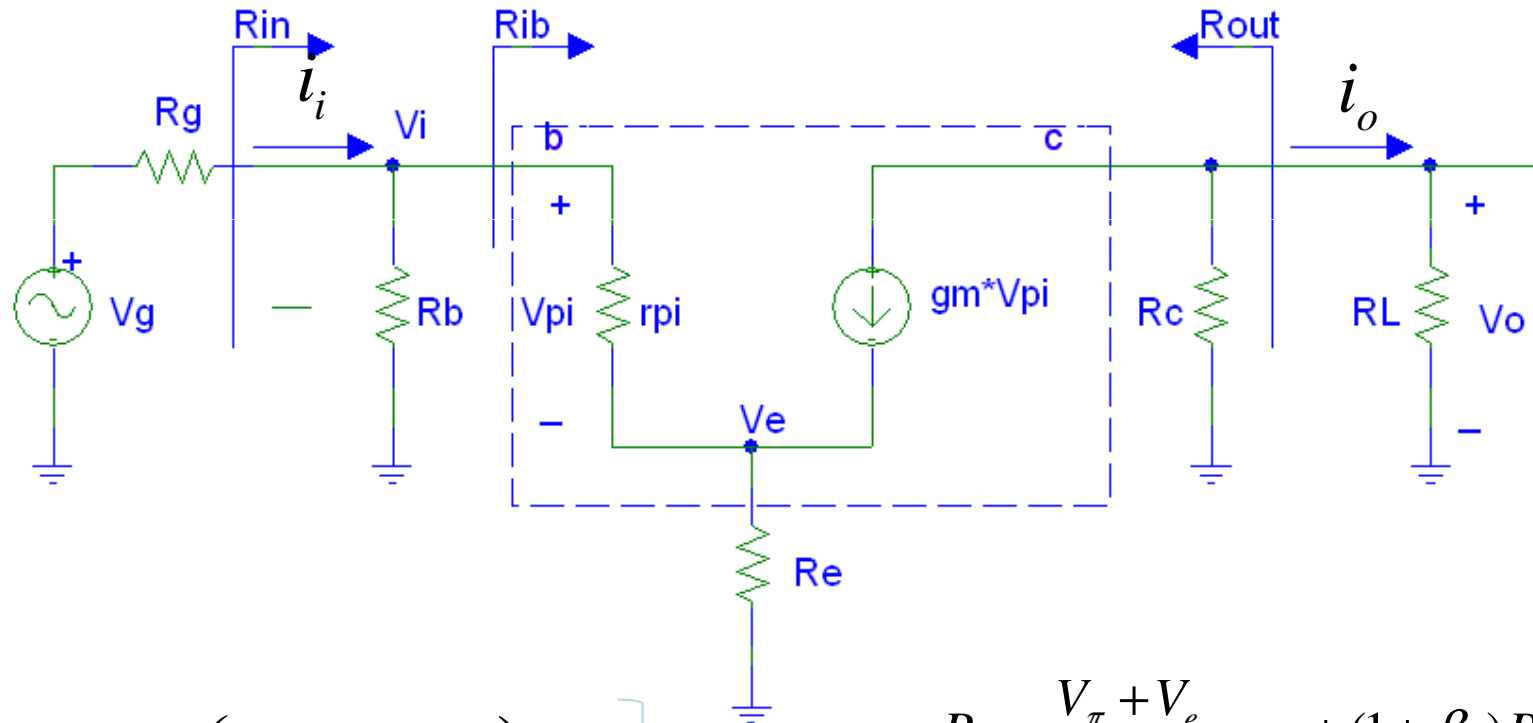

$$V_e = \left(\frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) \cdot R_e$$


$$V_i = V_{\pi} + V_e$$

$$R_{ib} = \frac{V_{\pi} + V_e}{V_{\pi}/r_{\pi}} = r_{\pi} + (1 + \beta_o) R_e$$

$$R_{in} = R_b \parallel [r_{\pi} + (1 + \beta_o) R_e]$$

$$R_{out} \Big|_{r_o \gg R_c} \approx R_c$$

Common-emitter with R_E (Small Signal)

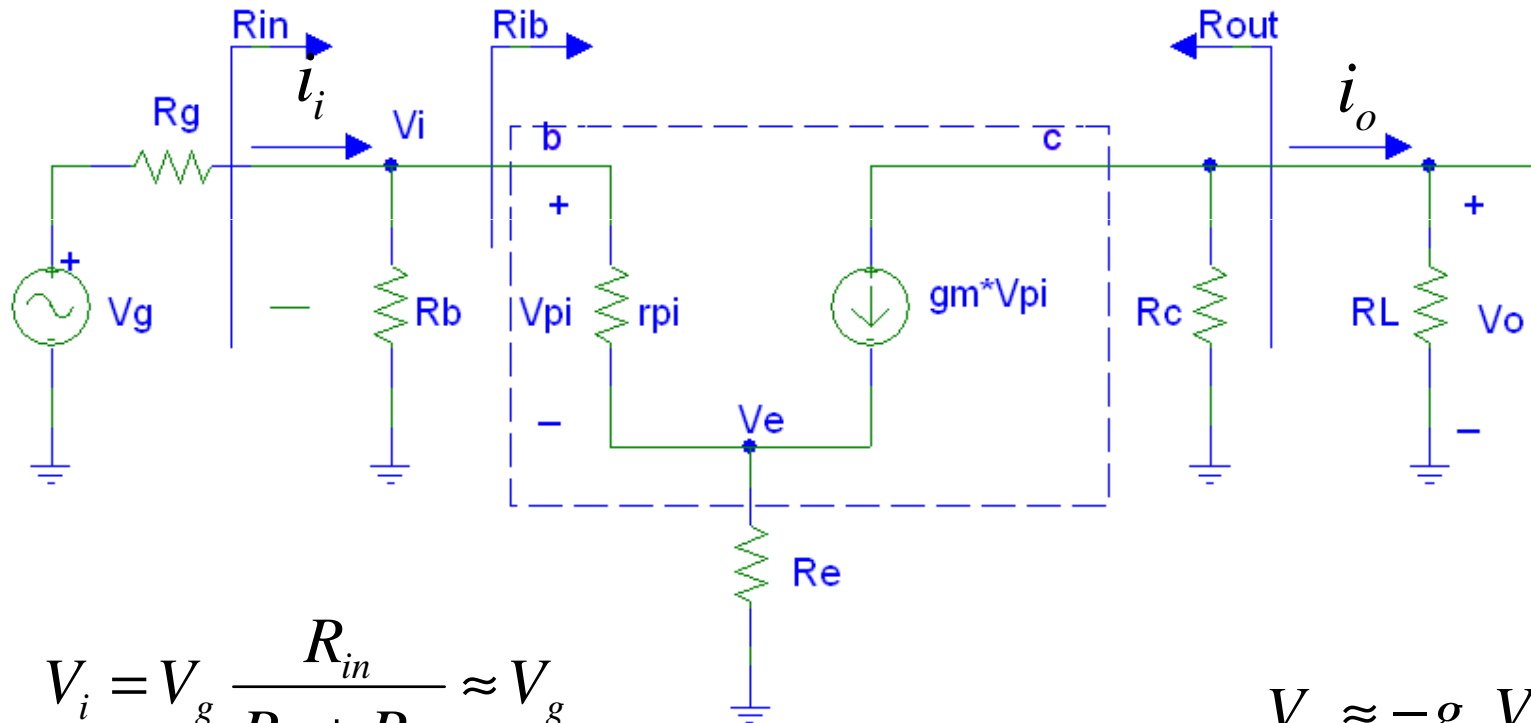

$$V_i = V_g \frac{R_{in}}{R_g + R_{in}} \approx V_g$$

$$V_e = \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) \cdot R_e$$

$$V_i = V_\pi + V_e$$


$$\frac{V_\pi}{V_i} \approx \frac{1}{1 + g_m R_e}$$

$$V_o \approx -g_m V_\pi (R_c \parallel R_L)$$

$$i_i = \frac{V_g}{R_g + R_{in}}$$

$$i_o = -g_m V_\pi \frac{R_{out}}{R_L + R_{out}}$$

Common-emitter with R_E (Gain)

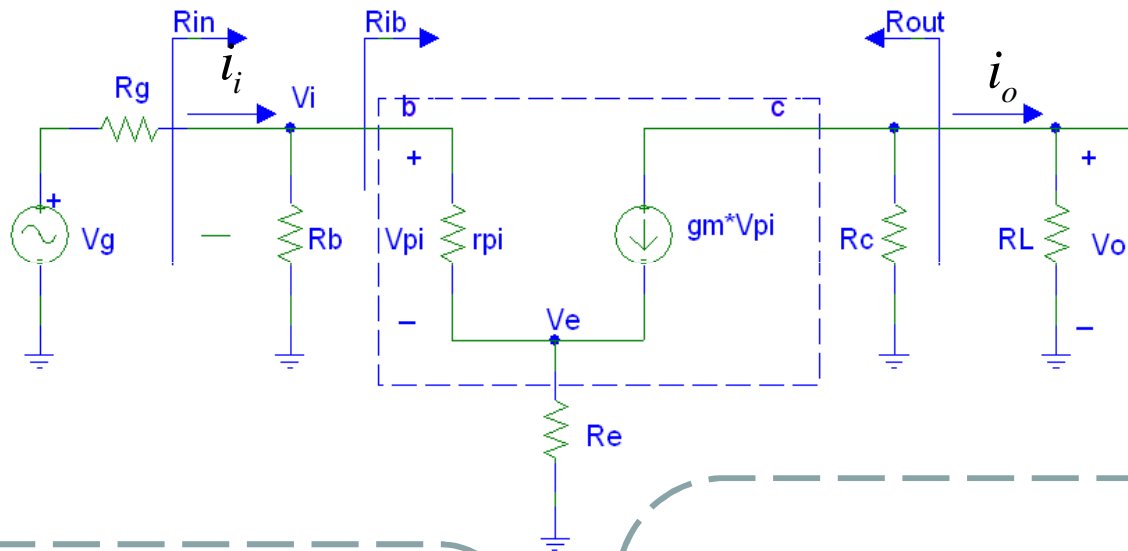

$$A_v = \frac{V_o}{V_i} = -\frac{\beta_o (R_c \parallel R_L)}{r_{\pi} + (1 + \beta_o) \cdot R_e}$$


$$A_i = \frac{i_o}{i_i} = -\beta_o \frac{R_c}{R_L + R_c} \frac{R_b + R_{ib}}{R_b}$$

$$G_v \Big|_{\substack{R_g \ll R_{in} \\ r_{\pi} \ll \beta_o R_e}} \approx -\frac{(R_c \parallel R_L)}{R_e} \approx -\frac{R_c}{R_e} \cdot \frac{R_L}{R_c + R_L}$$

$$A_{vo} = -\frac{\beta_o R_c}{r_{\pi} + (1 + \beta_o) R_e} \approx -\frac{g_m R_c}{1 + g_m R_e}$$

$$A_{i(sc)} \Big|_{\substack{R_g \ll R_{in} \\ R_b \gg R_{ib}}} \approx -\beta_o$$


Common-collector amplifier (CC)

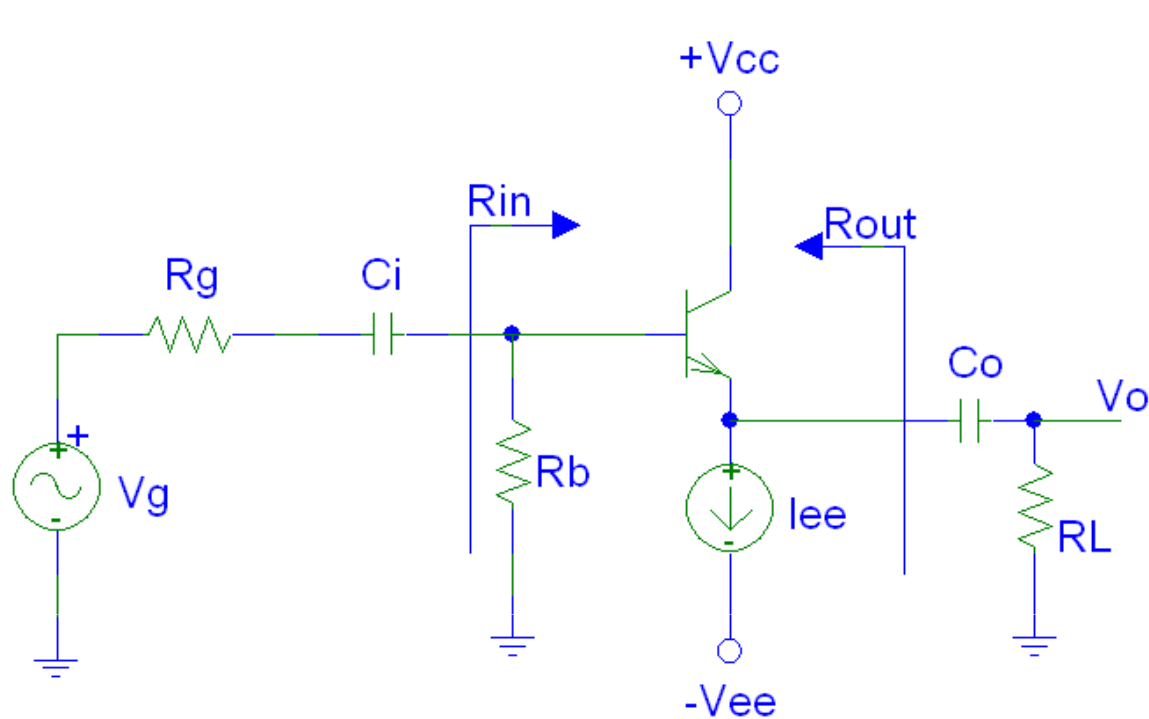

EXAMPLE

▪ ...


$$I_{CQ} \approx 1\text{mA}$$

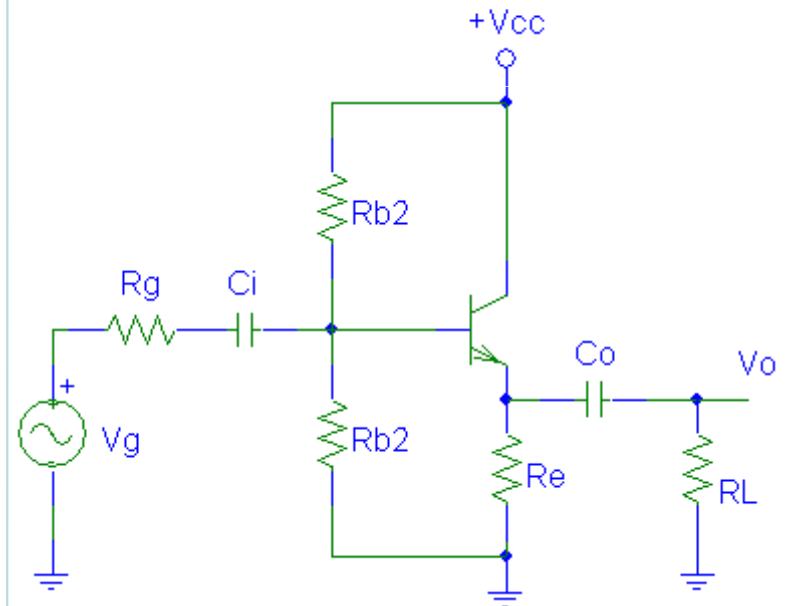

$$R_b = R_{b1} // R_{b2}$$

$$R_{EMITTER} = R_e // R_L$$

Common-collector (Impedances)

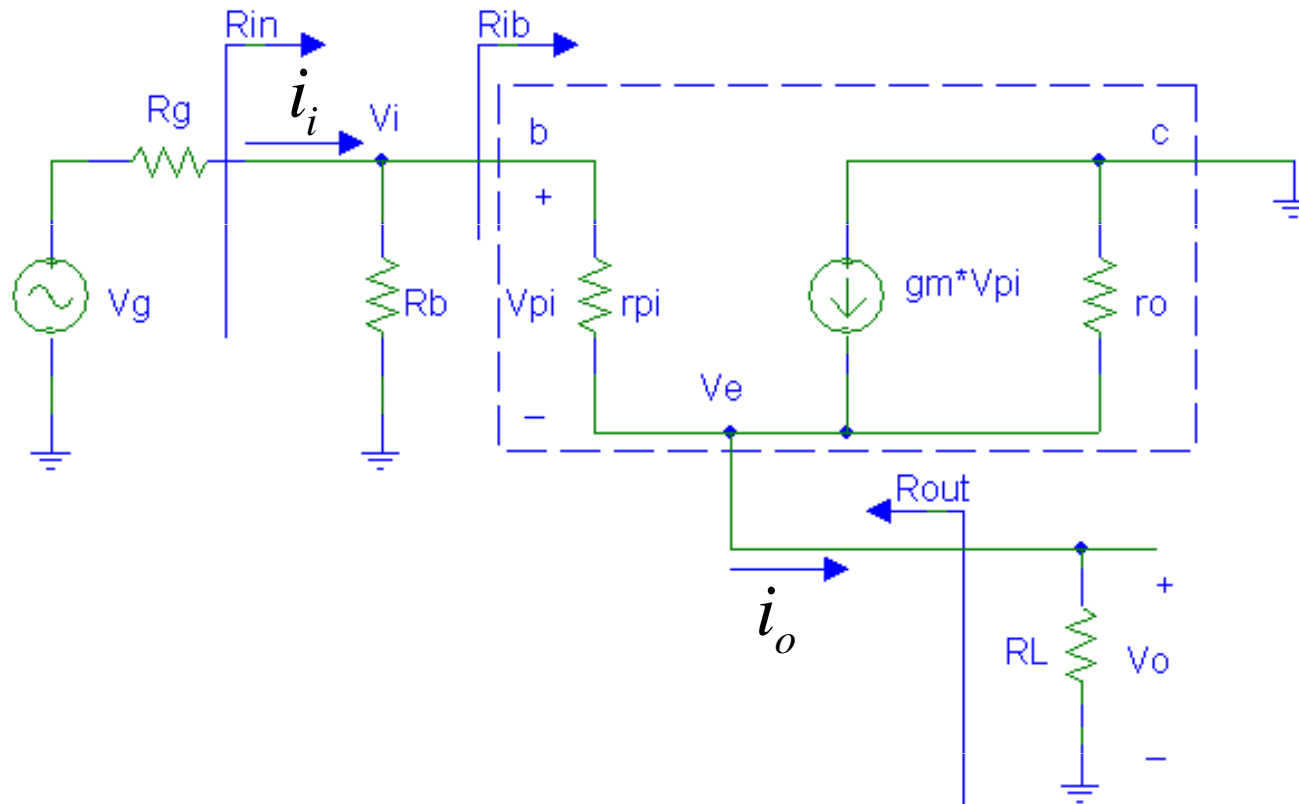


$$R_{EM} = r_o \parallel R_L$$

$$R_{out} = r_o \parallel \frac{r_\pi + (R_b \parallel R_g)}{1 + \beta_o} \approx \frac{r_\pi + (R_b \parallel R_g)}{1 + \beta_o}$$

$$R_{ib} = \frac{V_\pi + V_e}{V_\pi / r_\pi} = r_\pi + (1 + \beta_o) \cdot R_{EM}$$

Common-collector (Small Signal)

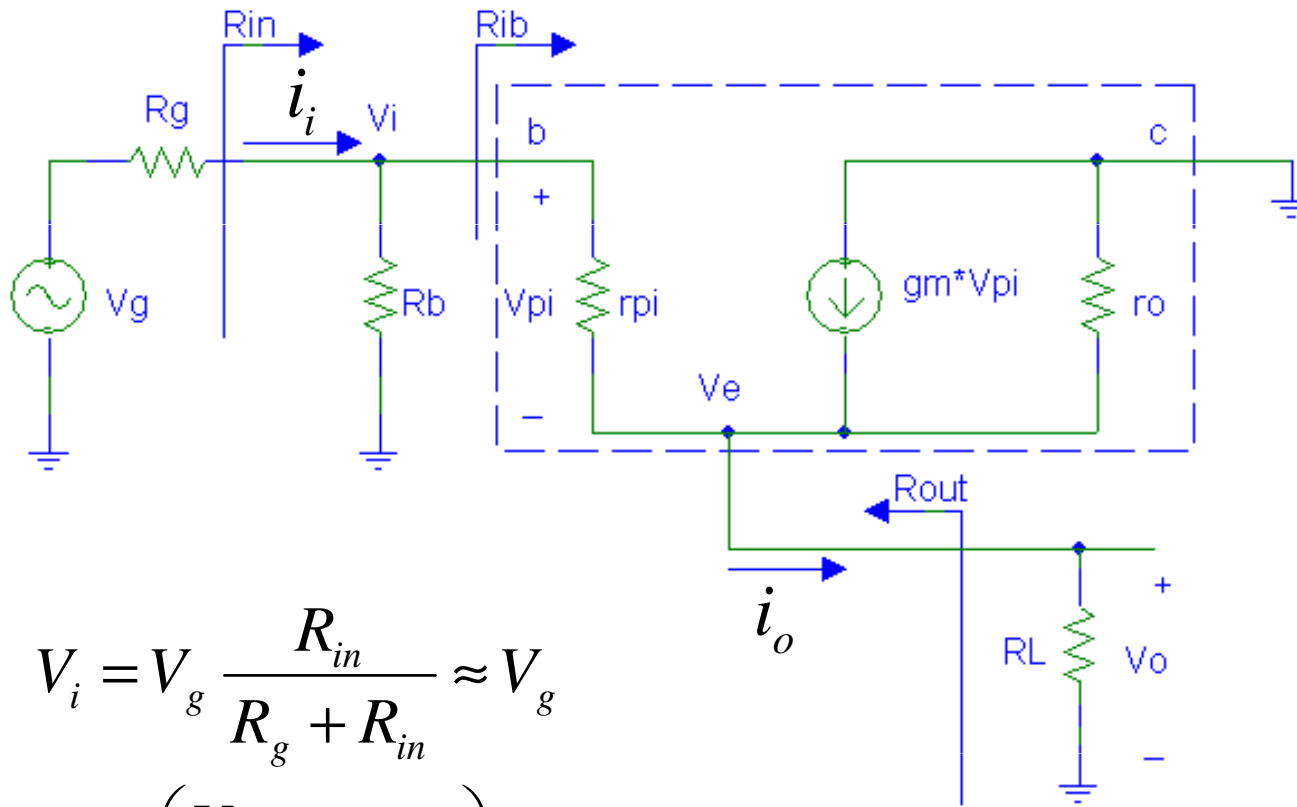

$$R_{EM} = r_o \parallel R_L$$

$$V_i = V_g \frac{R_{in}}{R_g + R_{in}} \approx V_g$$

$$V_e = \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) \cdot R_{EM}$$


$$V_i = V_\pi + V_e$$

$$V_o = V_e$$

$$i_i = \frac{V_g}{R_g + R_{in}}$$

$$i_o = \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) \left(\frac{r_o}{r_o + R_L} \right)$$

Common-collector (Gain)

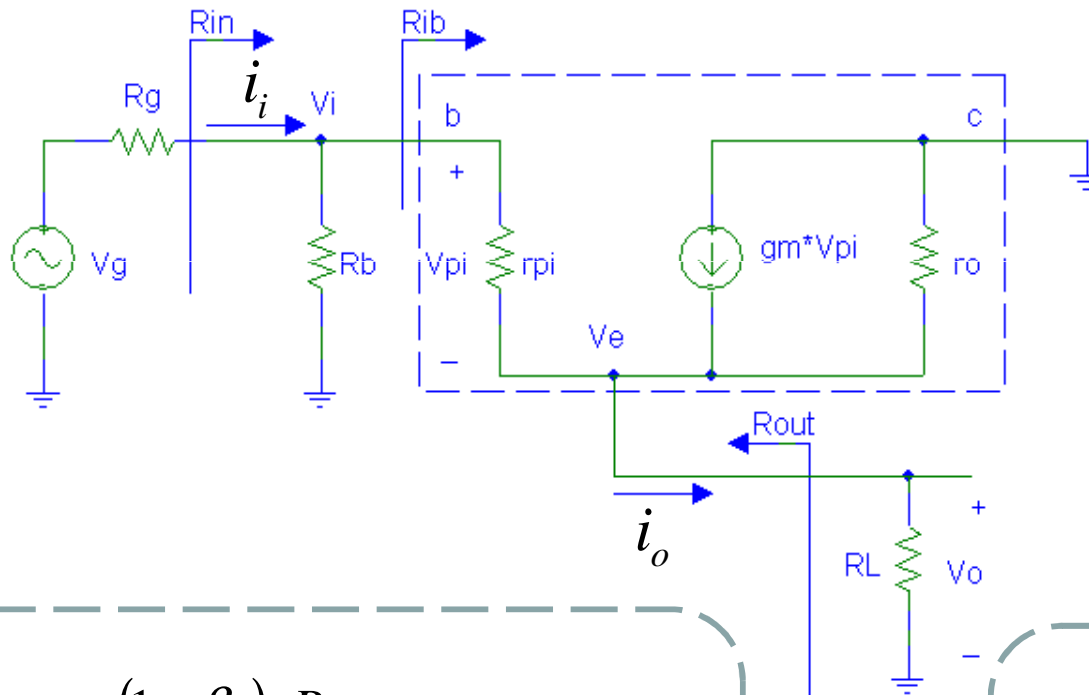


$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta_o) \cdot R_{EM}}{r_\pi + (1 + \beta_o) \cdot R_{EM}}$$

$$A_i = \frac{i_o}{i_i} = (1 + \beta_o) \frac{r_o}{r_o + R_L} \frac{R_b + R_{ib}}{R_b}$$

$$G_v = \frac{V_o}{V_g} \approx 1$$

$$A_{i(sc)} \Big|_{\substack{R_g \ll R_{in} \\ R_b \gg R_{ib}}} \approx 1 + \beta_o$$


Common-base amplifier (CB)

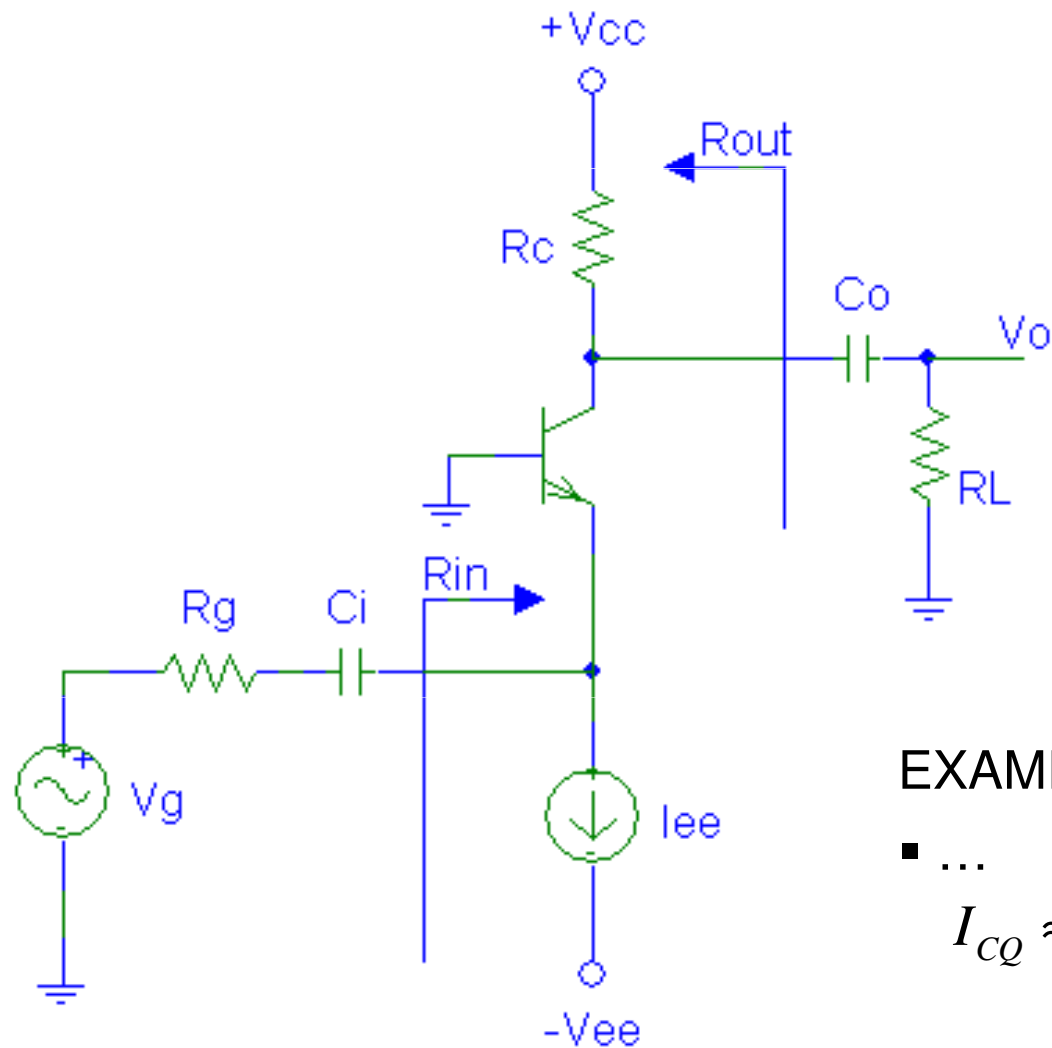

EXAMPLE

- ...
 $I_{CQ} \approx 1mA$

Common-base (Small Signal)

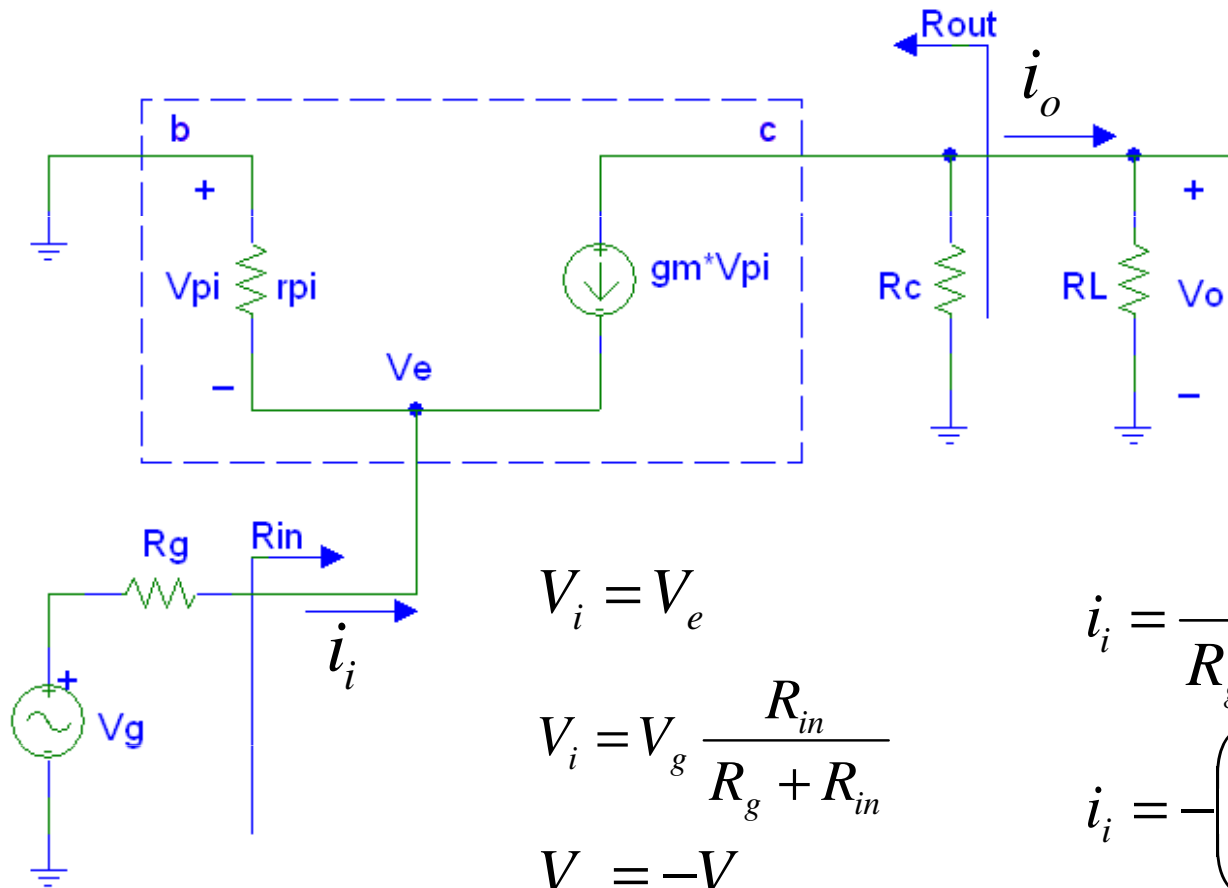

$$V_i = V_e$$

$$V_i = V_g \frac{R_{in}}{R_g + R_{in}}$$

$$V_e = -V_{\pi}$$


$$V_o \approx -g_m V_{\pi} (R_c \parallel R_L)$$

$$i_i = \frac{V_g}{R_g + R_{in}}$$

$$i_i = -\left(\frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right)$$

$$i_o = -g_m V_{\pi} \frac{R_{out}}{R_L + R_{out}}$$

Common-base (Characteristics)

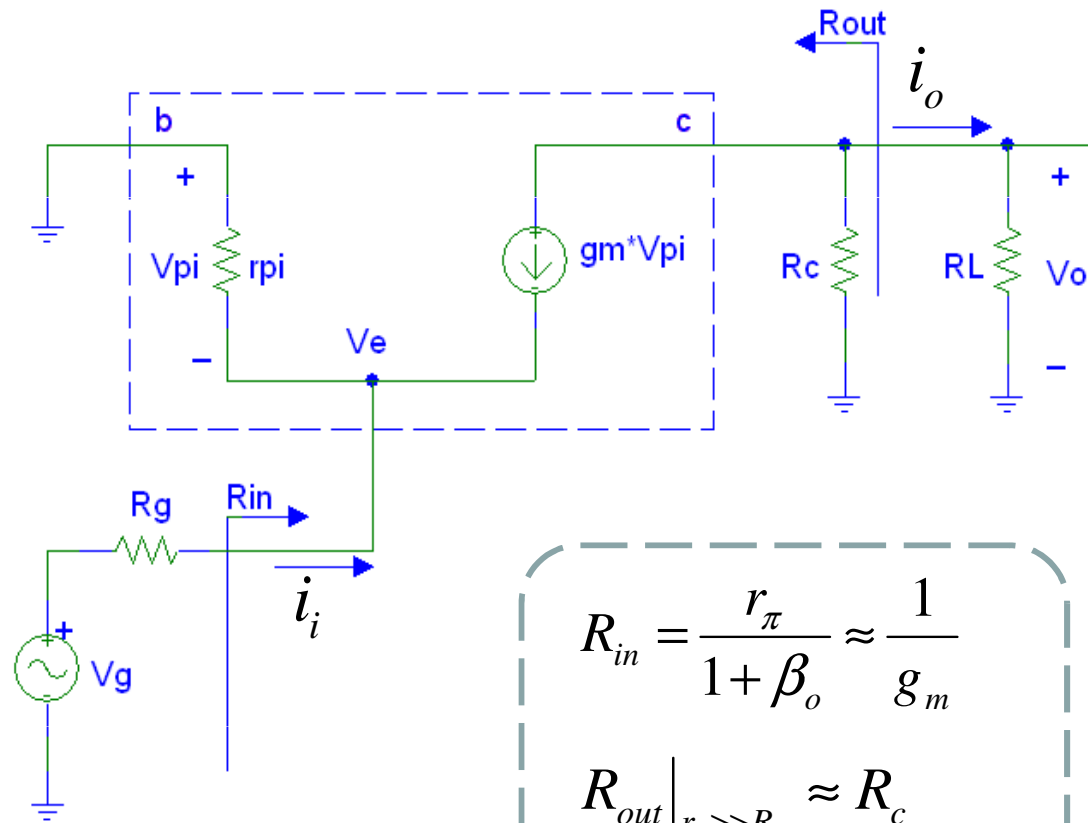

$$A_v = \frac{V_o}{V_i} = +g_m (R_c // R_L)$$

$$R_{in} = \frac{r_{\pi}}{1 + \beta_o} \approx \frac{1}{g_m}$$

$$R_{out} \Big|_{r_o \gg R_c} \approx R_c$$

$$A_{vo} = +g_m R_c$$

$$A_{i(sc)} = \alpha$$

Comparison


Stage	R _{in}	R _{out}	A _v	A _{i(sc)}
CE	$R_b // r_\pi \approx r_\pi$	$R_c // r_o$	★ $-g_m (r_o // R_c // R_L)$	$-g_m R_{in} \approx -\beta_o$
CE-RE	★ $R_b // [r_\pi + (1 + \beta_o) R_e]$	R_c	★ $-\frac{\beta_o (R_c // R_L)}{r_\pi + (1 + \beta_o) R_e}$	$-\beta_o \frac{R_b + R_{ib}}{R_b} \approx -\beta_o$
CC	★ $R_b // [r_\pi + (1 + \beta_o) R_{EM}]$	★ $\frac{r_\pi + (R_b // R_g)}{1 + \beta_o}$	$\frac{(1 + \beta_o) \cdot R_{EM}}{r_\pi + (1 + \beta_o) \cdot R_{EM}} \approx 1$	$(1 + \beta_o) \frac{R_b + R_{ib}}{R_b}$
CB	$\frac{r_\pi}{1 + \beta_o} \approx \frac{1}{g_m}$ ★	R_c	$+g_m (R_c // R_L)$	$\frac{\beta_o}{(1 + \beta_o)} = \alpha$

$$G_v = A_v \frac{R_{in}}{R_g + R_{in}}$$

$$G_v|_{CE}^{max} \approx -g_m r_o = -\frac{V_A}{V_T}$$

$$G_v|_{CC}^{max} \approx 1$$

ANNEX 1: Characteristics CE

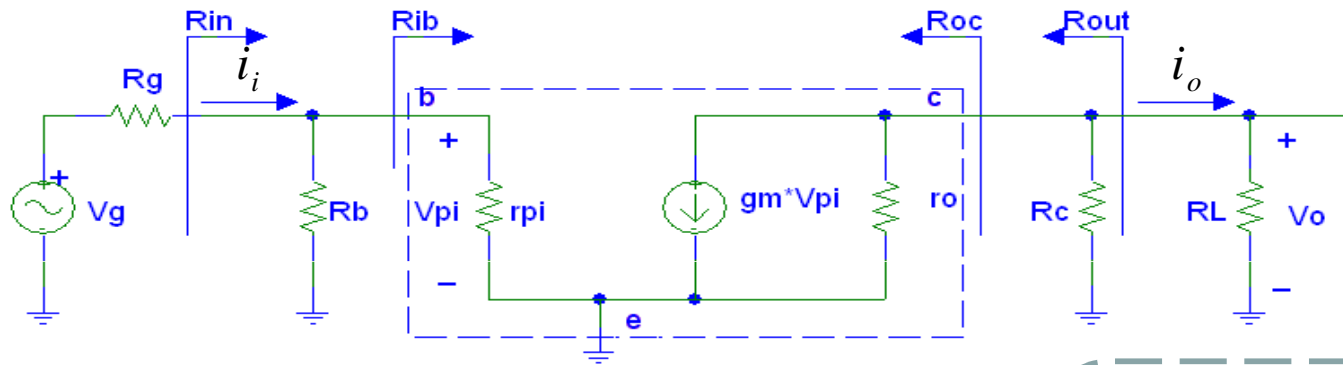

$$R_{ib} = r_{\pi}$$

$$R_{oc} = r_o$$

$$R_{in} = R_b \parallel r_{\pi} \quad R_{in} \Big|_{R_b \gg r_{\pi}} \approx r_{\pi}$$

$$R_{out} = R_c \parallel r_o \quad R_{out} \Big|_{r_o \gg R_c} \approx R_c$$

$$A_v = \frac{V_o}{V_{\pi}} = -g_m (r_o \parallel R_c \parallel R_L)$$

$$A_{vo} = -g_m (r_o \parallel R_c)$$

$$A_{vo} \Big|_{r_o \gg R_c} \approx -g_m R_c$$

$$G_v = \frac{V_o}{V_g} = -g_m (r_o \parallel R_c \parallel R_L) \frac{R_{in}}{R_g + R_{in}}$$

$$G_v \Big|_{R_b \gg r_{\pi}} \approx -\frac{\beta_o}{R_g + r_{\pi}} (r_o \parallel R_c \parallel R_L)$$


$$G_v \Big|_{\substack{R_g \ll r_{\pi} \\ R_b \gg r_{\pi}}} \approx -g_m (r_o \parallel R_c \parallel R_L)$$

$$A_i = \frac{i_o}{i_i} = -g_m \frac{R_{out}}{R_L + R_{out}} R_{in}$$

$$A_{i(sc)} = -g_m R_{in}$$

$$A_{i(sc)} \Big|_{R_b \gg r_{\pi}} = -\beta_o$$

ANNEX 2: Characteristics CE with R_E

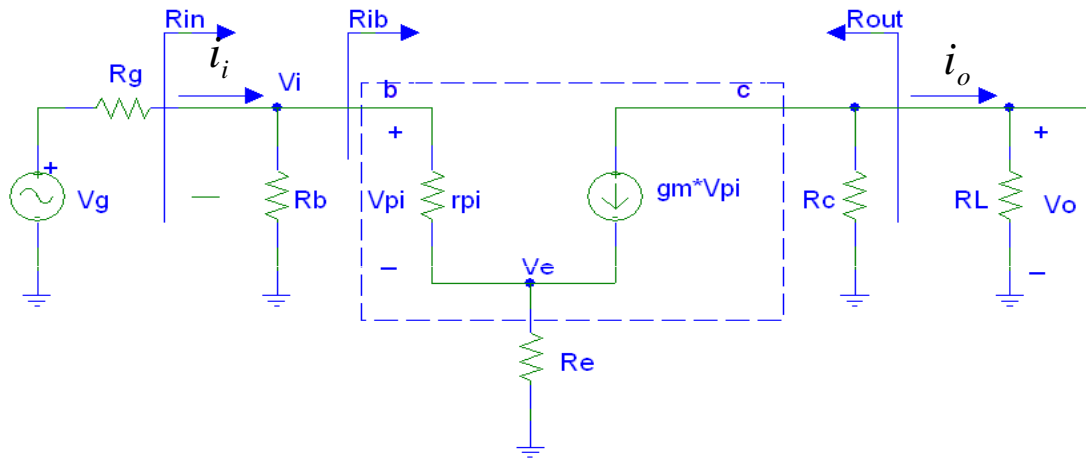

$$R_{ib} = \frac{V_\pi + V_e}{V_\pi / r_\pi} = r_\pi + (1 + \beta_o) R_e$$

$$R_{in} = R_b \parallel [r_\pi + (1 + \beta_o) R_e]$$

$$R_{out} \Big|_{r_o \gg R_c} \approx R_c$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta_o (R_c \parallel R_L)}{r_\pi + (1 + \beta_o) R_e}$$

$$G_v = \frac{V_o}{V_g} = -\frac{\beta_o (R_c \parallel R_L)}{r_\pi + (1 + \beta_o) R_e} \cdot \frac{R_{in}}{R_g + R_{in}}$$


$$A_i = \frac{i_o}{i_i} = -\beta_o \frac{R_c}{R_L + R_c} \frac{R_b + R_{ib}}{R_b}$$

$$A_{v_o} = -\frac{\beta_o R_c}{r_\pi + (1 + \beta_o) R_e} \approx -\frac{g_m R_c}{1 + g_m R_e}$$

$$G_v \Big|_{\substack{R_g \ll R_{in} \\ r_\pi \ll \beta_o R_e}} \approx -\frac{(R_c \parallel R_L)}{R_e} \approx -\frac{R_c}{R_e} \cdot \frac{R_L}{R_c + R_L}$$

$$A_{i(sc)} = -\beta_o \frac{R_b + R_{ib}}{R_b} \quad A_{i(sc)} \Big|_{\substack{R_g \ll R_{in} \\ R_b \gg R_{ib}}} \approx -\beta_o$$

ANNEX 3: Characteristics CC

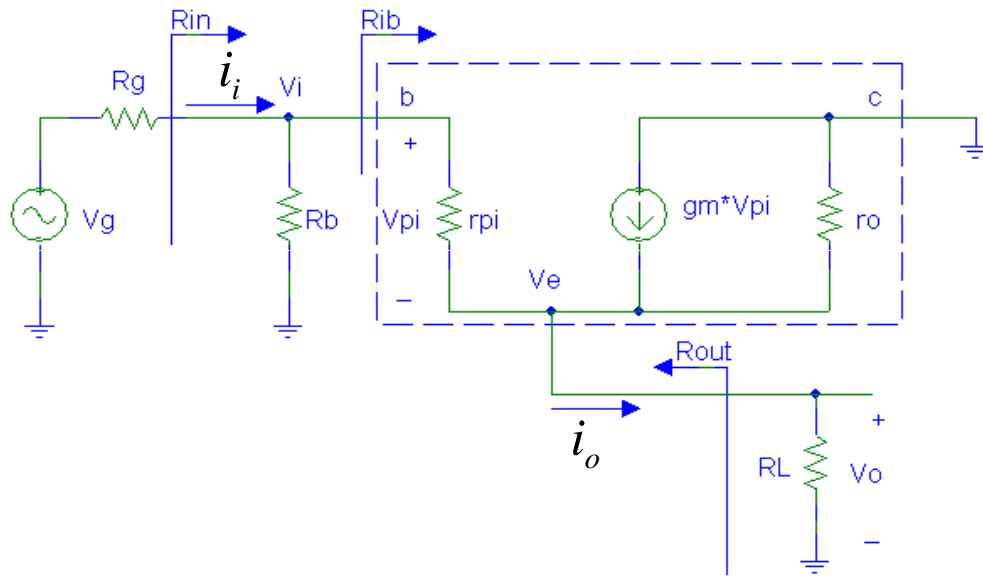

$$R_{ib} = \frac{V_{\pi} + V_e}{V_{\pi}/r_{\pi}} = r_{\pi} + (1 + \beta_o) \cdot R_{EM}$$

$$R_{in} = R_b \parallel [r_{\pi} + (1 + \beta_o) \cdot R_{EM}]$$

$$R_{out} = r_o \parallel \frac{r_{\pi} + (R_b \parallel R_g)}{1 + \beta_o} \approx \frac{r_{\pi} + (R_b \parallel R_g)}{1 + \beta_o}$$

$$G_v = \frac{V_o}{V_g} = \frac{(1 + \beta_o) \cdot R_{EM}}{r_{\pi} + (1 + \beta_o) \cdot R_{EM}} \cdot \frac{R_{in}}{R_g + R_{in}} \approx 1$$

$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta_o) \cdot R_{EM}}{r_{\pi} + (1 + \beta_o) \cdot R_{EM}}$$


$$A_{v_o} = \frac{(1 + \beta_o) \cdot r_o}{r_{\pi} + (1 + \beta_o) \cdot r_o} \approx 1$$

$$A_i = \frac{i_o}{i_i} = (1 + \beta_o) \frac{r_o}{r_o + R_L} \frac{R_b + R_{ib}}{R_b}$$

$$A_{i(sc)} = (1 + \beta_o) \frac{R_b + R_{ib}}{R_b}$$

$$A_{i(sc)} \Big|_{\substack{R_g \ll R_{in} \\ R_b \gg R_{ib}}} \approx 1 + \beta_o$$

ANNEX 4: Characteristics CB

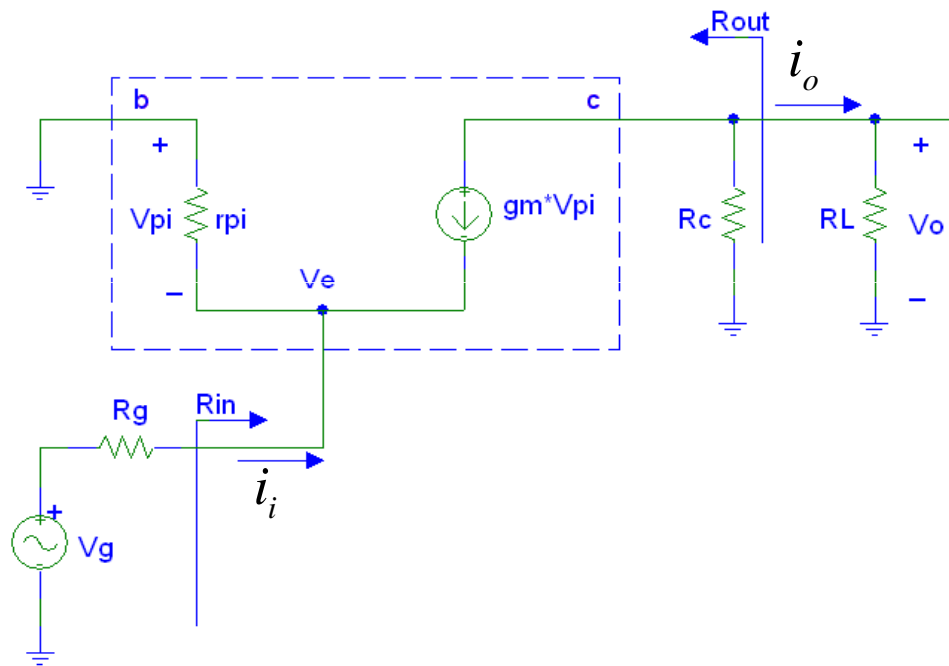

$$R_{in} = \frac{r_{\pi}}{1 + \beta_o} \approx \frac{1}{g_m}$$

$$R_{out} \Big|_{r_o \gg R_c} \approx R_c$$

$$A_v = \frac{V_o}{V_i} = +g_m (R_c // R_L)$$

$$A_{v_o} = +g_m R_c$$

$$G_v = \frac{V_o}{V_g} = +g_m (R_c // R_L) \frac{R_{in}}{R_g + R_{in}}$$

$$G_v = \frac{V_o}{V_g} = g_m (R_c // R_L) \frac{1}{1 + g_m R_g}$$

$$A_i = \frac{i_o}{i_i} = \frac{\beta_o}{(1 + \beta_o)} \frac{R_c}{R_c + R_L} = \alpha \frac{R_c}{R_c + R_L}$$

$$A_{i(sc)} = \alpha$$