



Universidad
Carlos III de Madrid
www.uc3m.es

Session 22

Multistage Amplifiers

Electronic Components and Circuits

Pablo Acedo / José A. García Souto

www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/PabloAcedo

Multistage Amplifiers

INDEX

- The need for multistage amplifiers.
- Multistage Amplifiers analysis methodology.
- Multistage Amplifier example
- Differential Amplifier.

The need for Multistage Amplifiers

Single-stage Amplifiers Characteristics


Scheme	R _{in}	R _{out}	A _v	A _{i(sc)}
CE	$R_b // r_\pi \approx r_\pi$	$R_c // r_o$	★ $-g_m(r_o // R_c // R_L)$	$-g_m R_{in} \approx -\beta_o$
CE-RE	★ $R_b // [r_\pi + (1 + \beta_o)R_e]$	R_c	★ $-\frac{\beta_o(R_c // R_L)}{r_\pi + (1 + \beta_o)R_e}$	$-\beta_o \frac{R_b + R_{ib}}{R_b} \approx -\beta_o$
CC	★ $R_b // [r_\pi + (1 + \beta_o)R_{EM}]$	★ $\frac{r_\pi + (R_b // R_g)}{1 + \beta_o}$	$\frac{(1 + \beta_o)R_{EM}}{r_\pi + (1 + \beta_o)R_{EM}} \approx 1$	$(1 + \beta_o) \frac{R_b + R_{ib}}{R_b}$
CB	$\frac{r_\pi}{1 + \beta_o} \approx \frac{1}{g_m}$ ★	R_c	$+g_m(R_c // R_L)$	$\frac{\beta_o}{(1 + \beta_o)} = \alpha$

$$G_v = A_v \frac{R_{in}}{R_g + R_{in}}$$

$$G_v|_{EC}^{max} \approx -g_m r_o = -\frac{V_A}{V_T}$$


$$G_v|_{CC}^{max} \approx 1$$

Multistage Amplifiers

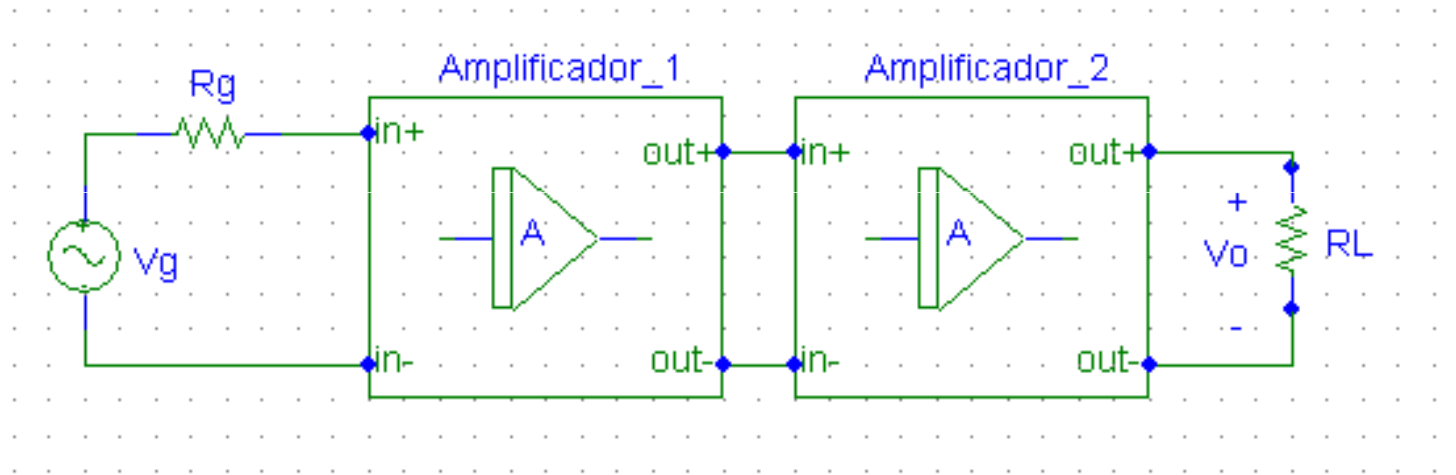


- All analog integrated circuits (IC) are made of several amplification stages, usually DC coupled, each of them with a specific objective.
- The first stage (input stage) fixes the input impedance. There is at least one gain stage and finally the output stage fixes the output impedance and delivers the output current to the load.

Methodology

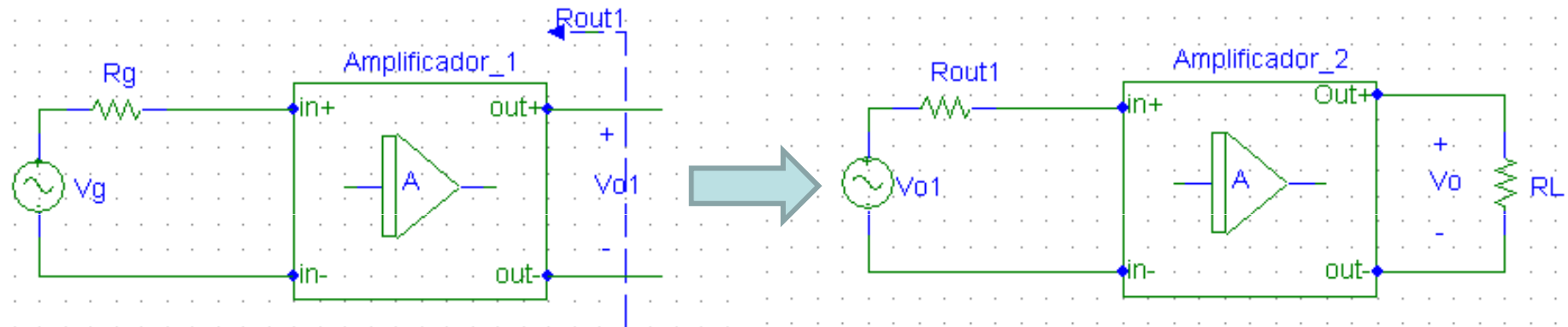


- We start with the determination of the characteristics of the first stage (isolated). The parameters needed are the output voltage (function of V_g) and the output impedance (R_{out1}).
- The following step includes driving the second stage with the first stage's output voltage using R_{out1} as the new generator impedance. With this new scheme, the characteristics for the second stage are determined (output voltage and output impedance).
- Repeat the process for all the stages.

Example (I)

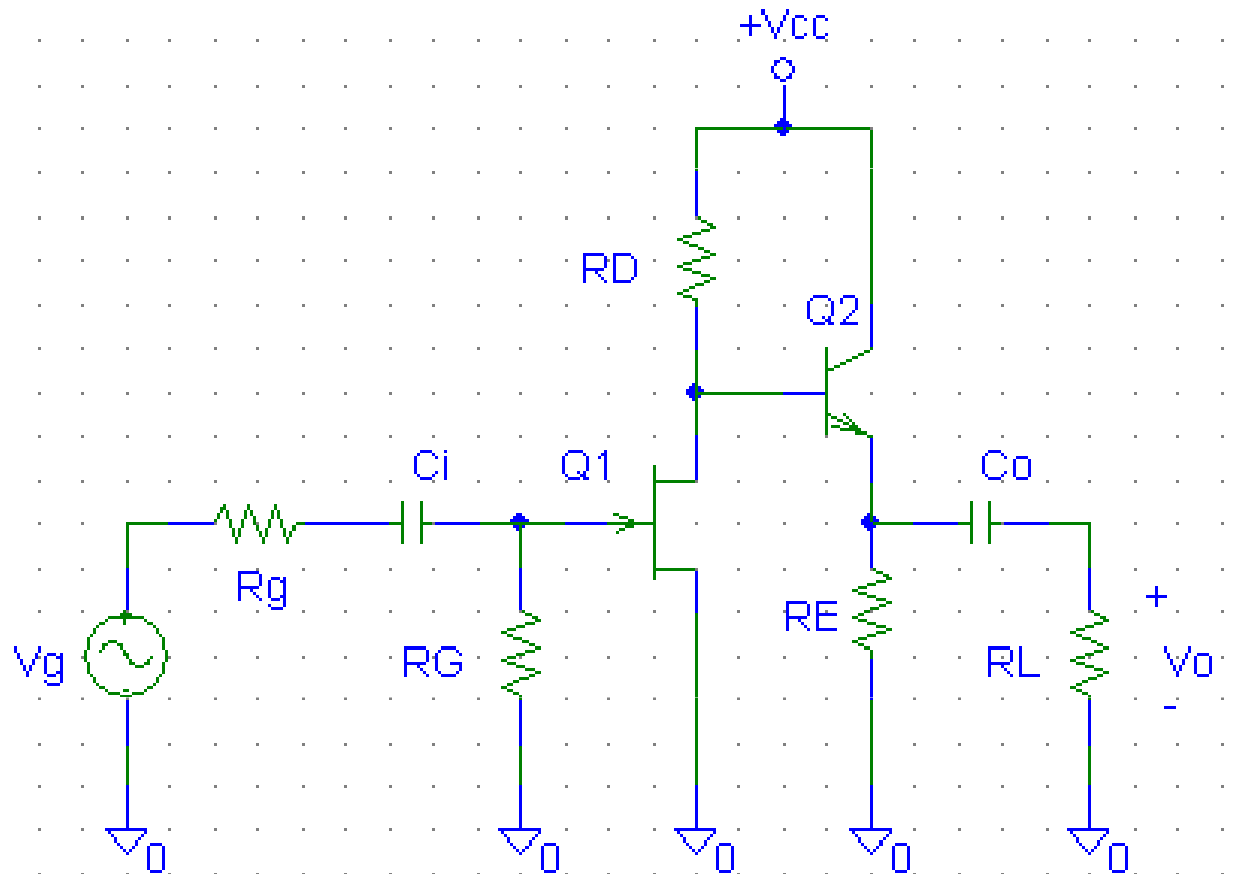


Example (II)

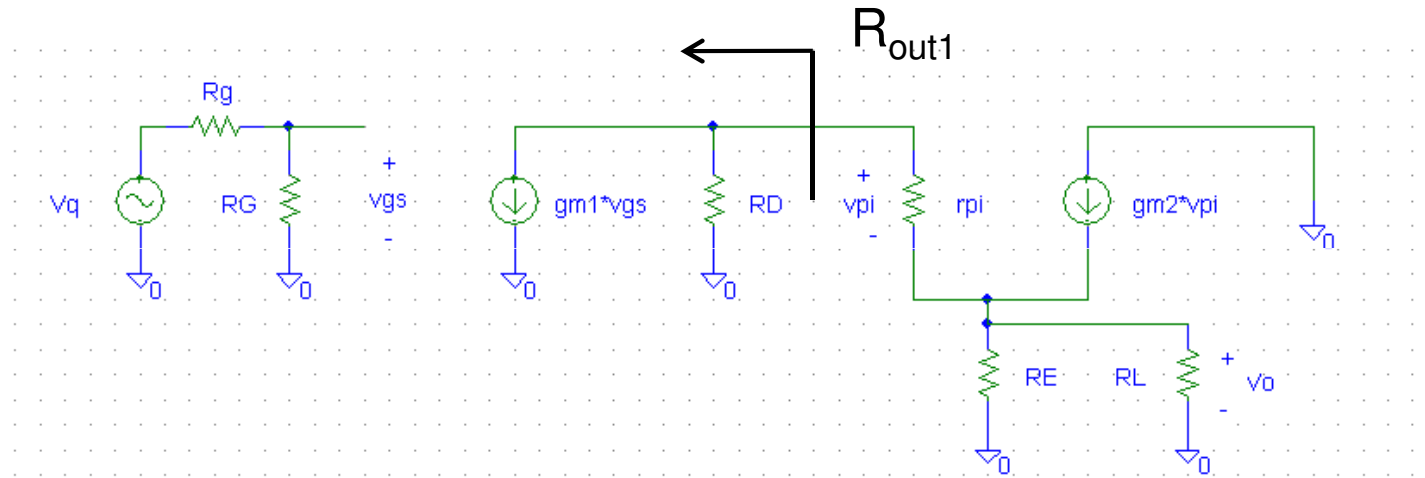

$$R_{out1} = R_D$$

$$V_{out1} = -\frac{R_G}{R_g + R_G} g_{m1} R_D V_g$$

Example (III)

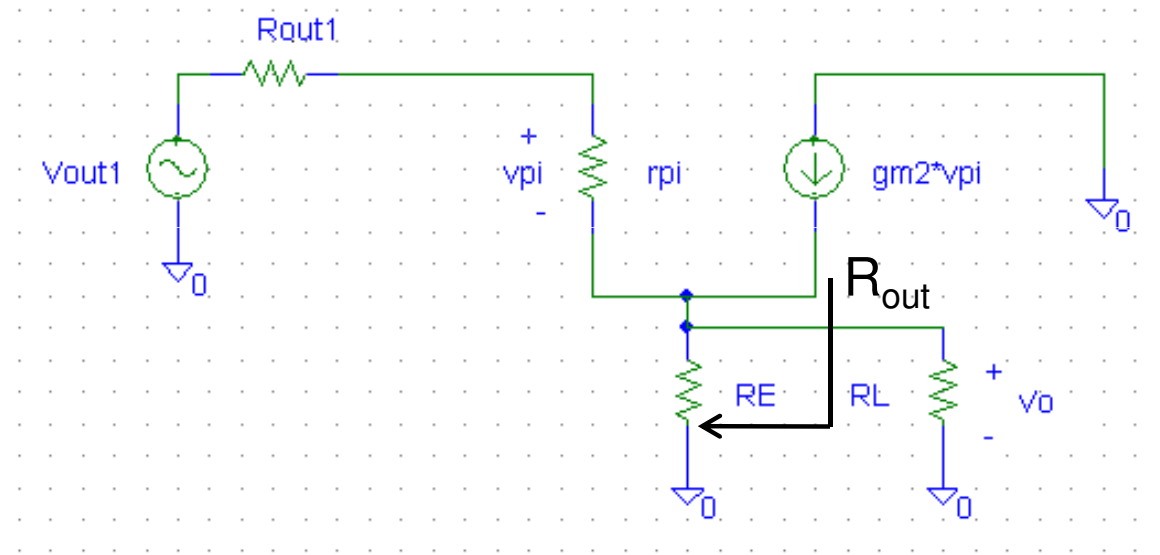


$$R_{out} = R_E // \frac{r_{\pi} + R_{out1}}{1 + \beta_0}$$

$$V_o = \frac{(1 + \beta_0) R_E // R_L}{R_{out1} + r_{\pi} + (1 + \beta_0) R_E // R_L} V_{out1}$$

Differential Amplifier

- Fundamental Circuit in Analog Electronics (as well as digital electronics).
- It allows differential signal amplification as well as direct coupling between stages (without coupling capacitors). Circuits with DC gain possible.
- Fundamental part of operational amplifiers (used in the lab).


Differential Amplifier

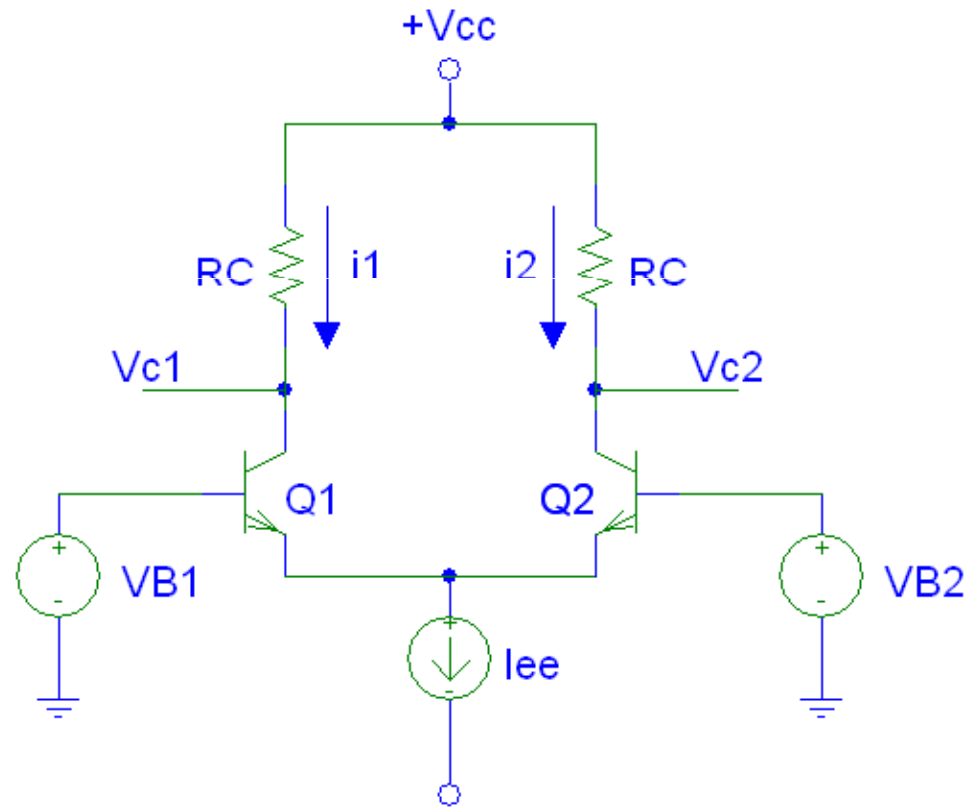

$$v_{id} = v_{B1} - v_{B2}$$


$$v_c = \frac{v_{B1} + v_{B2}}{2}$$

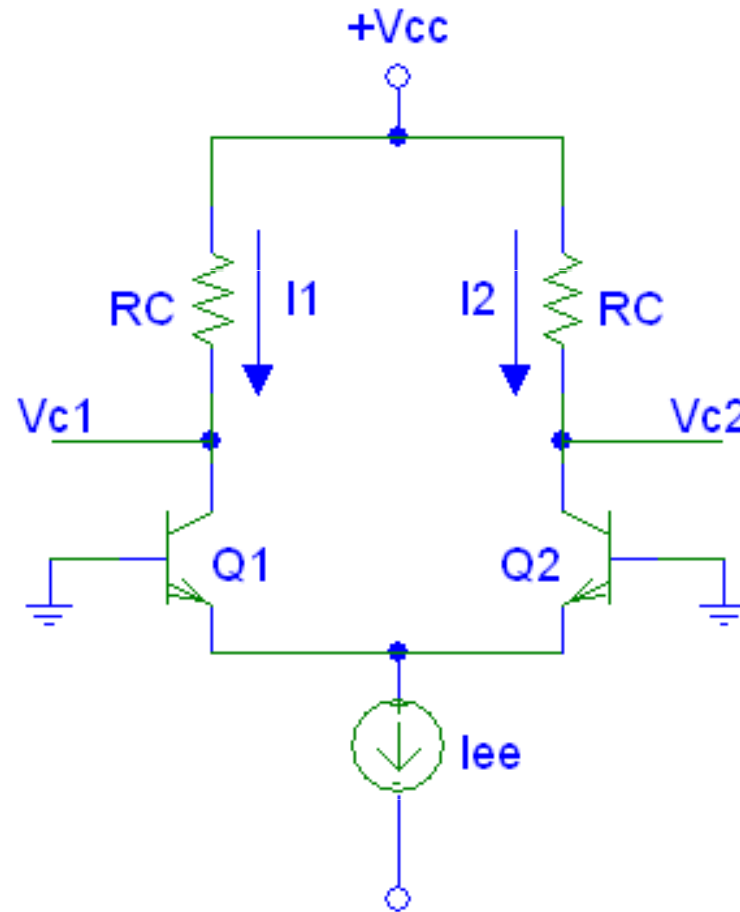DC analysis of the Differential Amplifier



$$I_{C1} = I_{C2} = \frac{I_{EE}}{2}$$

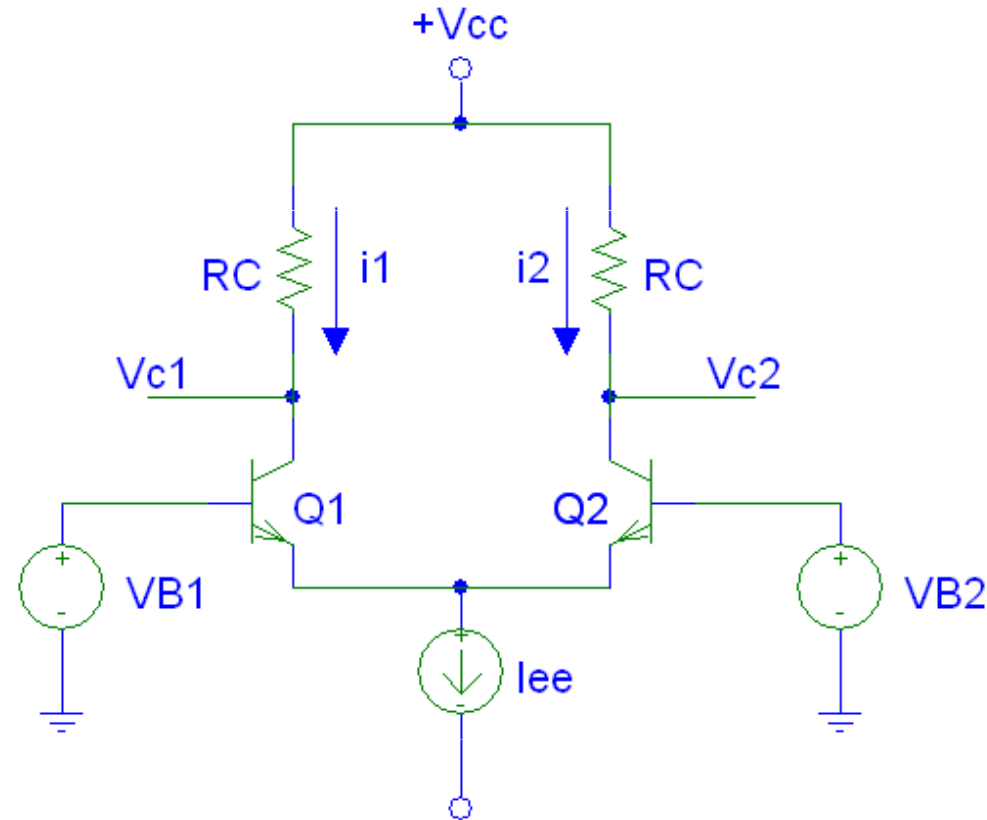
Small-signal Analysis of the Differential Amplifier



$$v_{c1} = A v_{B1} + B v_{B2} \quad \Rightarrow \quad v_{c1} = A_{DM} v_{id} + A_{CM} v_c$$


Differential Amplifier Small Signal Analysis

Differential Mode (I)

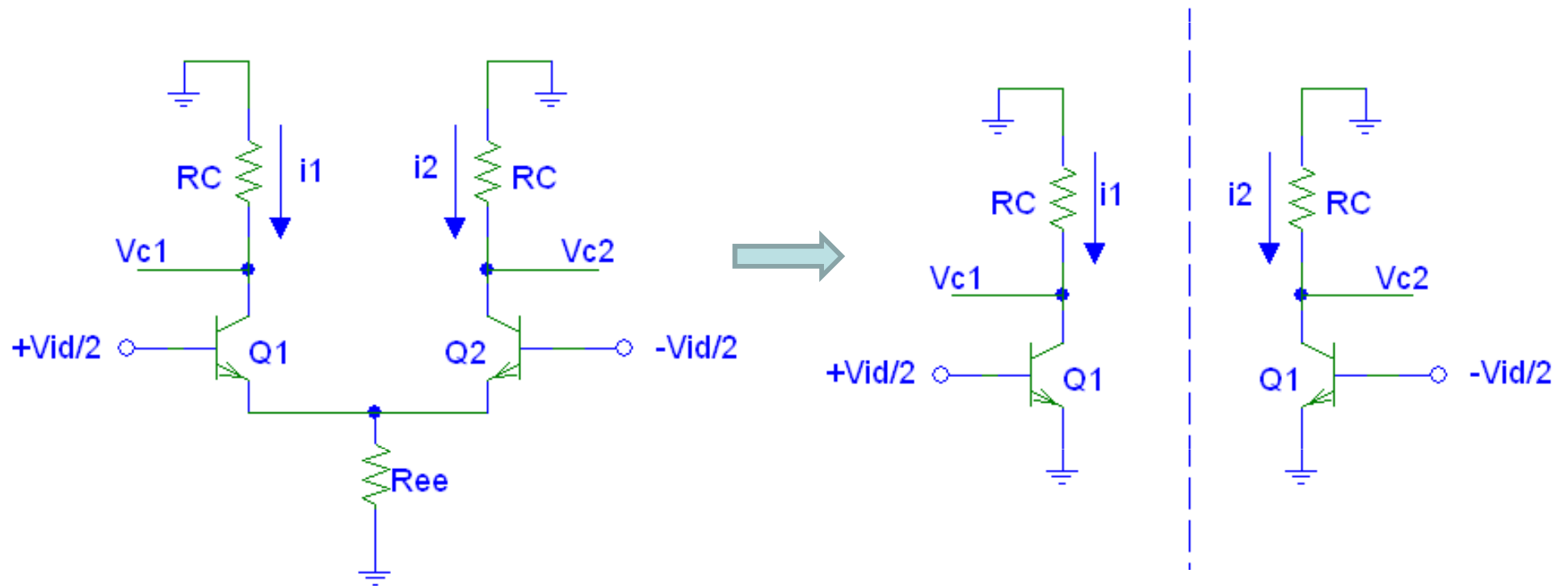

Differential Amplifier Small Signal Analysis

Differential Mode (II)

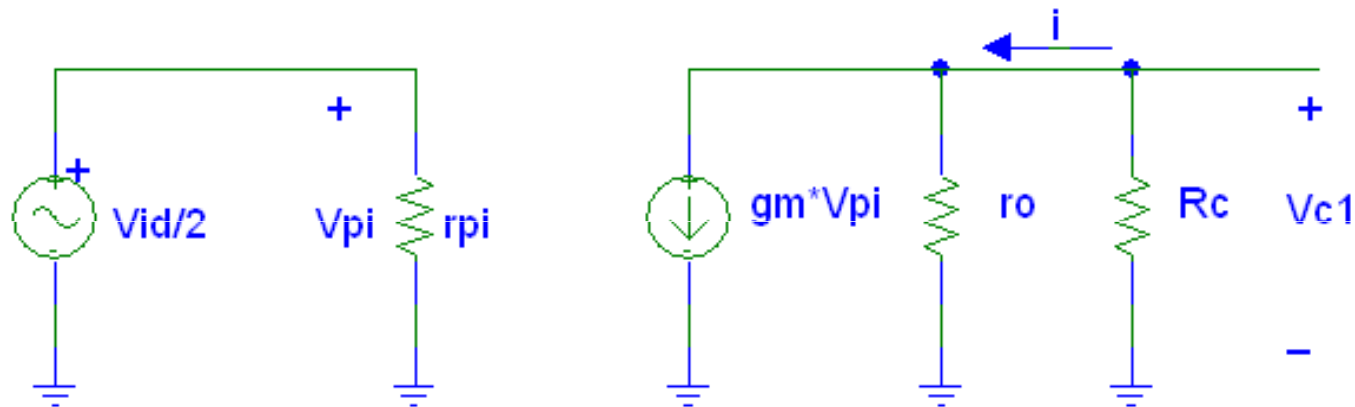


- The output can be the signal that appears between both collectors (differential output):


$$V_o = V_{c1} - V_{c2}$$

- Or directly the voltage of one of them referenced to ground (single-ended output)

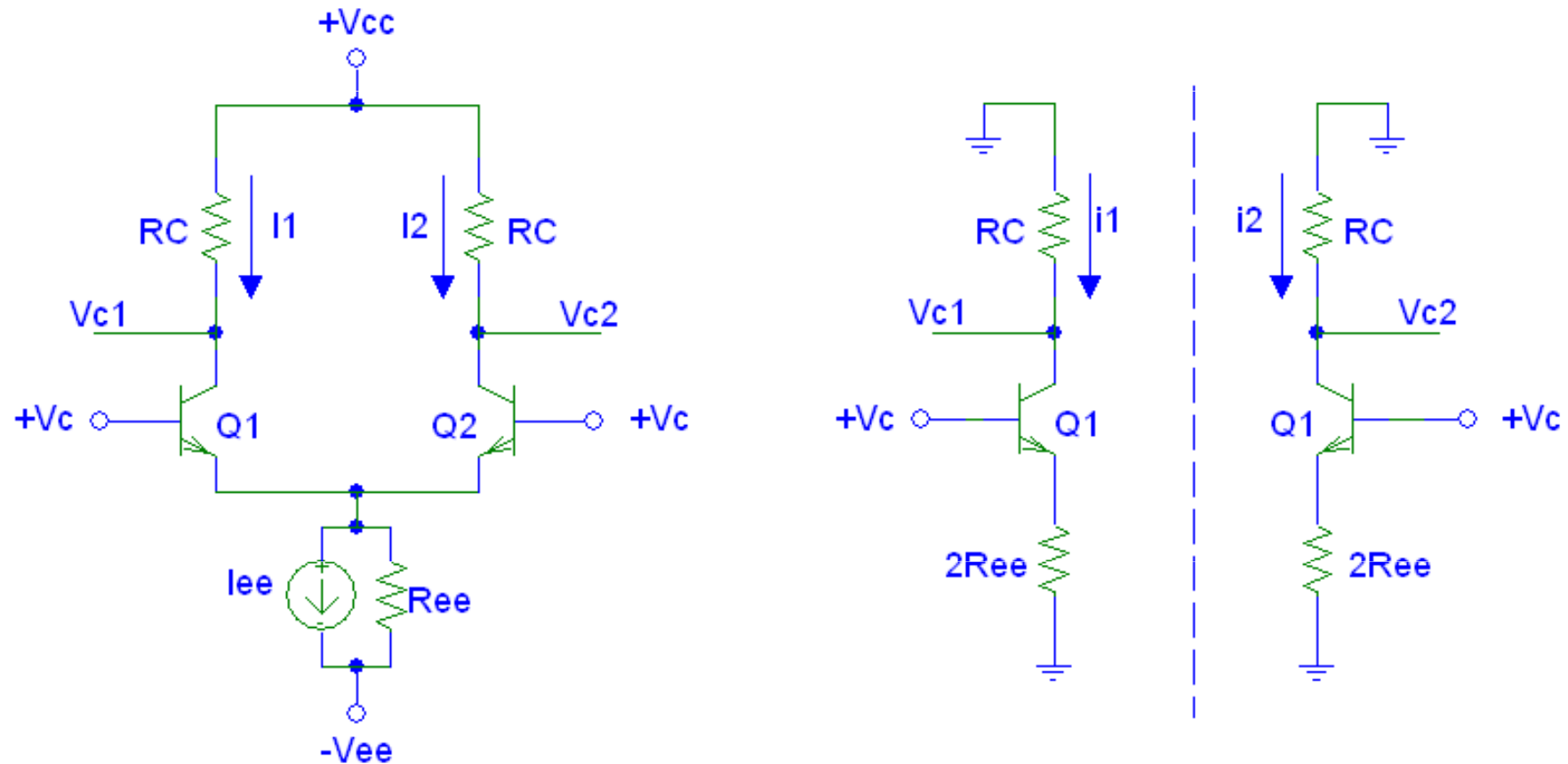Differential Amplifier Small Signal Analysis Common Mode (I)



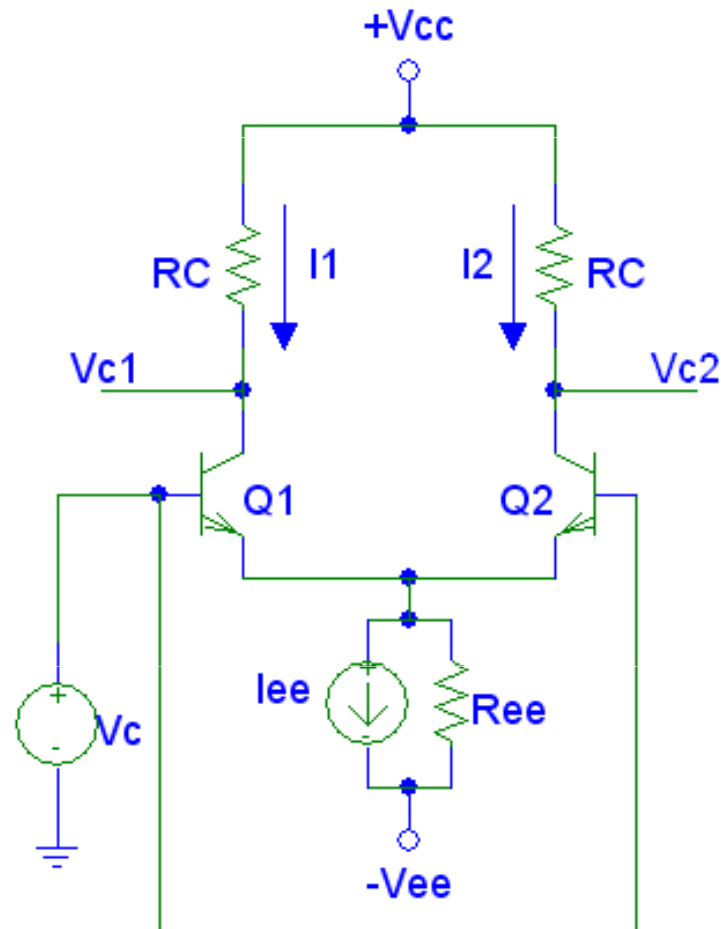Differential Amplifier Small Signal Analysis Common Mode (II)



Differential Amplifier Final Considerations (I)

- Common-mode rejection ratio (CMRR):

$$CMRR = \frac{A_{DM}}{A_{CM}}$$

- This way:


$$v_o = A_{DM} \left(v_{id} + \frac{v_c}{CMRR} \right)$$

Differential Amplifier

Final Considerations (II)

- The determination of the different impedances associated to the equivalent circuits are left as an exercise for the students.
- The determination of the frequency response will be covered in the proposed exercise

Proposed Exercise

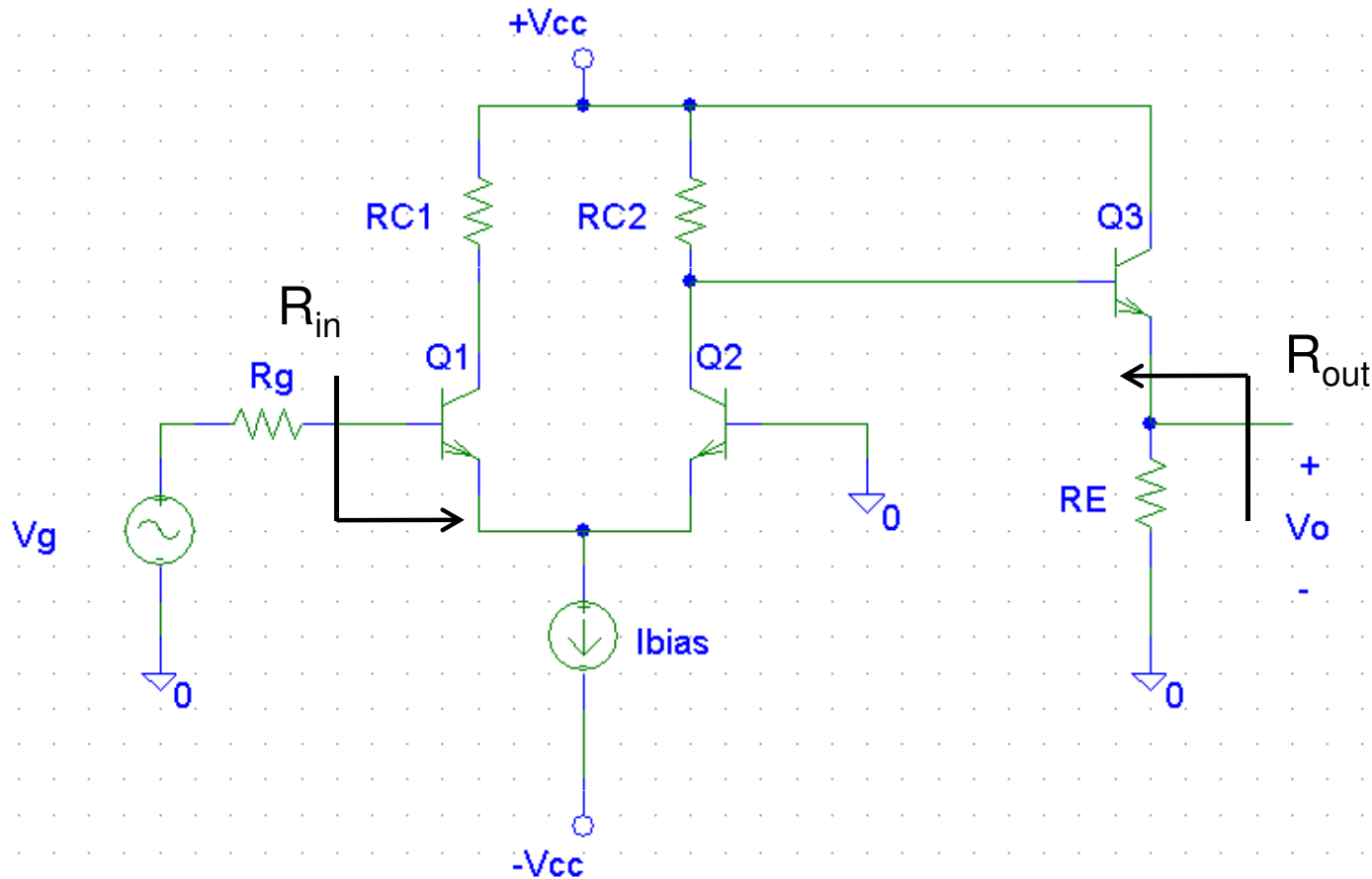

$$V_{CC} = 15 \text{ V}$$

$$I_{bias} = 1 \text{ mA}$$

$$R_{C1} = R_{C2} = 10 \text{ k}\Omega$$

$$R_E = 560 \Omega$$

$$R_g = 50 \Omega$$

BJTs:

$$\beta_0 = \beta_F = 250, V_T = 25 \text{ mV}, V_{BE} = 0.6 \text{ V}, C_\pi = 2 \text{ pF}, C_\mu = 0.7 \text{ pF}$$