



Universidad
Carlos III de Madrid
www.uc3m.es

Session 24

Introduction to OA

Operational Amplifier

Electronic Components and Circuits

José A. Garcia Souto / Isabel Perez



www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia

Introduction to Operational Amplifier

OBJECTIVES

- To know the basic parameters of the ideal operational amplifier
- To understand the methodology of linear circuit analysis with ideal operational amplifiers: virtual short-circuit
- To understand and use the gain-bandwidth product concept
- To know some basic OA applications


Introduction: amplifier

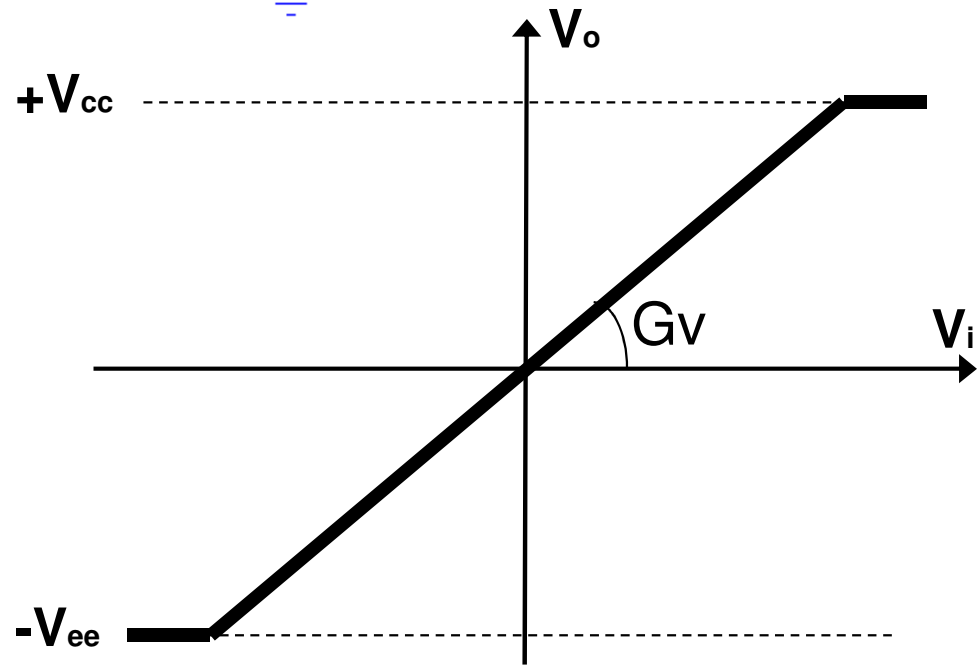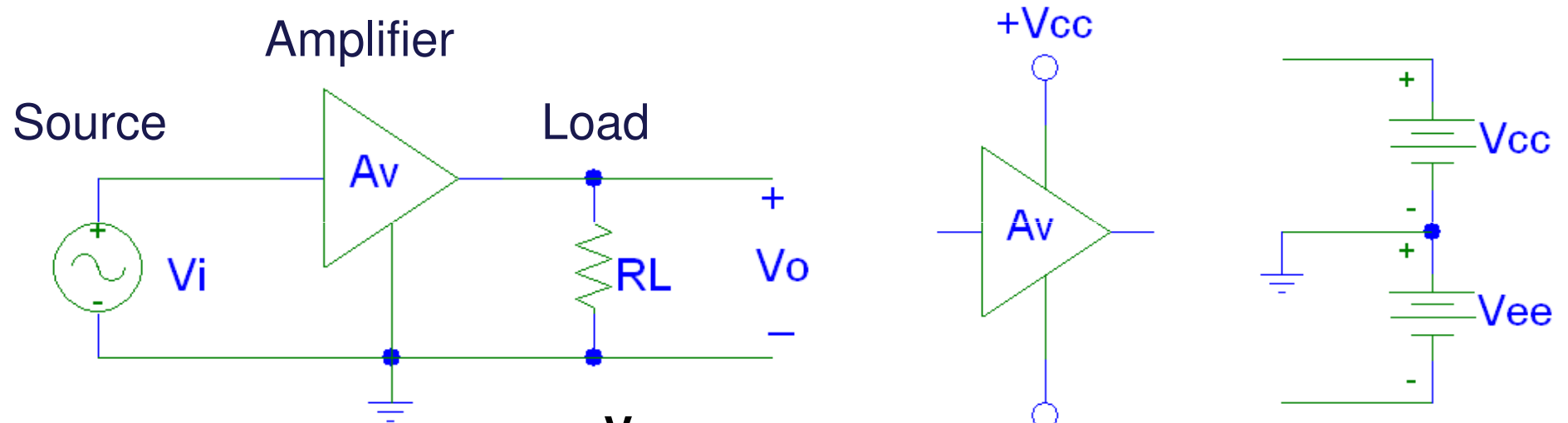

Introduction: Voltage amplifier


REAL

Voltage amplifier

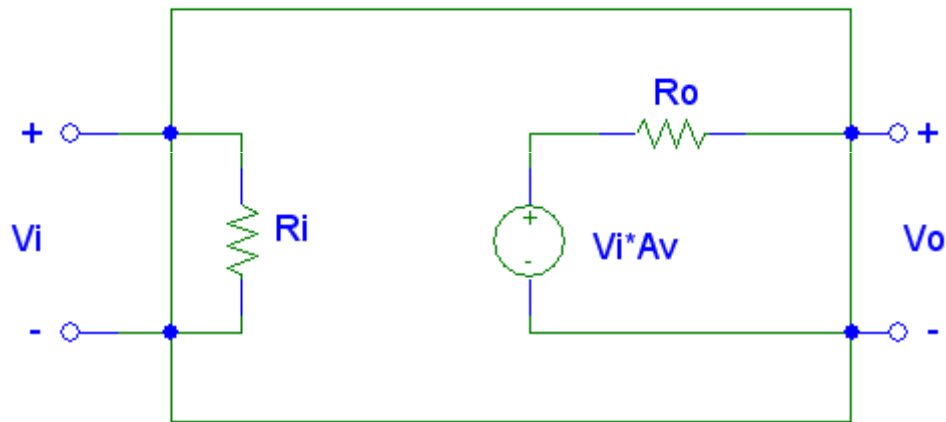


IDEAL

Voltage amplifier

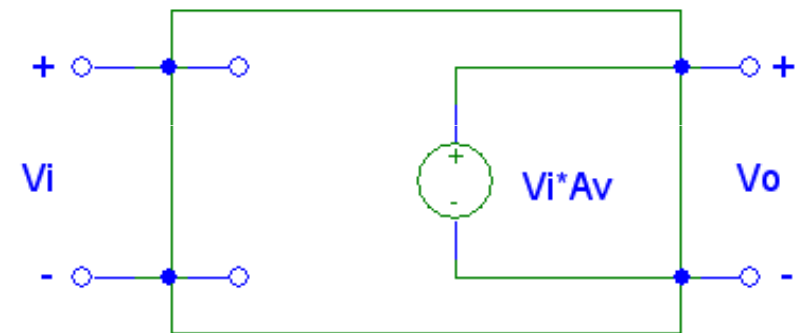


Voltage amplifier

LOADING
EFFECT

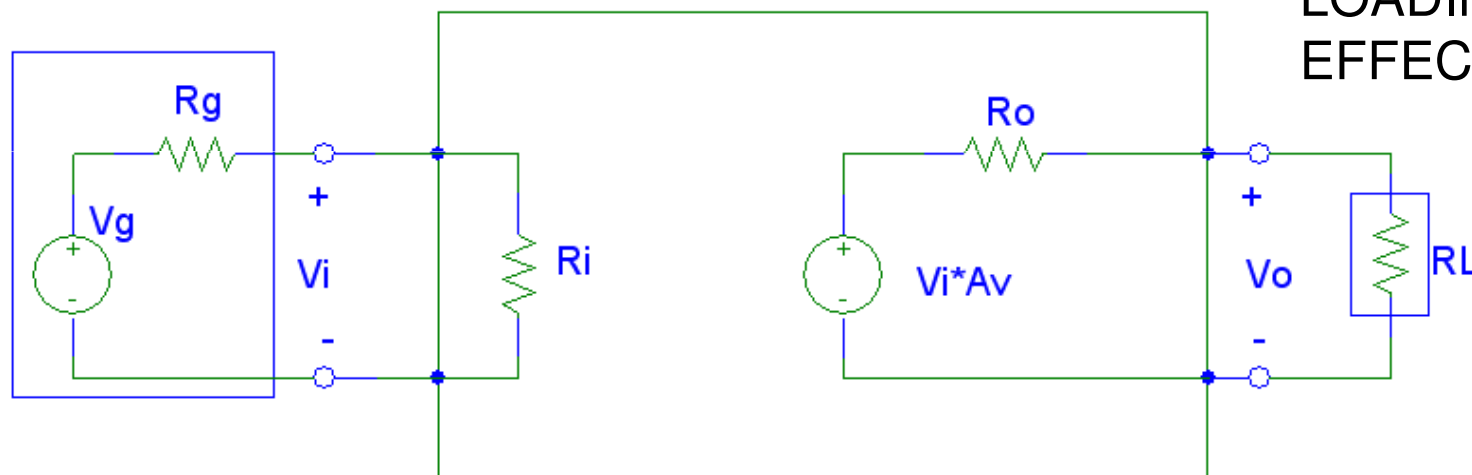

Introduction: Differential Amplifier

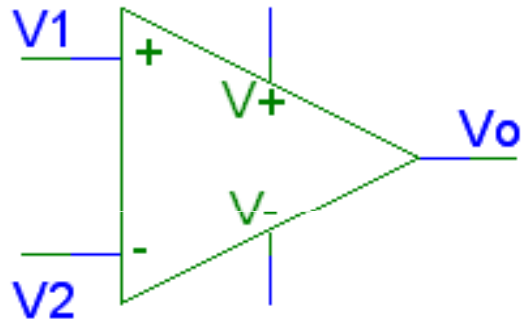

Differential input

$$V_{id} = V_1 - V_2$$

Common mode input

$$V_{ic} = \frac{V_1 + V_2}{2}$$

Differential gain and common mode gain

$$V_o = A_{DM} \cdot V_{id} + A_{CM} \cdot V_{ic}$$



Common mode rejection ratio (CMRR)

$$V_o = A_{DM} \left(V_{id} + \frac{V_{ic}}{CMRR} \right)$$

If $CMRR \rightarrow \infty$

$$V_o = A_{DM} \cdot V_{id}$$

IDEAL operational amplifier

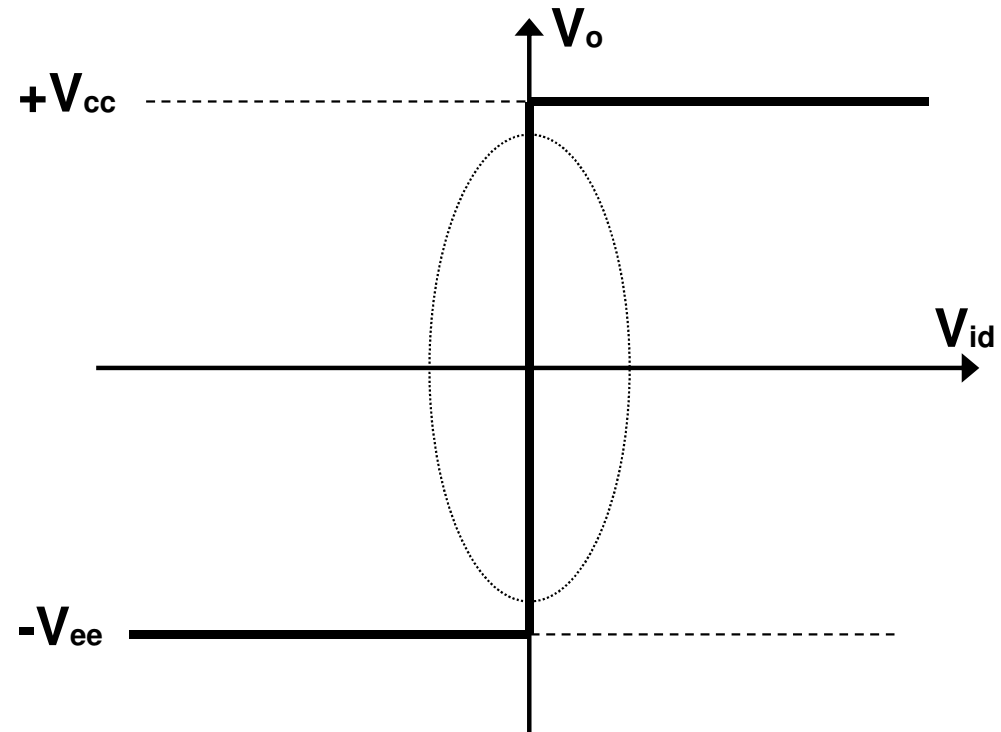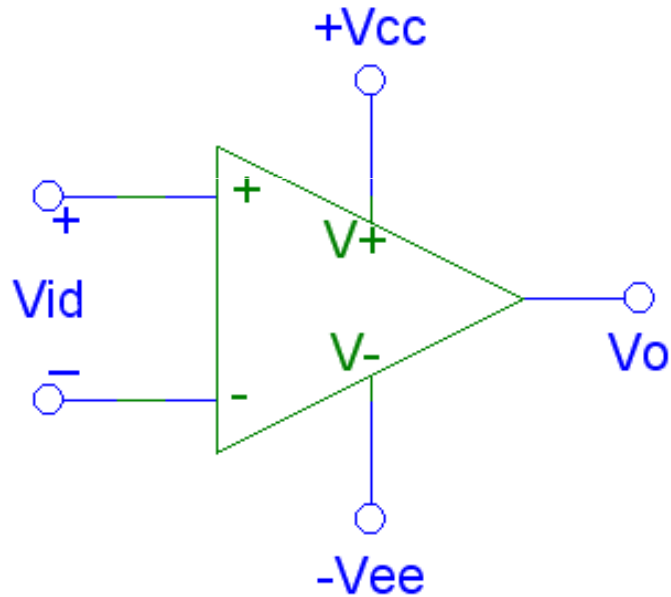

Linear behavior

$$V_o = A_v \cdot V_{id}$$

Within the output range

$$-V_{ee} \leq v_o \leq +V_{cc}$$


Ideally $A_v \rightarrow \infty$

Parameters of the IDEAL operational amplifier

- Open loop gain (A_v) $\rightarrow \infty$
- Input impedance (R_i) $\rightarrow \infty$
- Output impedance (R_o) $\rightarrow 0$
- Common mode rejection ratio (CMRR) $\rightarrow \infty$
- Bandwidth (BW) $\rightarrow \infty$
- Input currents (bias) $\rightarrow 0$
- Offset voltage $\rightarrow 0$


Introduction: Negative feed-back

OPEN LOOP
AMPLIFICATION

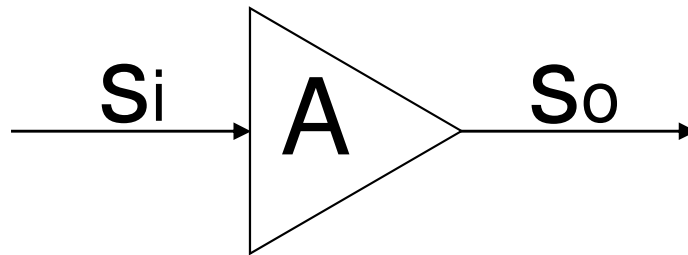

$$S_o = A \cdot S_i$$

FEED-BACK
AMPLIFICATION

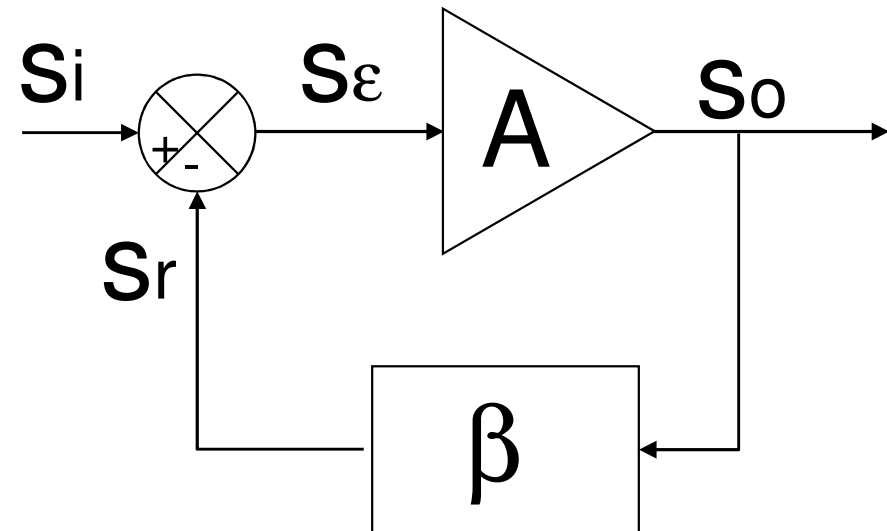

$$S_o = G \cdot S_i$$

$$G = \frac{S_o}{S_i} = \frac{A}{1 + A\beta}$$


$$S_\epsilon = S_i - S_r$$

$$S_o = A \cdot S_\epsilon$$

$$S_r = \beta \cdot S_o$$

Introduction: Negative feed-back

IDEAL FEED-BACK AMPLIFIER


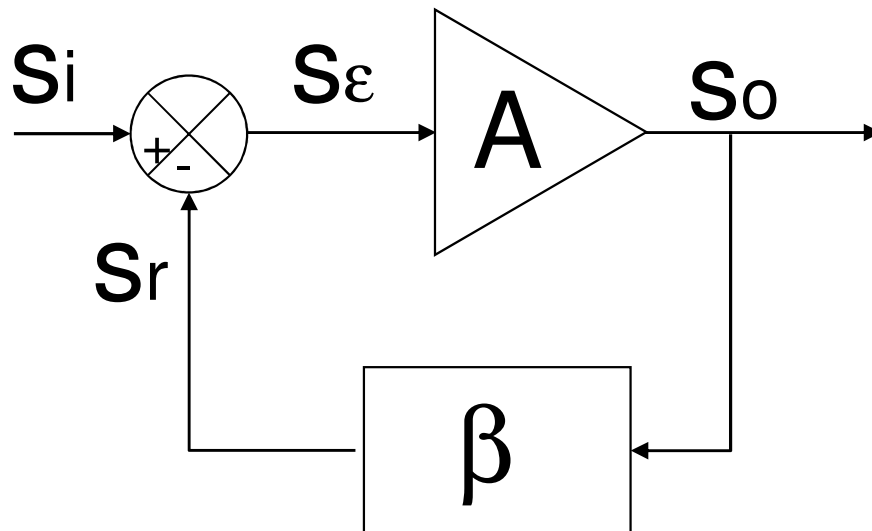


$$S_o = G \cdot S_i$$

$$G = \frac{S_o}{S_i} = \frac{A}{1 + A\beta}$$

$$\begin{array}{l} A\beta \gg 1 \\ [A \rightarrow \infty] \end{array} \quad \Rightarrow \quad \begin{array}{l} G \approx \frac{1}{\beta} \\ S_\epsilon \rightarrow 0 \end{array} \quad \Rightarrow \quad S_o \approx \frac{1}{\beta} \cdot S_i$$

Example: Non-inverting OA

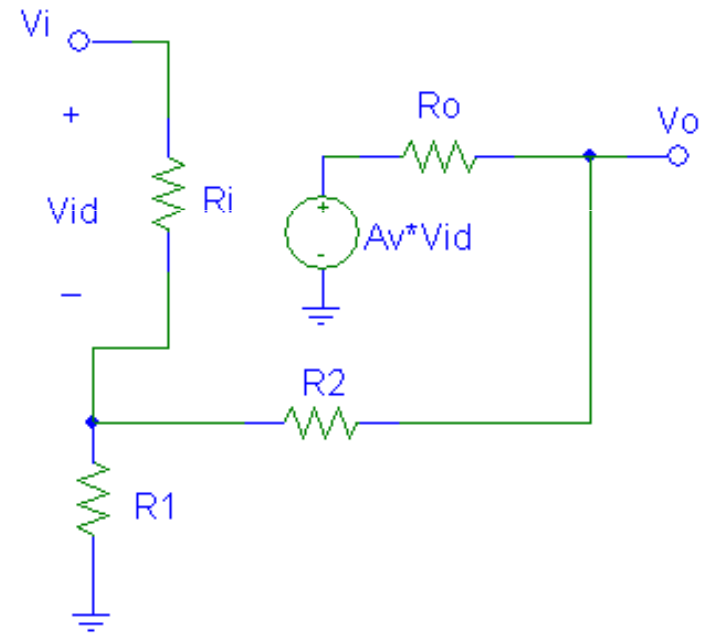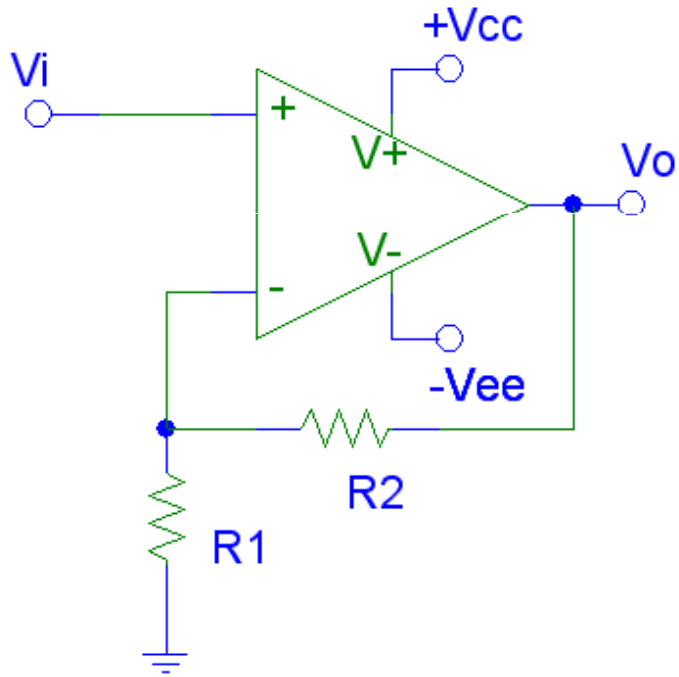


$$R_i \rightarrow \infty, R_o \rightarrow 0$$





$$A_v \rightarrow \infty$$

$$G_v \approx \frac{A_v}{1 + A_v \frac{R_1}{R_1 + R_2}}$$

$$G_v \approx 1 + \frac{R_2}{R_1}$$

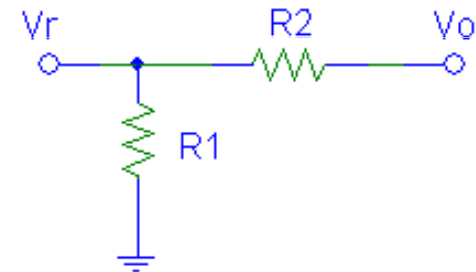

Example: Inverting OA

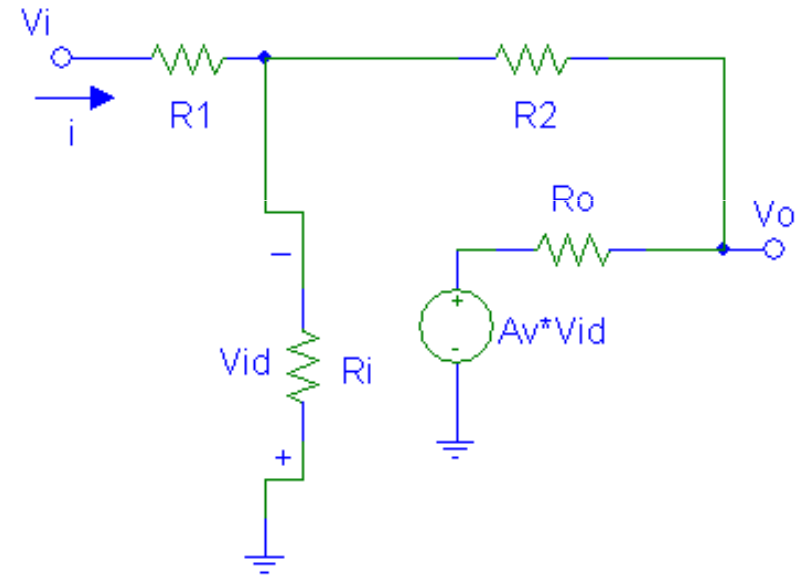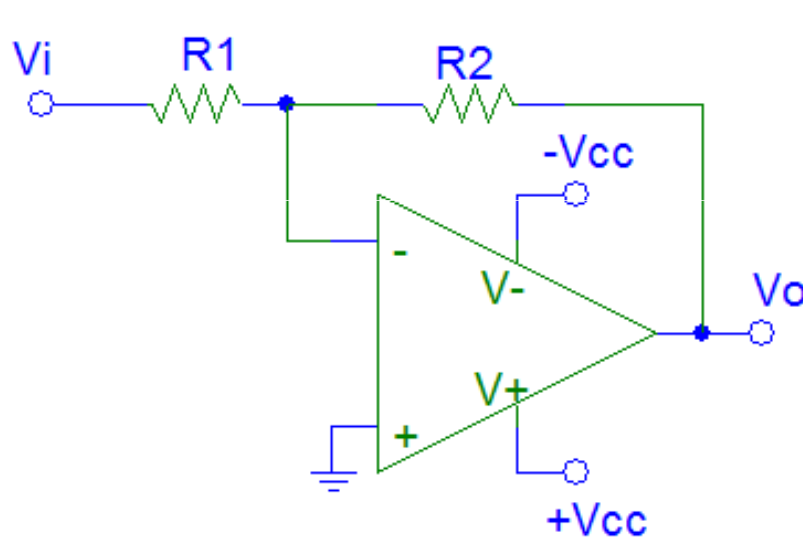


$$R_i \rightarrow \infty, R_o \rightarrow 0$$




$$A_v \rightarrow \infty$$

$$G_v \approx -\frac{A_v (R_1 \parallel R_2)}{1 + \frac{A_v}{R_2} (R_1 \parallel R_2)} \cdot \frac{1}{R_1}$$

$$G_v \approx -\frac{R_2}{R_1}$$

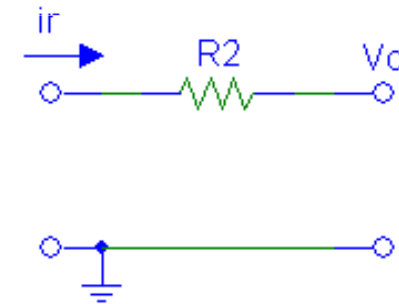


Linear application IDEAL-OA

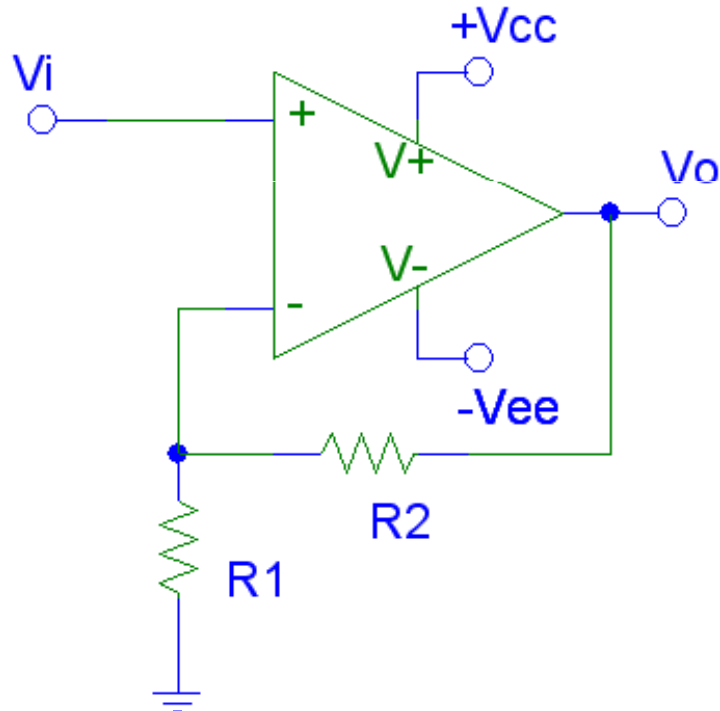

Linear behaviour

$$V_o = A_v \cdot V_{id}$$

Negative feed-back

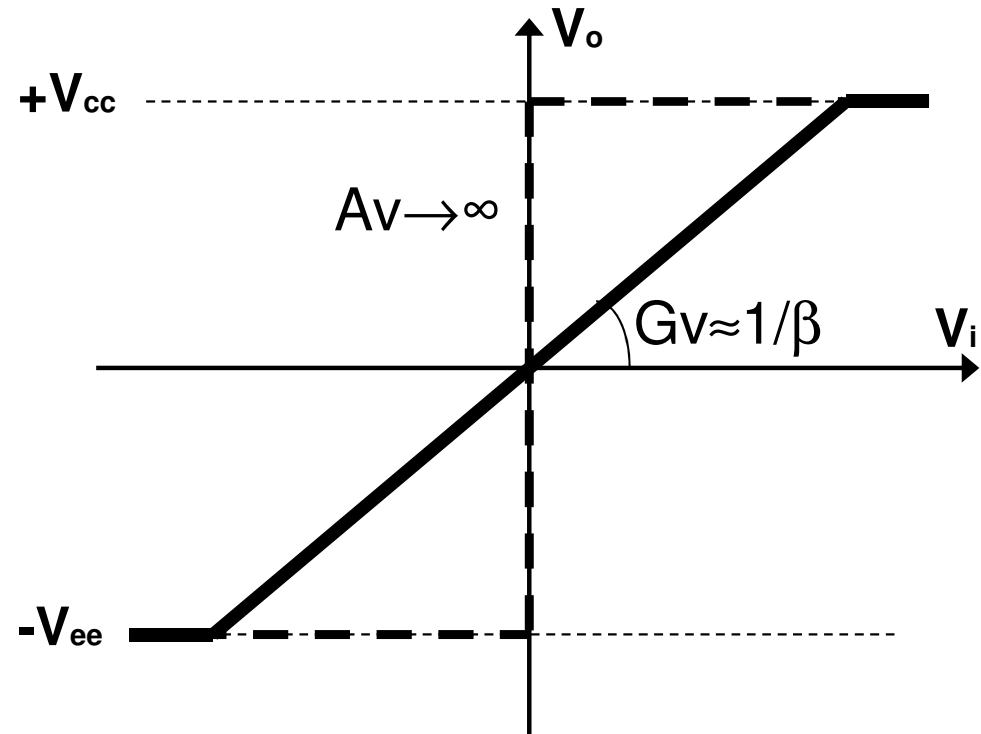


Virtual short-circuit

$$V_{id} = 0$$

$$V_+ = V_-$$

Examples: Virtual short-circuit

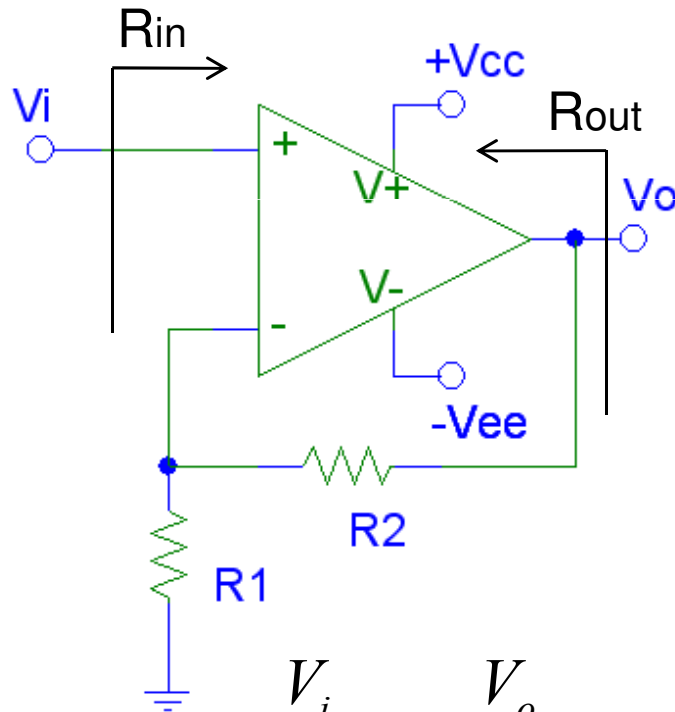


$$V_+ = V_-$$

$$i_+ = i_- = 0$$

$$\frac{V_i}{R_1} = \frac{V_o}{R_1 + R_2}$$

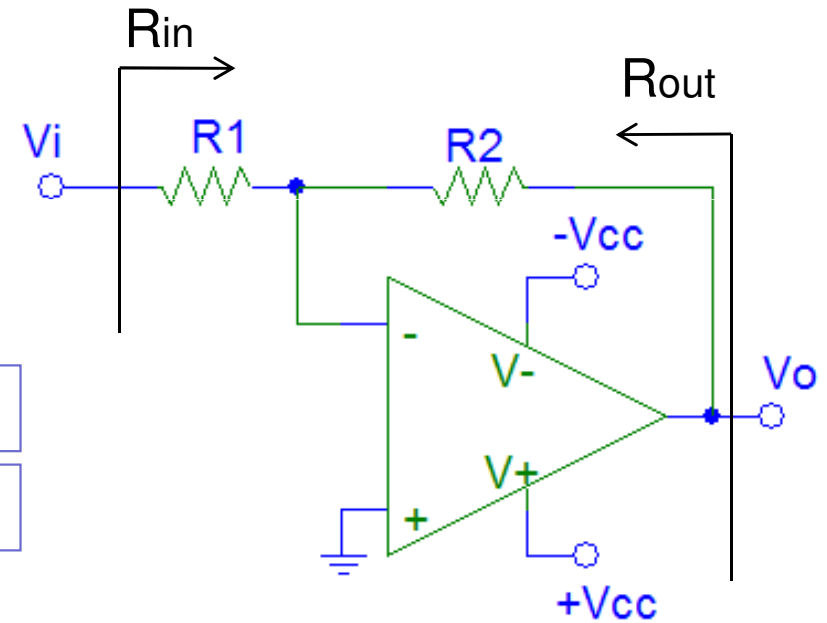
$$G_V = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1} \quad \begin{array}{l} R_{in} \rightarrow \infty \\ R_{out} \rightarrow 0 \end{array}$$



$$\frac{V_i}{R_1} = -\frac{V_o}{R_2}$$

$$G_V = \frac{V_o}{V_i} = -\frac{R_2}{R_1} \quad \begin{array}{l} R_{in} \rightarrow R_1 \\ R_{out} \rightarrow 0 \end{array}$$

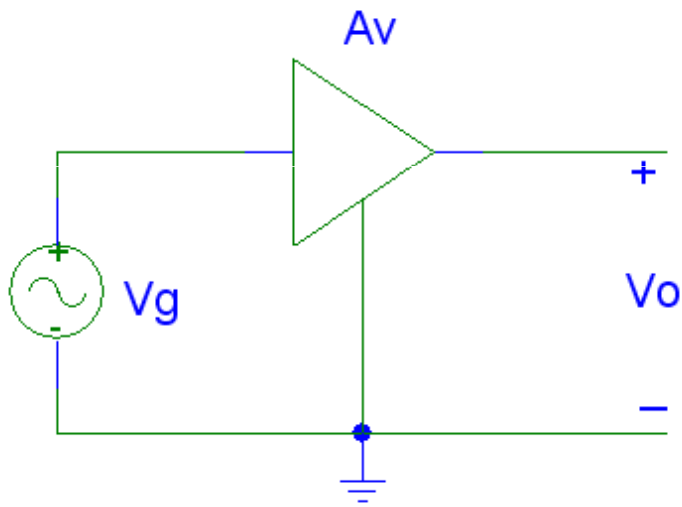
Frequency response of the operational amplifier: continuous coupled



$$A_v(j\omega) = \frac{V_o(j\omega)}{V_g(j\omega)}$$



$$A_0 = A_v(\omega = 0)$$

Gain x Bandwidth = constant

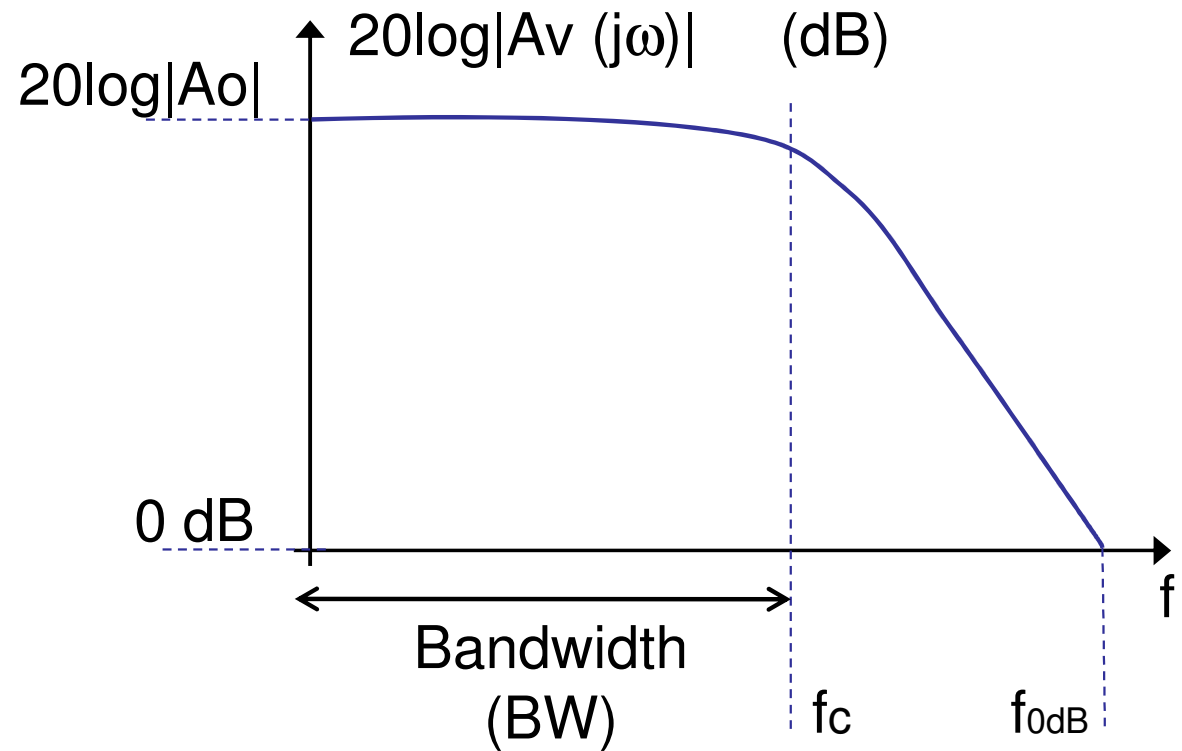

$$A_0 \cdot f_c = 1 \cdot f_{0dB}$$

Gain x Bandwidth = constant

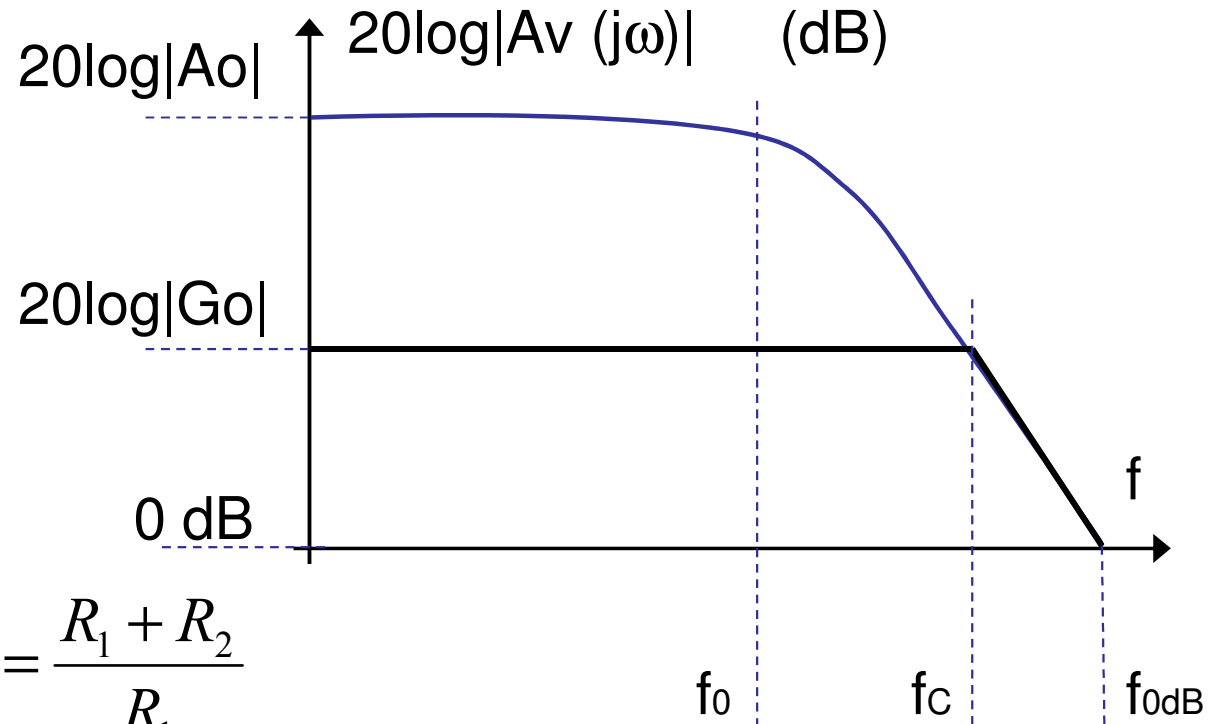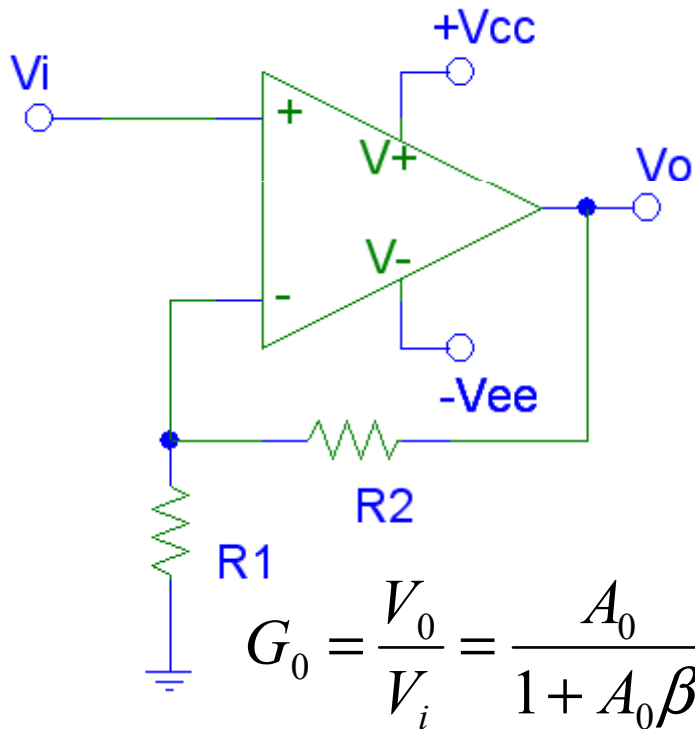

Open Loop Bandwidth (f_0)

$$G_0 \cdot f_C = A_0 \cdot f_0 = f_{0dB}$$

Feed-back amplifier Bandwidth (f_c)


$$f_C = (1 + A_0\beta) \cdot f_0$$

Linear applications of operational amplifier

INDEX

- Voltage follower
- Inverting adder
- Differential amplifier
- Current-voltage converter
- Voltage-current converter
- Low-pass filter / Integrator


Voltage follower

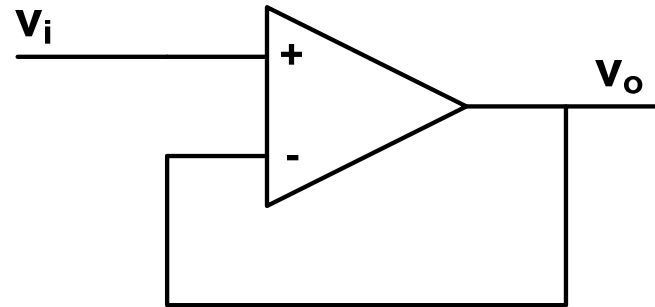

- Virtual short-circuit: $v_+ = v_-$ $v_o = v_i \Rightarrow \frac{v_o}{v_i} = 1$

$$\left. \begin{array}{l} R_i \rightarrow \infty \\ R_o \rightarrow 0 \end{array} \right\} \Rightarrow \text{IMPEDANCE MATCHING}$$


Inverting adder

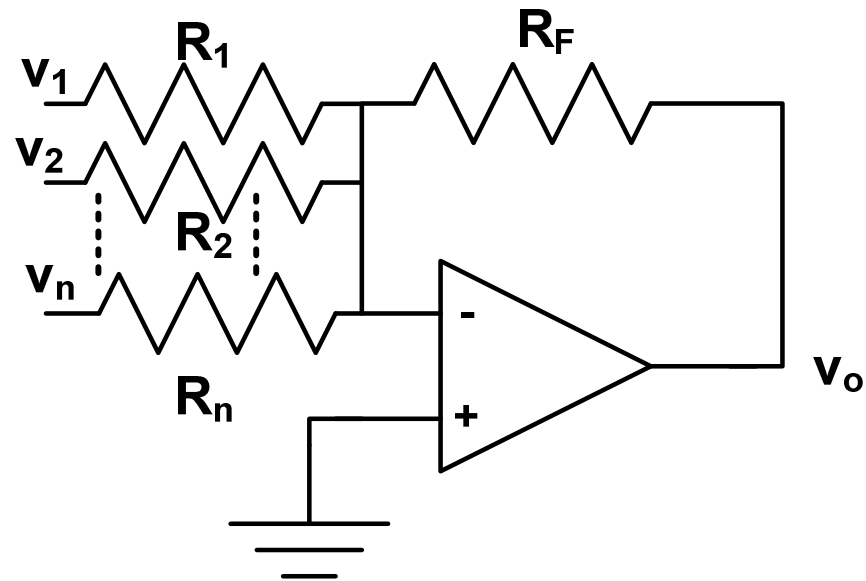

- Virtual short-circuit: $v_+ = v_- = 0$
- $i(R_F) = i(R_1) + i(R_2) \dots + i(R_n)$

$$\frac{-v_o}{R_F} = \frac{v_1}{R_1} + \frac{v_2}{R_2} \dots + \frac{v_n}{R_n} \Rightarrow v_o = - \left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 \dots + \frac{R_F}{R_n} v_n \right)$$

Differential amplifier

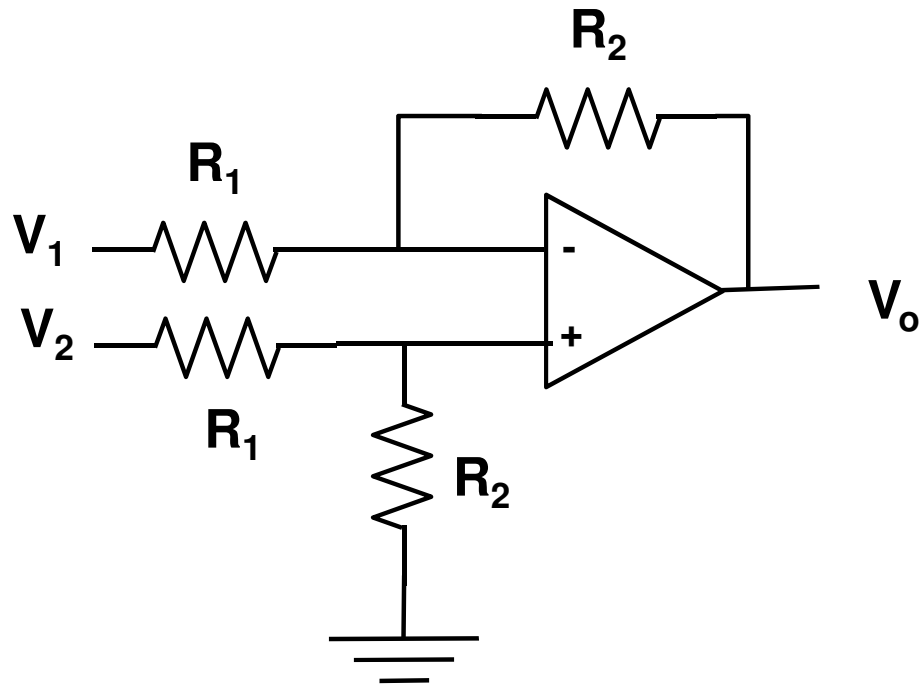

- Superposition


$$v_o = v_o|_{v_1} + v_o|_{v_2}$$

$$v_o|_{v_1} = -\frac{R_2}{R_1} v_1$$

$$v_o|_{v_2} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{R_2}{R_1 + R_2} \cdot v_2 = \frac{R_2}{R_1} \cdot v_2$$


$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

Current-voltage converter


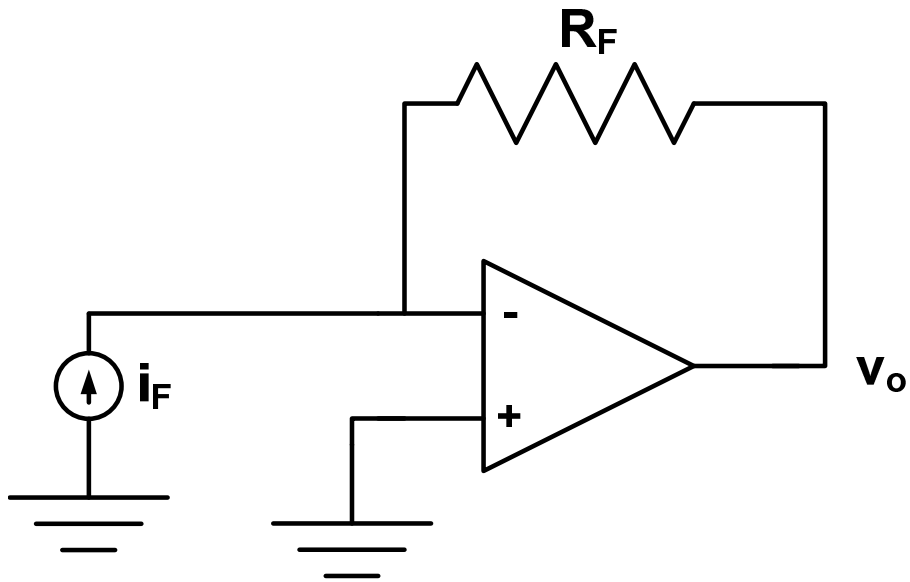


$$v_o = -R_F \cdot i_F$$

Conditioning circuit of photodiode


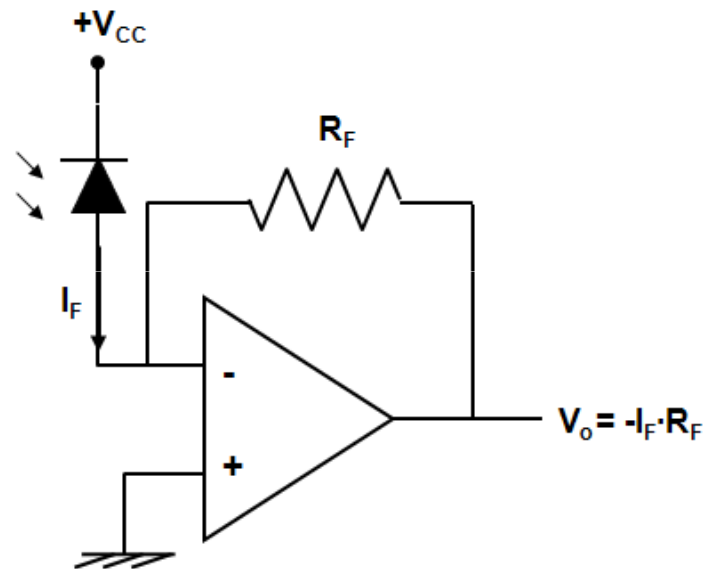


Low pass filter / integrator

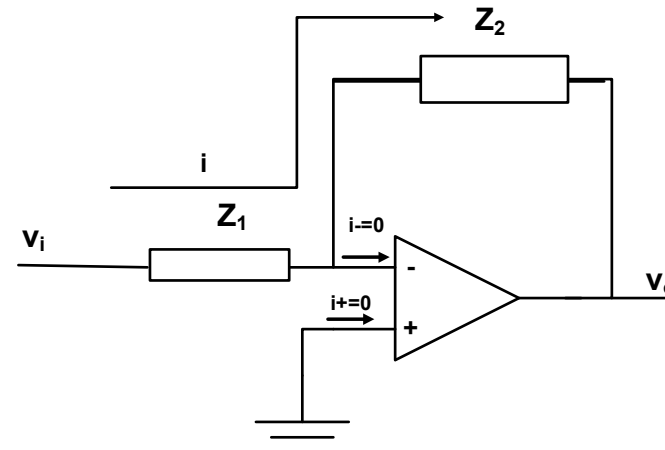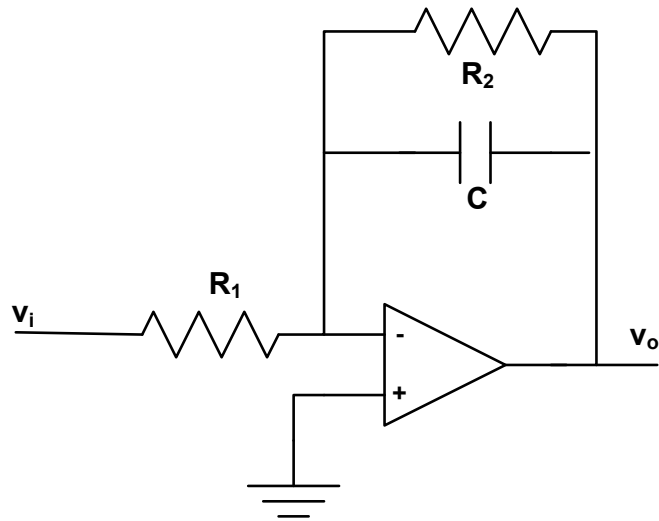

- Virtual short circuit: $v_+ = v_-$
- $i(Z_1) = i(Z_2) = i$
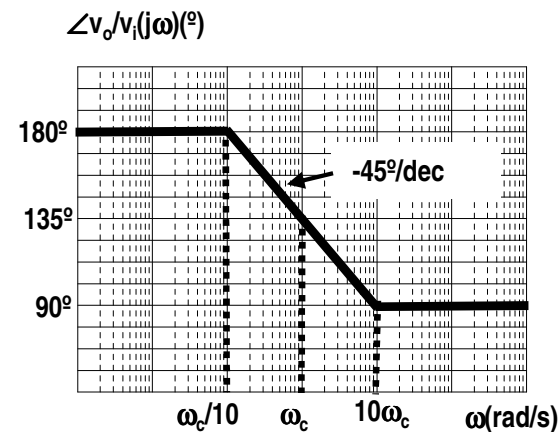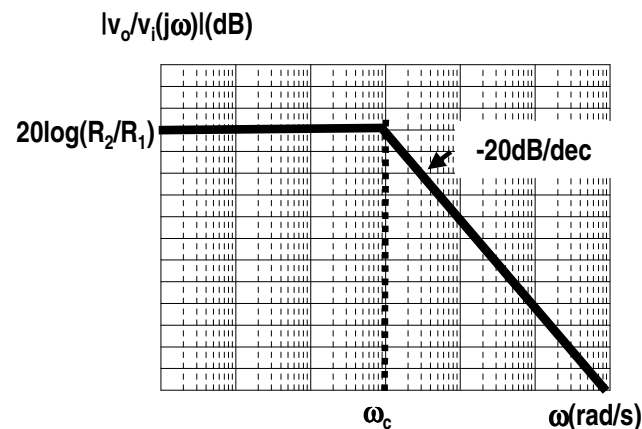
$$\frac{v_o}{v_i}(j\omega) = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + j\omega R_2 C} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_2 C} \quad \text{Pole: } \omega_c = \frac{1}{R_2 C}$$







Non-linear applications of operational amplifier





INDEZ

- Circuits with diodes in the feed-back loop
Limiters and rectifiers
- Comparators with a reference (saturated operation of OA)



Basic Limiter (analogously)

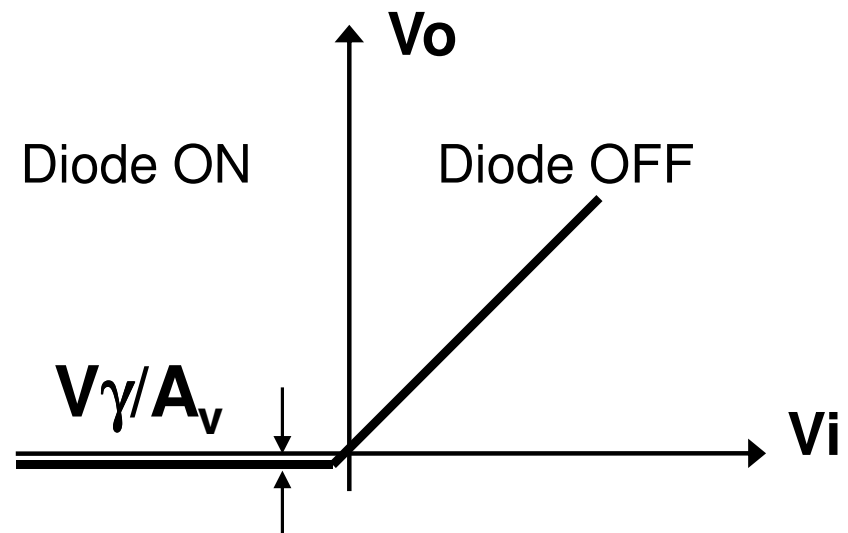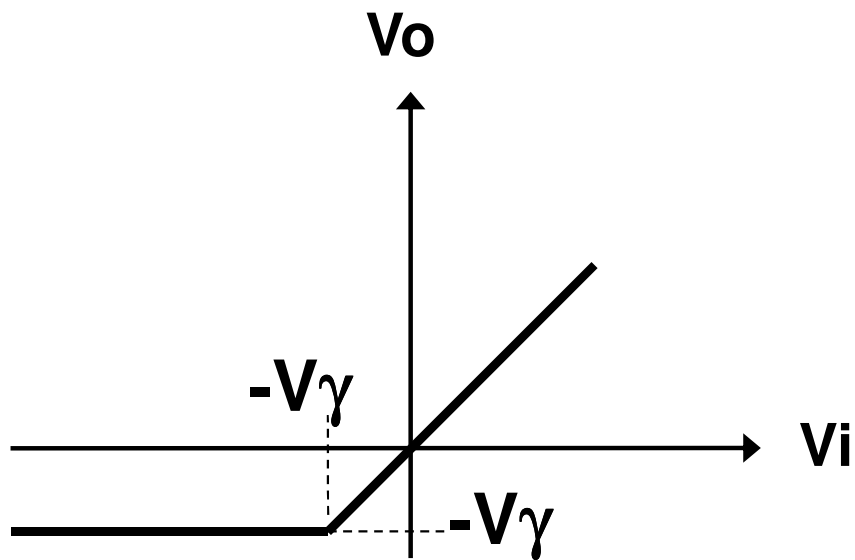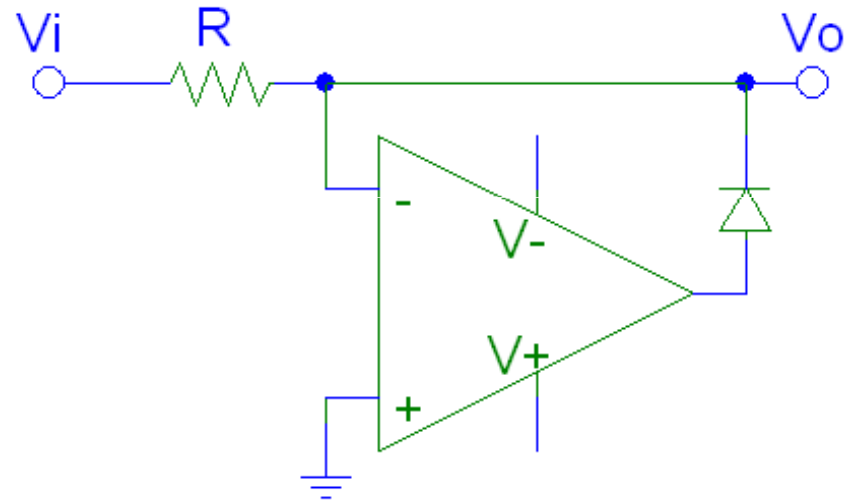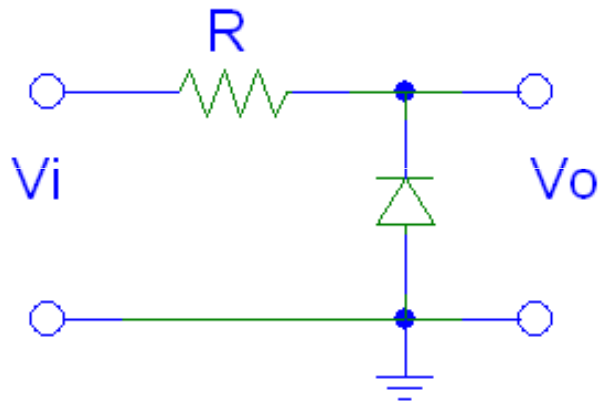


Other limiters

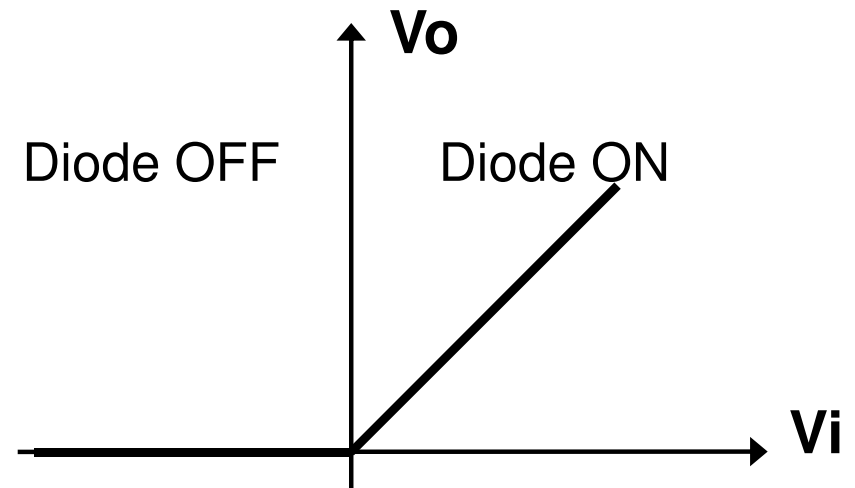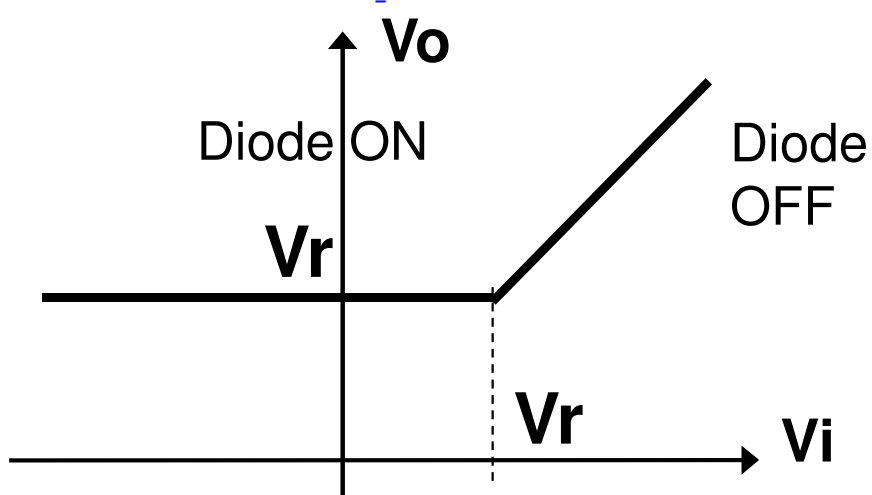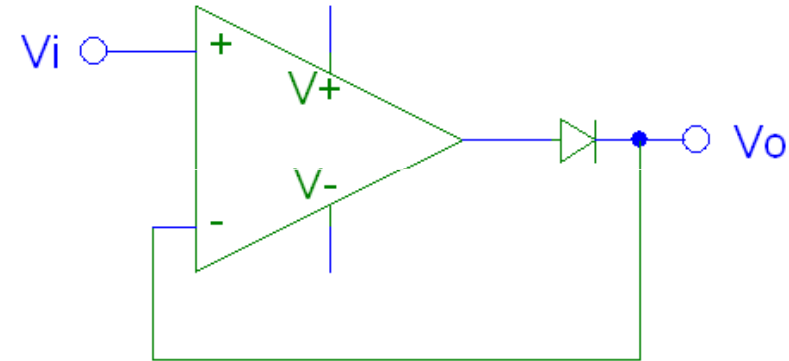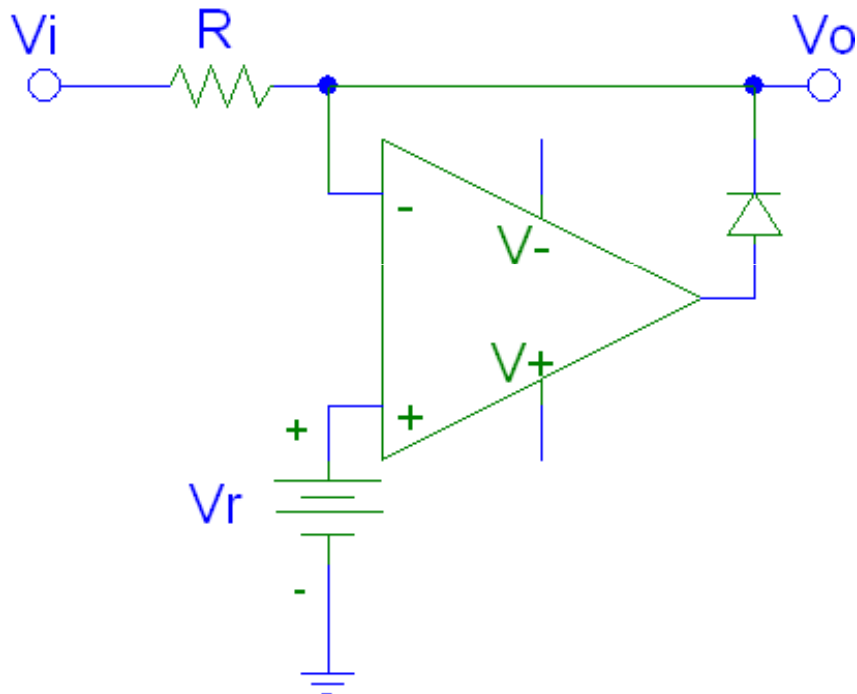



Precision half-wave rectifier

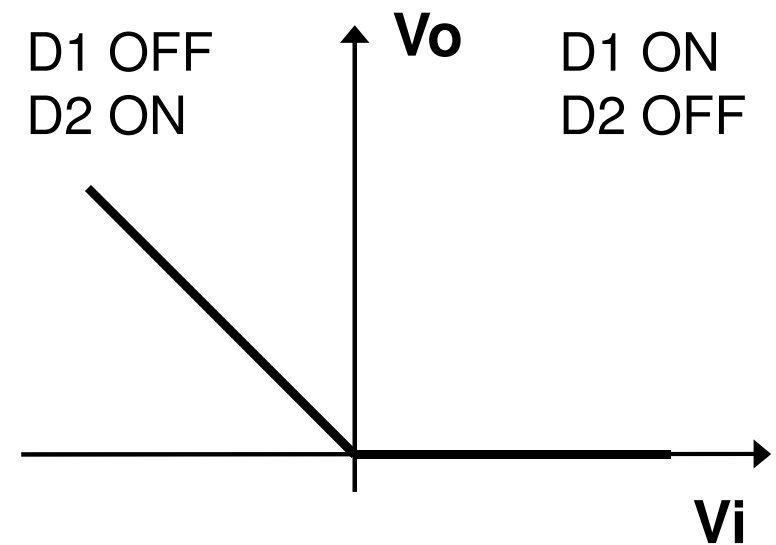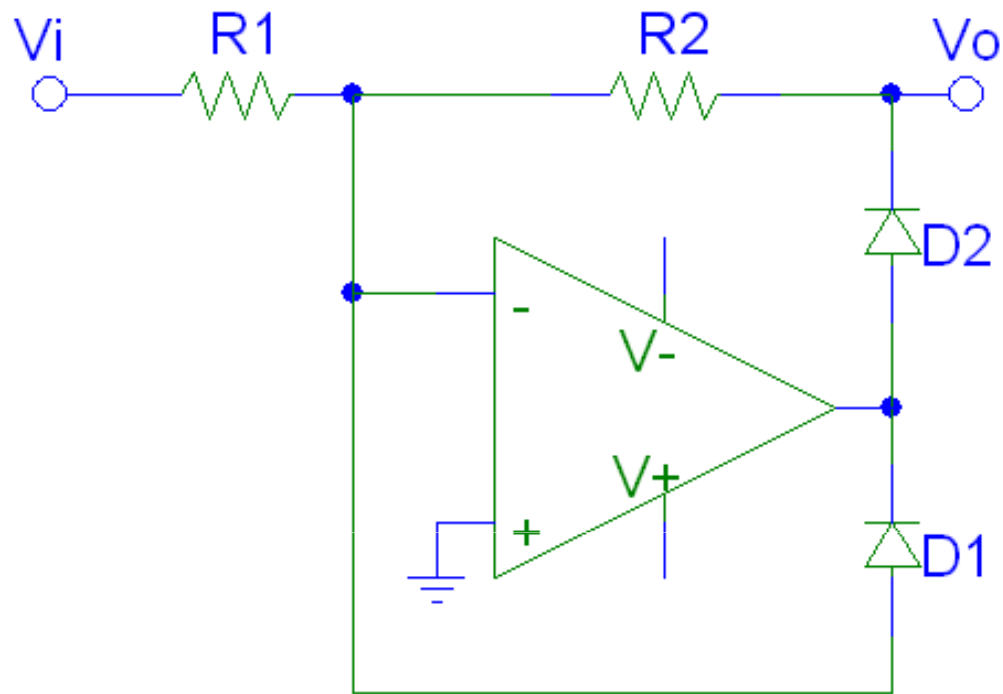



Precision full-wave rectifier

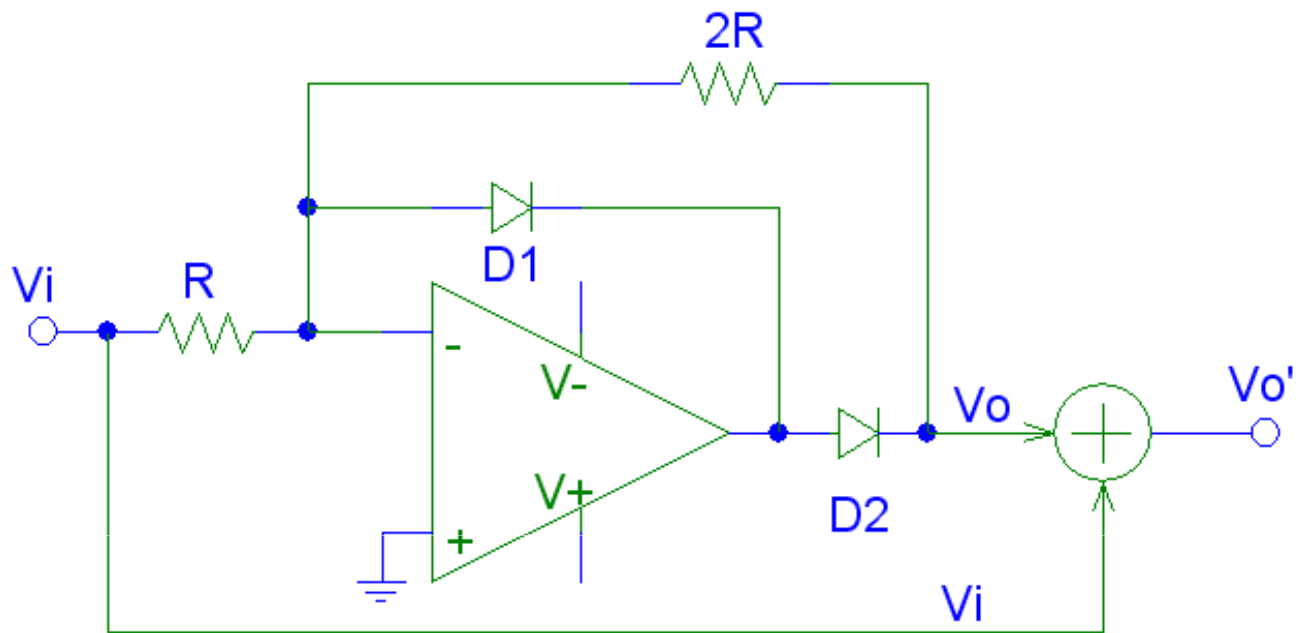



O.A. as a comparator

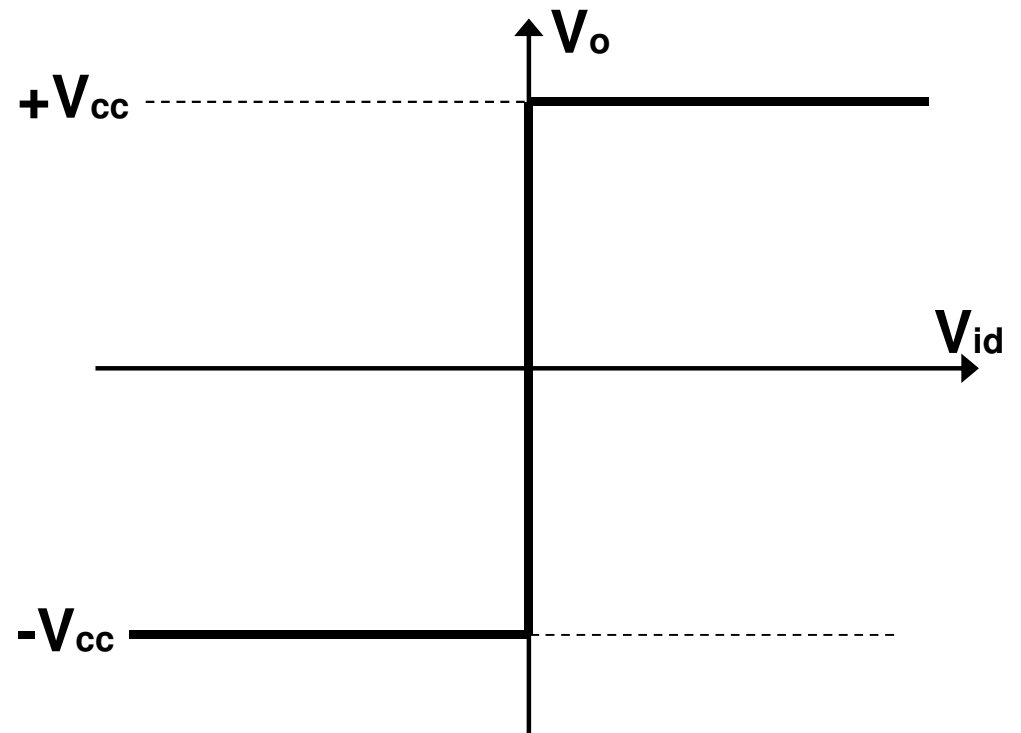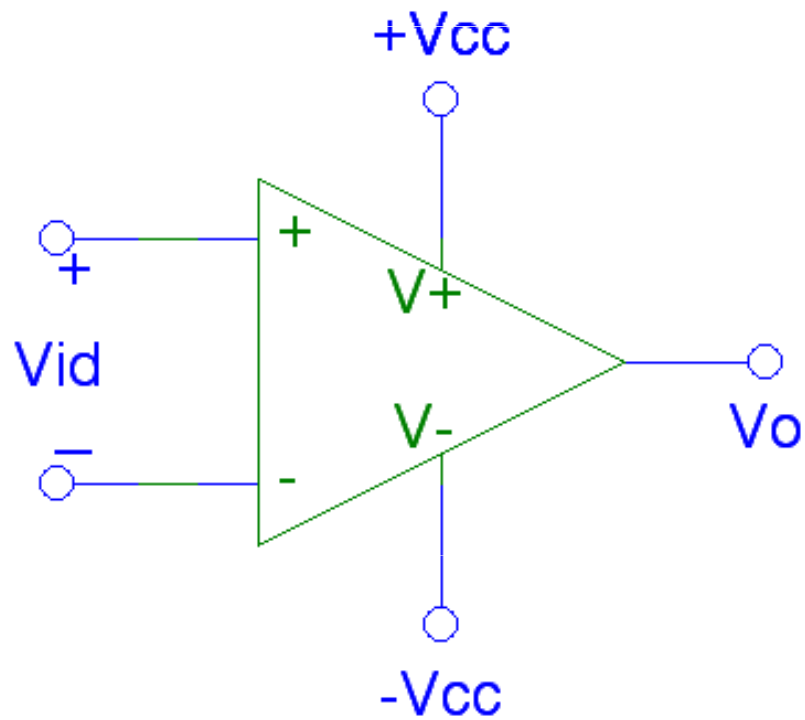

Non-inverting comparator

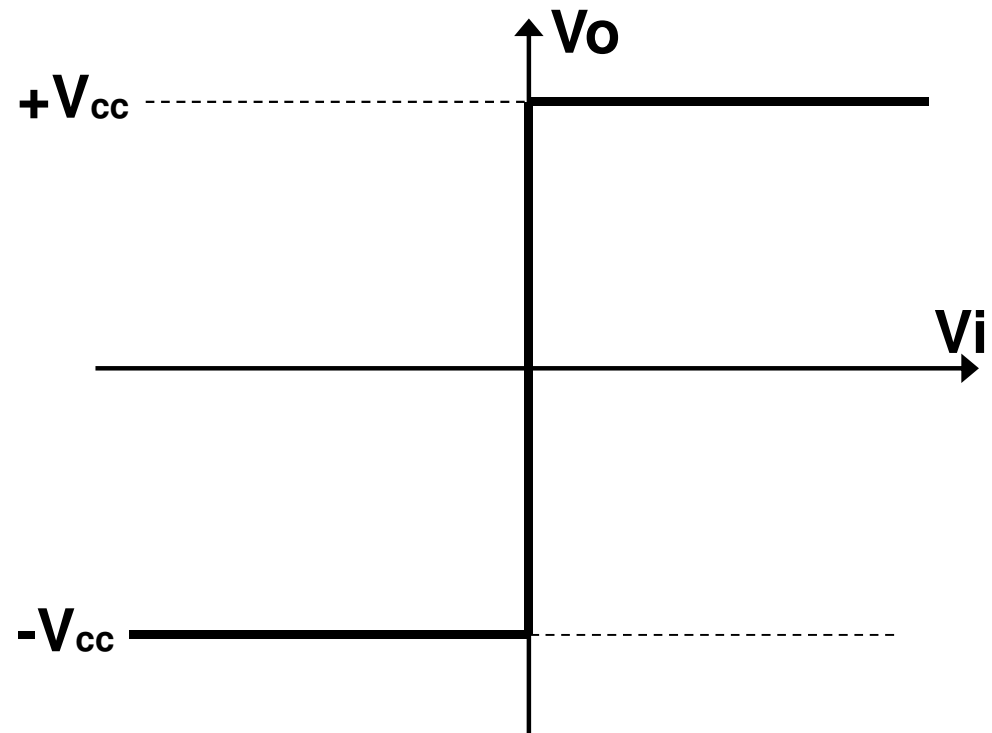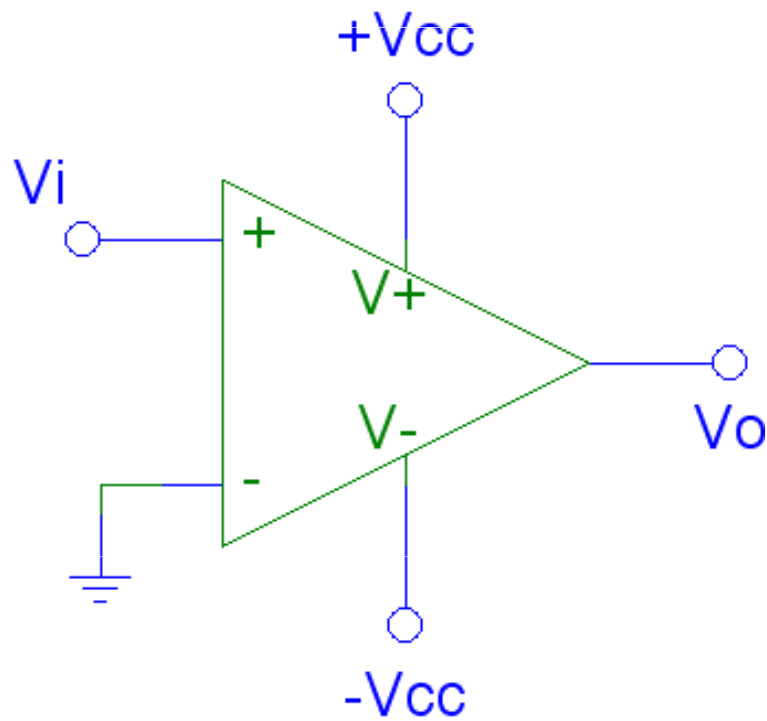

Inverting comparator

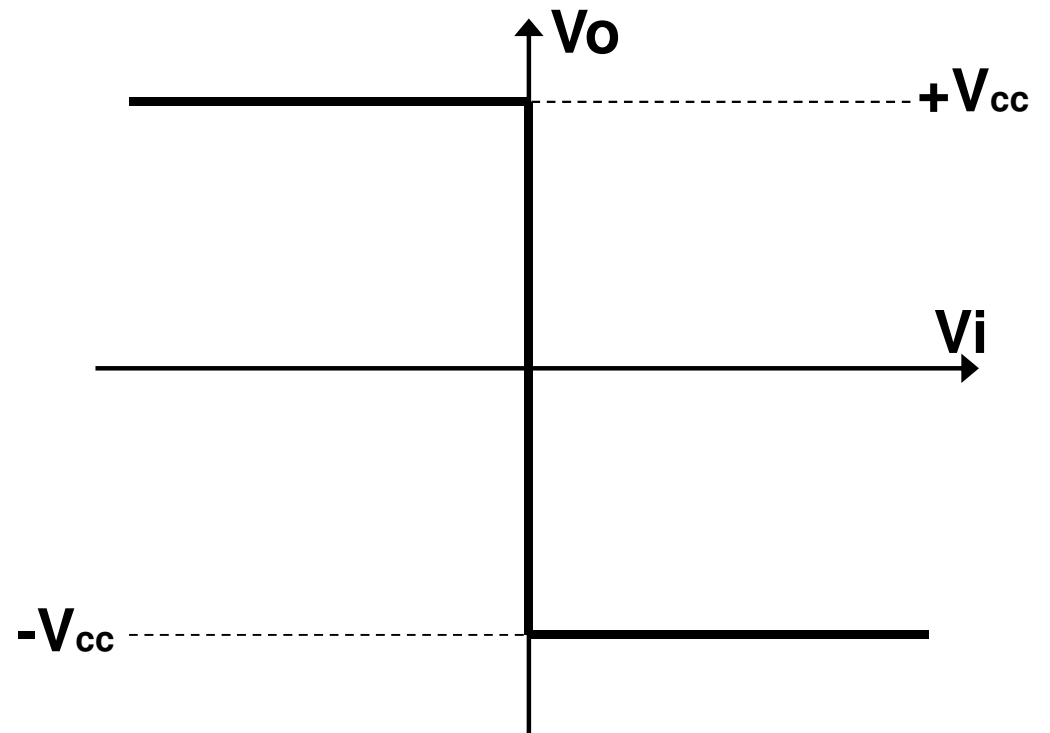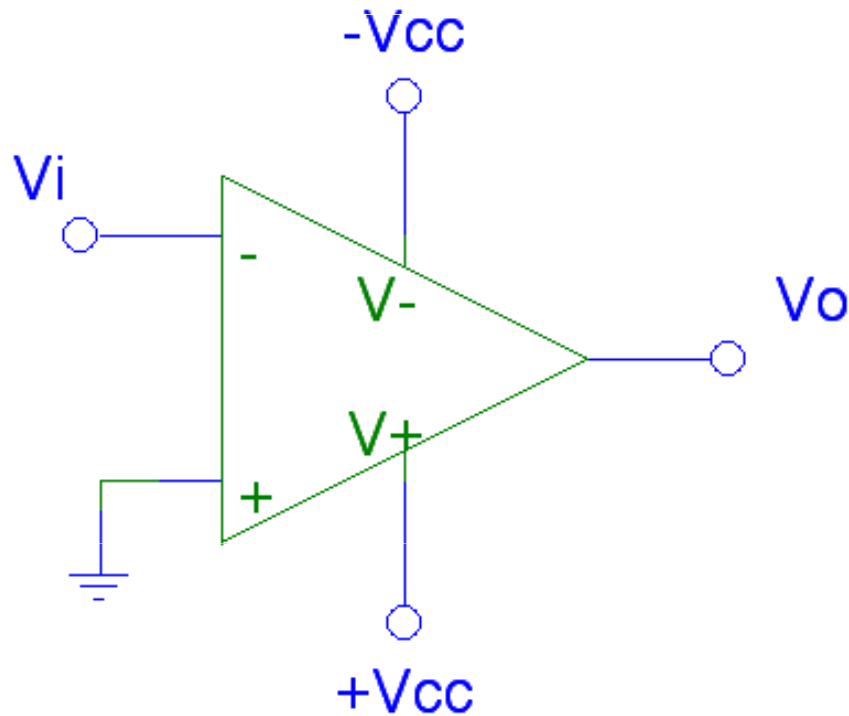

Comparator with a reference

