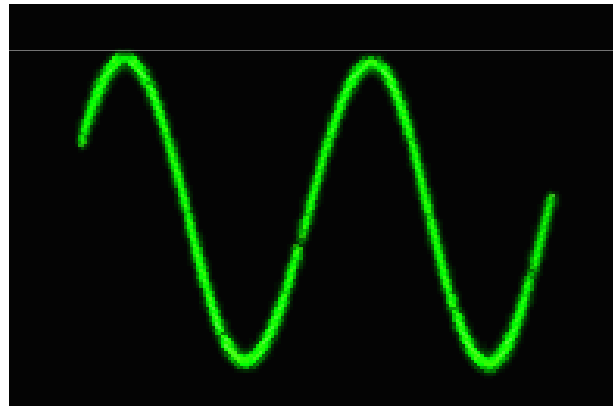


(Analog) Electronics II


Lesson II

Stability of Feedback Amplifiers



Ideal Configuration of a Feedback Amplifier

With negative feedback !

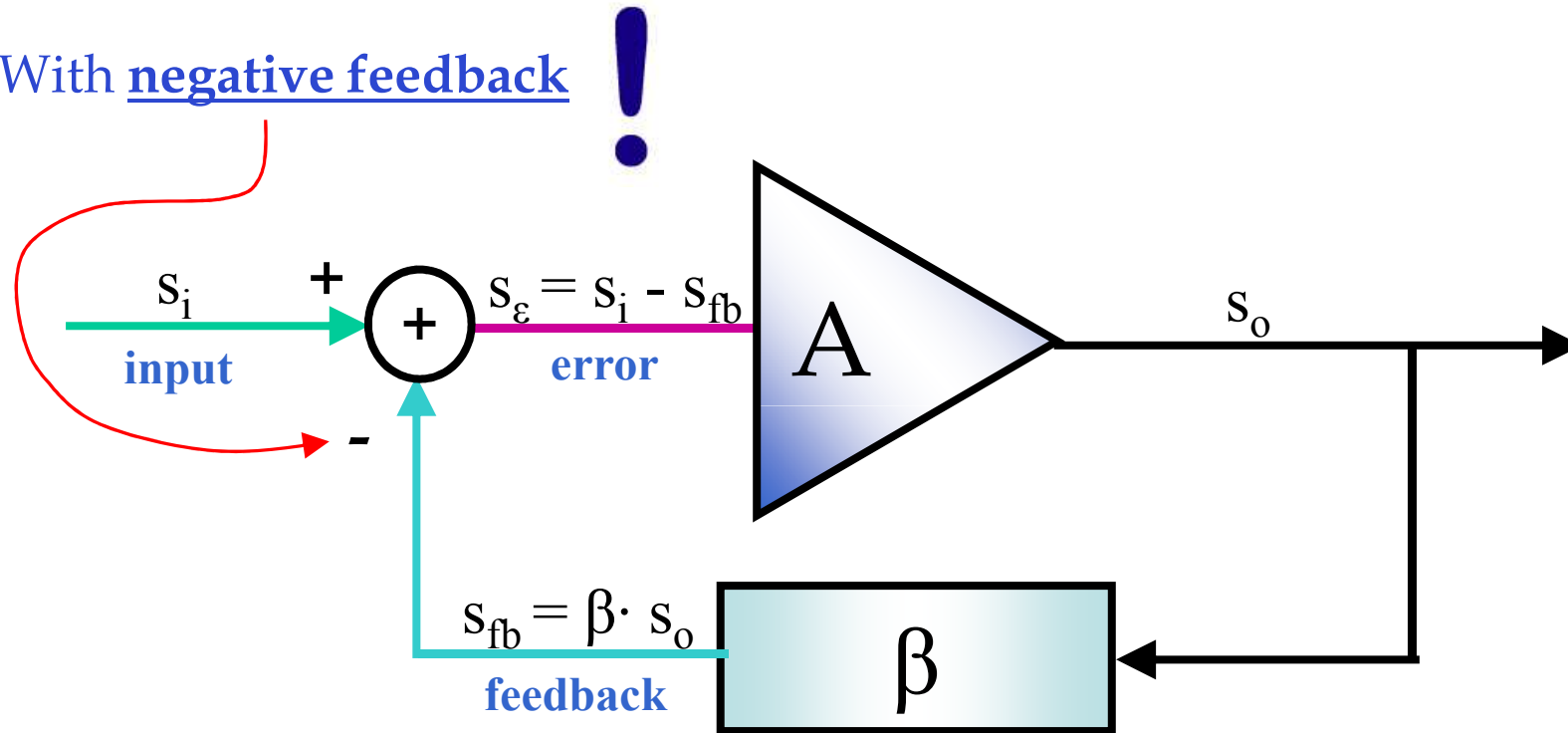

$$A = \frac{a}{1 + a f}$$

What happens with the frequency response?

$$A(s) = \frac{a(s)}{1 + a(s)f(s)}$$

How can we explore the effect of feedback on the frequency response of the amplifier?

Does feedback affect it anyway?

Why did we use feedback anyway?


At the cost of **GAIN REDUCTION**, we obtain

An amplifier closer to ideal characteristics:

- Insensitivity against active component parameter dispersion.
- Linear Gain
- Input/Output Impedances

However, the circuit has tendency toward
OSCILLATION.


Oscillation ??????????

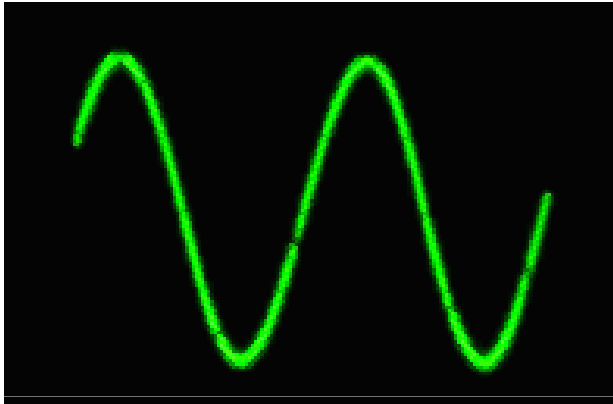

What frequency?

What amplitude?

Why?

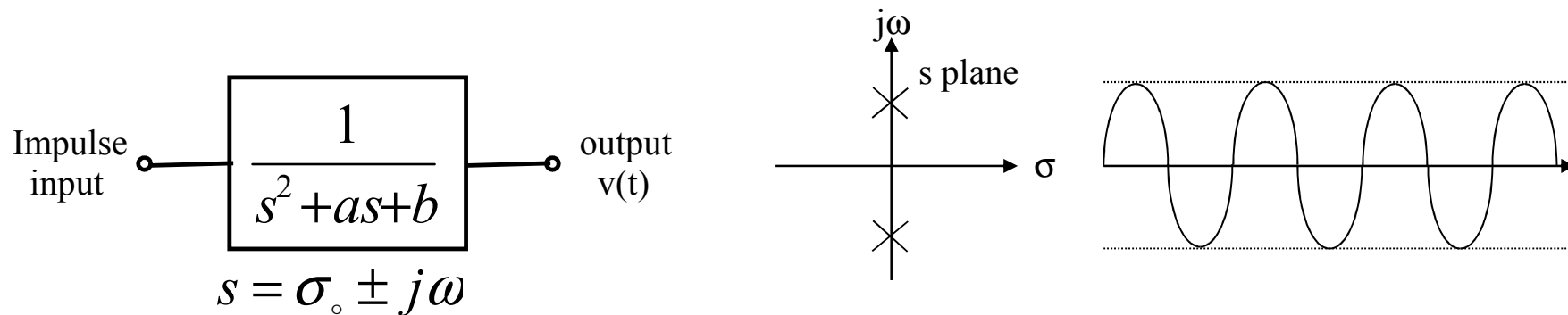


$$v(t) = e^{\sigma_o t} [e^{j\omega_n t} + e^{-j\omega_n t}] = 2e^{\sigma_o t} \cos(\omega_n t)$$

Feedback, Poles and Stability


1. One pole system
2. Two pole system
3. More than two poles



Feedback, Poles and Stability

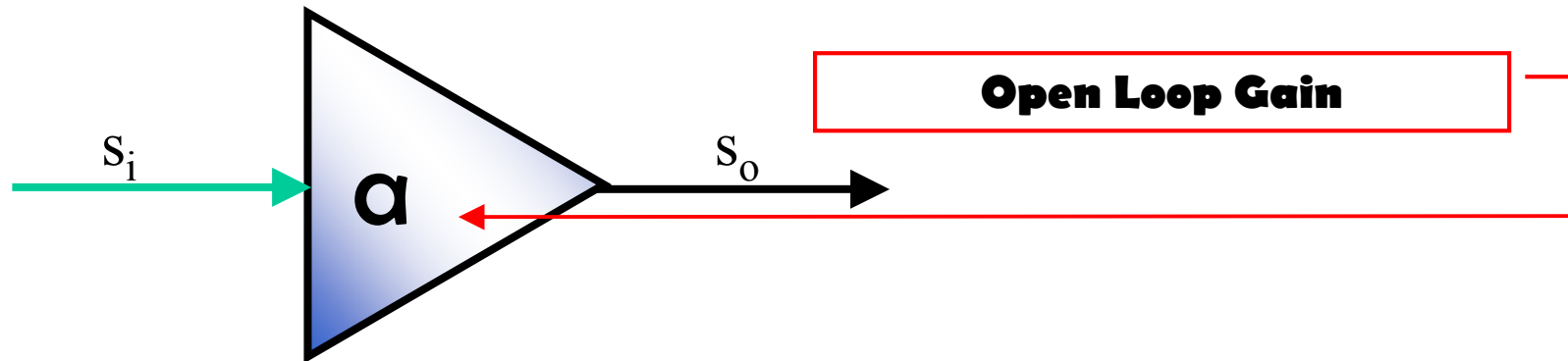
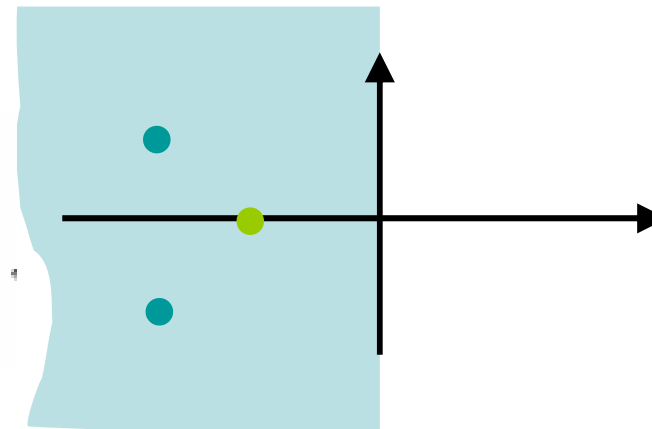
$$A(s) = \frac{K}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)\cdots\left(1 - \frac{s}{p_n}\right)}$$



Open loop amplifiers are always STABLE systems

Feedback, Poles and Stability

Case 1. $A(s)$ has one pole

Frequency Domain

Gray-Meyer

$$a(s) = \frac{K}{1 - \frac{s}{p_1}}$$


Sedra-Smith

$$a(s) = \frac{A_0}{1 + \frac{s}{\omega_P}}$$


Time Domain

$$v_{out} + \frac{1}{\omega_P} \frac{dv_{out}}{dt} = A_0 v_{in}$$

Frequency Domain

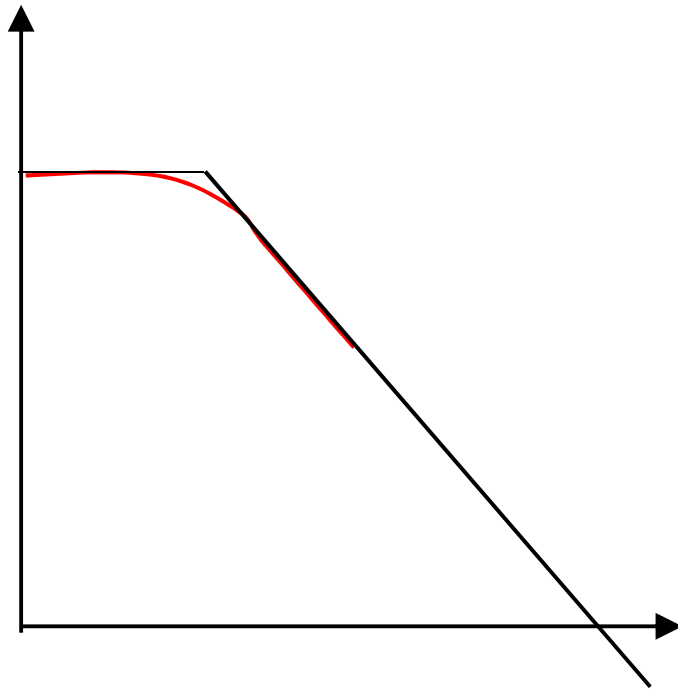


Time Domain

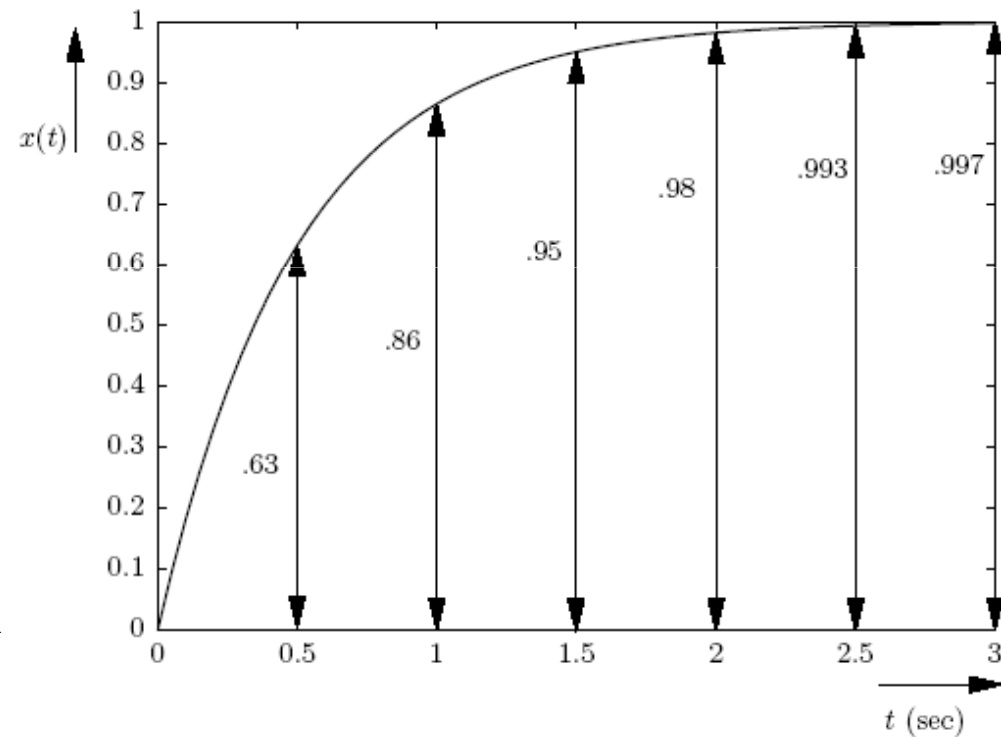

Feedback, Poles and Stability
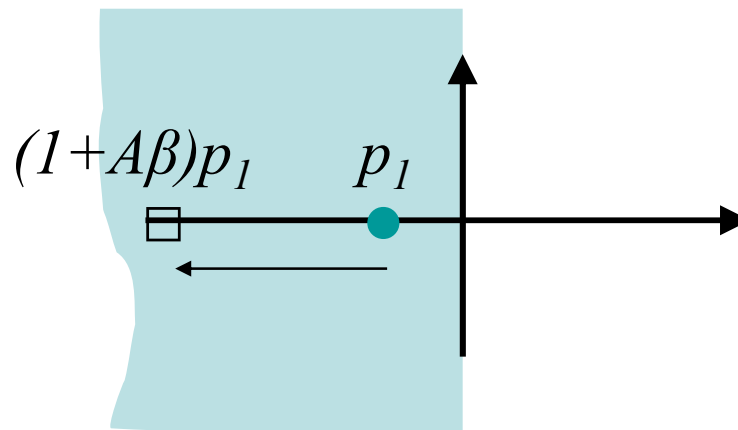
$$A(s) = \frac{K}{1 + Kf} \frac{1}{1 - \frac{s}{p_1(1 + Kf)}}$$




unconditionally STABLE

Feedback, Poles and Stability


Gain x Bandwidth Product

$$A(s) = \frac{K}{1 + K f} \frac{1}{1 - \frac{1}{p_1(1 + K f)}} \quad \longrightarrow$$

	Basic	Feedback
GAIN	K	$\frac{K}{1 + K f}$
BW	p_1	$p_1(1 + K f)$

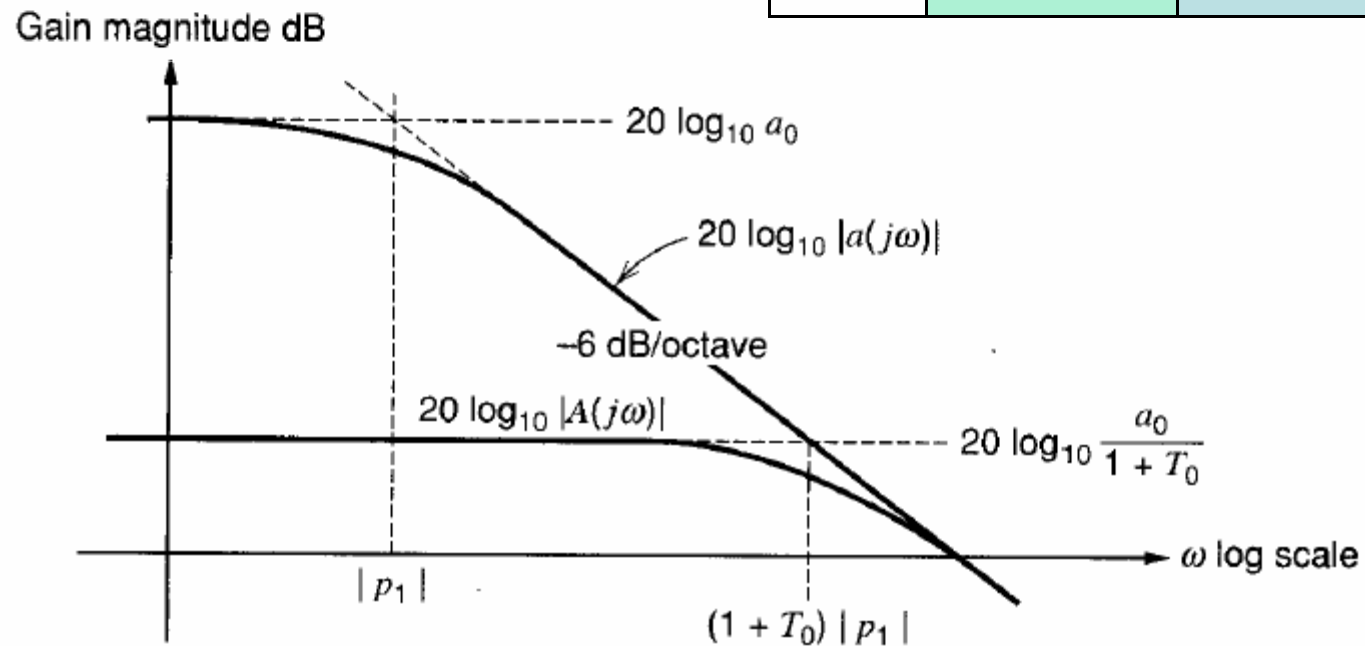

Feedback, Poles and Stability

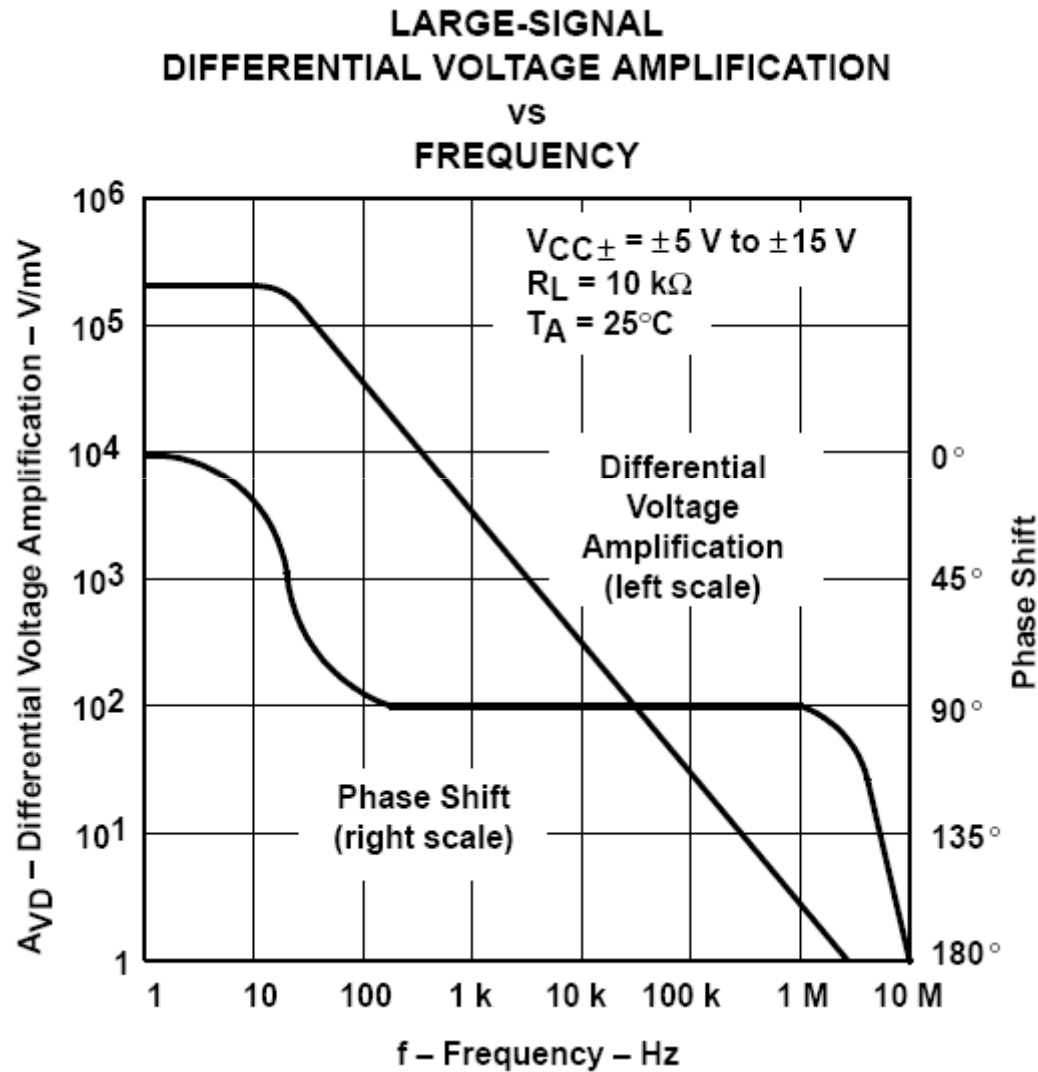


Feedback, Poles and Stability

Hints on what happens with higher order systems

Case 2. $a(s)$ has two poles
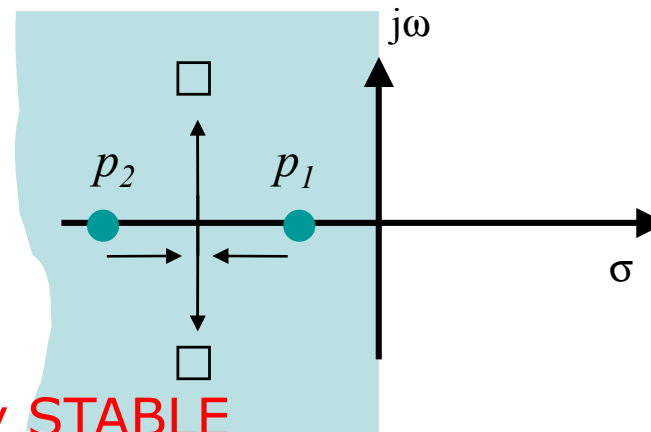
$$A(s) = \frac{K}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)}$$




unconditionally STABLE

Feedback, Poles and Stability

Case 3. $a(s)$ more than two poles

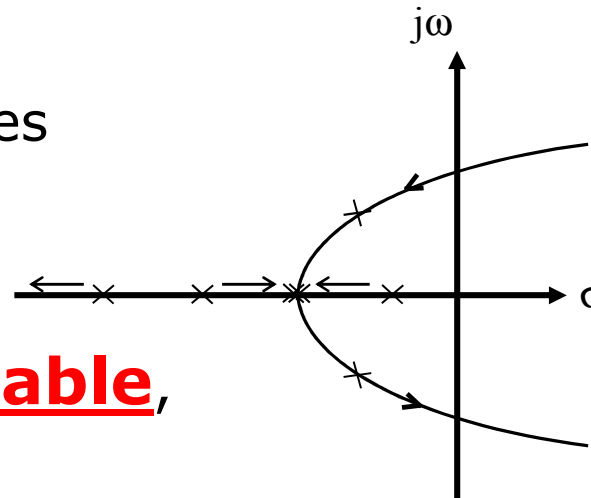System can become **unstable**,
depending on f strength.



Origin of the instability



Origin of the instability

IF feedback can turn our system unstable . . .

. . . . means that poles of $a(s)$ are not the poles of $A(s)$

$$A(s) = \frac{a(s)}{1 + a(s)f(s)} \quad \longrightarrow \quad 1 + \underbrace{a(s)f}_{L(s)} = 0 \quad \text{characteristic equation}$$

$$A(j\omega) = \frac{a(j\omega)}{1 + a(j\omega)f} \quad \longrightarrow \quad 1 + a(j\omega)f = 0$$
$$1 + |a(j\omega)f| e^{j\phi(\omega)} = 0$$


Origin of the instability

¿What happens when $\phi = \pi$?

- $|a(\omega_\pi f) e^{j\pi}| = -|a(\omega_\pi) f|$

- $A(j\omega) = \frac{a(j\omega)}{1 - |a(j\omega)|f}$

What is significant here?

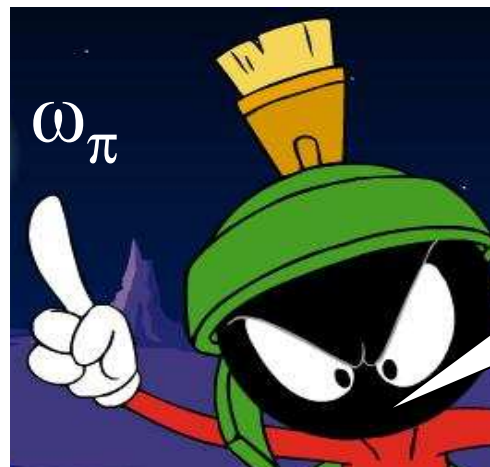


Be careful
with it !!!!

Origin of the instability

Phase change in the loop gain $A\beta$ has influence in the type of feedback of the amplifier :

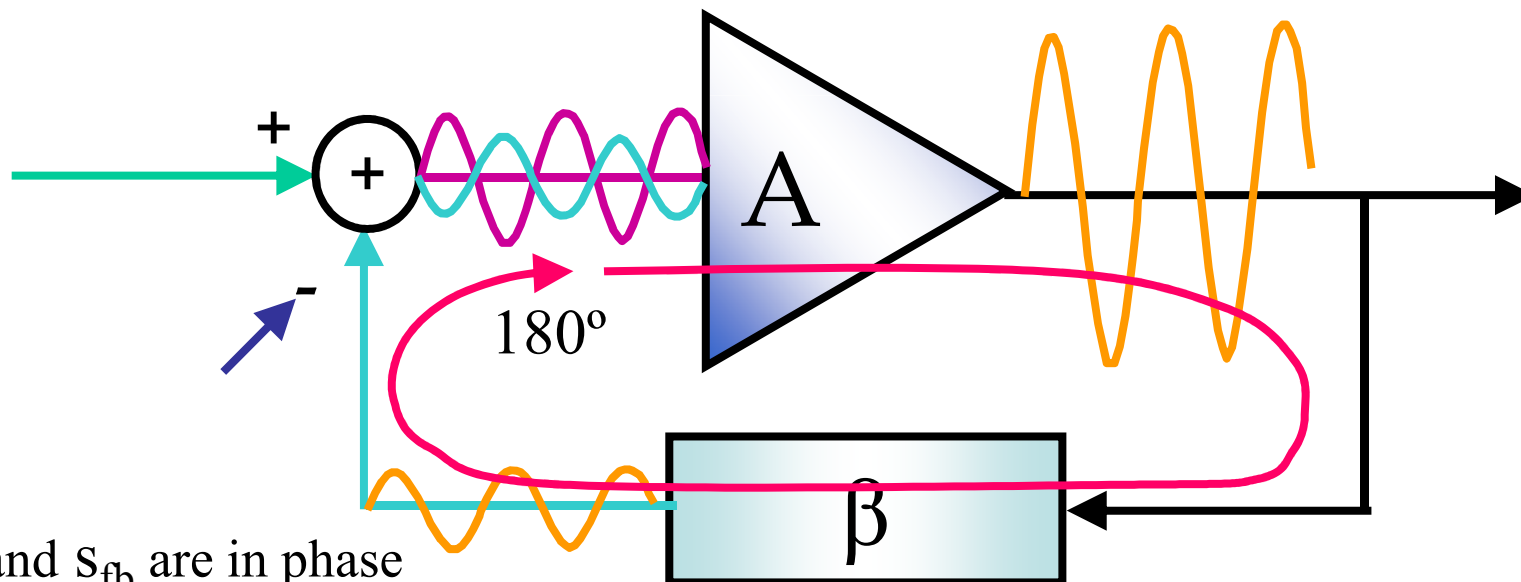- $\beta < 1$
- $A\beta$ is always positive




S_e and S_{fb} are in phase
..... thus the comparator SUBTRACTS

Origin of the instability

At ω_π :

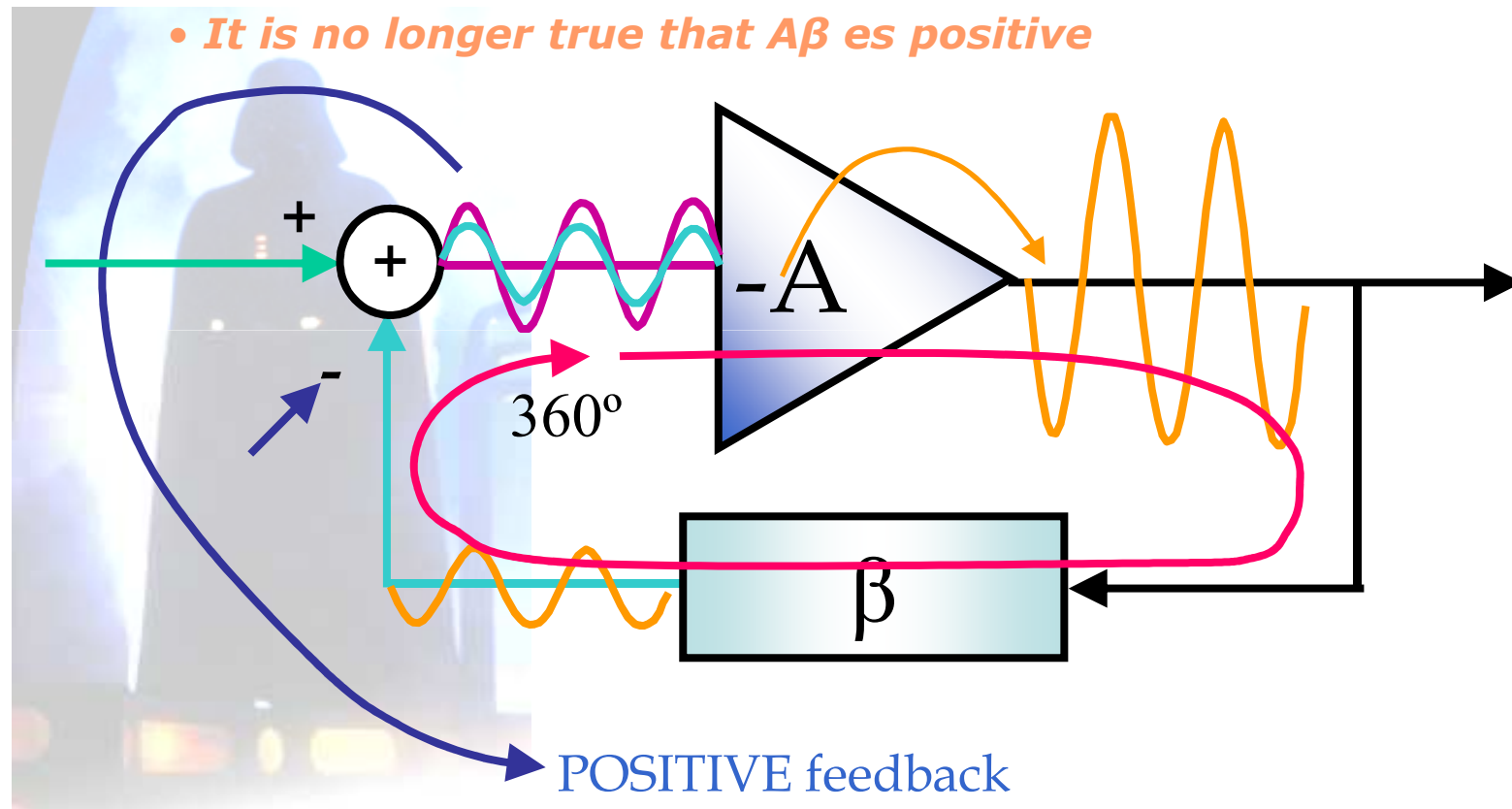- It is no longer true that $A\beta$ is positive




Origin of the instability


- We have clear out the **OSCILLATION FREQUENCY**.
- How about the conditions for oscillation,
... Why does it depend on f ?

Origin of the instability

$$a(\omega_\pi) f < 1$$

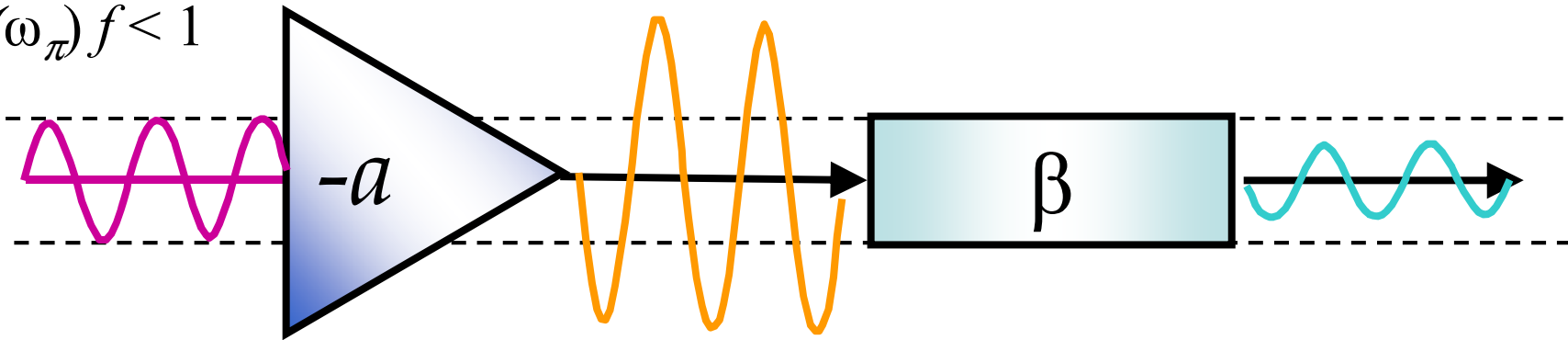

$$a(\omega_\pi) f > 1$$

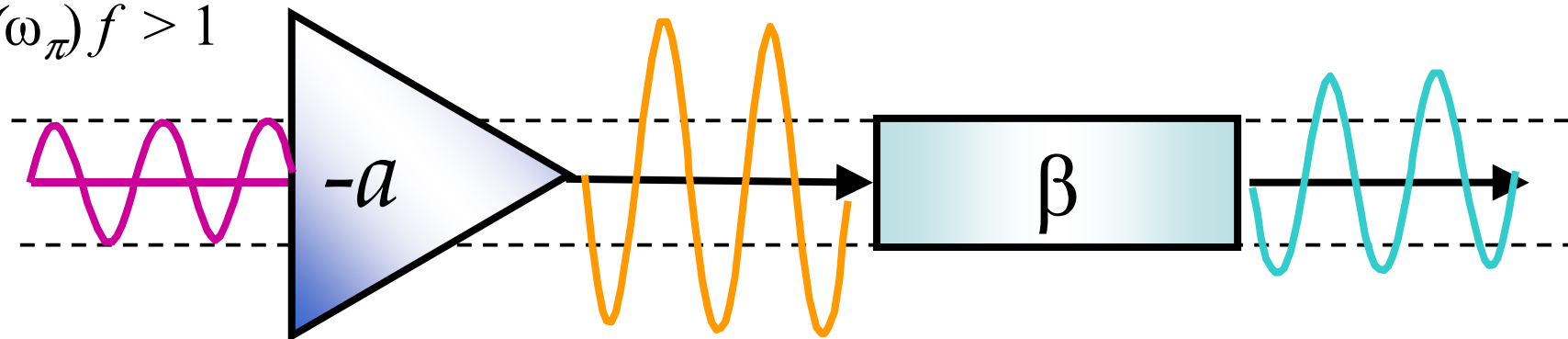

Tools to analyze the stability of feedback amplifiers




Tools to analyze the stability . . .

The secret is within the LOOP GAIN, $a(s) f$

$$a(j\omega) f$$


$$|a(j\omega) f| e^{j\phi(\omega)}$$

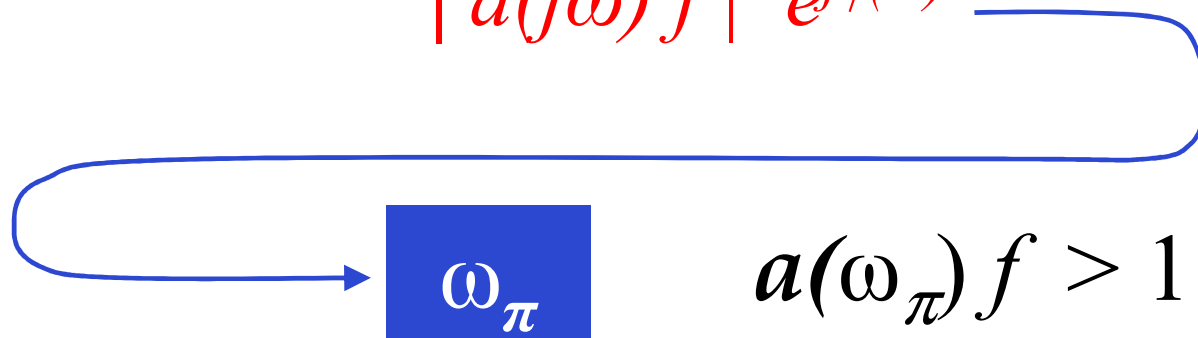

Tools to analyze the stability . . .

Starting point

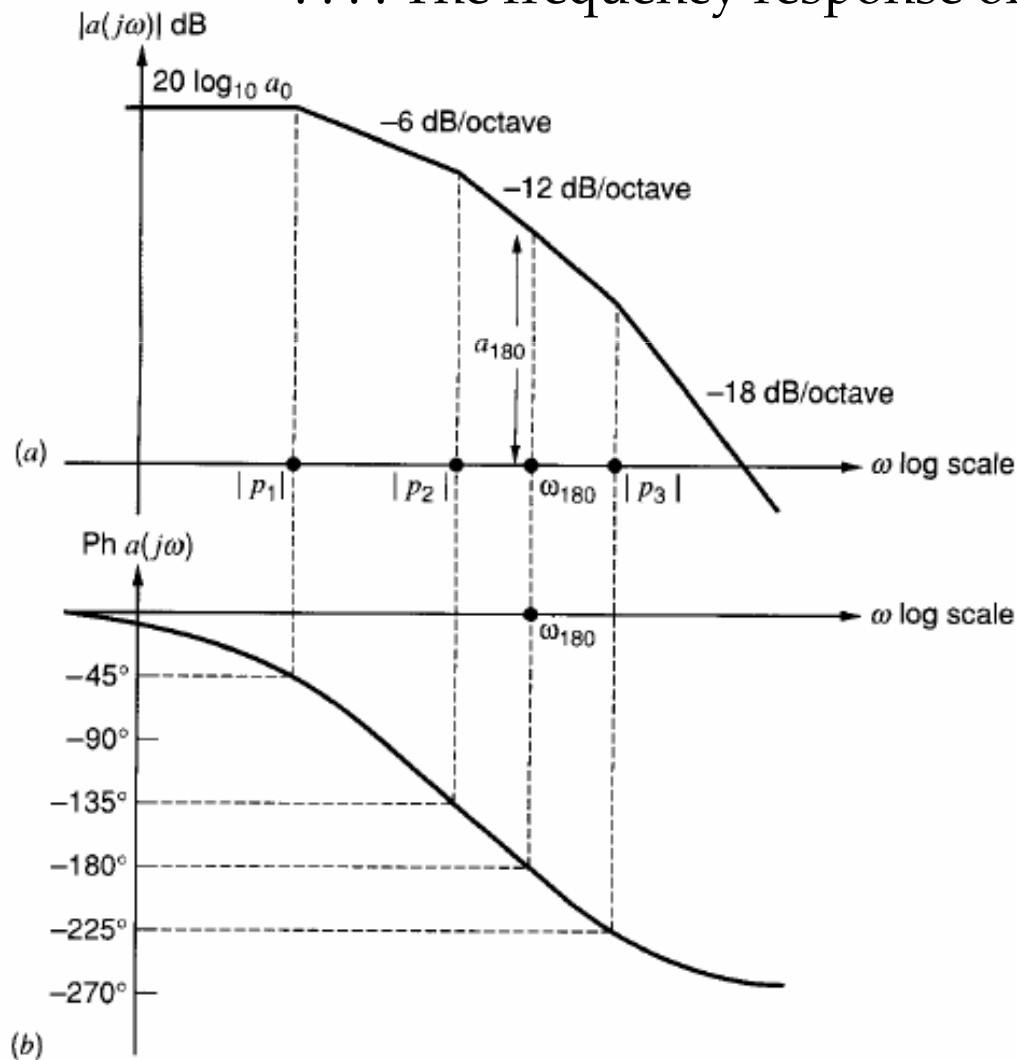
. . . . The frequency response of the BASIC AMPLIFIER



Tools to analyze the stability . . .

Nyquist diagram


Polar representation of $a(j\omega)f$

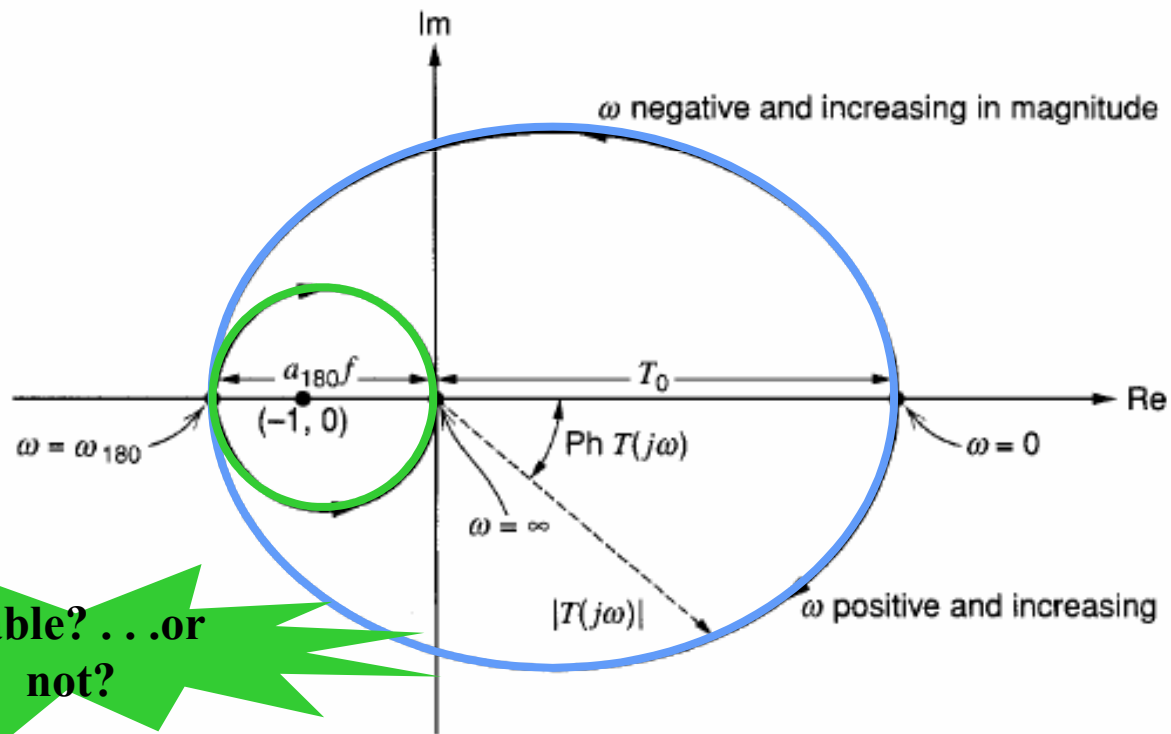

Stable? . . .or
not?

Tools to analyze the stability . . .

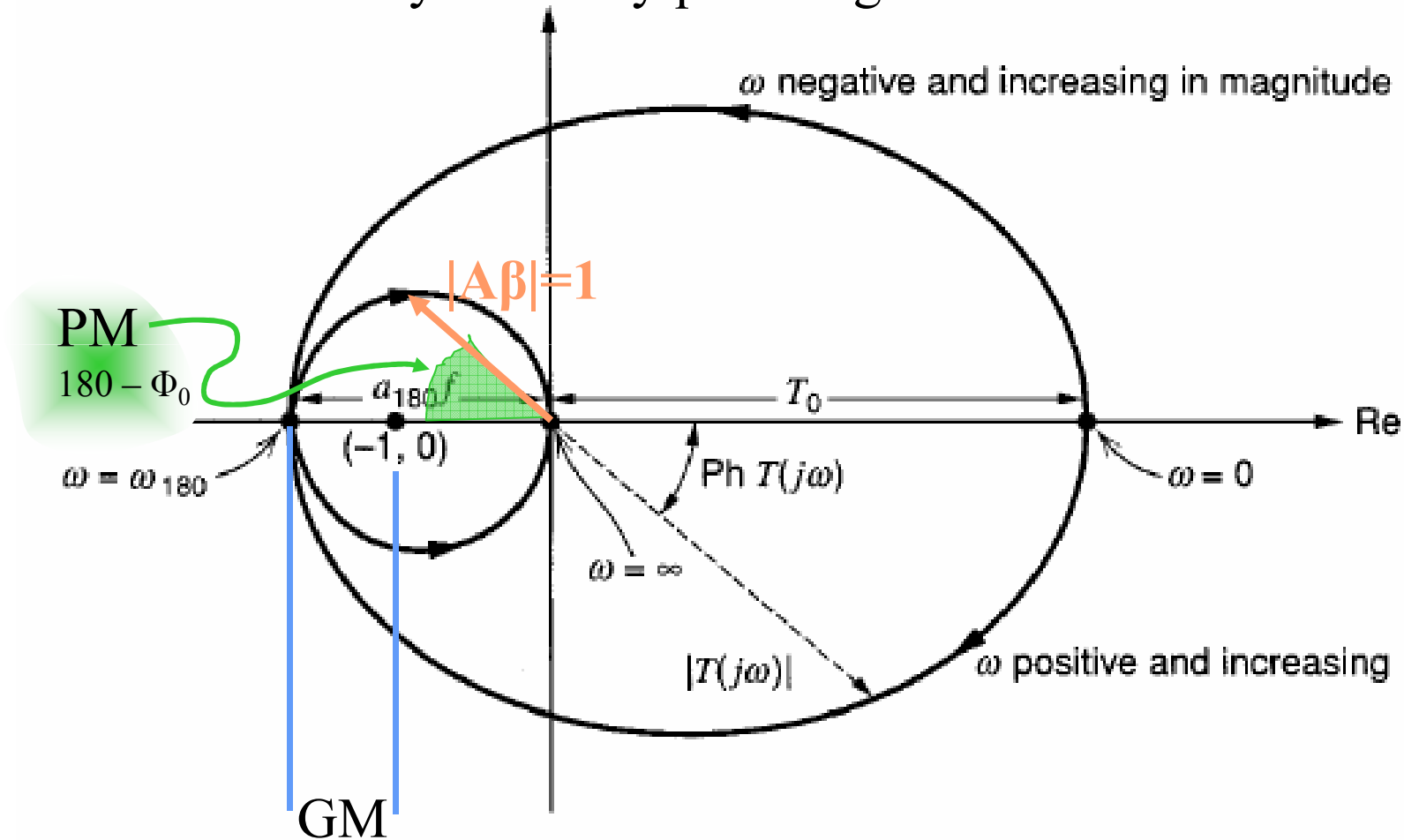Criteria for stability in the Nyquist diagram



Tools to analyze the stability . . .


$a(j\omega)f$ in the Bode plot

$$\begin{aligned}20 \log_{10}(a(j\omega)f) &= 20 \log_{10} [a(j\omega)] + 20 \log_{10} [f] = \\ &= 20 \log_{10} [a(j\omega)] - 20 \log_{10} [1/f] = \\ &= 20 \log_{10} [a(j\omega)] - 20 \log_{10}(A)\end{aligned}$$

(feedback network is resistive and presents a flat frequency response)

Tools to analyze the stability . . .

Two basic reference frequencies,

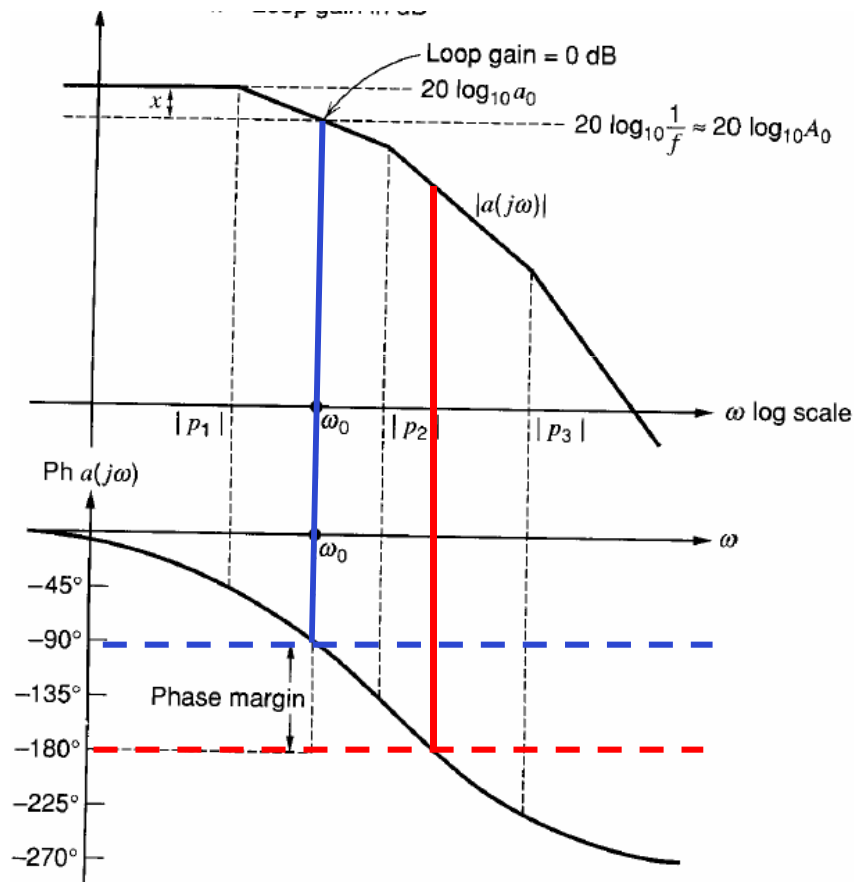

	f_0	f_π
$a(f)$	a_0	a_π
$\Phi(f)$	Φ_0	Φ_π

donde, $a_0 = A (=1/f)$


$\Phi_\pi = -180$

$$\text{PM} = 180^\circ + \Phi_0$$

$$\text{GM} = G - a_\pi$$



Tools to analyze the stability . . .

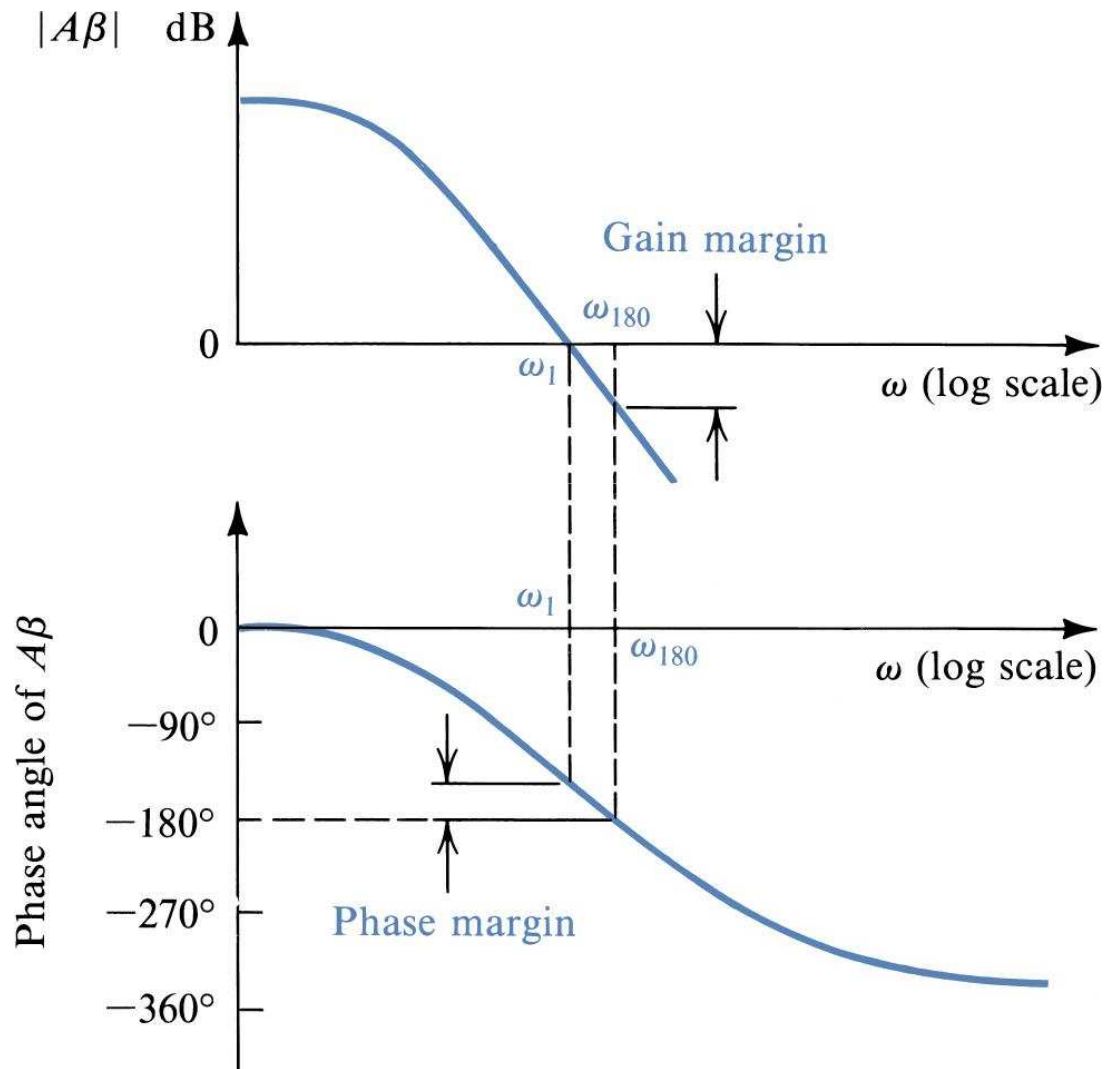

Tools to analyze the stability . . .

The importance of the Phase Margin,


For ω_0

$$A_f(j\omega_0) = \frac{a(j\omega_0)}{1+a(j\omega_0)f}$$
$$= \frac{(1/f) e^{-j\theta_0}}{1+e^{-j\theta_0}}$$

en las que

$$\theta_0 = 180 - \text{PM}$$

$$\left| A_f(j\omega_0) \right| = \frac{(1/f)}{\left| 1+e^{-j\theta_0} \right|}$$

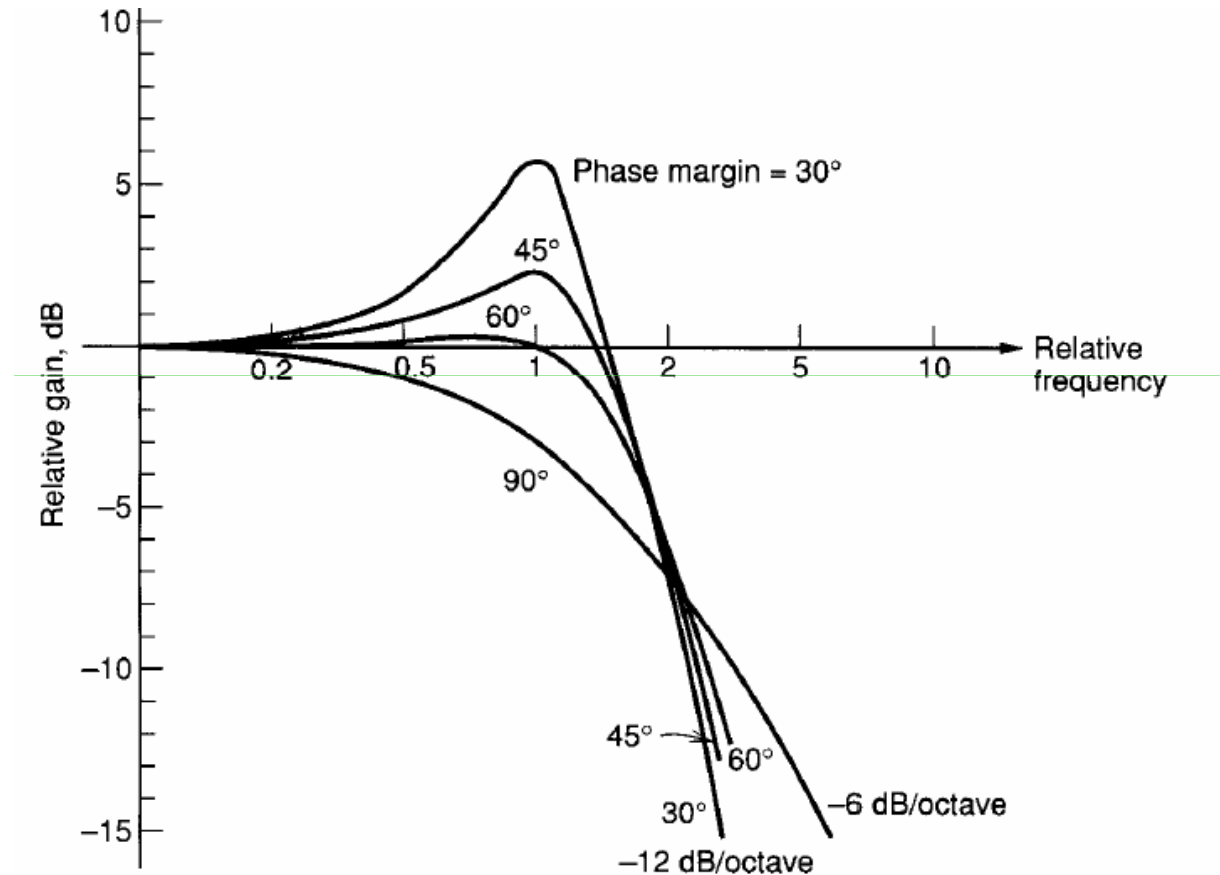

Compensation



Compensation

Tools to control the gain/phase margins

Modify the BASIC AMPLIFIER freq. response $a(s)$, by:

- **DOMINANT POLE:**

Place a new pole at LF


- **POLE-ZERO:**

Place a new pole at LF and cancel lowest frequency pole of basic amplifier with a new zero.

AIM: Keep the phase change in the loop below -180° at all frequencies where the loop gain is greater than unity (UNITY GAIN COMPENSATION)



Compensation

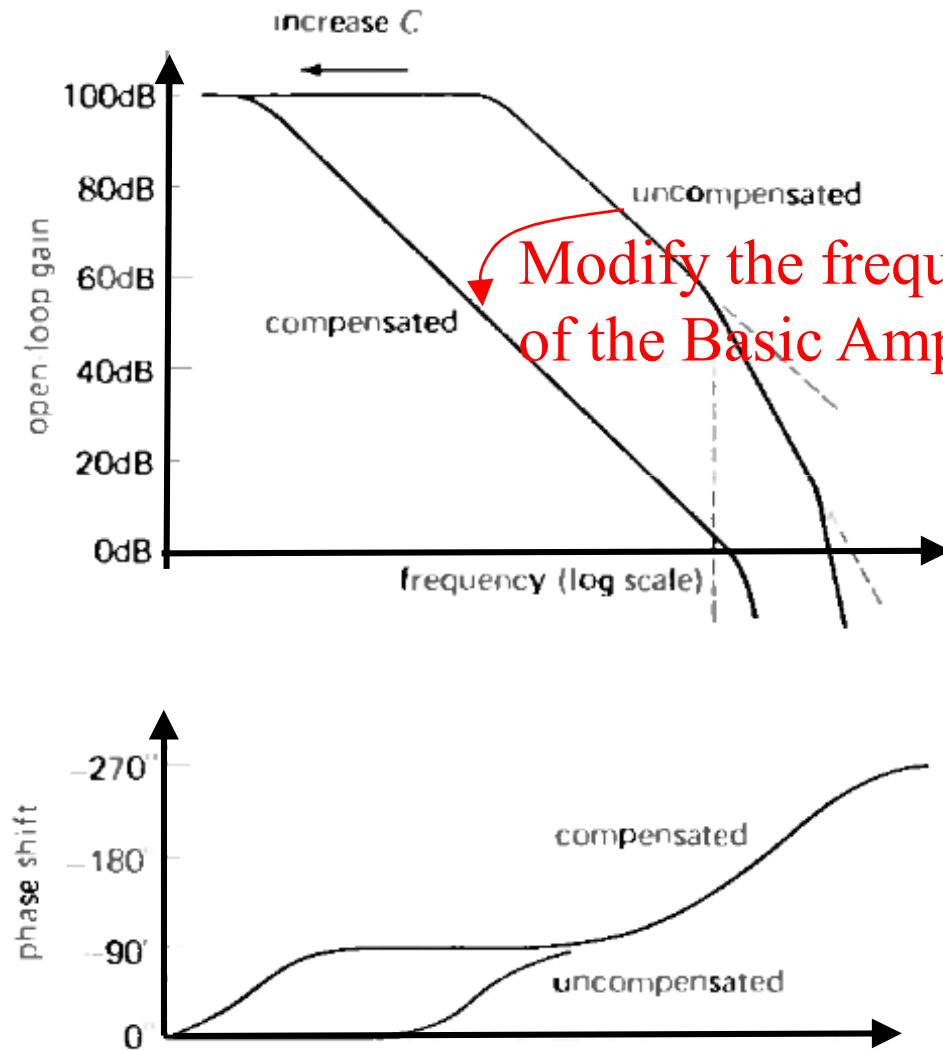


Modify the frequency response of the Basic Amplifier



Compensation

OP AMP 741 before

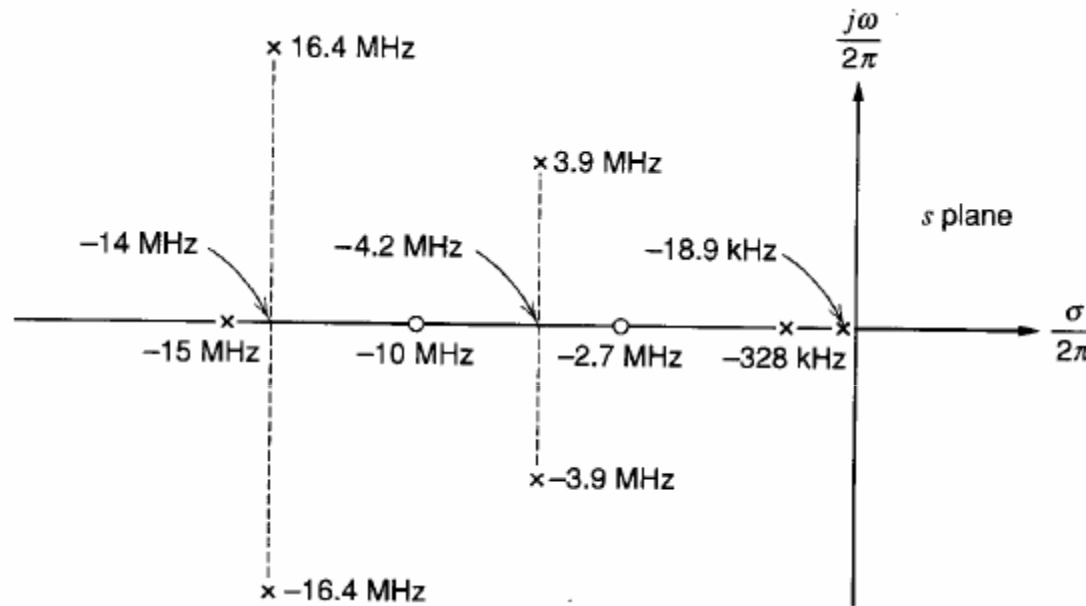


$$A_{DC} = 120 \text{ dB}$$





Compensation

... and after compensation

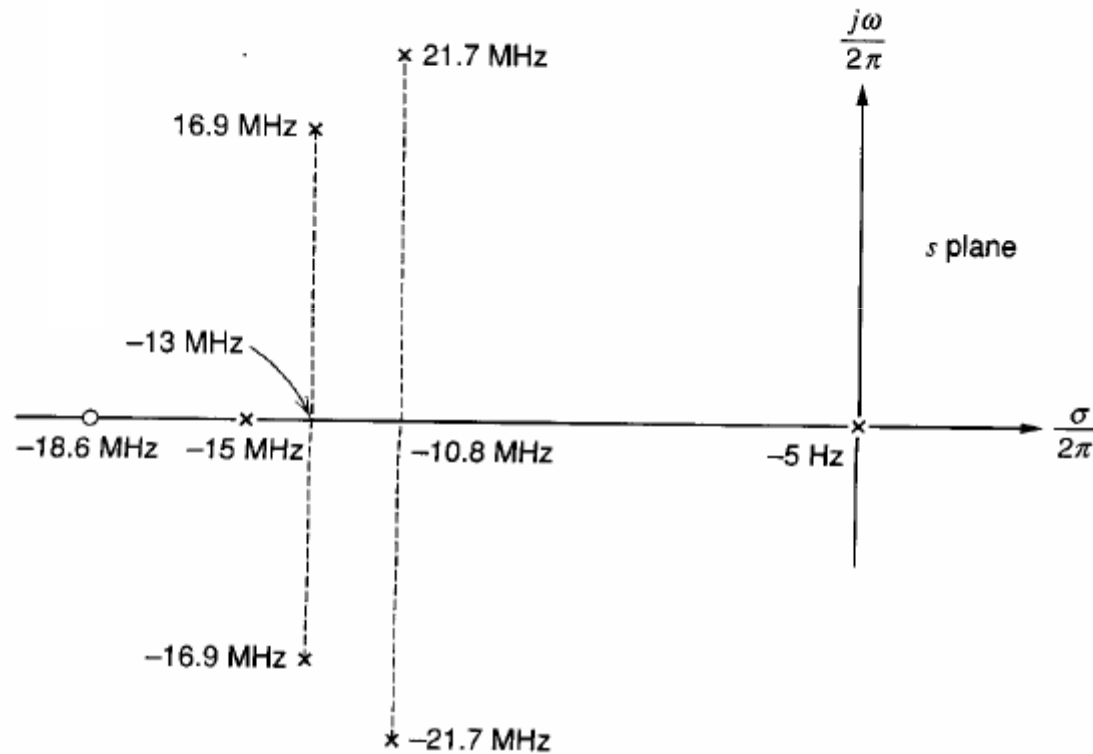

Compensation

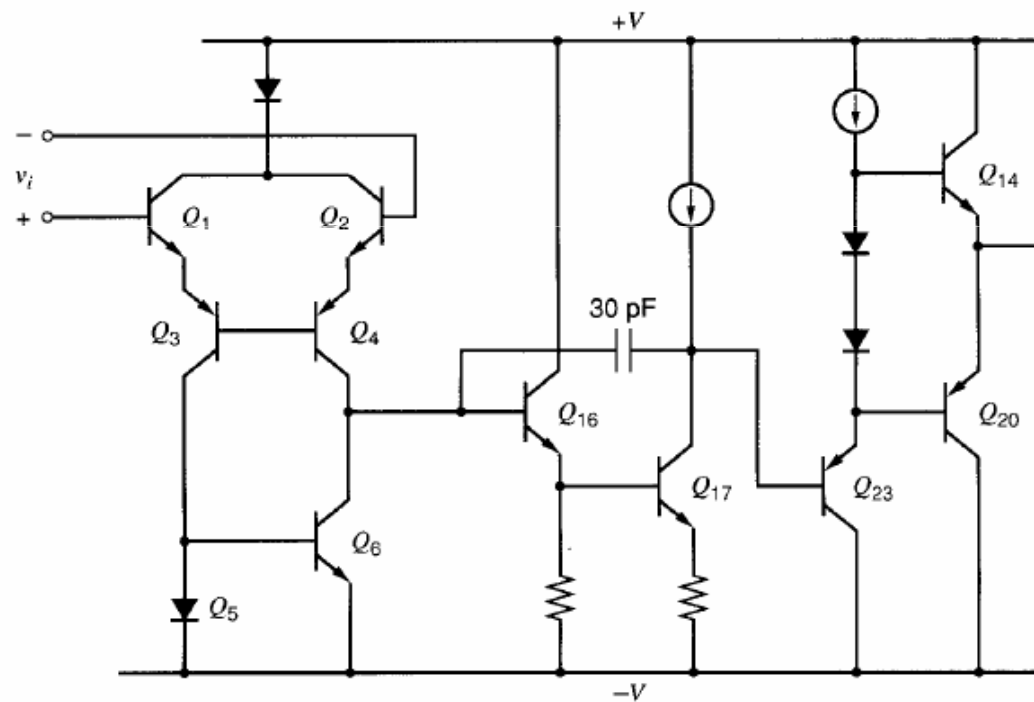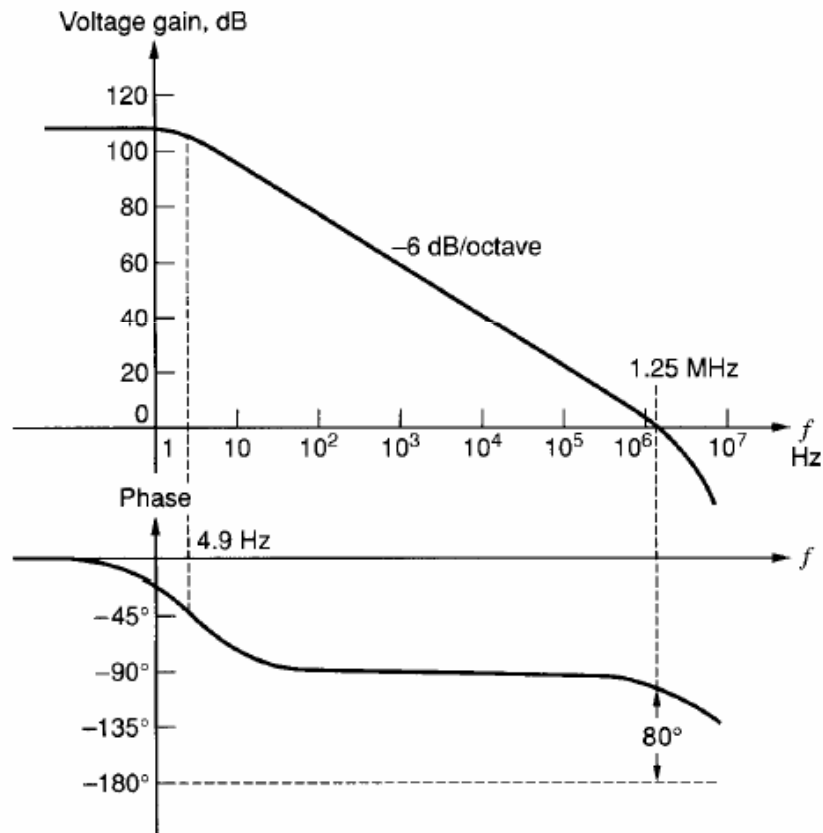

Compensation

