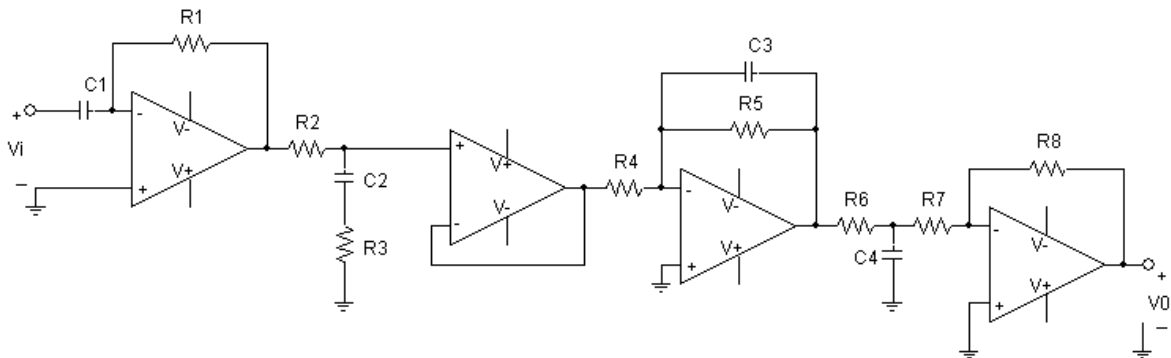


# Handout 1: Analysis of Amplifier Transfer Functions


For each of the different cases in which an amplifier can be expressed, do the following:

1. Obtain the expression of the transfer function, output voltage ( $V_0$ ) over input voltage ( $V_i$ ).
2. Provide the value of pass-band (mid-frequency) gain and the location of the poles and zeroes of the system.

## CASE 1: Expressed as a chain of Ideal OP AMPS


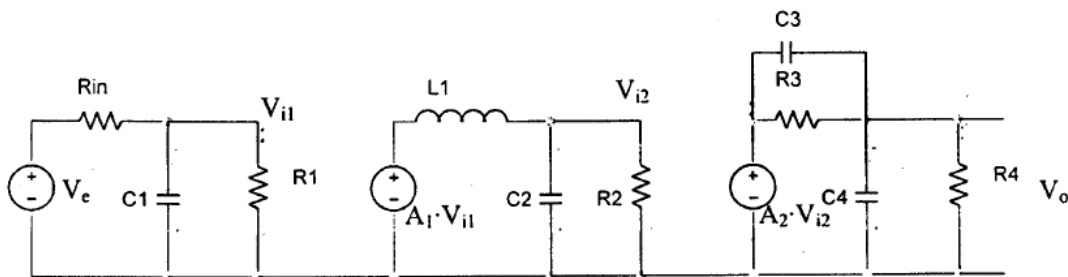
## CASE 2: Expressed as a chain of voltage dependent sources and passive discrete components



$$C_1 = 1\text{nF}, C_2 = 1.5\text{nF}, C_3 = 16\text{nF}, C_4 = 40\text{nF}, L_1 = 1.7\text{ mH}.$$

$$R_{in} = 75\Omega, R_1 = 2\text{K}\Omega, R_2 = 320\Omega, R_3 = 300\Omega, R_4 = 4.6\text{K}\Omega.$$

$$A_1 = 10^3, A_2 = 10^4.$$

## CASE 3: Poles and Zeroes analytical expression

$$A(s) = \frac{A_0 * s * (1 + \frac{50000s}{\pi})}{(1 + \frac{500s}{\pi})(1 + \frac{2,5s}{\pi})(1 + \frac{10^{-7}s}{\pi})(1 + \frac{10^{-9}s}{\pi})(1 + \frac{10^{-11}s}{\pi})} \quad A_0 = 2500/\pi, s = j\omega \text{ y } f \text{ en Hz.}$$