

Handout 2: Feedback Amplifiers


Problem 1

$$C_1 = 2\mu\text{F}, C_5 = 10\mu\text{F}$$

$$C_{\pi 2} = 5\text{pF} \text{ y } C_{\mu 2} = 1\text{pF}$$

$$C_2, C_3, C_4 = \infty$$
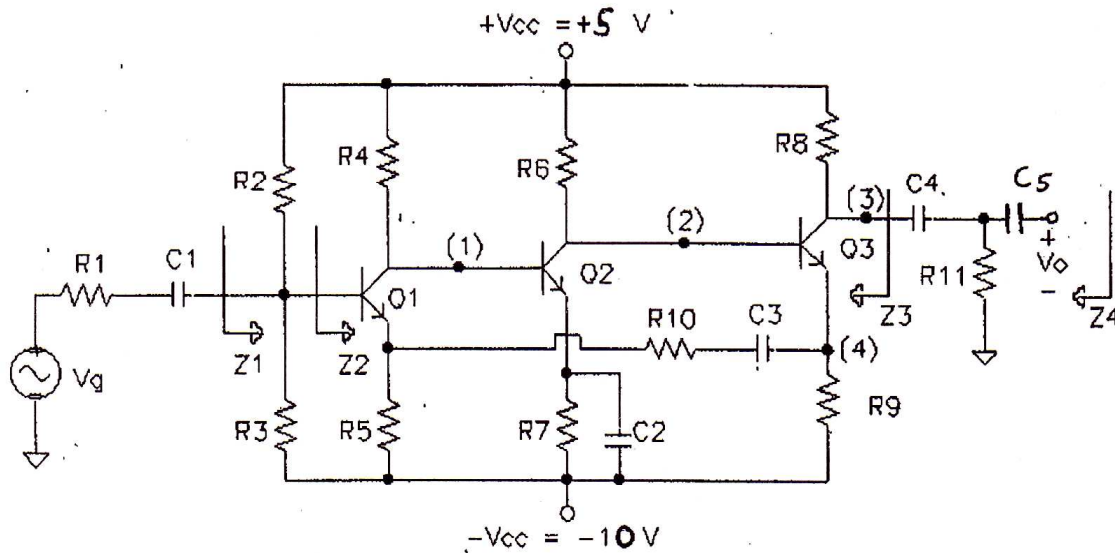
$$C_{\pi 1} = C_{\pi 3} = C_{\mu 1} = C_{\mu 3} = 0 \text{ pF.}$$



$$V_{BE} = 0,7\text{V}$$

$$\beta_F = \beta_O = 100$$

$$V_T = 25\text{mV}$$

$$r_o \rightarrow \infty$$

$$R_1 = 1 \text{ K}\Omega$$

$$R_4 = 12,8 \text{ K}\Omega$$

$$R_7 = 1,5 \text{ K}\Omega$$

$$R_{10} = 25 \text{ K}\Omega$$

$$R_2 = 34,5 \text{ K}\Omega$$

$$R_5 = 500 \Omega$$

$$R_8 = 2 \text{ K}\Omega$$

$$R_{11} = 2 \text{ K}\Omega$$

$$R_3 = 3 \text{ K}\Omega$$

$$R_6 = 12,3 \text{ K}\Omega$$

$$R_9 = 500 \Omega$$


Analyze the circuit under the condition that the feedback network is placed so that C3 rests on point (4).

- 1) Draw the small signal equivalent circuit of the above amplifier.
- 2) What is the electronic magnitude sensed at the output?
What is the electronic magnitude feedback to the input?
- 3) Draw on the circuit where is the error signal produced. What is the corresponding feedback configuration?

Based on the previous analysis, answer the following:

- 4) Draw the feedback network, and calculate the loading effects of the feedback network.
- 5) Load the basic amplifier and calculate the gain A'
- 6) What is the meaning of Z2? and of Z1? Calculate.
- 7) What is changed when the feedback network is placed so that C3 rests on point (3).

Problem II.

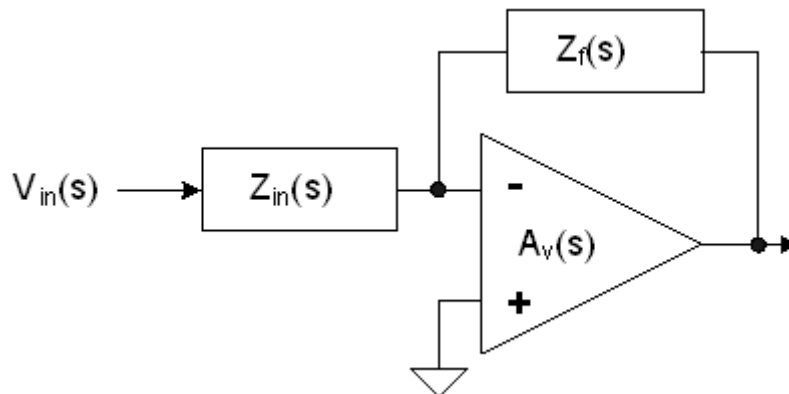

For the electronic feedback OP AMP scheme shown above, answer the following questions:

- 1) What type of feedback configuration does it present?
- 2) Assuming that the impedances shown are established through resistances, draw the feedback network. Calculate the feedback factor and the loading effects of the feedback network.
- 3) Using the following equivalent for the OP AMP, draw the Basic Amplifier including the loading effects of the feedback network, and calculate the gain A' .

