

## Handout on Feedback Stability

Given a basic amplifier that is composed of two stages, which have the characteristics given in the following table:

	Stage 1 (Input)	Stage 2 (Output)
Impedancia de Entrada	$\rightarrow \infty$	$3 \text{ M}\Omega$
Gain [f in MHz]	$\frac{jf10^6}{(1+jf10^9)(1+jf)}$	$\frac{10^6}{(1+jf0.1)^2}$
Output Impedance	$3 \text{ M}\Omega$	$\rightarrow 0$

Obtain the expression for the transfer function of the amplifier

Plot the Bode diagram in Amplitude and Phase.

Which is the maximum  $\beta$  that we can use to maintain the amplifier stable?

In the case that we want to be able to use this amplifier in a voltage follower configuration, please state if we need to introduce any compensation. In case that it is needed, indicate the location for the dominant pole to achieve a gain margin of 10dB.

