



Universidad  
Carlos III de Madrid  
[www.uc3m.es](http://www.uc3m.es)

# Session 11

## Introduction to bipolar junction transistor (BJT)

Electronic Components and Circuits

José A. Garcia Souto

[www.uc3m.es/portal/page/portal/dpto\\_tecnologia\\_electronica/Personal/JoseAntonioGarcia](http://www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia)


# Bipolar Junction Transistor

## BJT


### OBJECTIVES

- Knowing the structure of the device and the transistor effect
- Knowing and distinguishing basic parameters related to BJT transistors:  $\alpha$ ,  $\beta$ ,  $h_{FB}$ ,  $h_{FE}$ ,  $I_{CBO}$ ,  $V_{BE(on)}$ ,  $V_{CE(sat)}$
- Reading the current-voltage characteristic of the device
- Identifying the operating regions  
Active, Cut-off, Saturation, Inverse Active
- Analyze basic cases in DC of BJT circuits

# Bipolar Transistor Structure

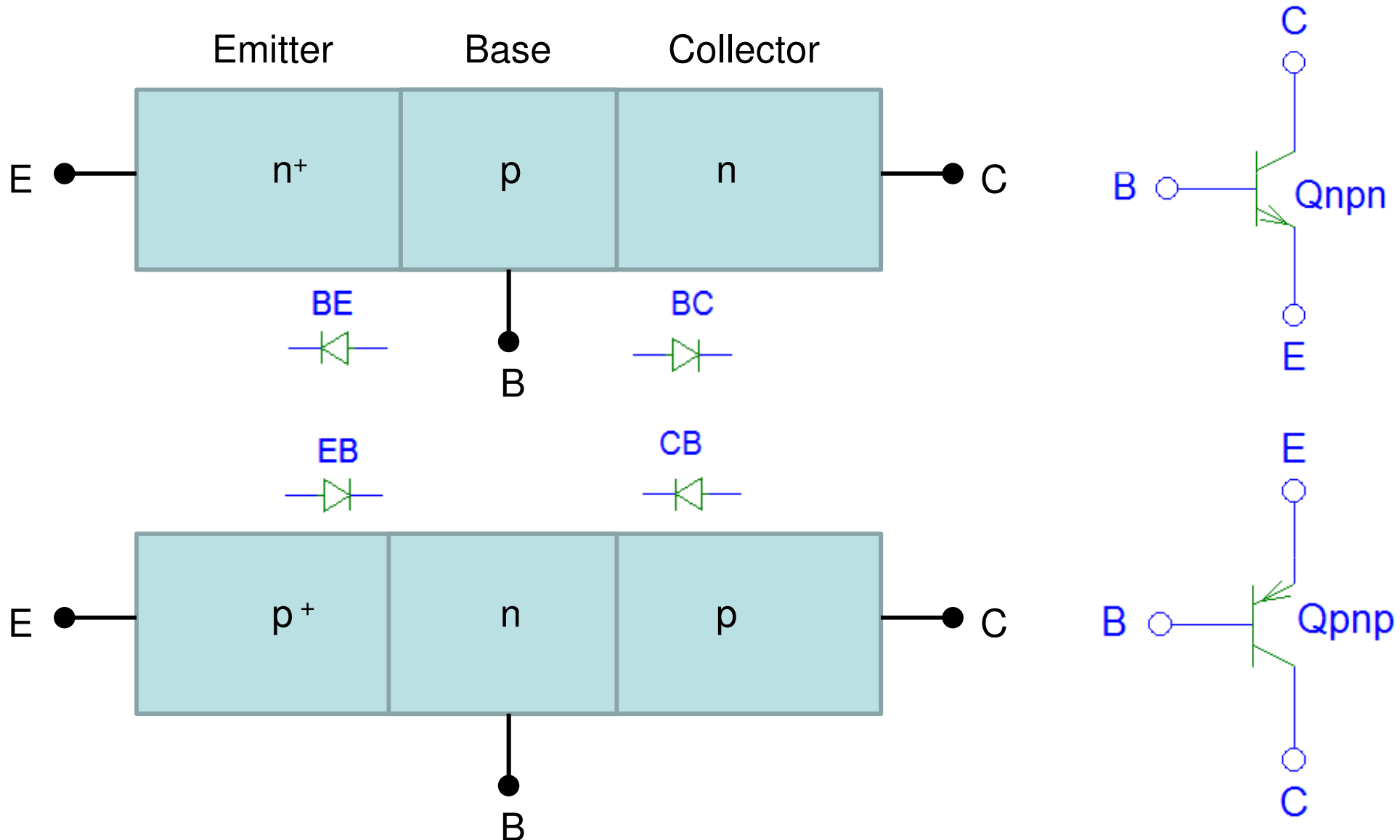

# Operation: Transistor Effect

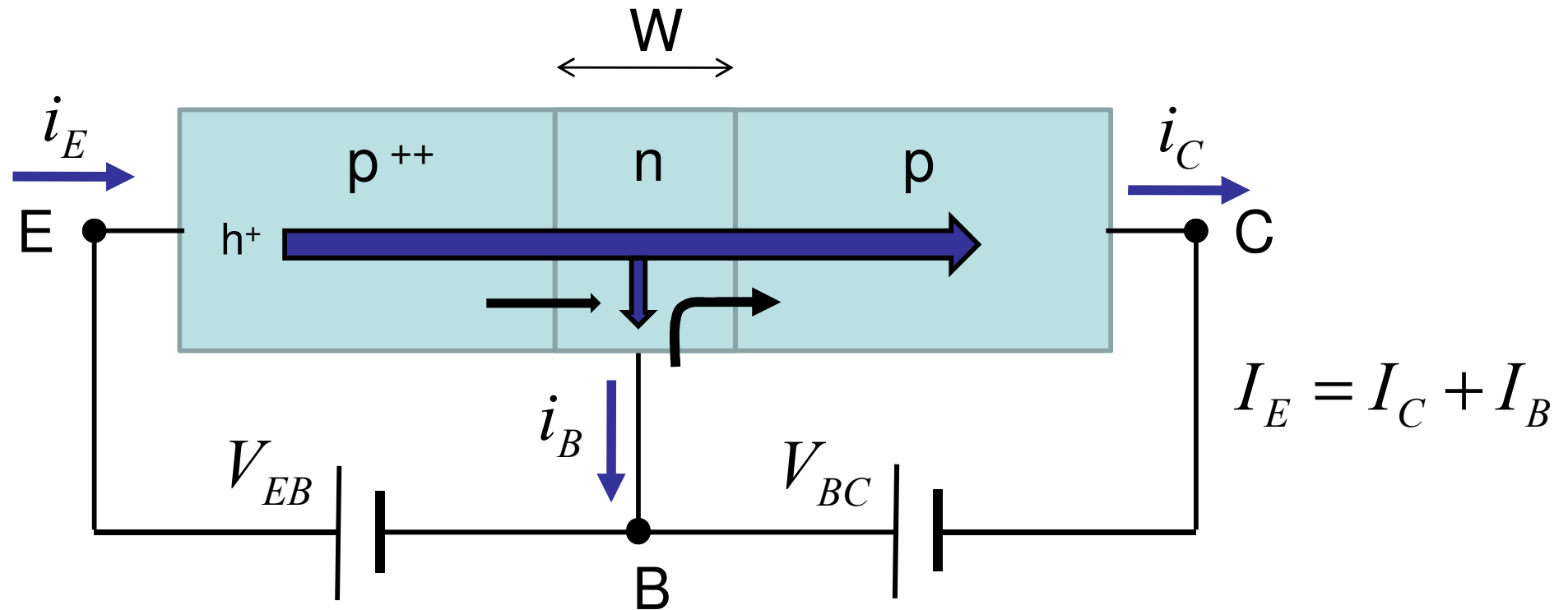

$$I_C = \alpha \cdot I_E + I_{CBO} \quad \alpha \approx 1$$

$$I_B = (1 - \alpha) \cdot I_E - I_{CBO} \quad I_C \approx I_E$$


# Characteristic parameters

- Physical Parameters


- $\alpha$        $I_C \approx \alpha \cdot I_E$        $\alpha \approx 1$        $\beta = \frac{\alpha}{1 - \alpha}$
- $\beta$        $I_C \approx \beta \cdot I_B$        $\beta \gg 1$
- $I_{CBO}$        $I_C = \alpha \cdot I_E + I_{CBO}$        $I_C = \beta \cdot I_B + I_{CBO}$

- Daasheet: Search BC547 in <http://www.fairchildsemi.com/>


- $h_{FB}$
- $h_{FE}$
- $I_{CBO}$

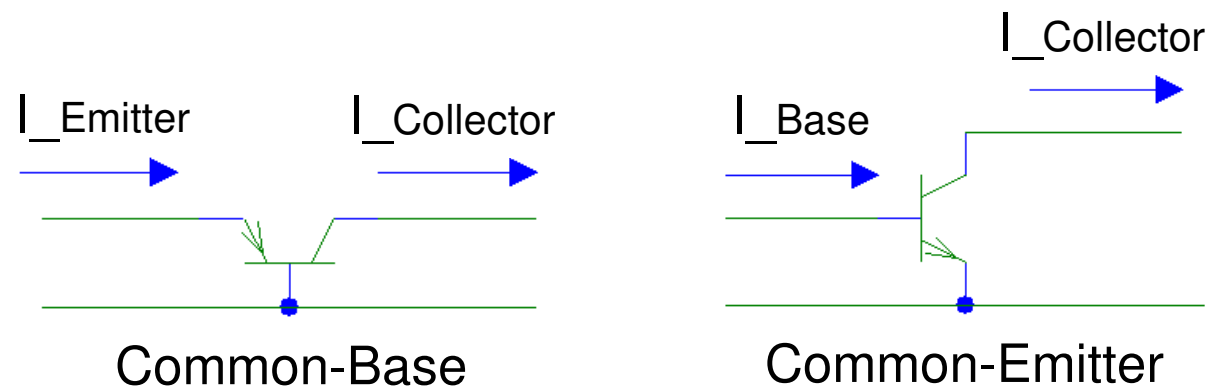

# Dual case: Transistor NPN

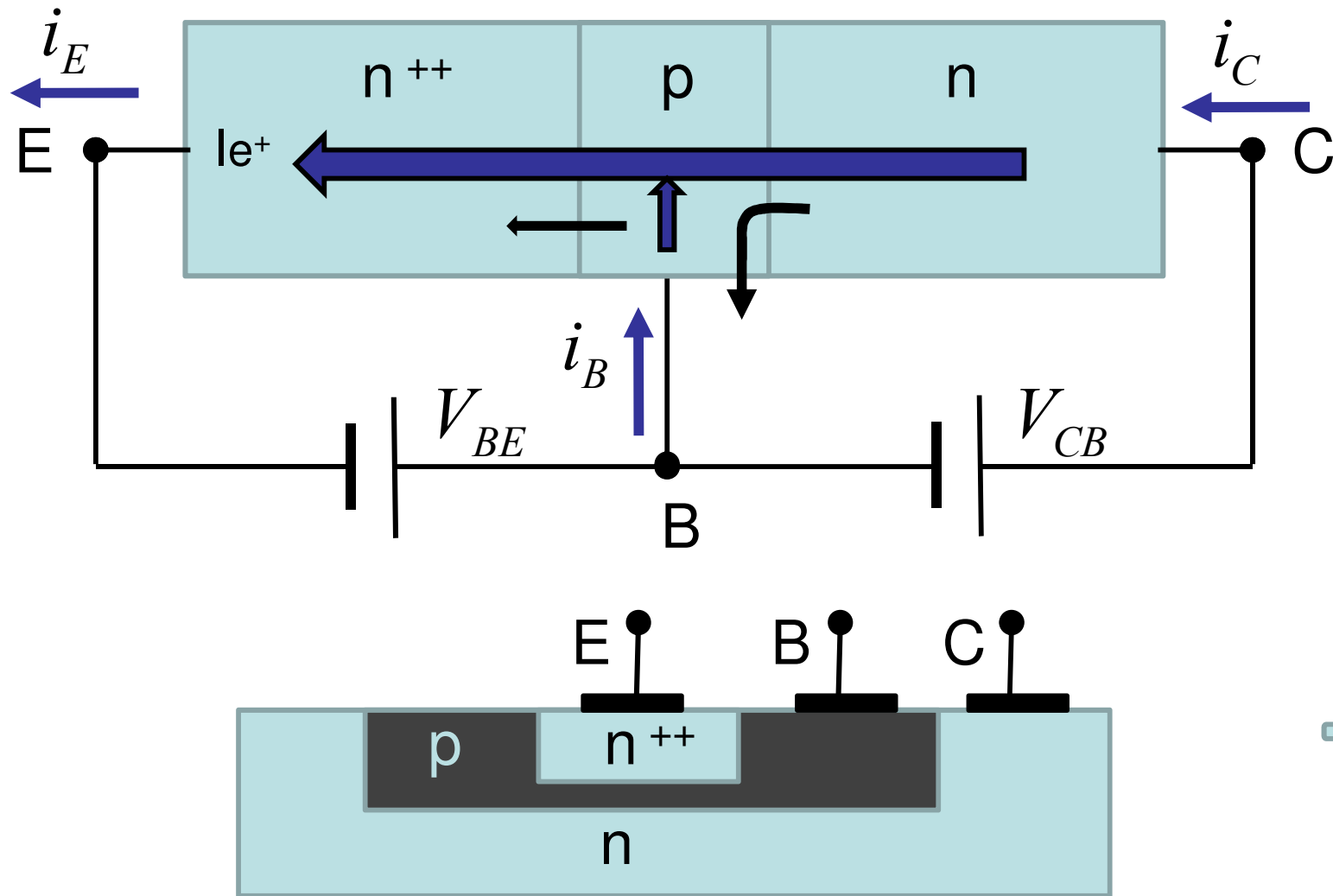
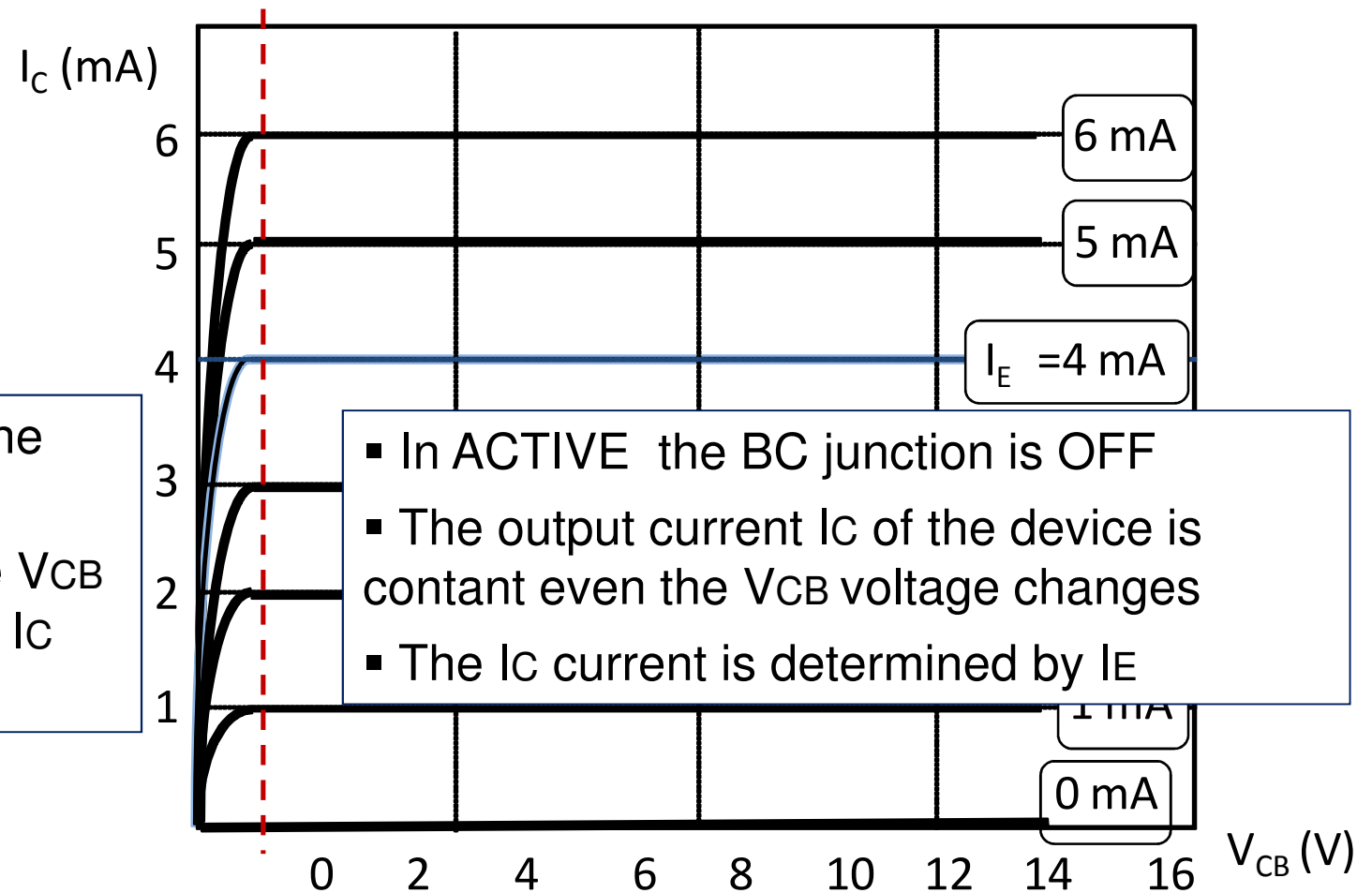
# Interpretation: current-voltage characteristic



- In SATURATION the BC junction is ON
- The output voltage  $V_{CB}$  is constant even the  $I_c$  current changes

- In ACTIVE the BC junction is OFF
- The output current  $I_c$  of the device is constant even the  $V_{CB}$  voltage changes
- The  $I_c$  current is determined by  $I_E$

There is a curve for each input value  $I_E$

# Operating Regions

| Region                | Base-Emitter Junction | Base-Collector Junction            |
|-----------------------|-----------------------|------------------------------------|
| <b>Cut-off</b>        | <b>Reverse(OFF)</b>   | Reverse                            |
| <b>Active</b>         | <b>Forward (ON)</b>   | <b>Reverse (Transistor Effect)</b> |
| <b>Saturation</b>     | <b>Forward (ON)</b>   | <b>Forward (Saturated)</b>         |
| <i>Active Reverse</i> | Reverse               | Forward                            |


| Region     | Conditions NPN  | Operation NPN                                       |
|------------|---|---|
| Cut-off    | $V_{BE} < V_{BE-ON}$ o $I_B = 0$                                | $I_B=0, I_C=I_E=0$                                  |
| Active     | $V_{BE-ON} \leq V_{BE} < V_{BE-SAT}$ y $V_{CE} > V_{CE-SAT}$    | $I_C \approx h_{FE} \cdot I_B$ $[V_{BE}=V_{BE-ON}]$ |
| Saturation | $V_{BE-ON} \leq V_{BE} < V_{BE-SAT}$ y $V_{CE} \leq V_{CE-SAT}$ | $V_{CE} = V_{CE-SAT}$ $[V_{BE}=V_{BE-SAT}]$         |

- Datasheet  $V_{BE(on)}$   $V_{CE(sat)}$   $h_{FE}$        $V_{BE(sat)}$

Search BC547 in <http://www.fairchildsemi.com/>



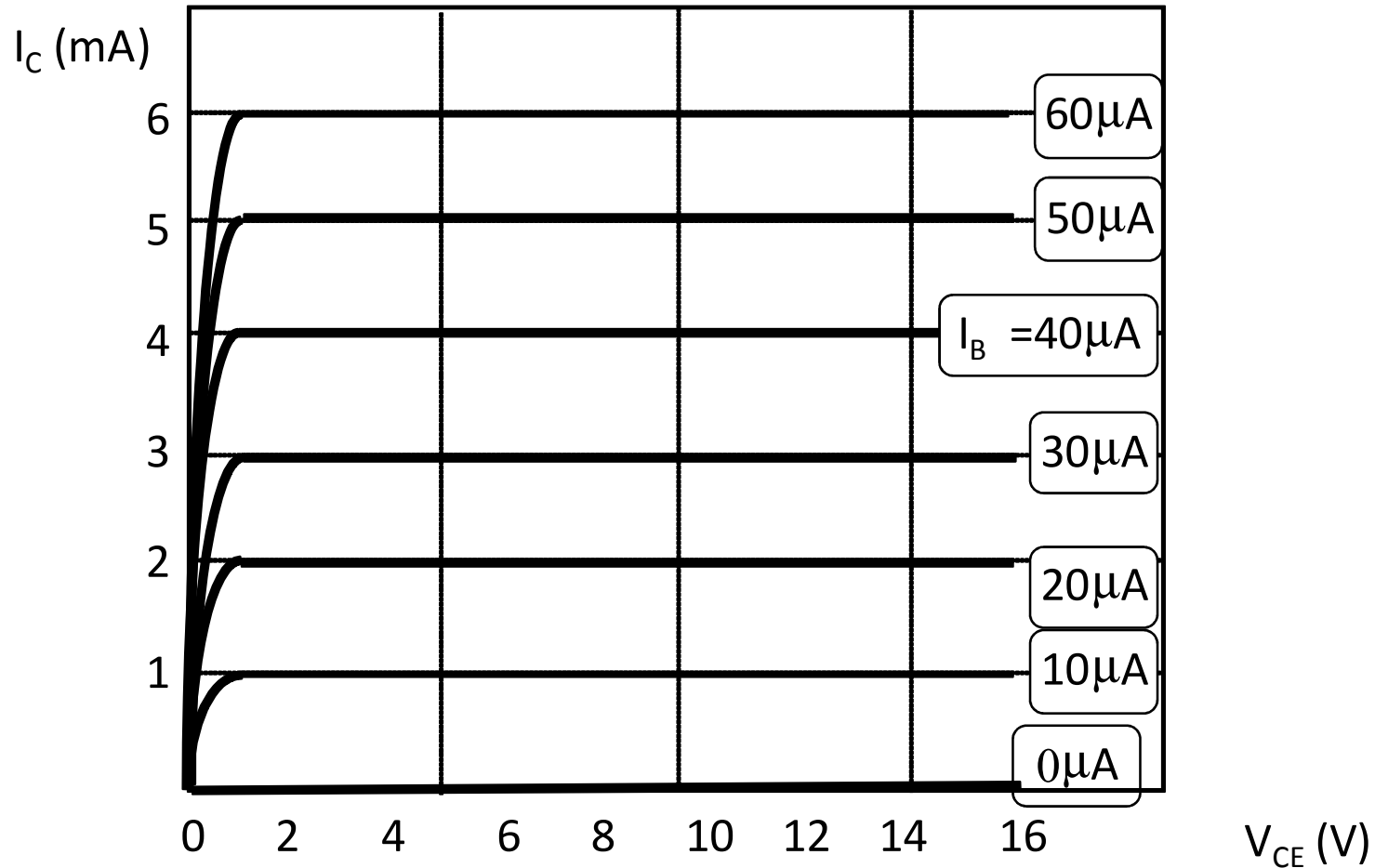
# Output Characteristics (Common - Emitter)



What input characteristic represent?

# Transfer Characteristic

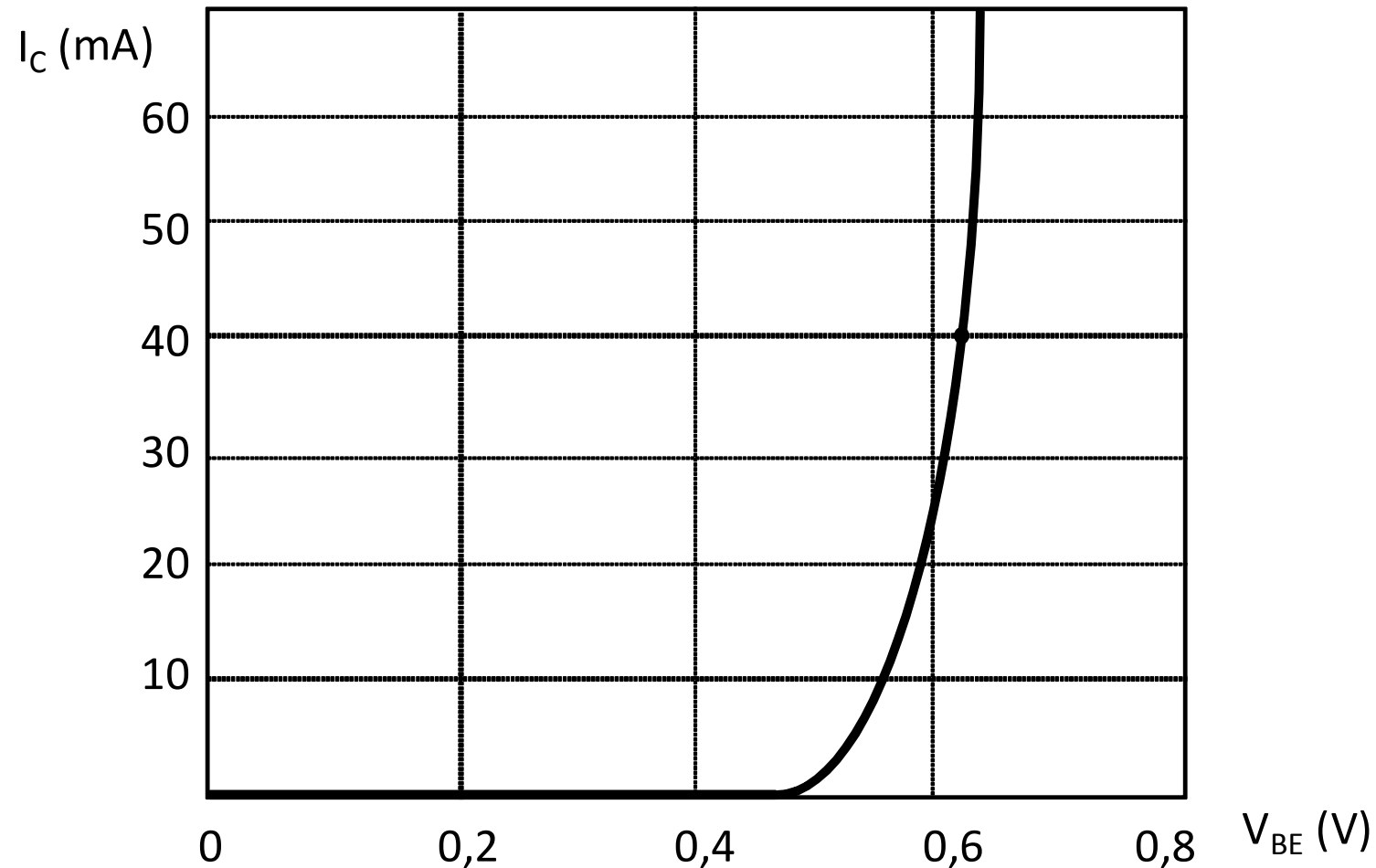


What operating regions can be identified?

# Example: Operating Regions

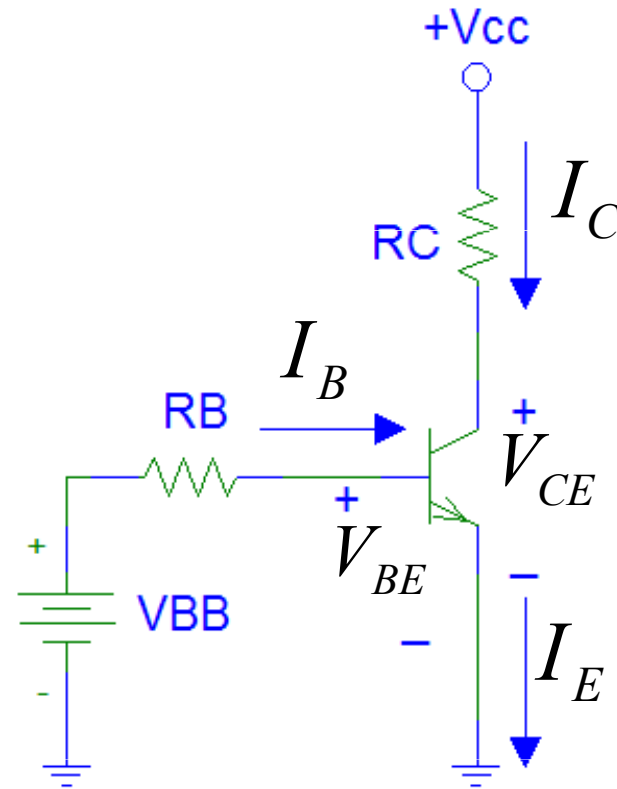
## EXAMPLE

- $R_C = 100 \Omega$
- $R_B = \dots$
- $V_{CC} = 10 \text{ V}$
- $V_{BB} = \dots$
- $V_{BE(\text{on})} = 0,7 \text{ V}$
- $V_{CE(\text{sat})} = 0,2 \text{ V}$
- $h_{FE} = 100$



| Case 1                     | Case 2                     | Case 3                     | Case 4                    |
|----------------------------|----------------------------|----------------------------|---------------------------|
| $V_{BB} = 0 \text{ V}$     | $I_B = 0$                  | $V_{BB} = 10 \text{ V}$    | $V_{BB} = 10 \text{ V}$   |
| $R_B = 10 \text{ k}\Omega$ | $R_B = 10 \text{ k}\Omega$ | $R_B = 10 \text{ k}\Omega$ | $R_B = 1 \text{ k}\Omega$ |

# Currents and Voltages of NPN and PNP

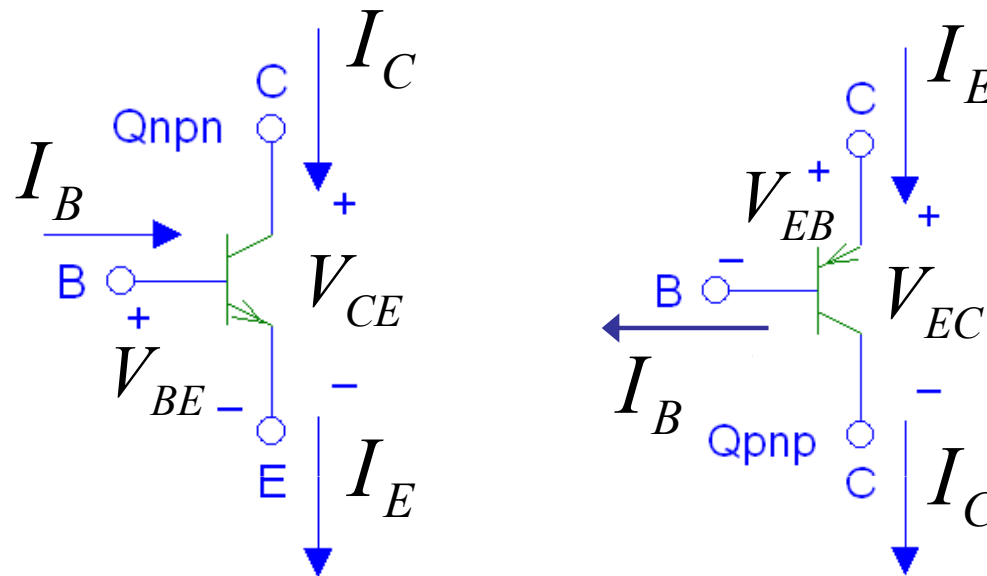

# Operating Regions

## Case of PNP transistor

- Datasheet  $V_{EB(on)}$   $V_{EC(sat)}$   $h_{FE}$   $V_{EB(sat)}$

Search BC557 in <http://www.fairchildsemi.com/>


| Region     | Emitter-Base Junction | Collector-Base Junction     |
|------------|-----------------------|-----------------------------|
| Cut-off    | Reverse(OFF)          | Reverse                     |
| Active     | Forward (ON)          | Reverse (Transistor Effect) |
| Saturation | Forward (ON)          | Forward (Saturated)         |

| Region     | Conditions PNP                      | Operation PNP   |
|------------|-------------------------------------|---|
| Cut-off    | $V_{EB} < V_{EB-ON}$ o $I_B = 0$    | $I_B=0, I_C=I_E=0$                                    |
| Active     | $V_{EB-ON}$ y $V_{EC} > V_{EC-SAT}$ | $I_C \approx h_{FE} \cdot I_B$ [ $V_{EB}=V_{EB-ON}$ ] |
| Saturation | $V_{EB-ON}$ y $V_{EC-SAT}$          | $V_{EC} = V_{EC-SAT}$ [ $V_{EB}=V_{EB-SAT}$ ]         |

# Exercise: Operating Regions
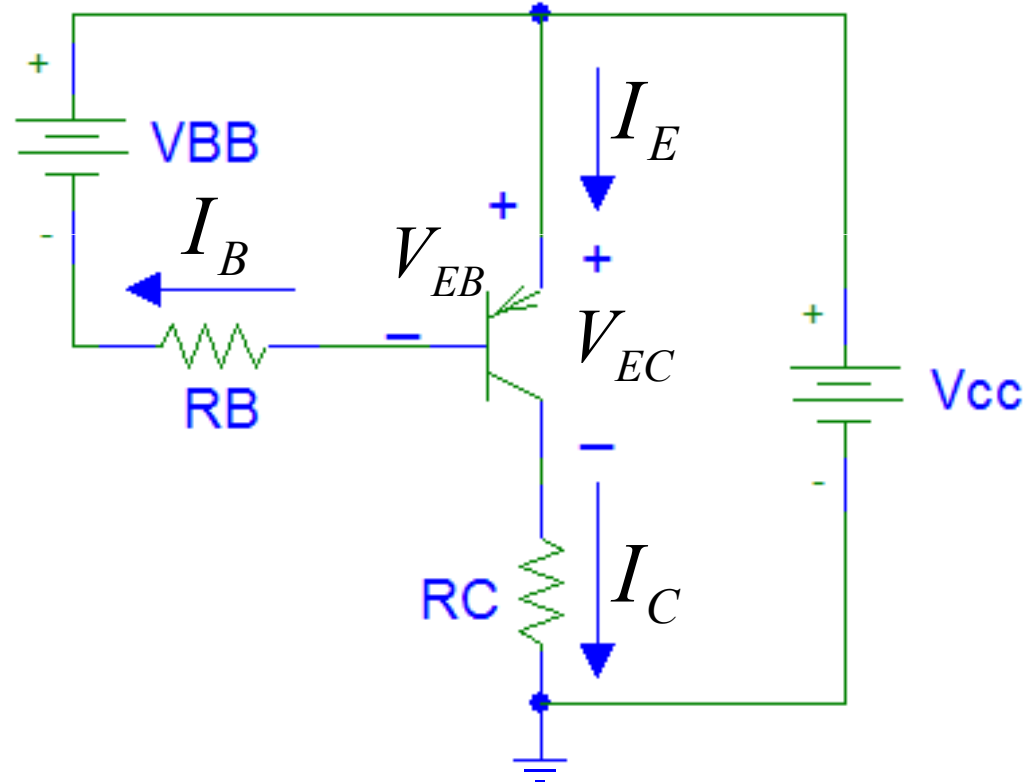
## DATA



- $R_C = 100 \Omega$
- $R_B = \dots$
- $V_{CC} = 10 \text{ V}$
- $V_{BB} = \dots$
- $V_{EB(\text{on})} = 0,7 \text{ V}$
- $V_{EC(\text{sat})} = 0,2 \text{ V}$
- $h_{FE} = 100$



| Case 1                     | Case 2                     | Case 3                     | Case 4                    |
|----------------------------|----------------------------|----------------------------|---------------------------|
| $V_{BB} = 0 \text{ V}$     | $I_B = 0$                  | $V_{BB} = 10 \text{ V}$    | $V_{BB} = 10 \text{ V}$   |
| $R_B = 10 \text{ k}\Omega$ | $R_B = 10 \text{ k}\Omega$ | $R_B = 10 \text{ k}\Omega$ | $R_B = 1 \text{ k}\Omega$ |

# Proposed exercise

Voltages and currents

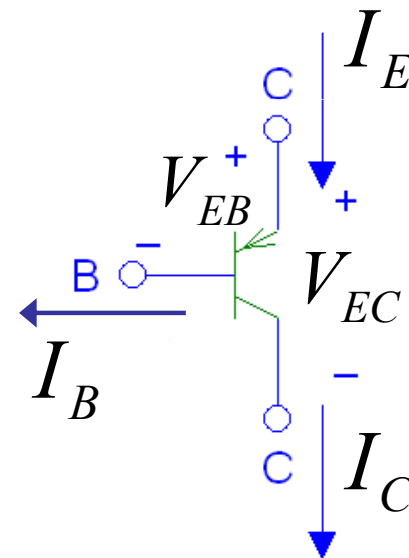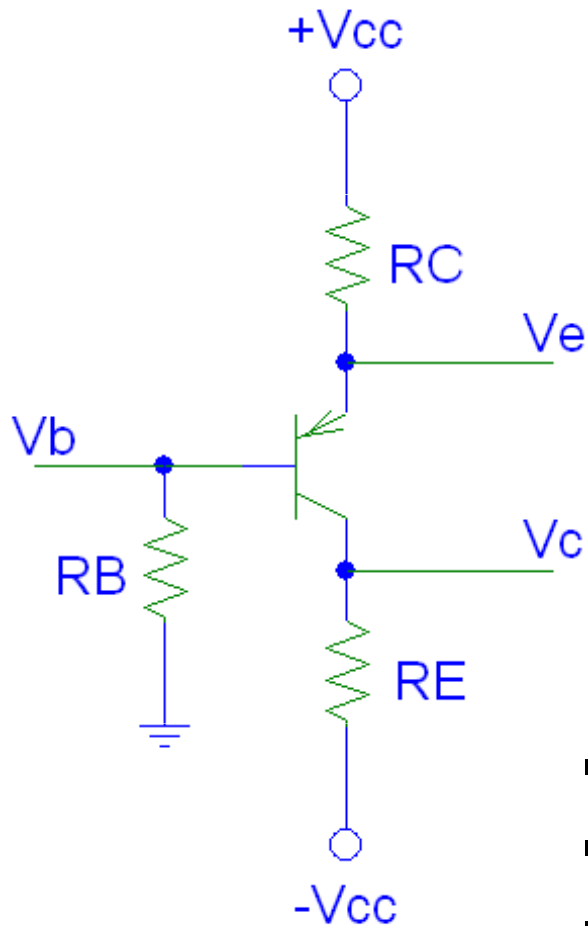

- Indicate what type of transistor is
- Reasoning the operating region
- Relate  $V_B$  and  $V_E$ ,  $V_B$  and  $I_B$ ,  $V_E$  and  $I_E$ ,  $I_E$  and  $I_B$ .
- Relate  $V_c$  and  $I_c$