



Universidad
Carlos III de Madrid
www.uc3m.es

Session 18

Amplifiers with FET transistors - Exercises


Electronic Components and Circuits
Enrique San Millán / Celia López

FET transistor amplifier configurations

Goals:

- Analysis of small-signal circuits corresponding to single-stage FET amplifiers:
 - Common-Source.
 - Common-Drain.
 - Common-Gate.

Amplifiers characteristic parameters

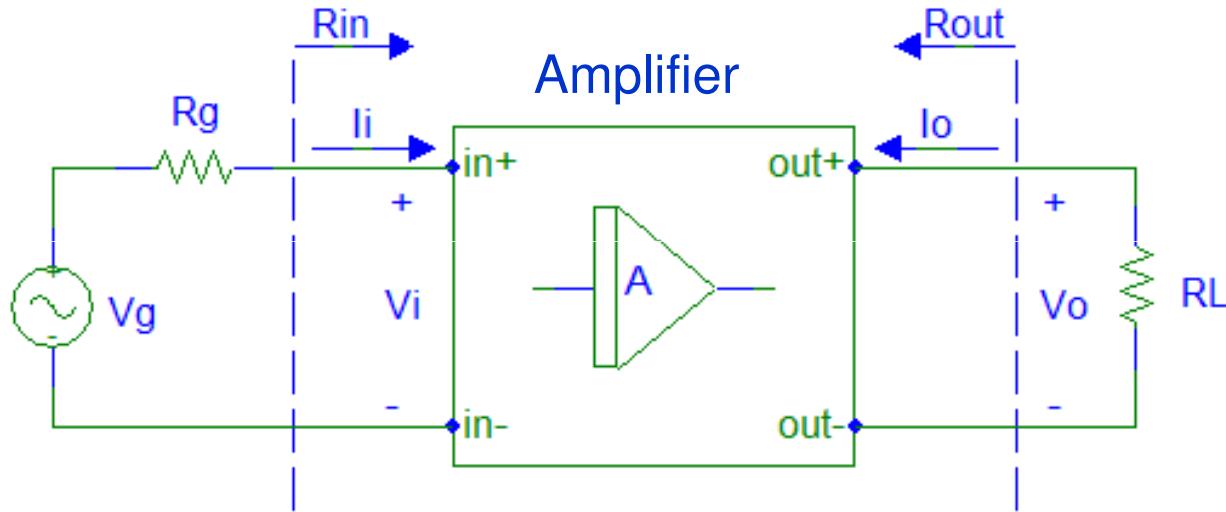


- Voltage Gain, A_v and G_v
- Current Gain, A_i
- Input resistance, R_{in}
- Output resistance, R_{out}


$$A_v = \frac{V_o}{V_i} \quad G_v = \frac{V_o}{V_g} \quad A_i = \frac{i_o}{i_i}$$

$$R_{in} = \frac{V_i}{i_i} \quad R_{out} = \frac{V_o}{i_o}$$

Measuring Input Resistance

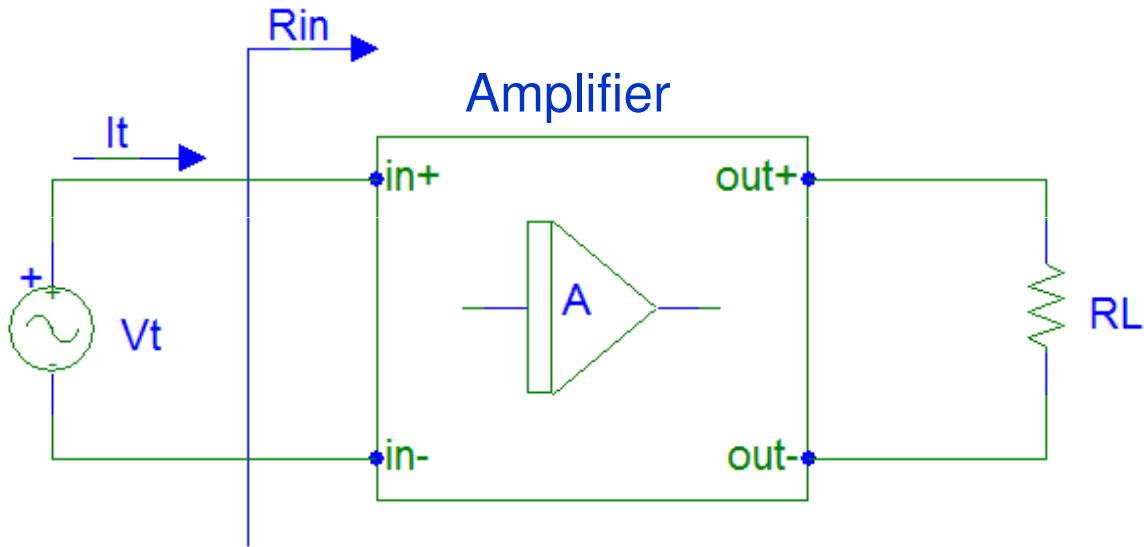


$$R_{in} = \frac{V_t}{i_t}$$

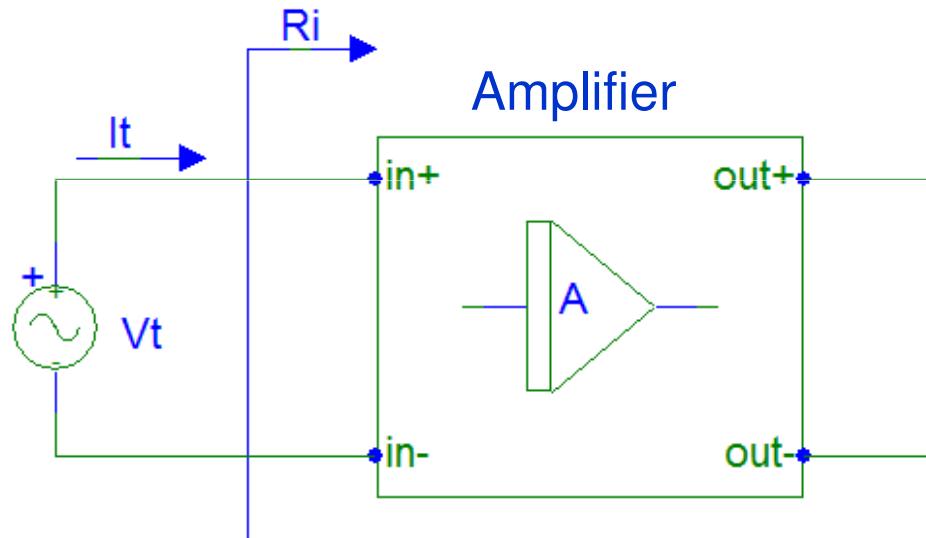


$$R_i = \left. \frac{V_t}{i_t} \right|_{R_L \rightarrow \infty}$$

Calculating Output Resistance

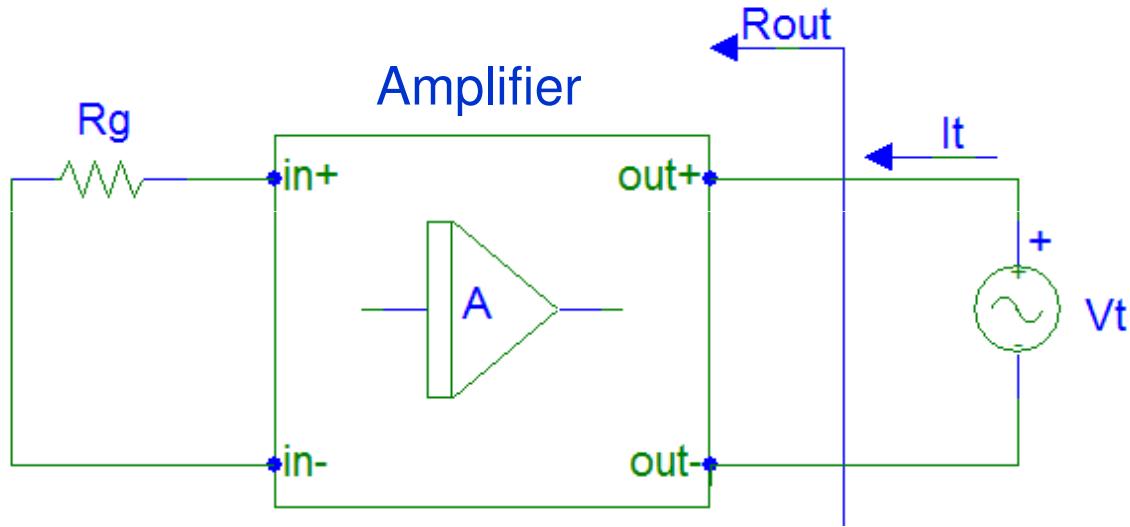


$$R_{out} = \left. \frac{V_t}{i_t} \right|_{V_g=0}$$

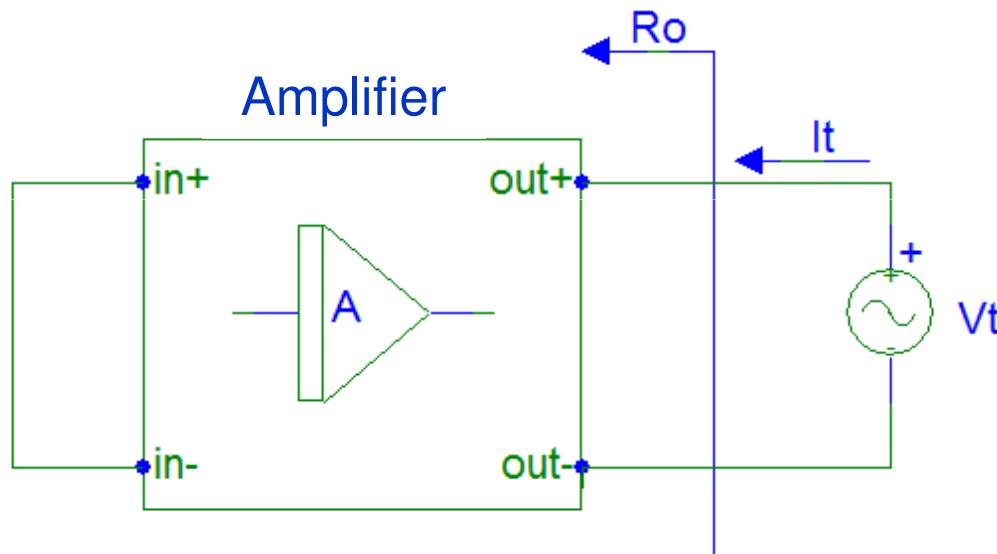

$$R_o = \left. \frac{V_t}{i_t} \right|_{V_i=0}$$

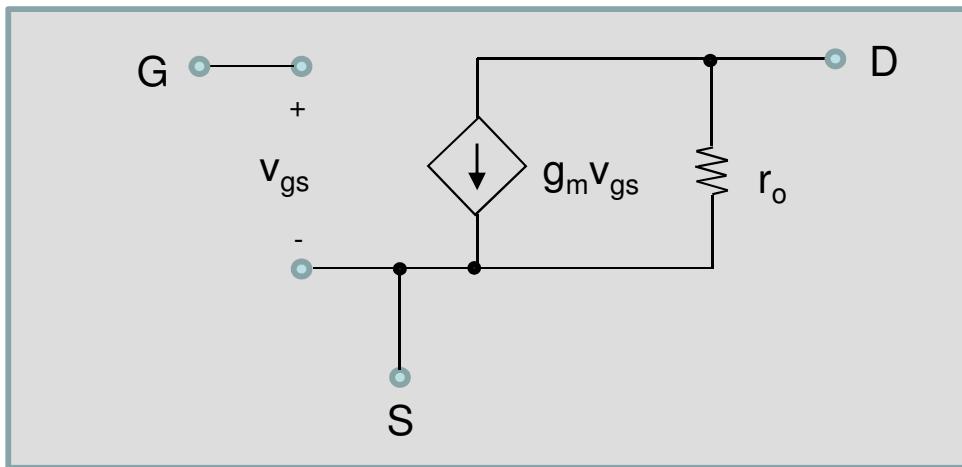Small-signal equivalent circuit (low and medium frequencies)



- With MOSFETs

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{v_{ds} = V_{DSQ}} = 2K(V_{GS} - V_t)$$

$$r_o = \frac{V_A}{I_D}$$

- With JFETs

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{v_{ds} = V_{DSQ}} = -2 \frac{I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$

Analysis of small-signal amplifier circuits


METHODOLOGY

1. Analyze the biasing circuit (DC), removing all power sources (superposition) and considering the coupling and decoupling capacitors as open-circuits. Find the bias point.
2. Find the transistor small-signal parameters (from the bias point voltages and currents).
3. Represent the small-signal equivalent circuit of the devices and the external circuit, removing the DC sources (superposition) and considering the capacitors at medium frequencies.
4. Find the amplifier characteristics.


Single-stage MOS amplifiers

- Common-Source amplifier
- Common-Drain or Source-Follower configuration
- Common-Gate amplifier


Common-Source

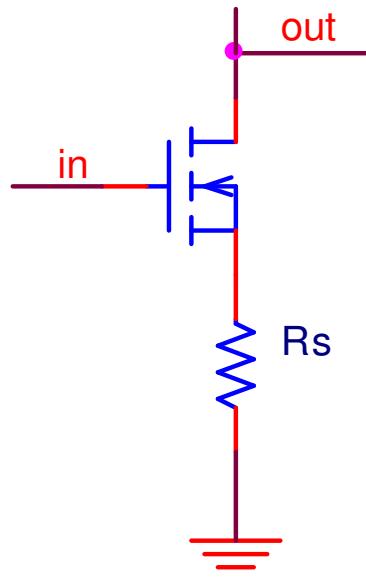


Common-Drain

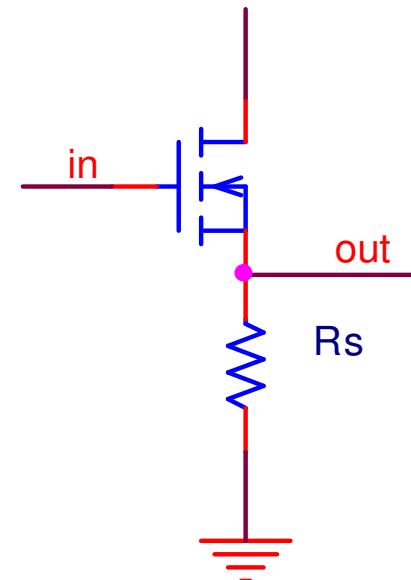

Common-Gate

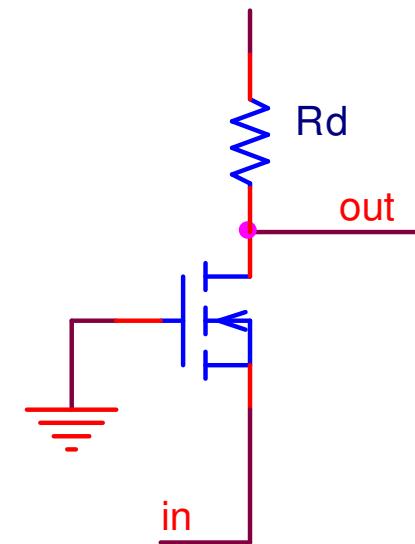

Class exercise 1

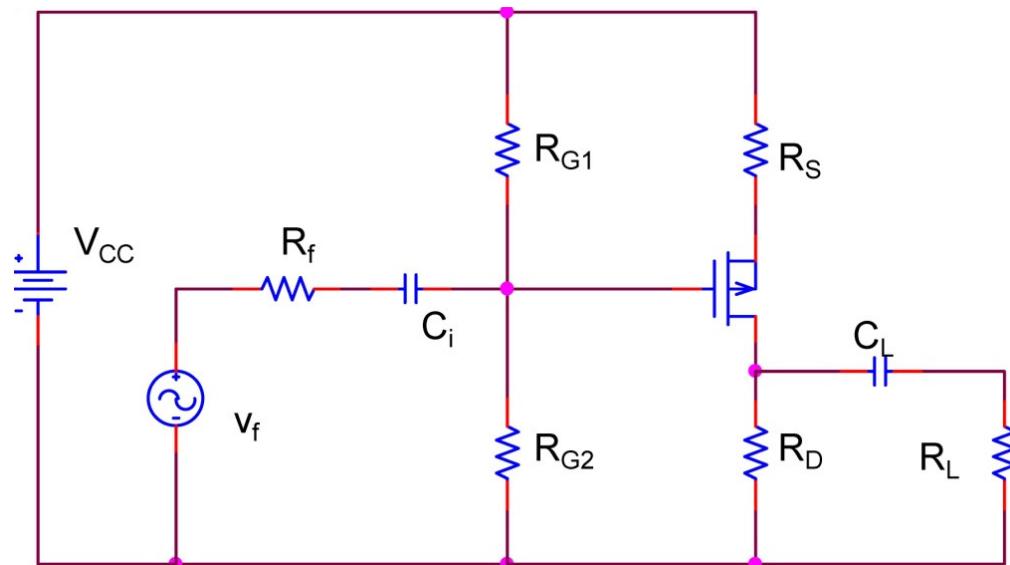


Data:

$V_{CC} = 10V$
 $R_{G1} = 100K\Omega$,
 $R_{G2} = 100K\Omega$,
 $R_s = 1k\Omega$,
 $R_D = 330\Omega$
 $R_L = 10k\Omega$
 $R_f = 50\Omega$
 $K=1 \text{ mA/V}^2$
 $|V_t|=3V$
 $|V_A|=\infty$

- Find the bias-point values: I_D , V_G , V_S and V_D
- Find the small-signal parameter g_m
- Find R_i , R_o and A_{v_o} for this amplifier
- Find the circuit gain A_v considering R_f and R_L

Class exercise 2

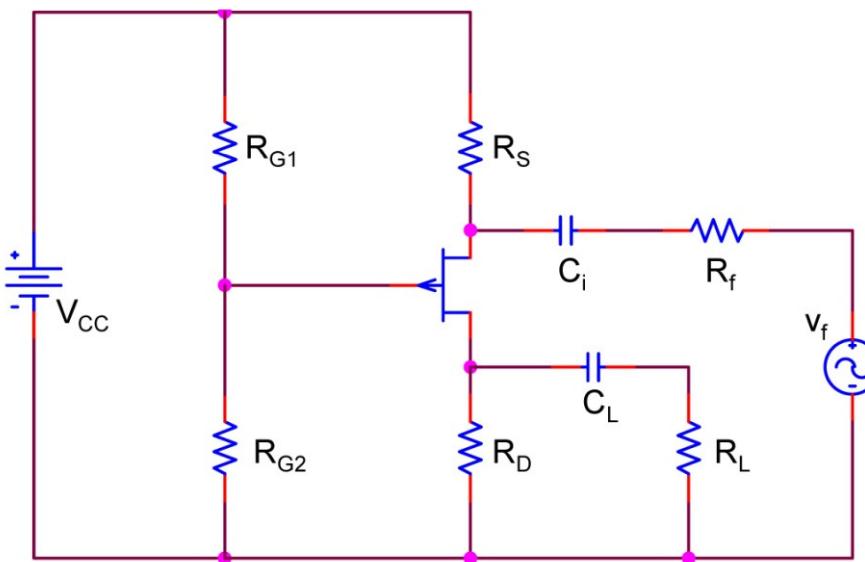

Data:

$V_{CC} = 20V$
 $R_{G1} = 39K\Omega$,
 $R_{G2} = 160K\Omega$,
 $R_S = 1K\Omega$,
 $R_D = 1.1K\Omega$
 $R_L = 1k\Omega$
 $R_f = 50\Omega$
 $|V_p| = 5V$
 $|V_A| = \infty$
 $I_{DSS} = 20mA$

- Find the bias-point values: I_D , V_G , V_S and V_D
- Find the small-signal parameter g_m
- Find R_i , R_o and A_{v_o} for this amplifier
- Find the circuit gain A_v considering R_f and R_L