



Universidad  
Carlos III de Madrid  
[www.uc3m.es](http://www.uc3m.es)

# Session 7

## Analysis of Diode Circuits

Componentes y Circuitos Electrónicos

José A García Souto


[www.uc3m.es/portal/page/portal/dpto\\_tecnologia\\_electronica/Personal/JoseAntonioGarcia](http://www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia)

# Analysis of Diode Circuits

## SKILLS

- To review the diode basic work as a circuit component and to review the diode models
- To understand the conduction threshold and its use in diode circuits
- To understand the waveforms in a rectifier circuit and to calculate their fundamental parameters
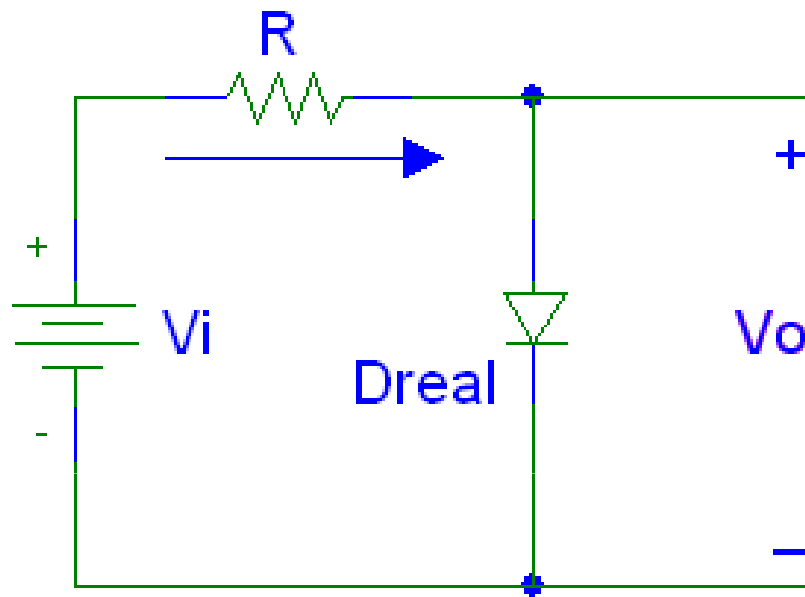
# Analysis of Diode Circuits (Analytic solution: equations)






$$I_D = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$


$$V_i = I_D \cdot R + V_D$$

# Diode Models


IDEAL

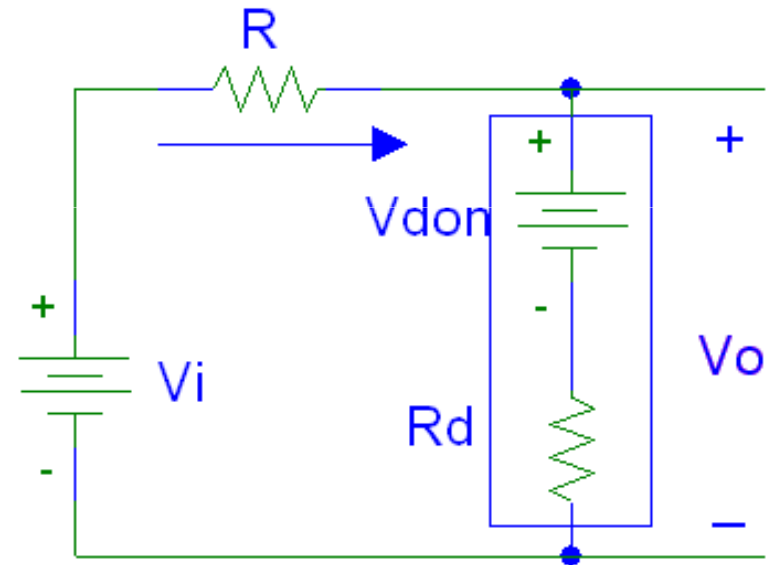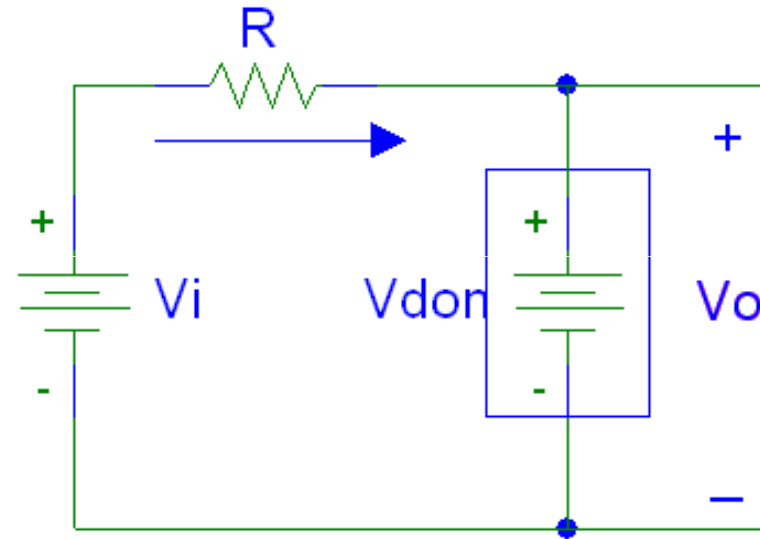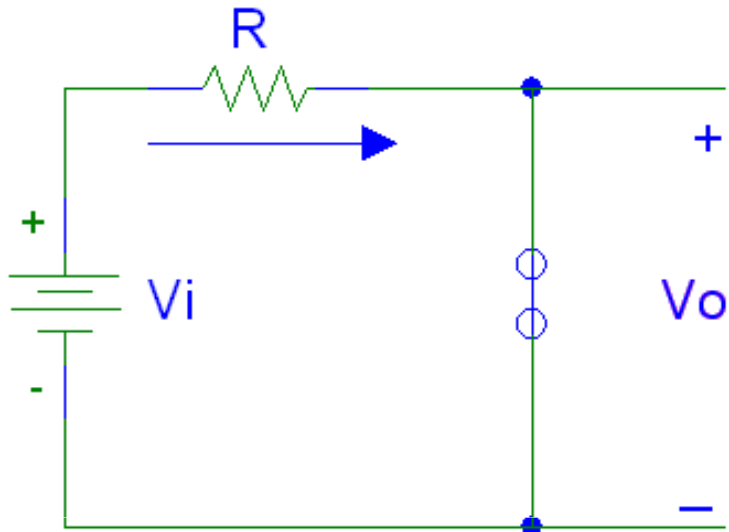
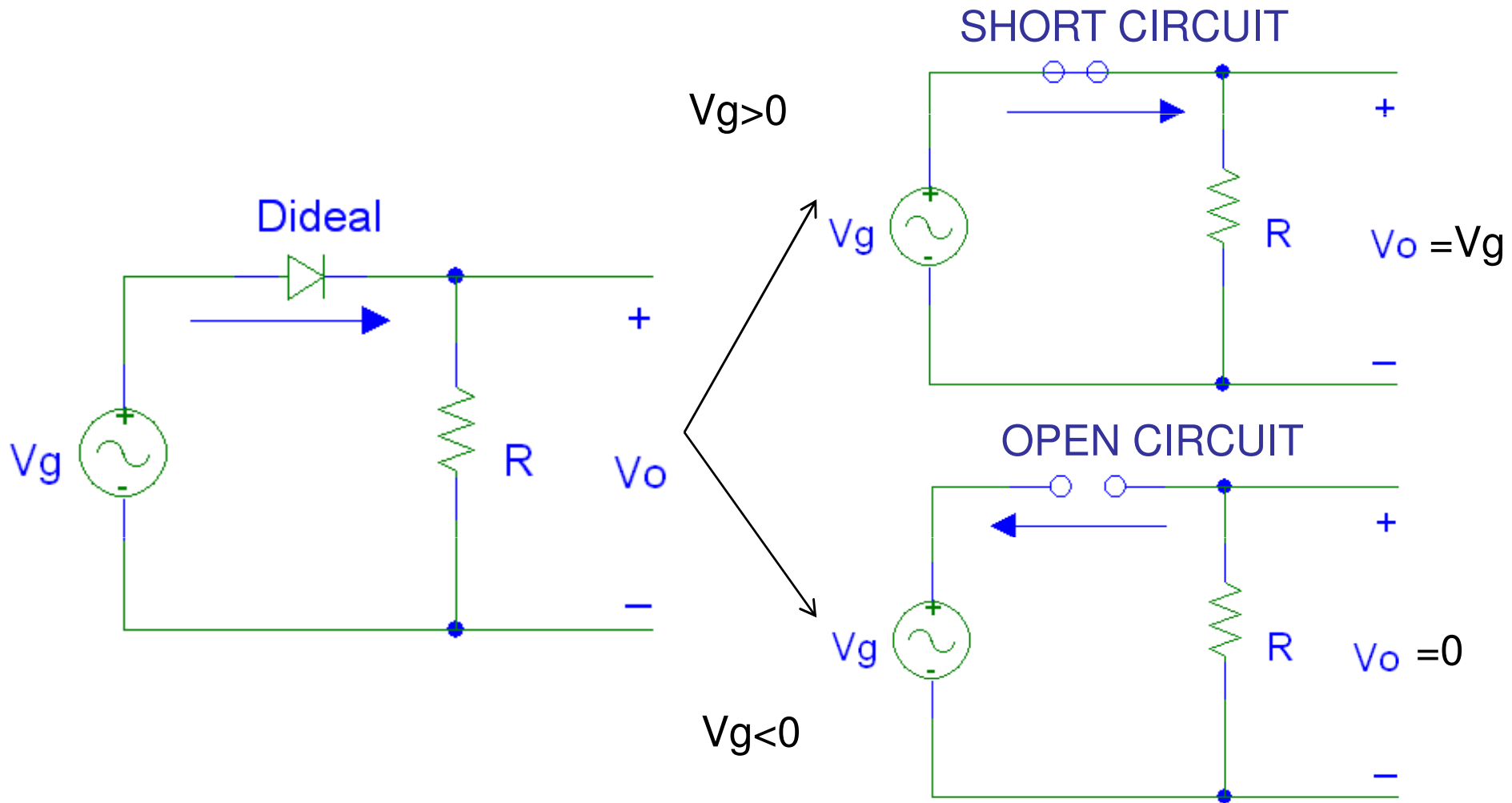
# Analysis of Diode Circuits (Two working regions)


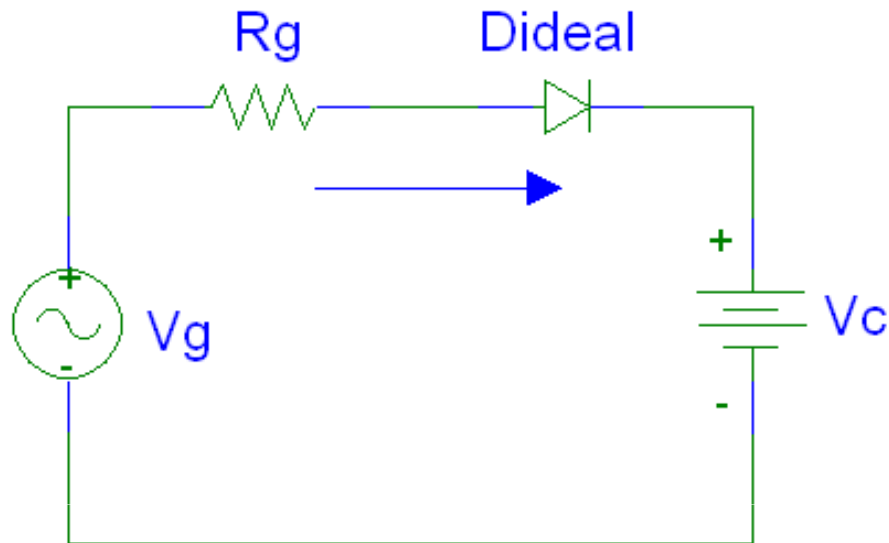
# Example: Battery Charger ("Conduction threshold")




$$V_g = 15 \text{ Vp}$$

- $R_g = 100 \ \Omega$
- $V_c = 9 \text{ V}$

- Draw the diode and resistor voltage waveforms
- Calculate the conduction angle:  $V_g = V_c$ .
- Calculate the mean current of battery charge (diode current).

# Exercice: Half-Wave Rectifier

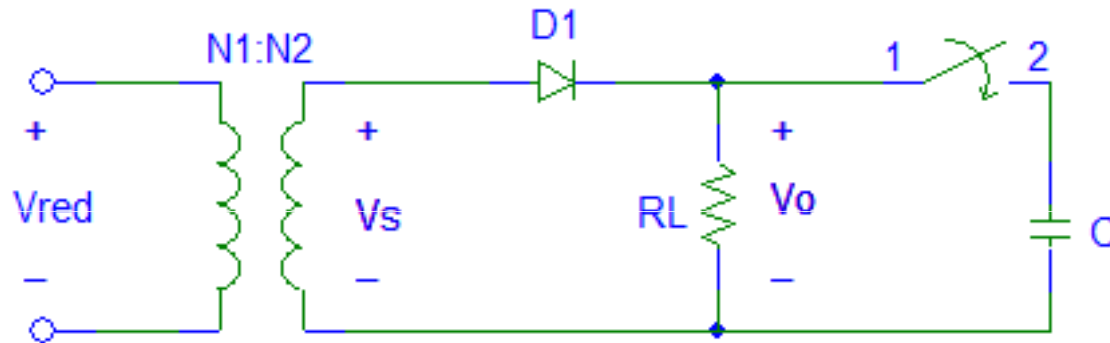

DATA:  $V_{red} = 220 \text{ V}_{rms}$ ; Frequency  $f = 50 \text{ Hz}$ ;  $N_1=190$ ;  $N_2=10$   
Ideal diodes D1 y D2  $V_{Don} = 0 \text{ V}$ ;  $R_L = 3\text{K}\Omega$ ;  $C = 100\mu\text{F}$

a) Without the capacitance C:

- Draw the voltage waveforms  $V_s$  and  $V_o$ .
- Calculate the mean value of  $V_o$ .
- Calculate the maximum current in  $R_L$ .
- Calculate the peak inverse voltage (PIV) that each diode may support

a) With the capacitance C:

- Draw the voltage waveforms  $V_s$  and  $V_o$ .
- Calculate the peak to peak value of ripple voltage and the mean value of  $V_o$ .