



Universidad  
Carlos III de Madrid  
[www.uc3m.es](http://www.uc3m.es)

# Session 3

## Electronic circuits analysis – Exercises –

Electronic Components and Circuits

José A. Garcia-Souto


[www.uc3m.es/portal/page/portal/dpto\\_tecnologia\\_electronica/Personal/JoseAntonioGarcia](http://www.uc3m.es/portal/page/portal/dpto_tecnologia_electronica/Personal/JoseAntonioGarcia)

# Electronic circuits analysis

## OBJECTIVES

- Example of superposition theorem
- Example of Thevenin and Norton theorems
- Examples of transient response: time constants
- Examples of SPR sinusoidal permanent regime and frequency response: attenuation, delay and cutoff frequency


# Example of superposition theorem

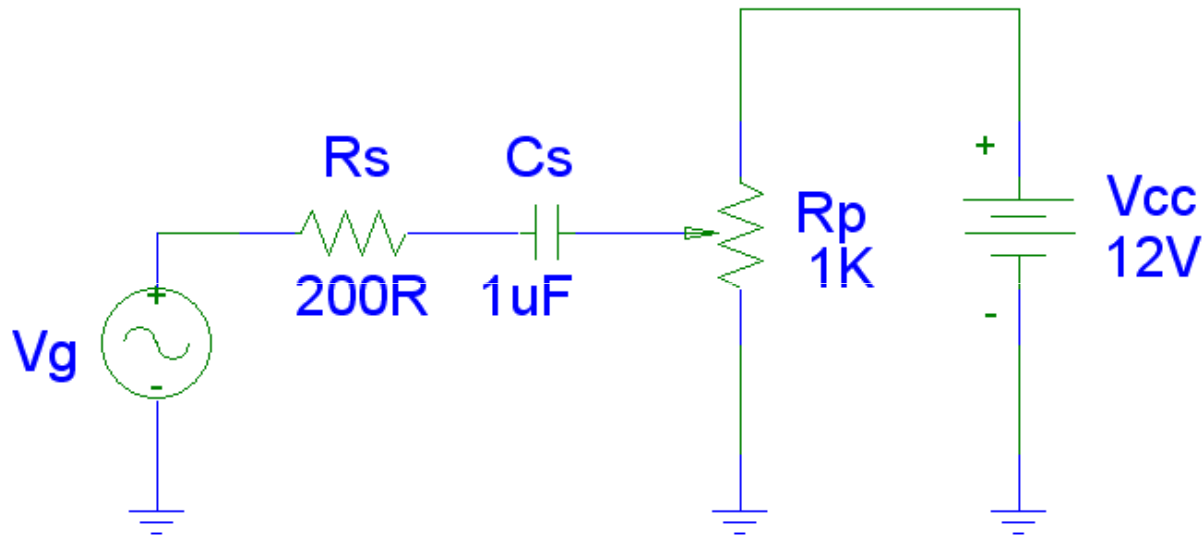

The circuit of the figure provides the superposition of an attenuated DC voltage ( $V_{cc}$  and  $R_p$ ) and AC coupling of the voltage  $V_g$ . The nominal value of the variable resistor  $R_p$  is  $1\text{k}\Omega$  and it is set to halfway ( $\alpha = 0.5$ ). The capacitor has a nominal value of  $1\mu\text{F}$  and the value of the resistance  $R_s$  is  $200\Omega$ .


- Calculate the DC power dissipated in the variable resistor  $R_p$ .
- Calculate the AC (rms) current through the capacitor  $C_s$ .
- Calculate the total power dissipated by the resistance  $R_s$ .
- Data:  $V_g$  sinusoidal 1 volt peak and 10 kHz.

# Example of Thevenin/Norton Theorems

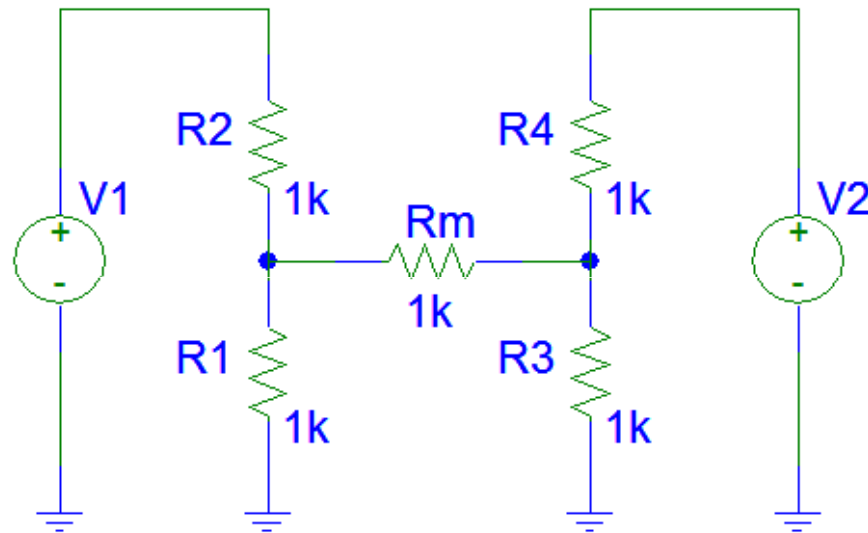


- Given the two-channel potentiometer circuit with measuring resistance  $R_m$  between both of them, calculate the current through  $R_m$  as a function of the voltage inputs  $V_1$  and  $V_2$  and the resistors  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ .
- Apply the Thevenin equivalent of each potentiometer circuit. What is the expression reduced to if all resistances are equal.
- In the case of  $V_1 = V_2$  (Wheatstone bridge) you may use the same methodology. Observe that it is in equilibrium if all resistances are equal.
- Do it again using the superposition theorem.

# RC circuit response exercise

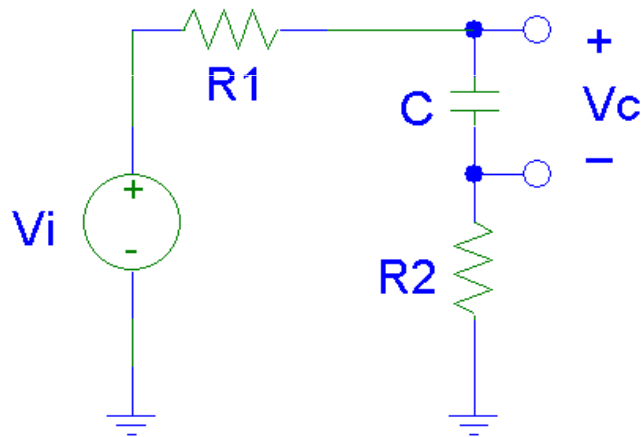

**Figure 1**

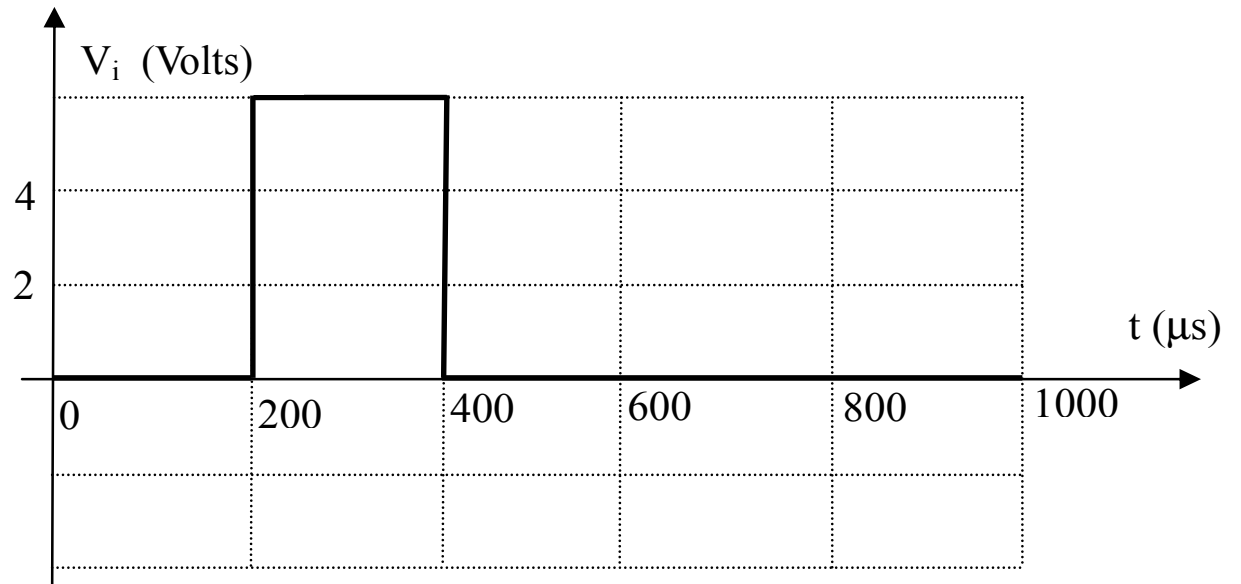


**Figure 2**


DATA:  $R1 = 1 \text{ k}\Omega$        $C = 100 \text{ nF}$        $R2 = 1 \text{ k}\Omega$

- Draw an equivalent circuit and calculate the time constant.*
- Plot the time response  $V_c(t)$  if  $V_i(t)$  is as in Figure 2.*
- Plot  $V_i(t)$  and  $V_c(t)$ , if  $V_i(t)$  is sinusoidal 6V (peak-peak) and 500Hz.*

# RC circuit response problem

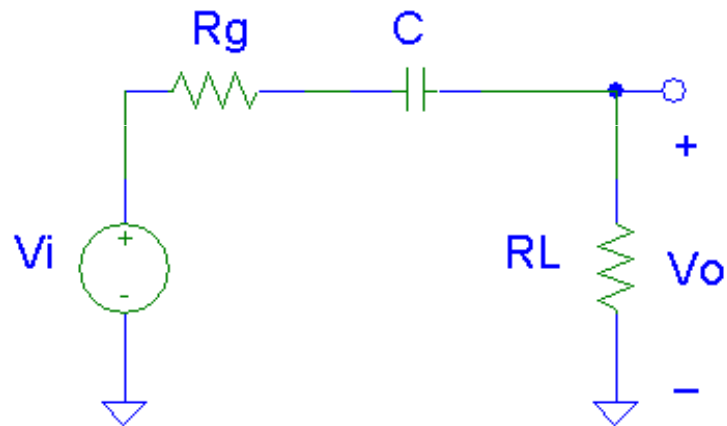

**Figure 1**

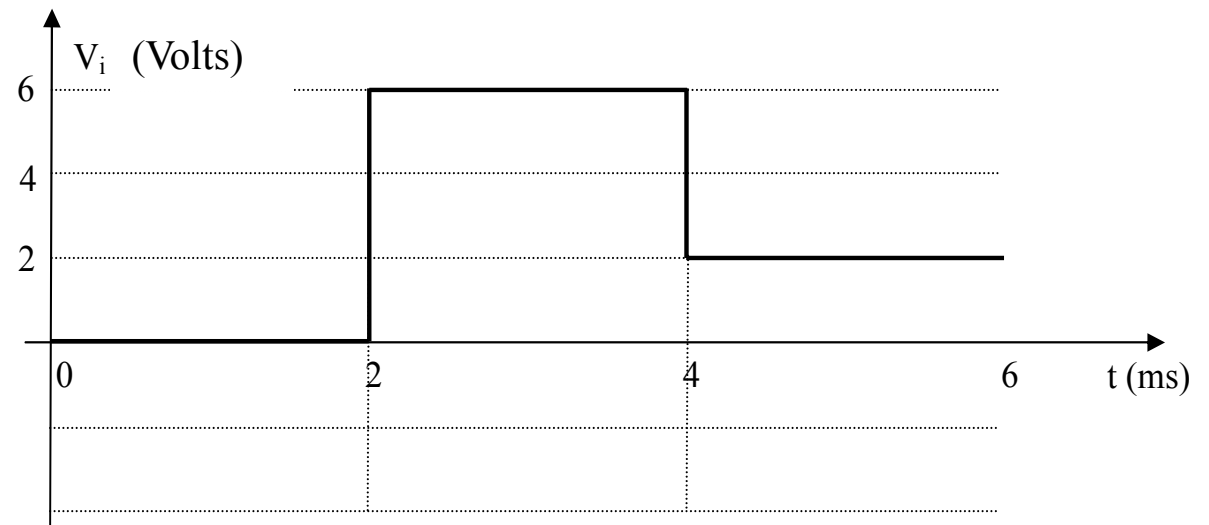

**Figure 2**

DATA (a) :             $R_g = 1 \text{ k}\Omega$ ;             $C = 100 \text{ nF}$ ;             $R_L = 1 \text{ k}\Omega$

a) Plot the time response  $V_c(t)$  and  $V_o(t)$  if  $V_i(t)$  is as shown in Figure 2.

DATA (b):             $R_g = 150 \text{ }\Omega$ ;             $C = 620 \text{ nF}$ ;             $R_L = 360 \text{ }\Omega$

b) Plot  $V_i(t)$  and  $V_o(t)$ , if  $V_i(t)$  is sinusoidal 6V (peak-peak) and 500Hz.