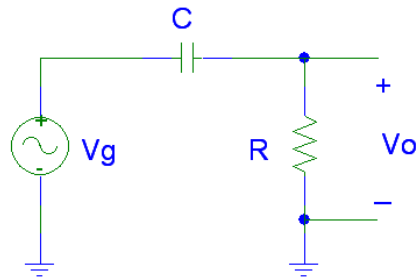






## EXERCISE 2

In the circuit of Figure 2,  $V_g$  is a sinusoidal voltage source whose amplitude is set to 1 V peak. The frequency can be changed.  $R = 1\text{K}\Omega$ ,  $C = 100\text{nF}$ .

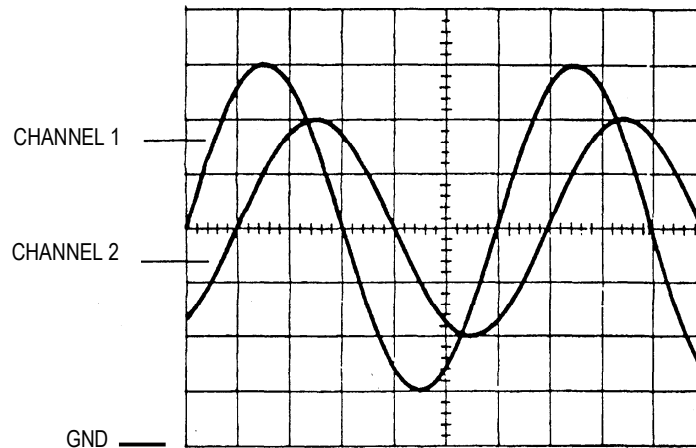


**Figure 2**

- Obtain the equation of  $V_o$  as a function of  $V_g$ ,  $C$ ,  $R$  and  $\omega$  (angular frequency).
- Calculate the amplitude of  $V_o$  in the case  $\omega = 1/(R \cdot C)$ .
- Calculate the phase shift between  $V_o$  and  $V_g$  in the case  $\omega = 10/(R \cdot C)$ .
- Why the RC circuit is a high-pass?

### EXERCISE 3

The signals in Figure 3 are observed in an oscilloscope with the following adjustments:  
 $10\mu\text{s}/\text{Div}$ ,  $200\text{ mV}/\text{Div}$ .



**Figure 3**

- Obtain the values of the period, the frequency and the amplitude of both signals.
- Calculate the phase shift between them (time shift in microseconds, phase shift in radians and degrees).

The signals are obtained in DC mode. The ground reference (GND) is in the bottom of the oscillogram.

- Calculate the voltage of channel 1 measured by a polimeter in DC mode.
- Calculate the voltage of channel 1 measured by a polimeter in AC mode.



#### EXERCISE 4

We want to fabricate a resistor with the following characteristics: nominal value  $2.2\text{K}\Omega$  and dissipation up to  $\frac{1}{4}\text{W}$ . A resistive film is used:

Film resistance:  $300\Omega/\square$       Maximum dissipation:  $1\text{W}/\text{cm}^2$

- a) Calculate the adequate length and width.

Information of the datasheet: Resistance  $2\text{K}\Omega$  (room temperature of  $25^\circ\text{C}$ ) and temperature coefficient  $10^{-4} \Omega/(\Omega\cdot^\circ\text{C})$

- b) Which is the value of the resistor at  $125^\circ\text{C}$ ?

- c) Answer again the question b with a nominal resistance of  $22\text{K}\Omega$ ?


- d) Give the range of values of a resistor with the following parameters:  
Nominal value  $2.2\text{K}\Omega$       Tolerance 10%





### EXERCISE 6

The scheme of the Figure 5 is an application circuit with diodes.  $V_{red}$  is the accessible voltage one can find in an electric plug at home.

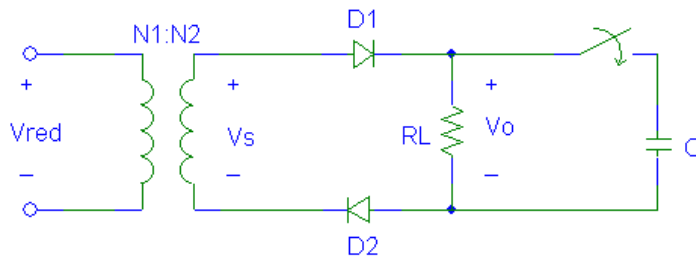


**Figure 5**

#### DATA:

$V_{red} = 220 \text{ Vrms}; 50 \text{ Hz}$   
 $N1/N2=26$   
Ideal diodes ( $V_{D-ON} = 0V$ )  
 $R_L = 300 \Omega$

a) Which type of application is?

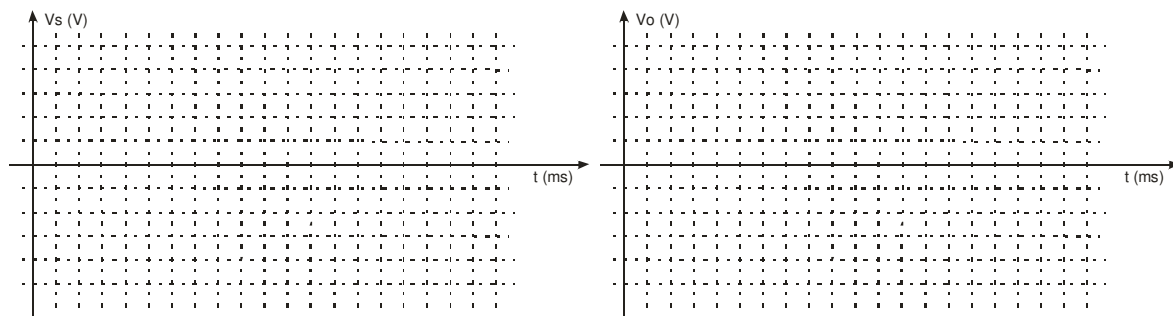b) If C is disconnected plot the voltages  $V_s$  and  $V_o$ . Give details of time and amplitude.



c) With the capacitor C connected, obtain the value of C so as the ripple is less than  $1V_{pp}$ .