



Universidad
Carlos III de Madrid
www.uc3m.es

Session 13

Introduction to Field Effect Transistors (FET)

Electronic Components and Circuits

Enrique San Millán / Celia López

Field Effect Transistors FET

OBJECTIVES

- To know the structure of the device and the transistor effect
- To know and distinguish different FET transistor types
- To understand the current-voltage characteristic of the device
- To identify the operating regions
Cut-off, Saturation, Ohm (triode)
- To analyze FET circuits basic cases in DC
- To know small-signal model for FET transistors







Field Effect Transistors (FET)

Types	Mode	Channel
MOSFET (Metal-Oxide Semiconductor FET)	Enhancement/ Accumulation	Channel N (or N-MOS) Channel P (or P-MOS)
	Depletion	Channel N (or N-MOS) Channel P (or P-MOS)
JFET (Joint FET)	Junction	Channel N Channel P



Basic characteristics

- Unipolar: only one carrier type (electrons in N-channel and holes in P-channel)
- Control of *Current (I)* through *Voltage (V)* (BJT devices control I through I)
- Three terminals:
 - Source (S): provides carriers
 - Gate (G): controls carriers flow
 - Drain (D): receives carriers

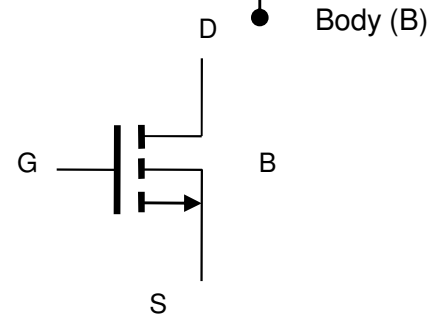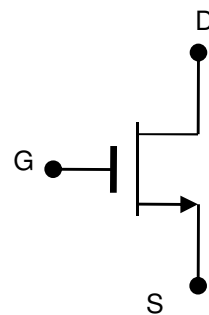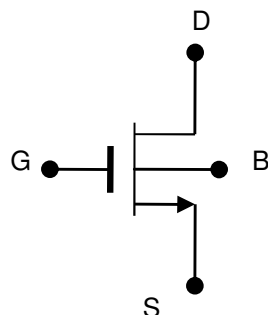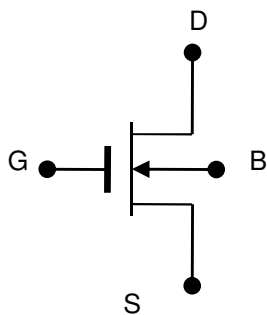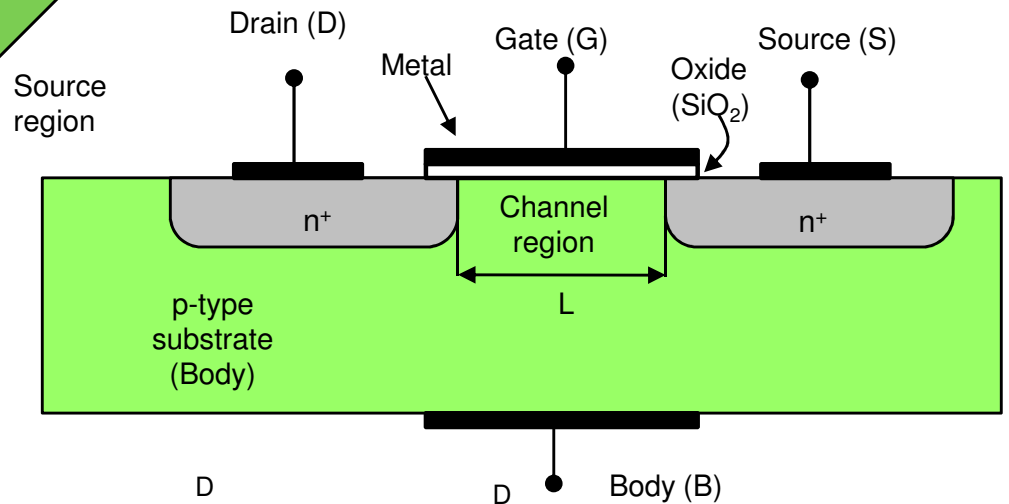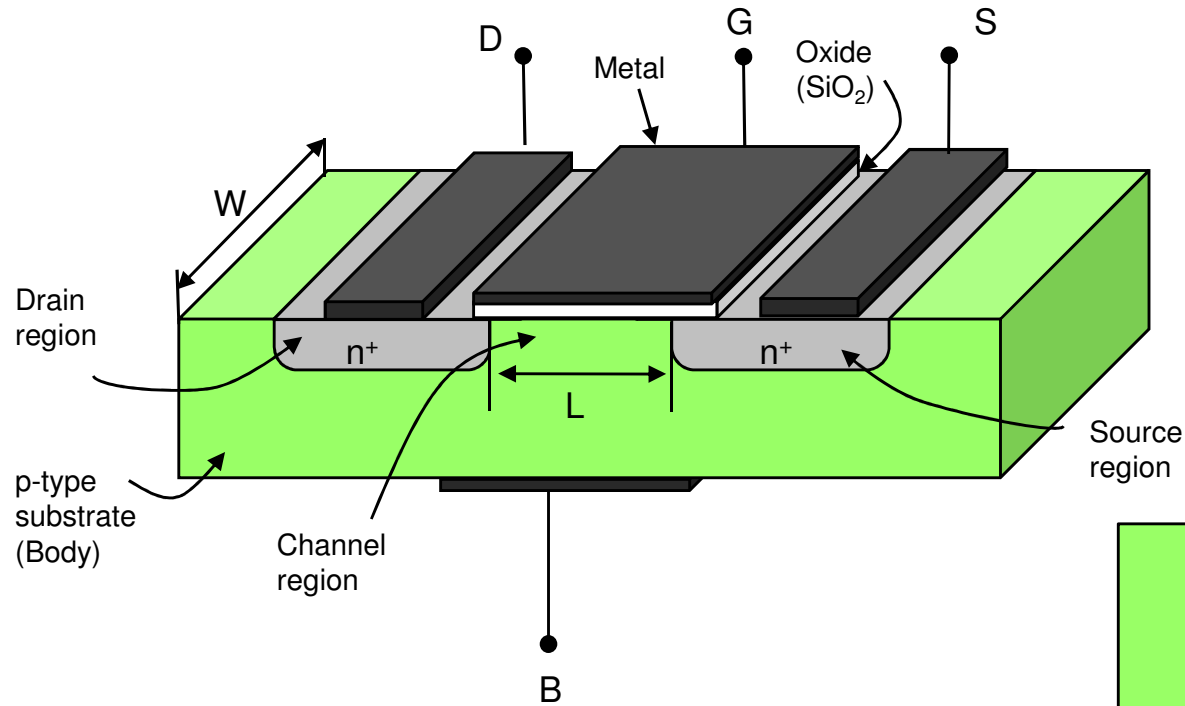
Structure of Channel-n Enhancement MOS Transistor




n-MOS Transistor Operation

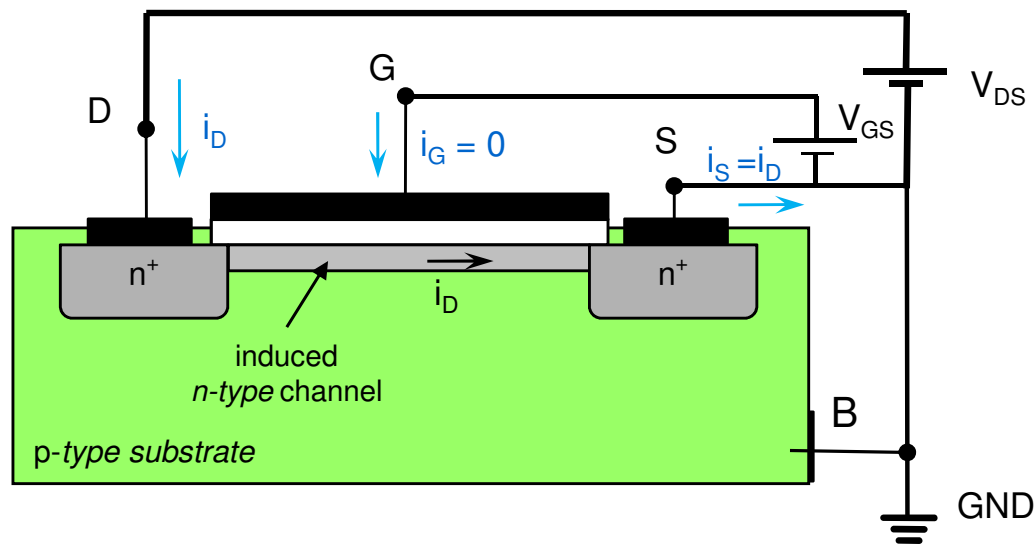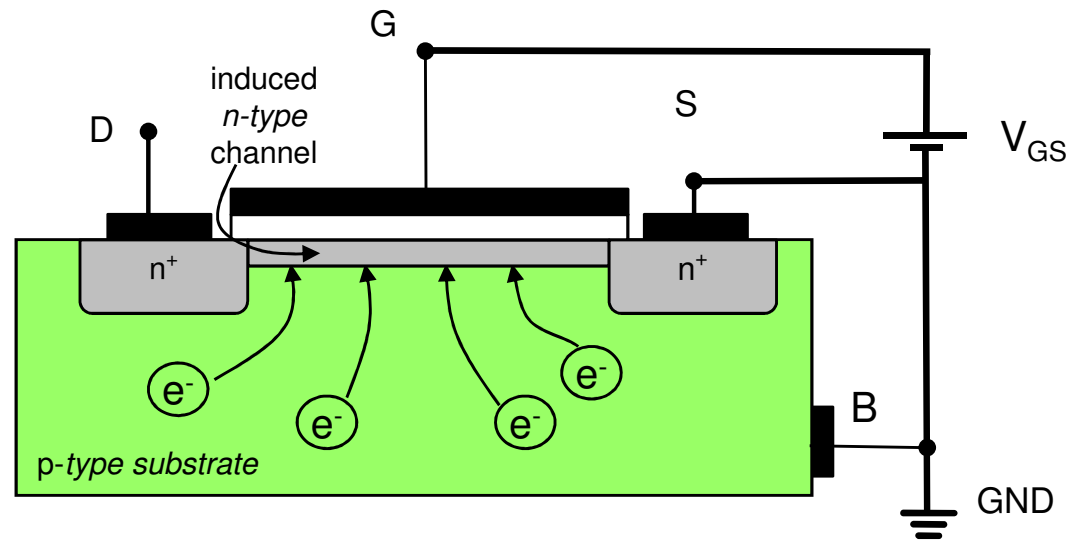



n-MOS Operation: Triode region

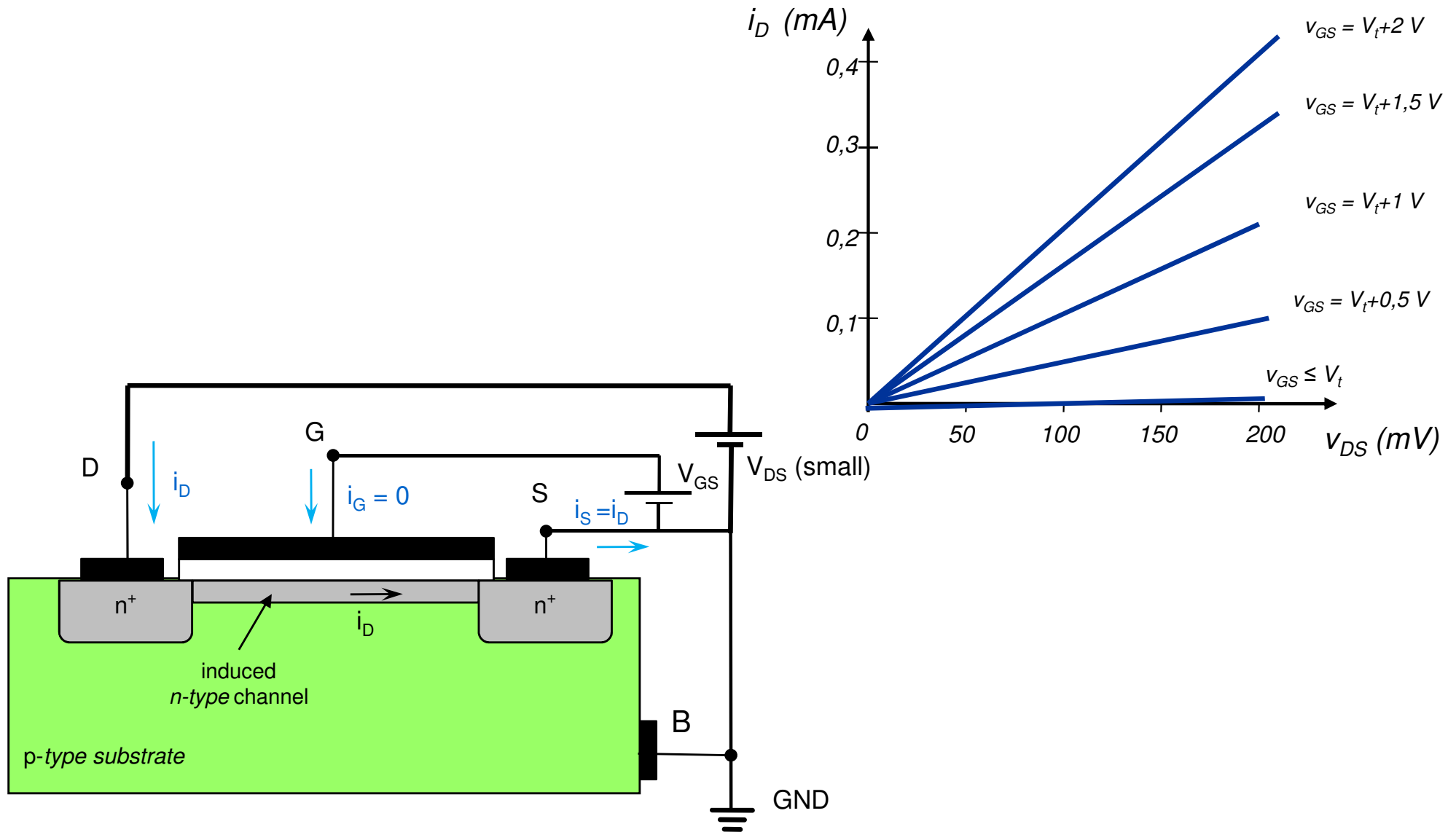

n-MOS Operation: Saturation region

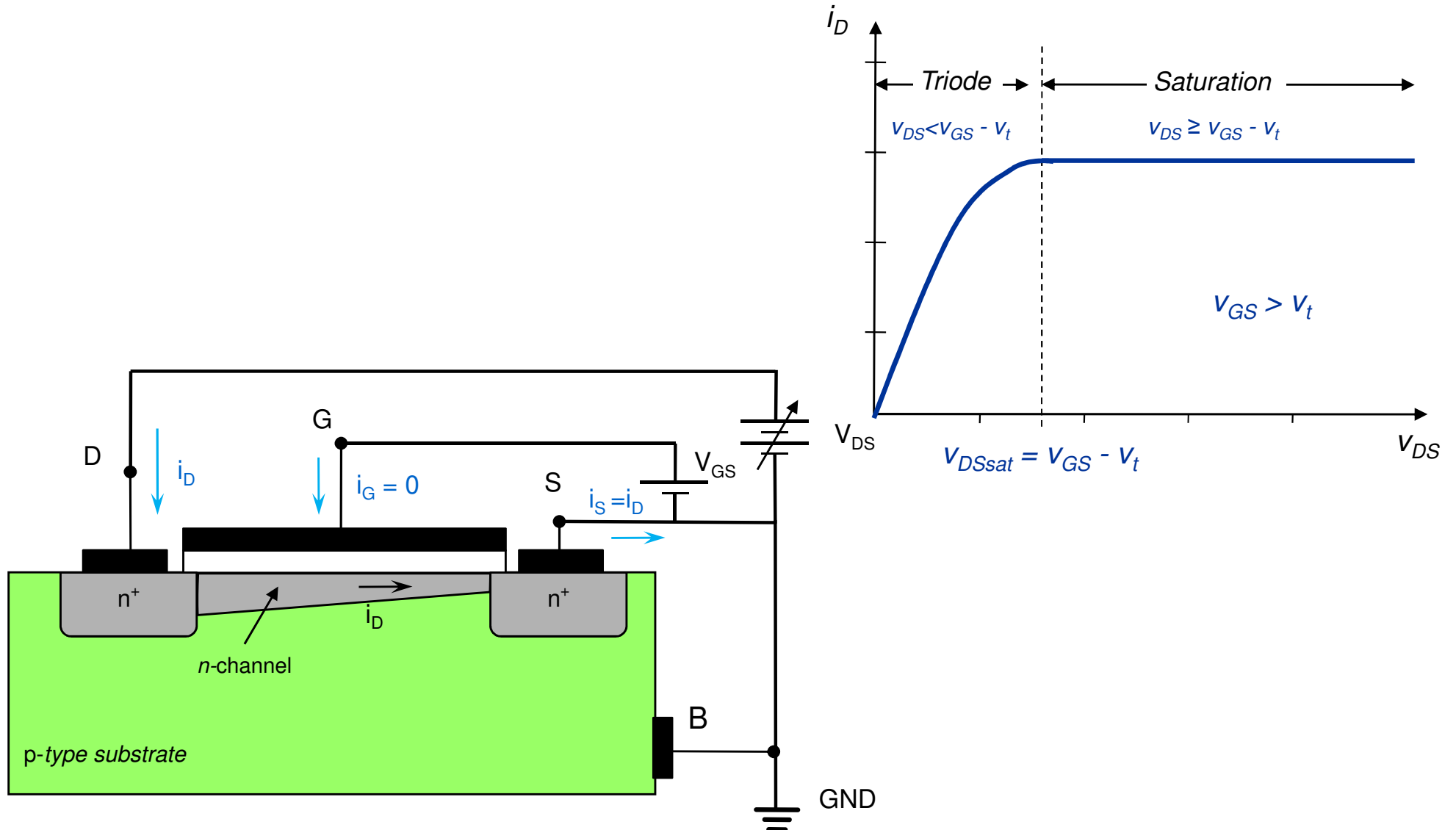

Current-Voltage Characteristic

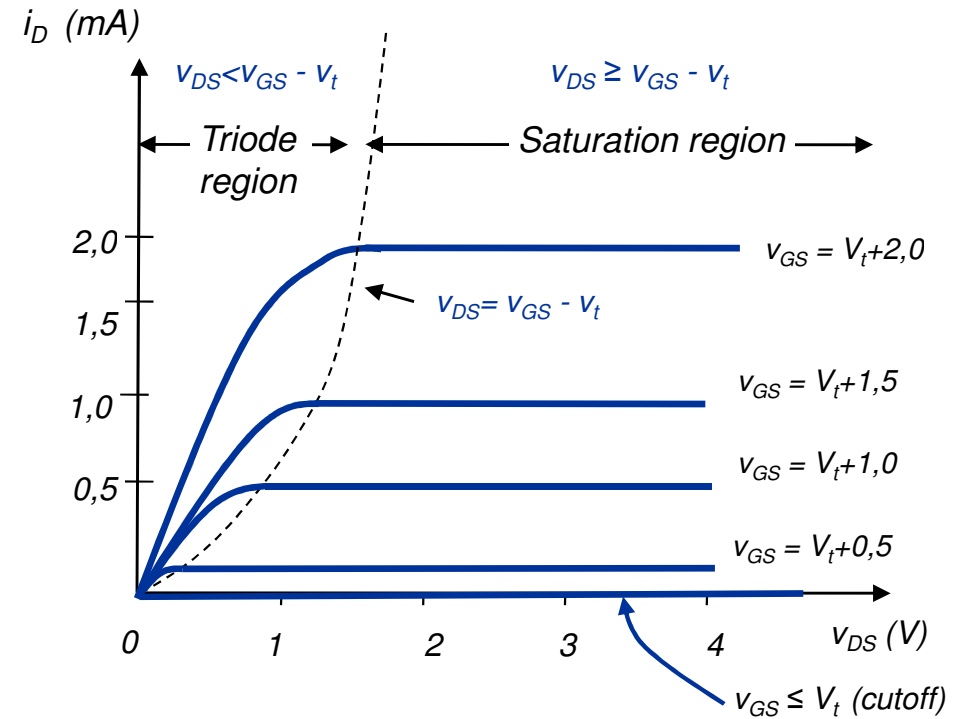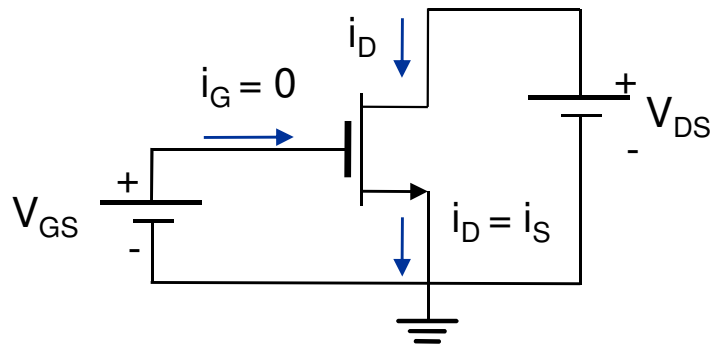

- Triode region


$$i_D = K \left[2(V_{GS} - V_t)V_{DS} - V_{DS}^2 \right]$$

- Saturation region (i_D does not depend on V_{DS})

$$i_D = K(V_{GS} - V_t)^2$$

$$K = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$$


Output Characteristics: Saturation

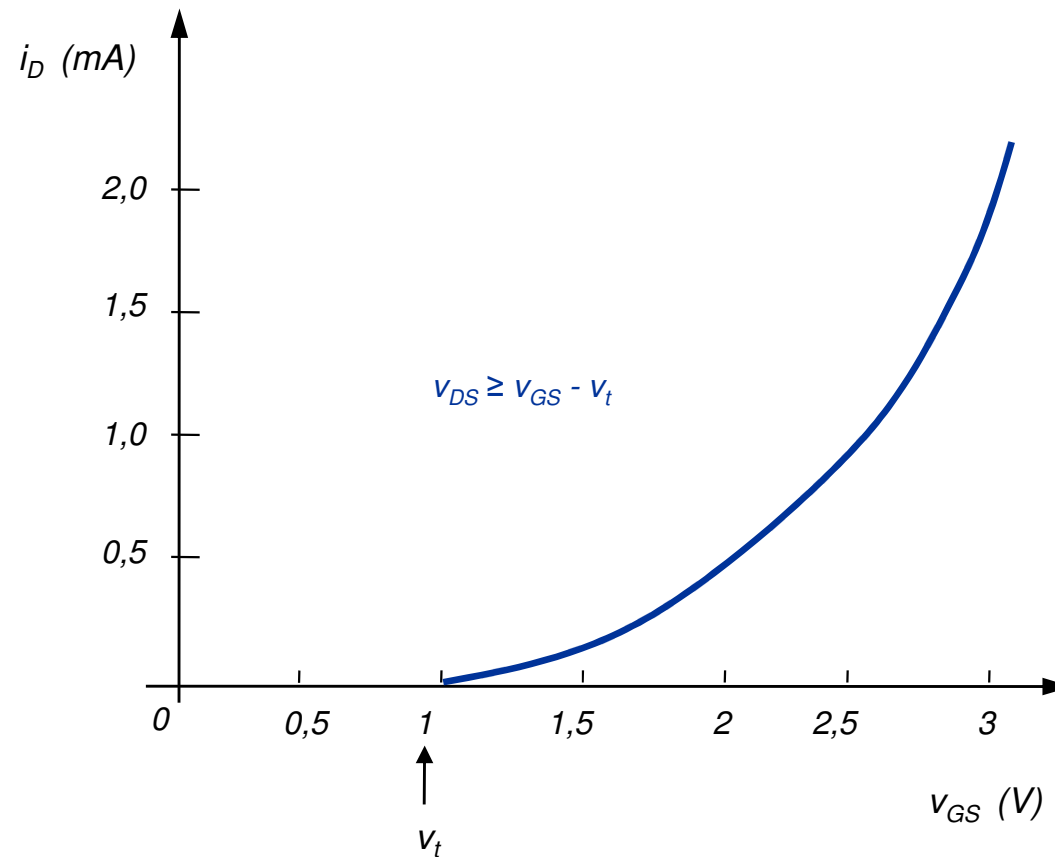

- Saturation region (i_D does not depend on V_{DS})

$$i_D = K(V_{GS} - V_t)^2$$

Current-Voltage Characteristic

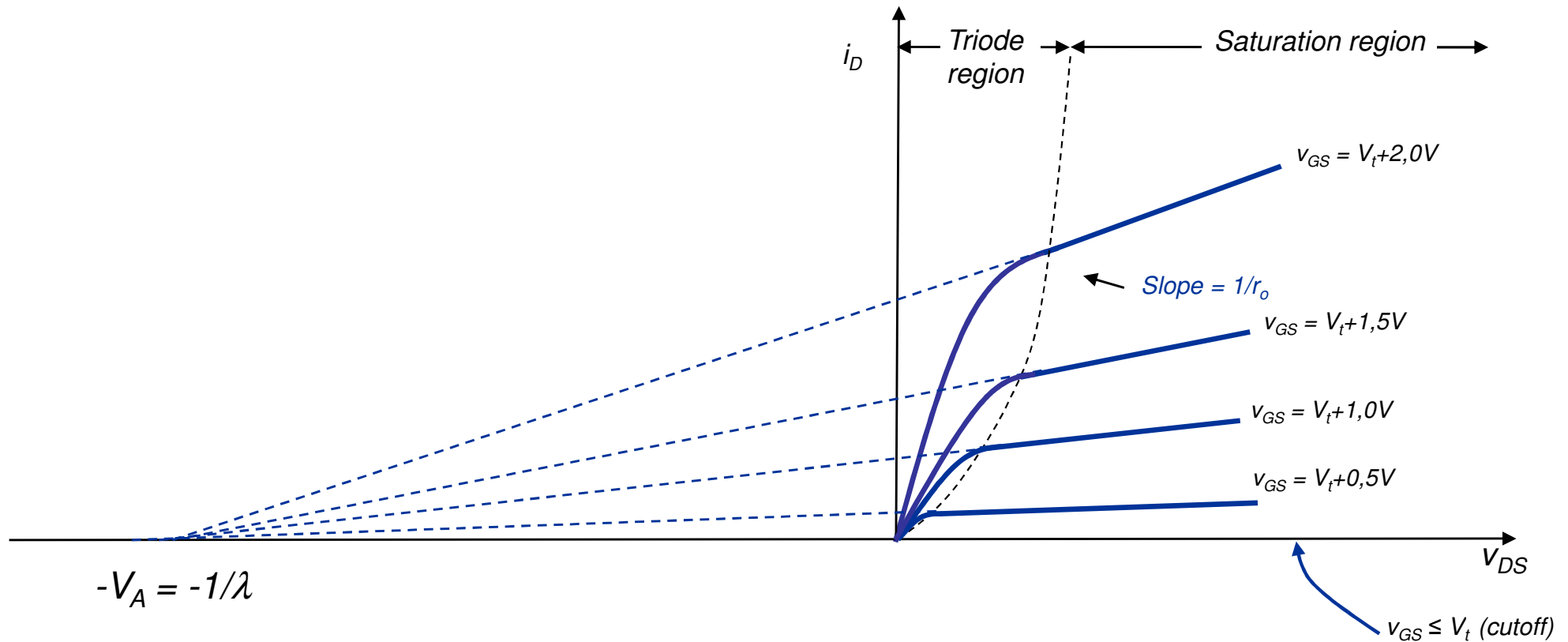


V_A is the channel modulation voltage, producing a similar effect to the Early voltage in BJT devices.

If we consider this effect then:

$$i_D = K(V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

p-channel MOSFET (P-MOS)

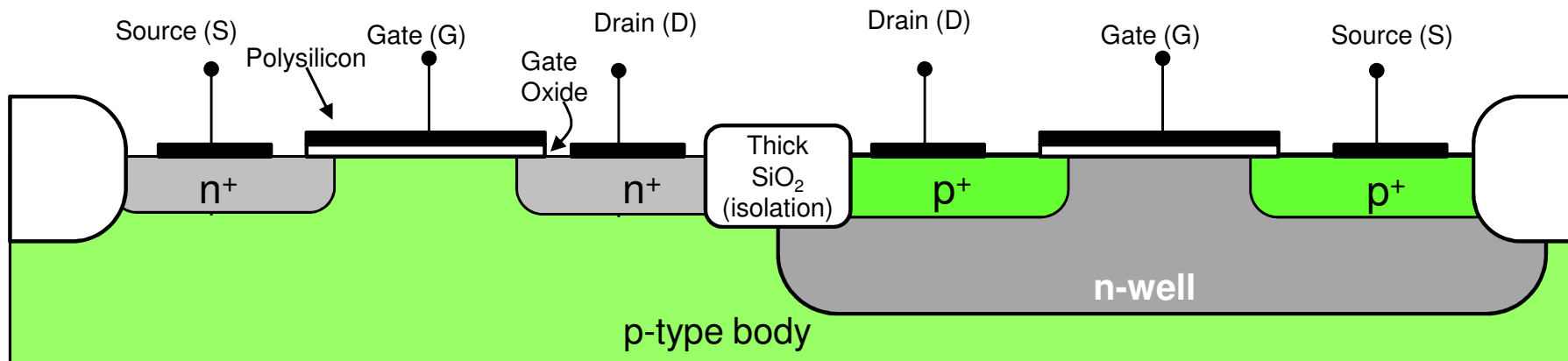


In *enhancement p-mos* there is a channel if:

$$V_{GS} \leq V_t < 0$$

$$V_{DS} \geq V_{GS} - V_t \text{ triode region}$$



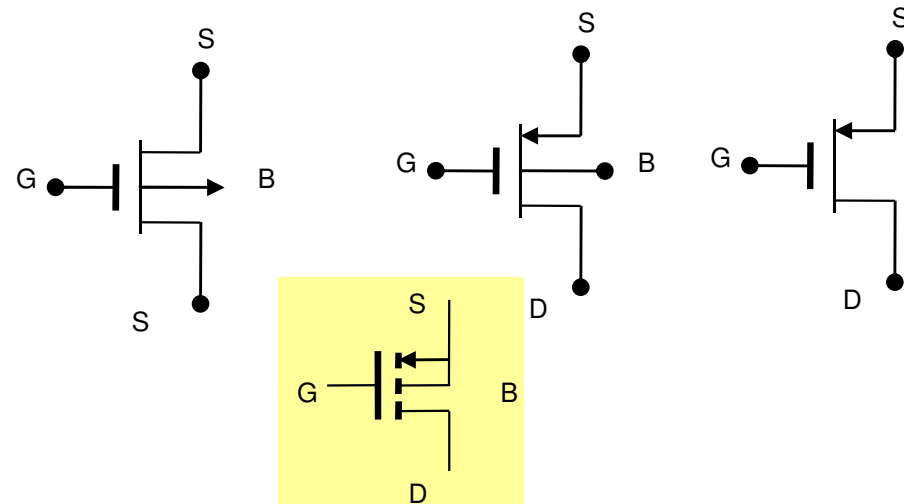
$$V_{DS} \leq V_{GS} - V_t \text{ saturation region}$$



Depletion MOSFET

Equivalent behavior to enhancement MOSFET devices, except for

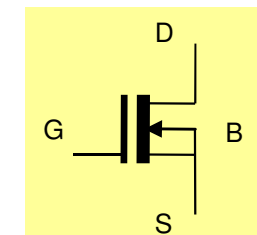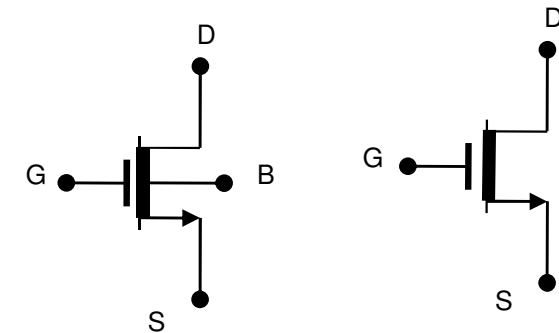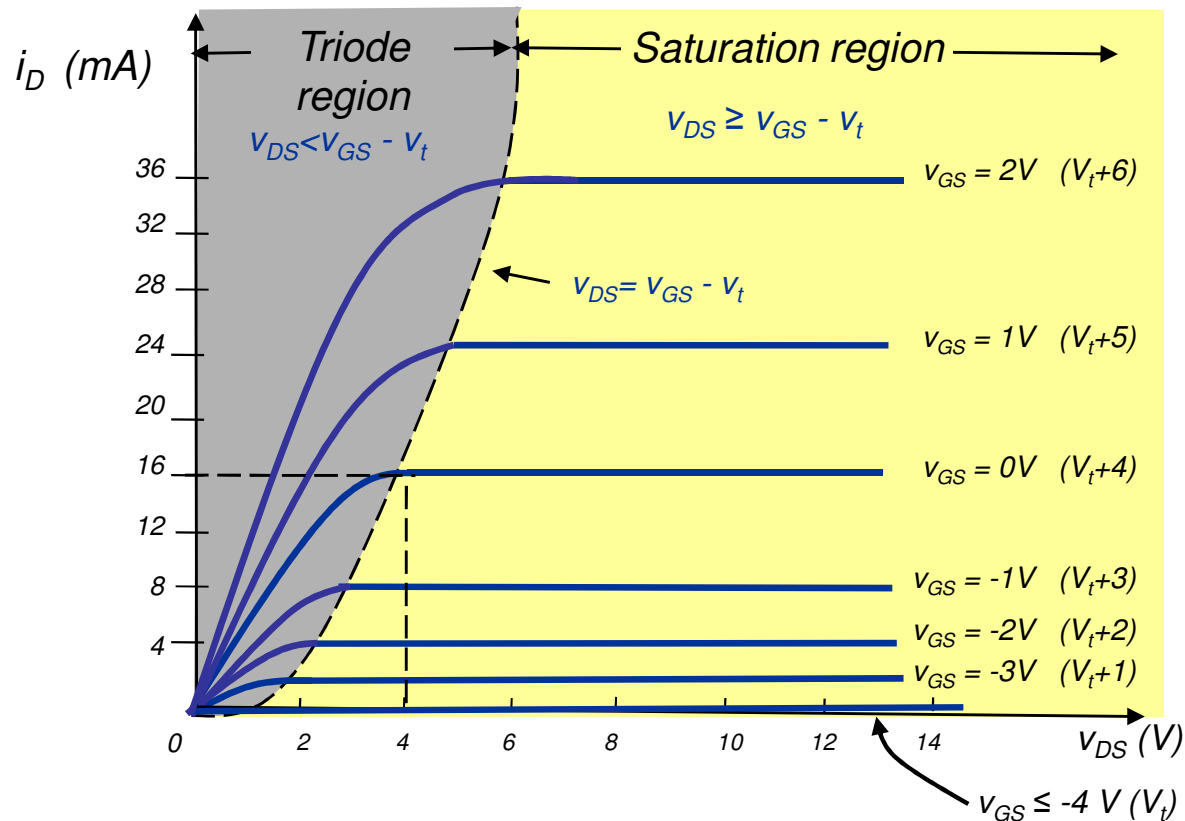- Manufactured channel:
 - When $V_{GS} < 0$ channel is reduced (e^- leave Gate region)
 - When $V_{GS} \leq V_t < 0$ channel disappears (*cut-off* region)



Summary

▪ In *enhancement* n-MOS there is a channel if: $V_{GS} \geq V_t > 0$


$V_{DS} \leq V_{GS} - V_t$ in triode region

$V_{DS} \geq V_{GS} - V_t$ in saturation region

▪ In *enhancement* p-MOS there is a channel if: $V_{GS} \leq V_t < 0$

$V_{DS} \geq V_{GS} - V_t$ in triode region

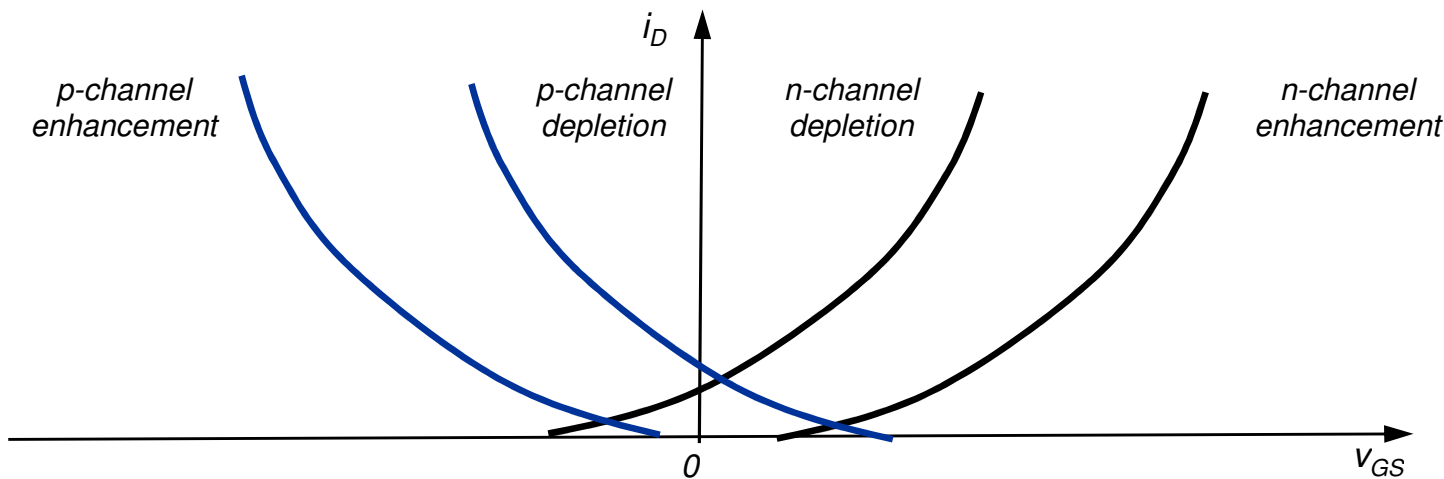$V_{DS} \leq V_{GS} - V_t$ in saturation region



▪ In *depletion* n-MOS there is a channel if: $V_{GS} \geq V_t, V_t < 0$

$V_{DS} \leq V_{GS} - V_t$ in triode region

$V_{DS} \geq V_{GS} - V_t$ in saturation region



▪ In *depletion* p-MOS there is a channel if: $V_{GS} \leq V_t, V_t > 0$

$V_{DS} \geq V_{GS} - V_t$ in triode region



$V_{DS} \leq V_{GS} - V_t$ in saturation region

Junction Field Effect Transistor (JFET)

N channel

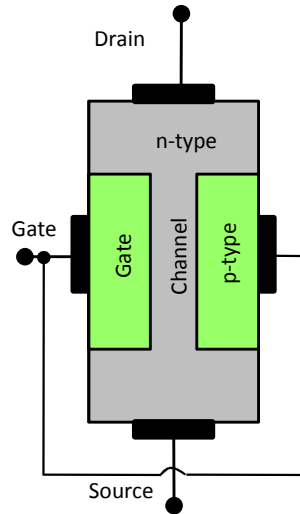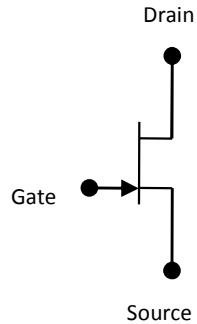


P channel

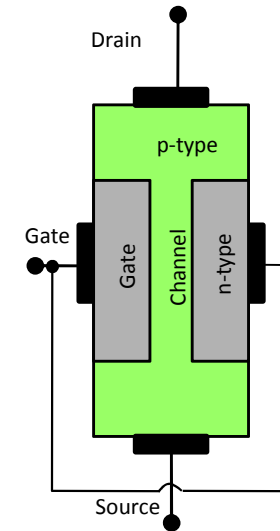
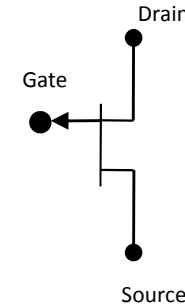


$$i_D = K(V_{GS} - V_p)^2, \quad K = I_{DSS} / V_p^2$$

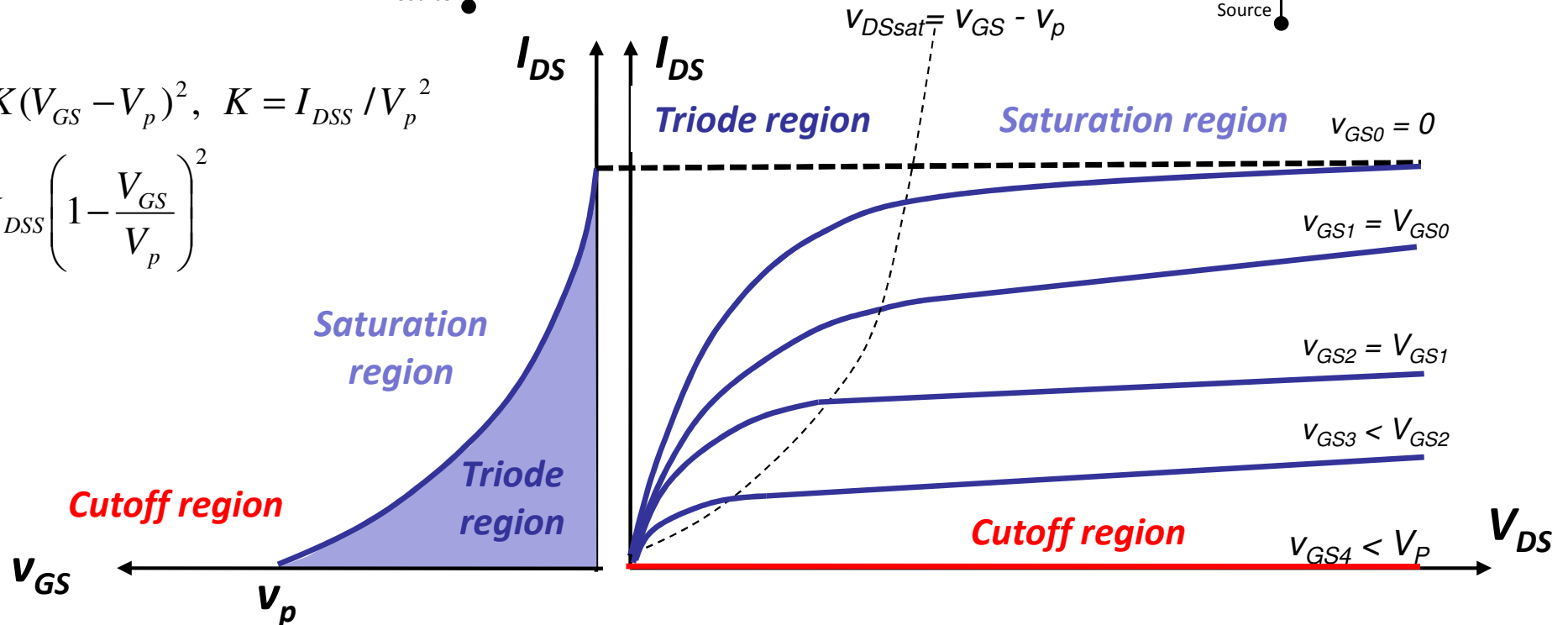
$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$







DC bias point: Load line

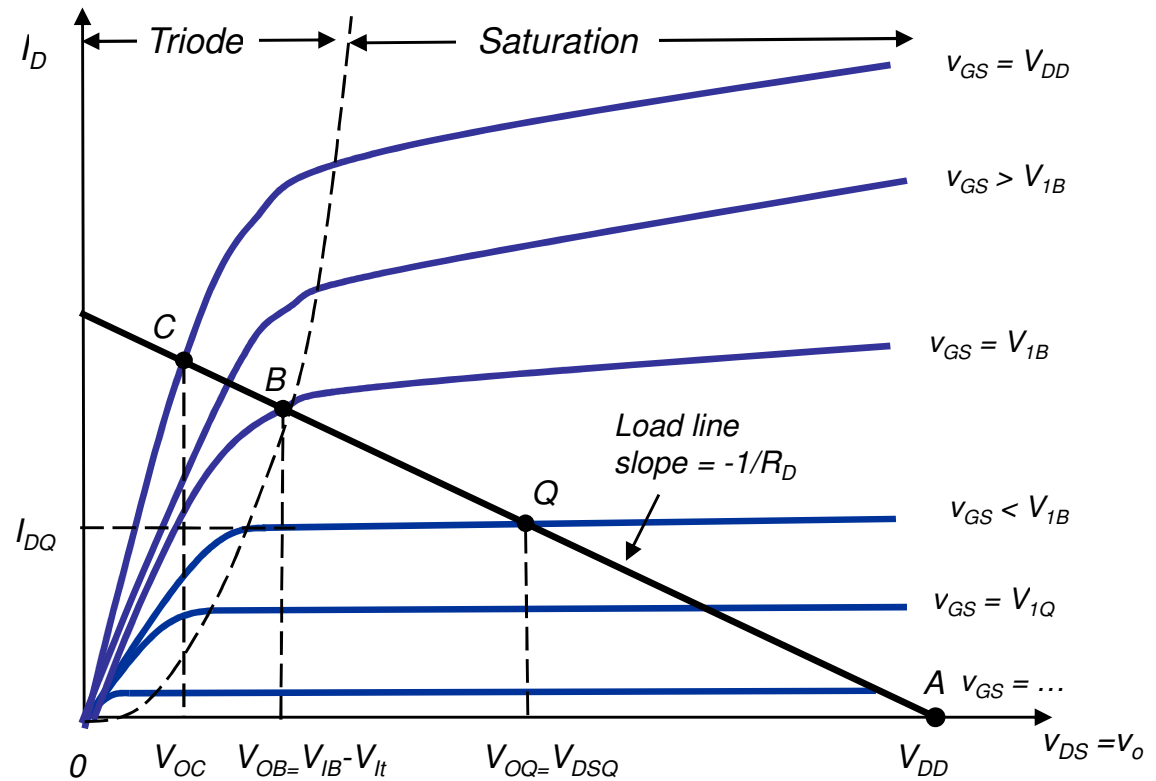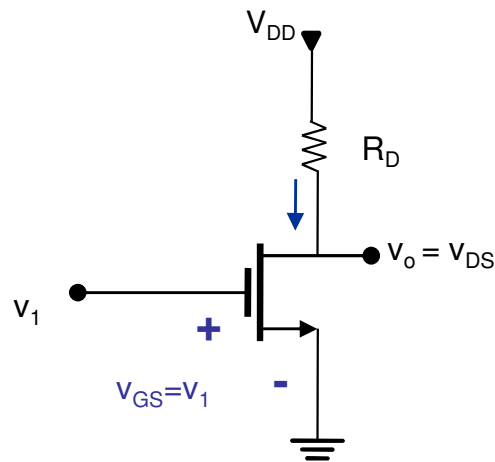



FET transistor as amplifier:

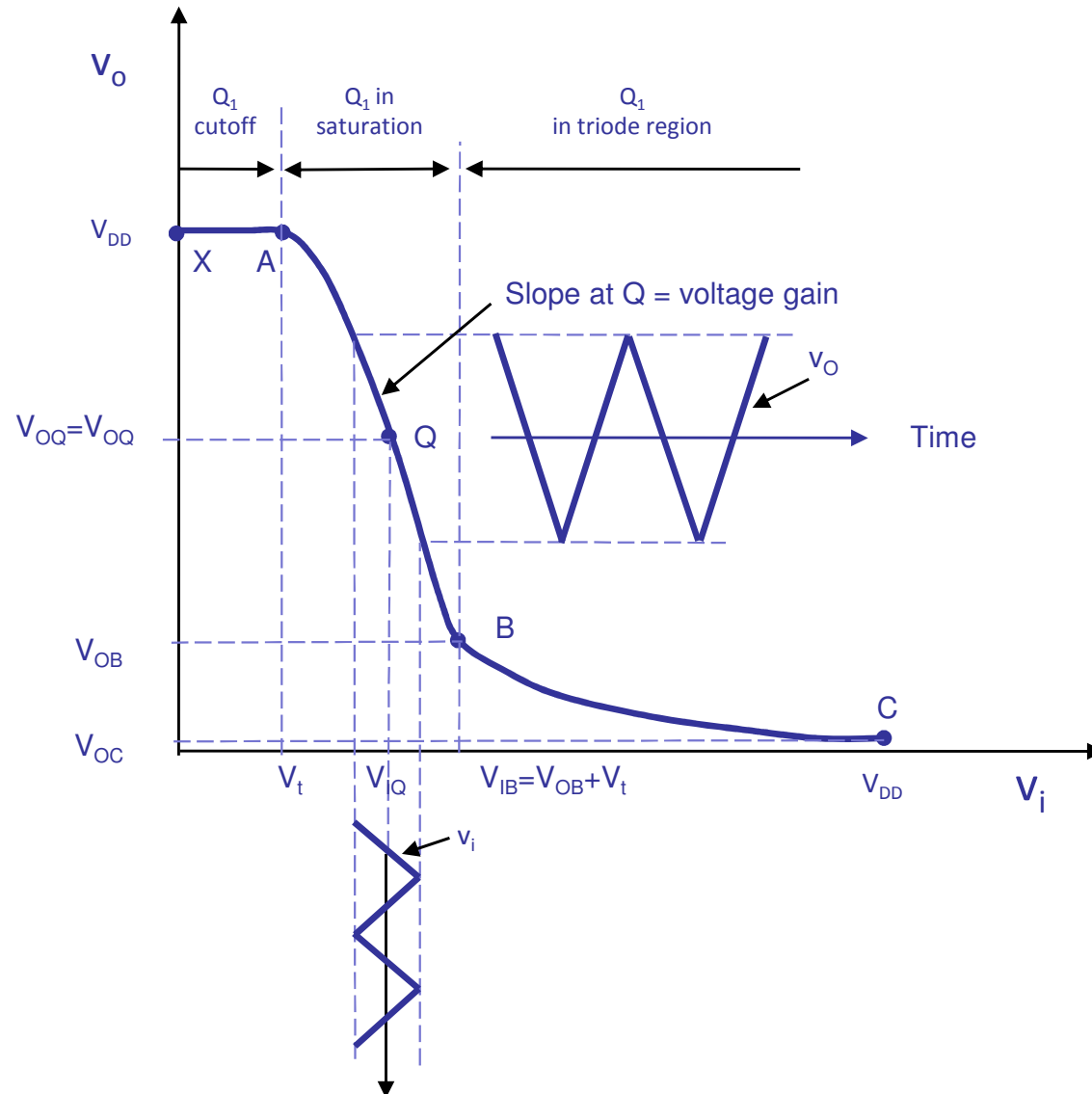

Small-signal model

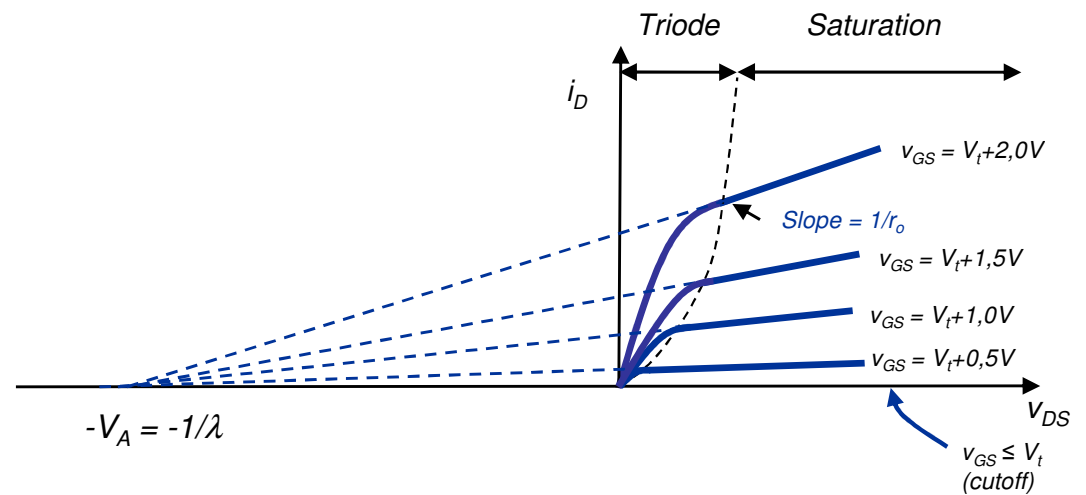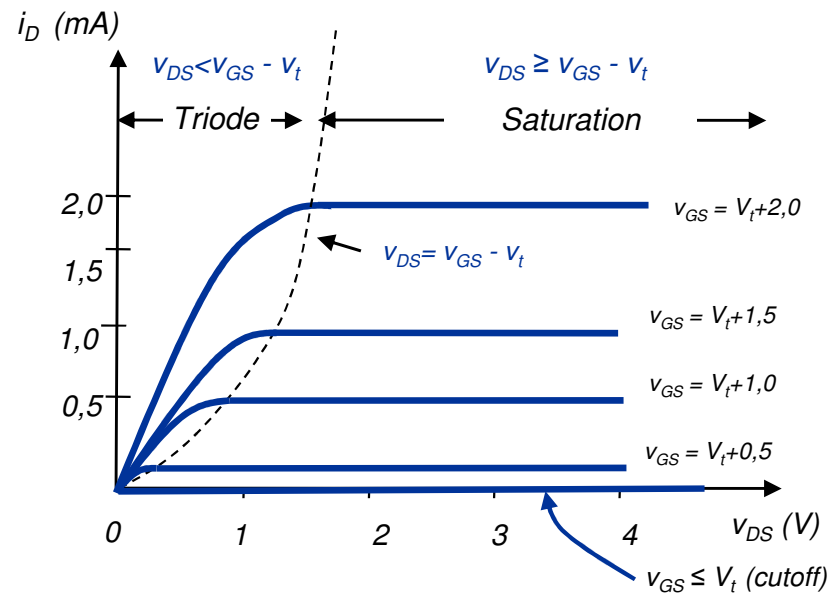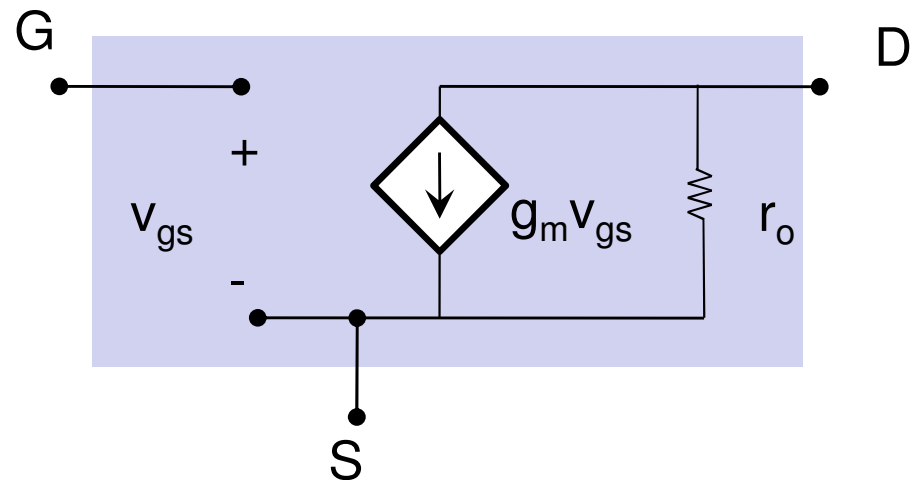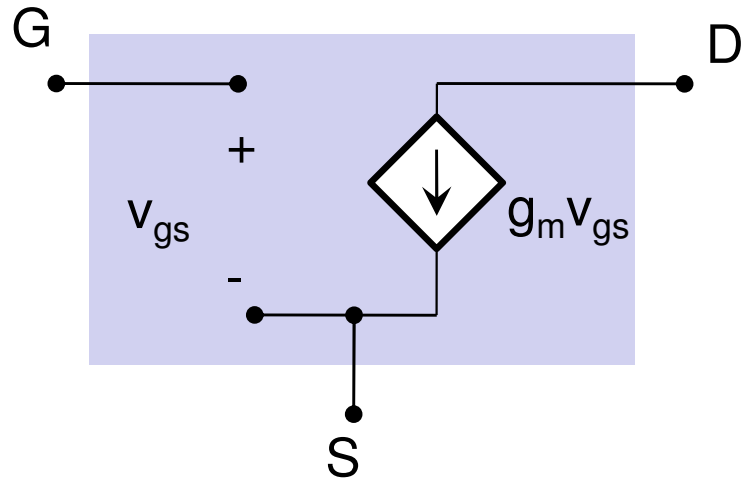

Small-signal parameters

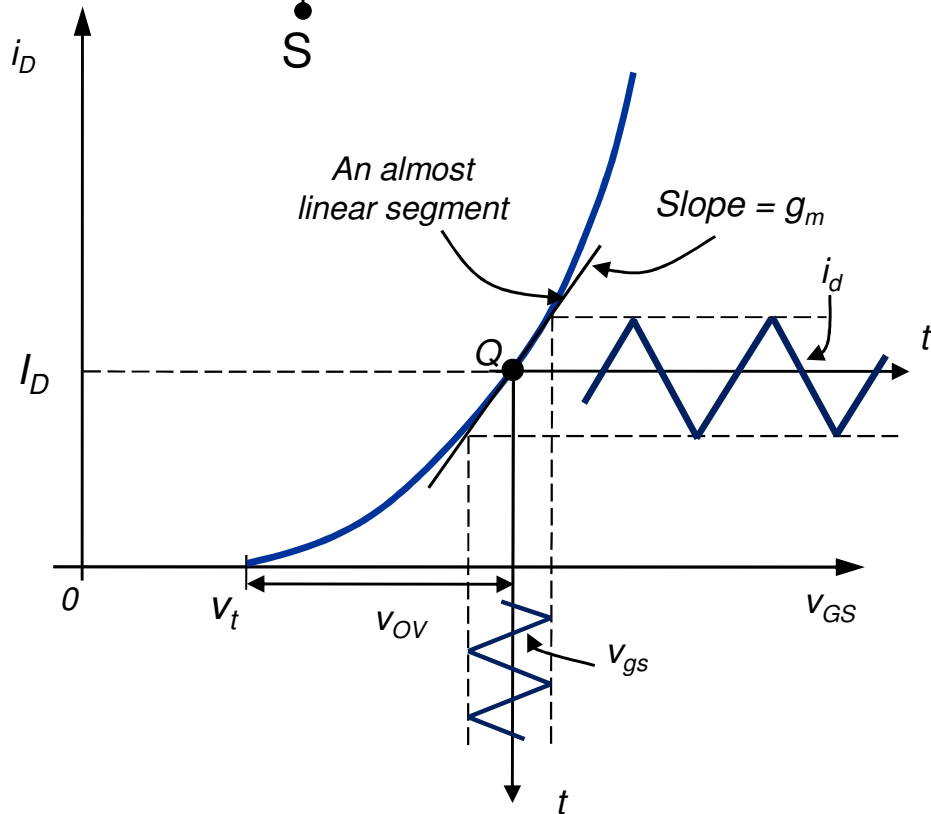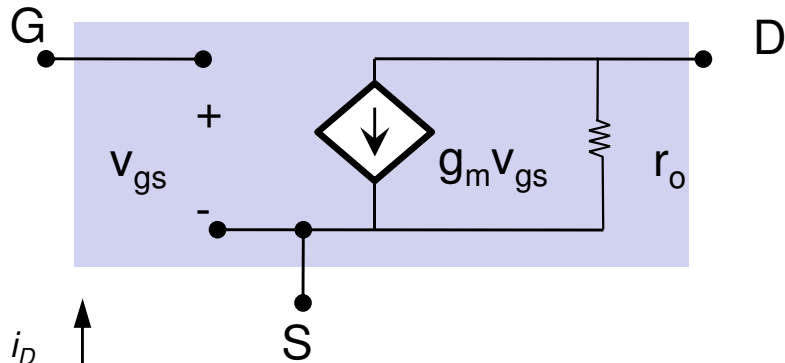



- In MOSFETs

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{v_{ds}=V_{DSQ}} = 2K(V_{GS} - V_t)$$

- In JFETs

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{v_{ds}=V_{DSQ}} = -2 \frac{I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$

Small-signal parameters

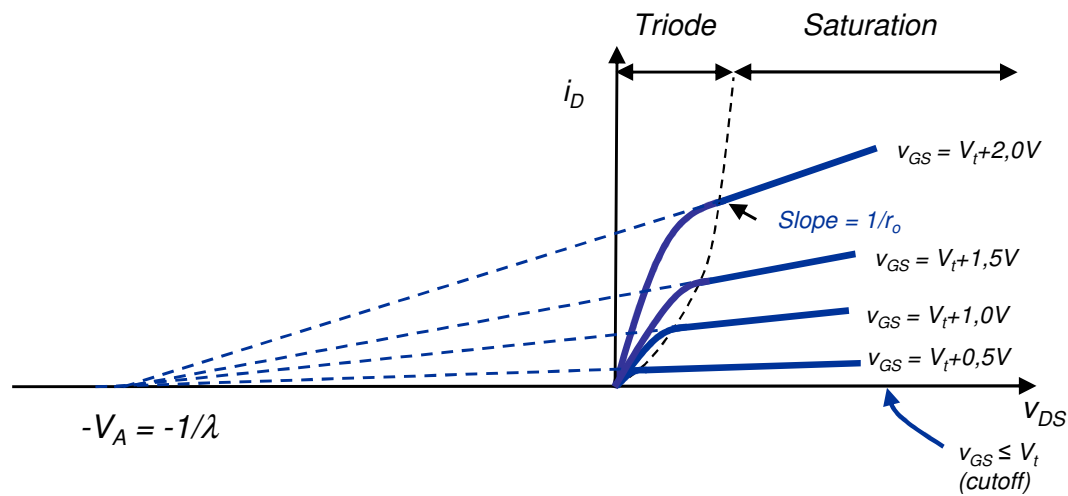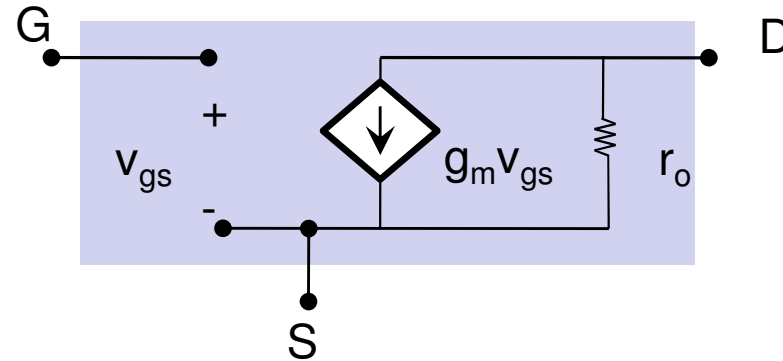

$$\frac{1}{r_o} = \frac{\partial i_D}{\partial v_{DS}} \approx \lambda I_D = \frac{I_D}{V_A}$$

$$r_o = \frac{V_A}{I_D}$$

Exercise:

Operation regions. Saturation

EXAMPLE


$$|V_t| = 2 \text{ V}$$

$$L = 10 \mu\text{m}$$

$$W = 100 \mu\text{m}$$

$$\lambda = 0$$
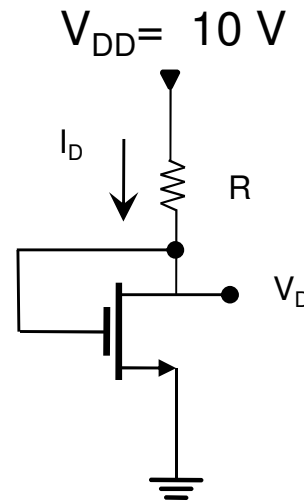
$$\mu_n C_{ox} = 20 \mu\text{A} / \text{V}^2$$




- Design the circuit in order to obtain a $I_D = 0.4 \text{ mA}$
- Calculate the value of R and voltage V_D for that value of current

Exercise:

Operation regions. Triode region


EXAMPLE

- $V_{DD} = 5 \text{ V}$
- $K = 0.5 \text{ mA/V}^2$
- $|V_t| = 1 \text{ V}$

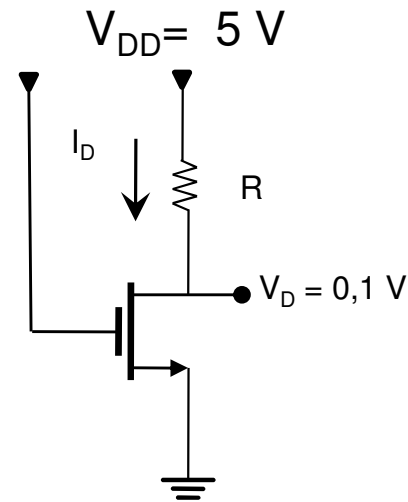

- Design the circuit for obtaining $V_D = 0.1 \text{ V}$
- Calculate the equivalent resistance of the transistor in this case

Proposed exercise

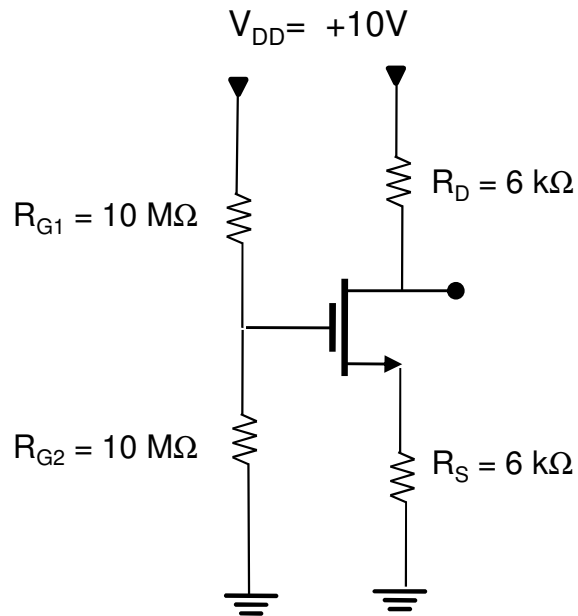

Example

- $K = 0.5\text{ mA/V}^2$
- $|V_t| = 1\text{ V}$

- Analyse this circuit and calculate the voltage in every node and the current in every line
- Obtain the equivalent small-signal circuit