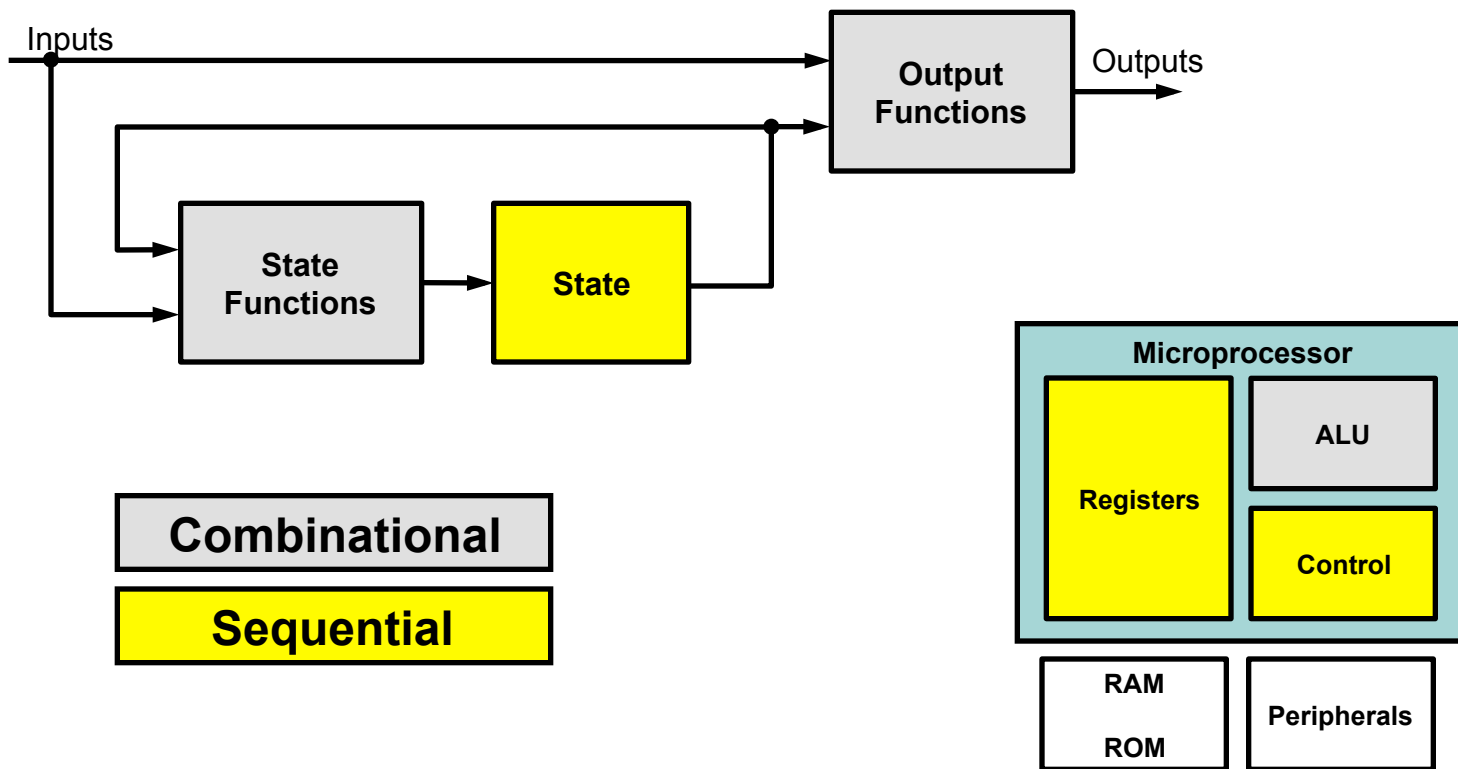


Flip-flops

© Luis Entrena, Celia López,
Mario García, Enrique San Millán
Universidad Carlos III de Madrid

Digital circuits and microprocessors



Outline


- Introduction
 - The flip-flop as the basic memory element
 - Flip-flop classification
- Asynchronous flip-flops
- Synchronous flip-flops
- Synchronous flip-flops with asynchronous inputs
- Flip-flop control logic
- Timing characteristics
- Synchronous circuits
- Circuits with flip-flops: chronograms

1. Introducción: flip-flops

- Definition:
 - Circuit storing an information bit. It has two stable states, logic 0 and logic 1. The state does not change until the control inputs allow it.
- Classification
 - Control logic: inputs determining the new state
 - D, T, SR, JK
 - Synchronism:
 - Asynchronous: can change the state in response to any input, at any time
 - Synchronous: they have a control input that states when the state can change
 - Level-triggered
 - Edge-triggered

 
2. Asynchronous flip-flop

- SR asynchronous flip-flop
 - S= '1' => Set
 - R= '1' => Reset
 - S=R= '0' => Keep state
- Characteristics
 - **Memory**: it keeps the state if inputs are not active
 - **Asynchronous**: the state changes immediately if R or S are activated




Asynchronous flip-flop

- State keeping circuit

 



- With control signals

 

S	R	Q	/Q	
0	0	Q	/Q	→ Keep state
1	0	1	0	→ Set
0	1	0	1	→ Reset
1	1	0	0	→ Forbidden state

  3. Level-triggered synchronous flip-flop




- It has a control signal that allows the state to be changed
- Level-triggered synchronous D Flip-flop (D-latch)
 - C= '1' => state changes to D value
 - C= '0' => keep state



C	D	Q	/Q	
0	X	Q	/Q	→ Keep state
1	0	0	1	→ Assign '0'
1	1	1	0	→ Assign '1'

Edge-triggered synchronous flip-flop



- Edge-triggered synchronous D flip-flop

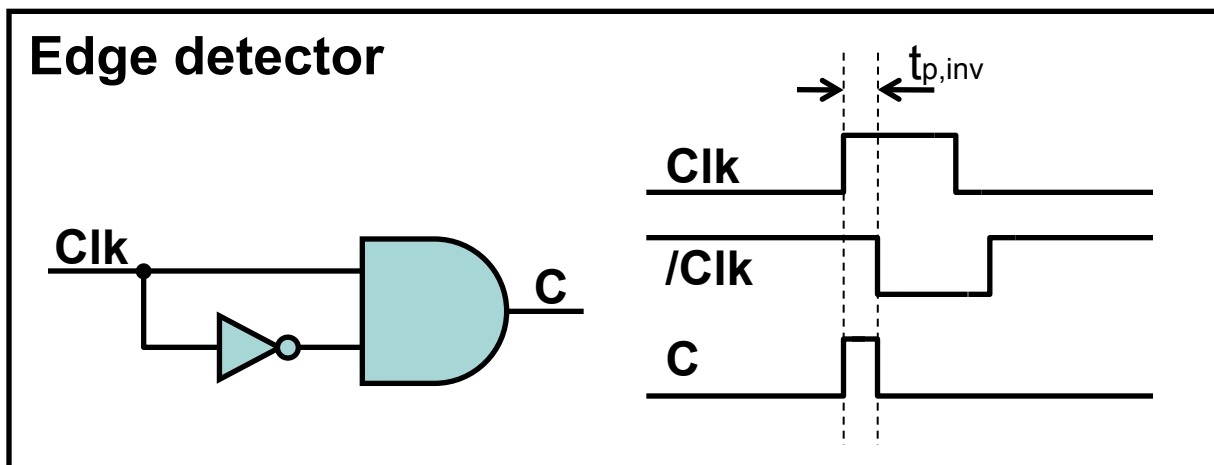  

Bad solution due to technology. Inverter delay is not controllable.

Master-Slave synchronous flip-flop

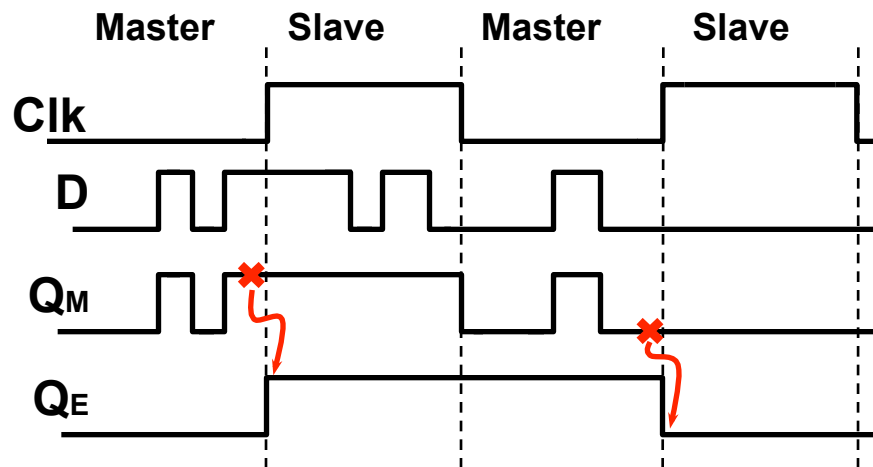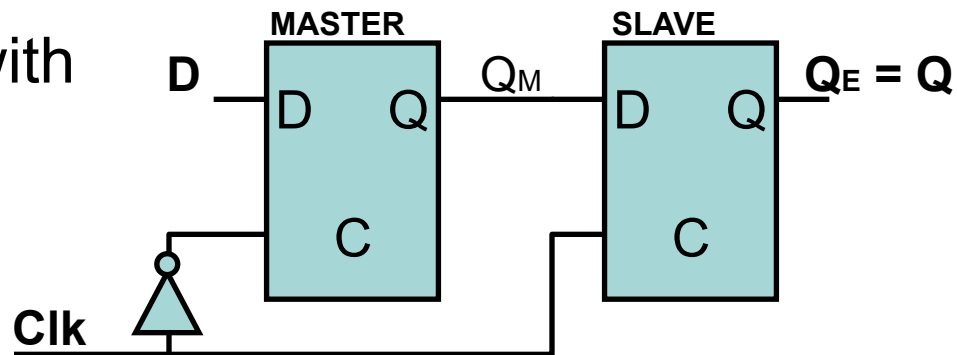
- Two latches active with opposite levels



- Q_E changes only in clock rising edges
- Q_E new value is D value just before the clock edge



Edge triggered synchronous D flip flop

 - The one used most
- Only changes in clock edges (normally rising edges)
- The output change takes place just before the edge
- The output new value is taken from D input just before the edge



  4. Synchronous flip-flops with asynchronous inputs

- Synchronous flip-flops with asynchronous inputs for initialization
 - Clear: asynchronous initialization to '0'
 - Preset: asynchronous initialization to '1'
 - Usually low-level active



5. Flip-flop control logic

- Flip-flop inputs control the way the state is changed
 - Kinds of flip-flops depending on the inputs:
 - D,T,JK,SR
 - Enable signal:
 - Allows/prevents the state to change
 - In not enabled, the state is kept
 - Synchronous initialization
 - Set to '0' or '1' in a synchronous way

Flip-flop control logic

- Working tables

- Describe functionality

D flip-flop
(Data)

D	Q'
0	0
1	1

T flip-flop
(Toggle)

T	Q'
0	Q
1	/Q

SR flip-flop
(Set-Reset)

S	R	Q'
0	0	Q
0	1	0
1	0	1

JK flip-flop
(Jump & Kill)

J	K	Q'
0	0	Q
0	1	0
1	0	1
1	1	/Q

- Transition tables

- Describes the new state in terms of the present state and input values

D flip-flop


D	Q	Q'
0	0	0
0	1	0
1	0	1
1	1	1

T flip-flop

T	Q	Q'
0	0	0
0	1	1
1	0	1
1	1	0

Flip-flop control logic

- Flip-flops with enable

 




D flip-flop

E	D	Q'
0	X	Q
1	0	0
1	1	1




T flip-flop

E	D	Q'
0	X	Q
1	0	Q
1	1	/Q

   


Flip-flop control logic

 - Flip-flop with synchronous initialization
 - Set: forces '1'
 - Reset: forces '0'
- Example: D flip-flop with Enable, Set and Reset
 - Priority: Reset, Set, Enable



 
6. Timing characteristics

- Timing flip-flop restrictions
 - Clock level length $\rightarrow (t_{0\min}, t_{1\min})$
 - Asynchronous signals length $\rightarrow (t_{\text{reset min}})$
 - Data insertion times $\rightarrow (t_{\text{setup}}, t_{\text{hold}})$



 
7. Synchronous circuits

- Synchronous circuit
 - Every flip-flop use the same clock
 - Every flip-flop is triggered by the same clock edge (usually the rising edge)
 - There is a common initialization signal called *Reset*



Synchronous circuits: the clock cycle

 - Critical path:
 - Path between two flip-flops with the larger delay
 - Slowest path between two flip-flops. It determines the maximum allowable clock frequency for the circuit.





$$t_{\text{Clk}} > t_{\text{hold}} + t_{\text{crítico}} + t_{\text{setup}}$$

$$f_{\text{Clk}} = 1 / t_{\text{Clk}}$$

$$t_{\text{Clk}} = 1\text{ns} \rightarrow f_{\text{Clk}} = 1\text{GHz}$$



7. Chronograms

- Edge detector

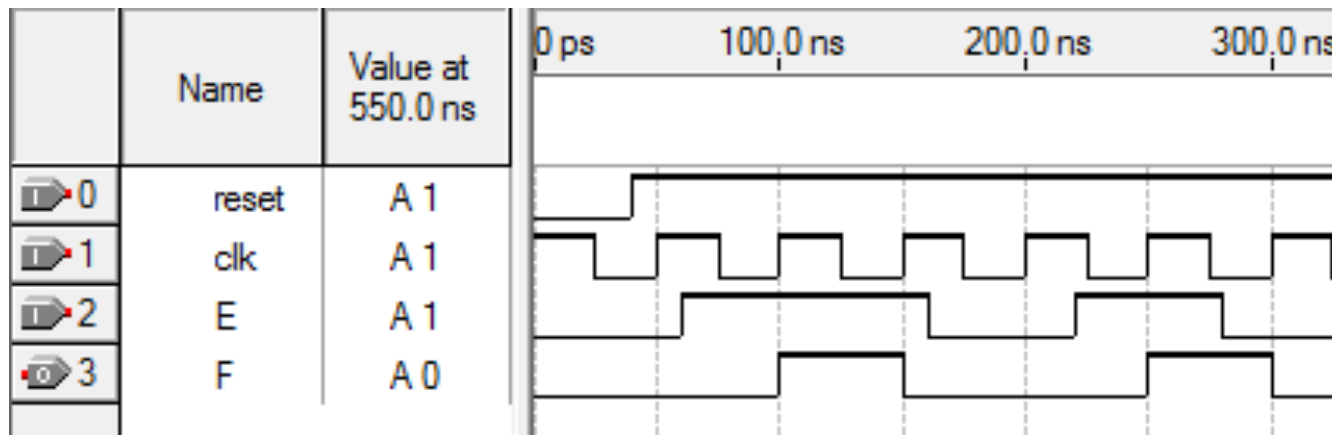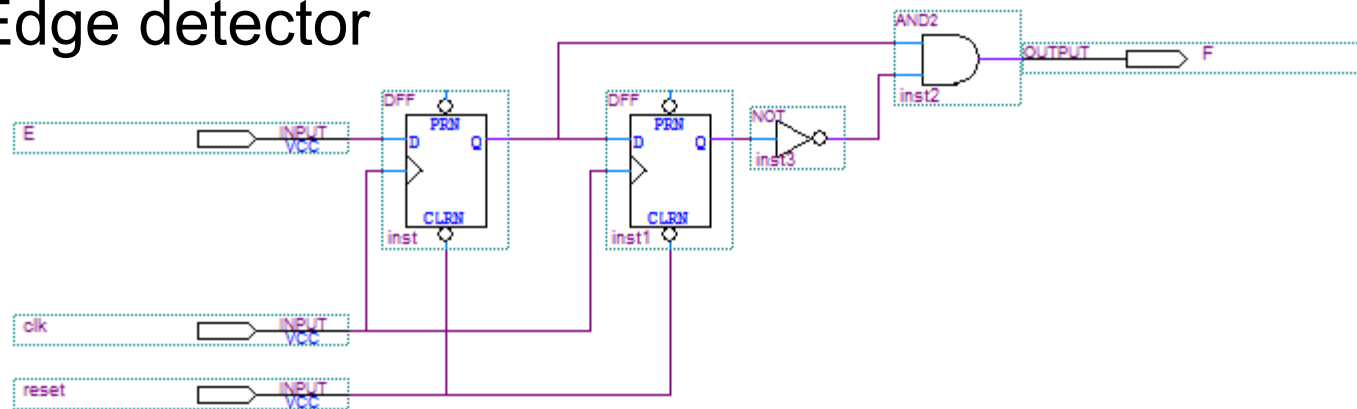

Chronograms

- Counter

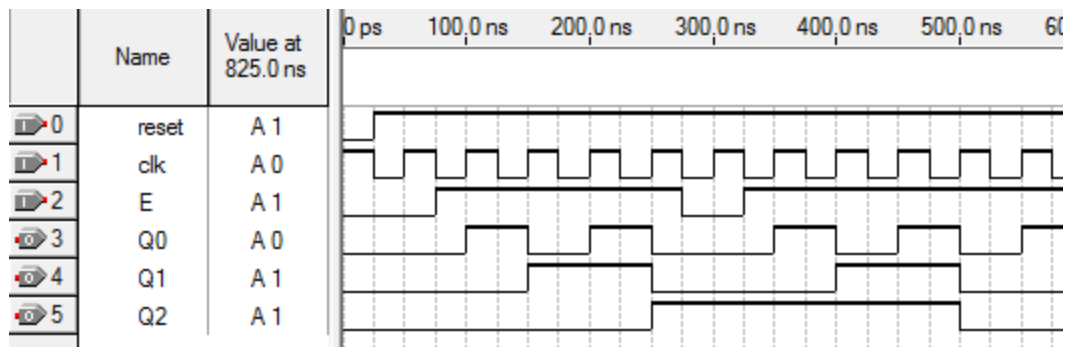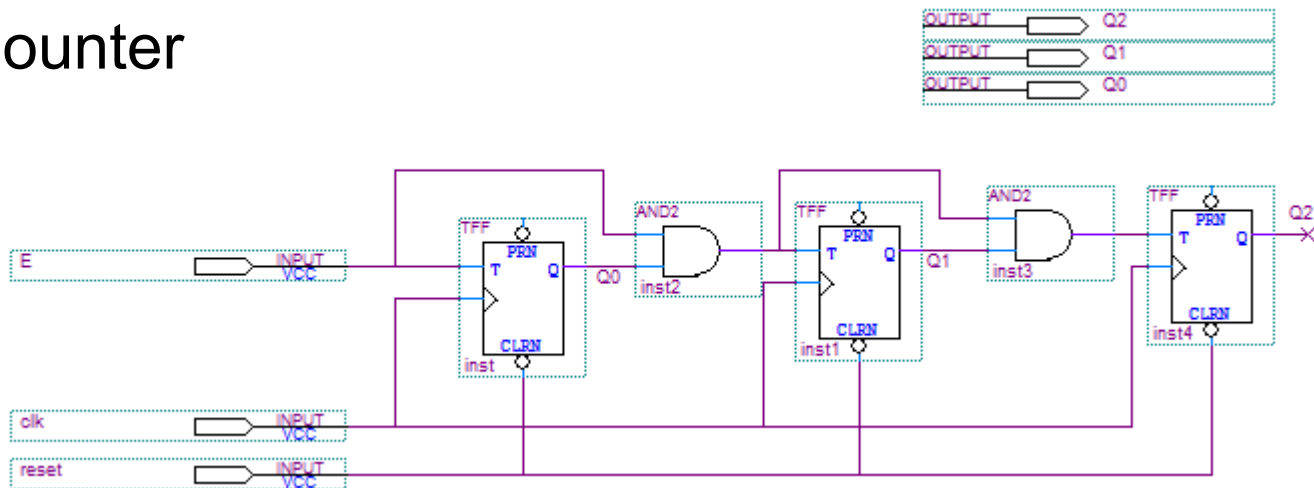

Bibliography

- “Circuitos y Sistemas Digitales”. J. E. García Sánchez, D. G. Tomás, M. Martínez Iniesta. Ed. Tebar-Flores
- “Electrónica Digital”, L. Cuesta, E. Gil, F. Remiro, McGraw-Hill
- “Fundamentos de Sistemas Digitales “, T.L Floyd, Prentice-Hall