

Synchronous Sequential Circuits

© Luis Entrena, Celia López, Mario García,
Enrique San Millán


Universidad Carlos III de Madrid

Outline

- Introduction
- Finite State Machines
 - Moore model
 - Mealy model
- Synchronous Sequential Circuits Analysis
- Synchronous Sequential Circuits Synthesis
- Examples

Introduction

 - General scheme of a synchronous sequential circuit:




- The block “State” is composed by flip-flops, all of them synchronized with the same clock signal

Finite State Machines

- The behaviour of a synchronous circuit can be represented with a Finite State Machine (FSM)
- A finite state machine has the following elements:
 - X = Inputs
 - Y = Outputs
 - Z = States (flip-flop values, they change with each clock edge)
 - δ = State functions (combinational functions of the flip-flop inputs)
 - λ = Output functions (combinational)
- A FSM is defined as a sequence of events in discrete times. The States change in each event (the changed value is defined by δ).

Moore Model

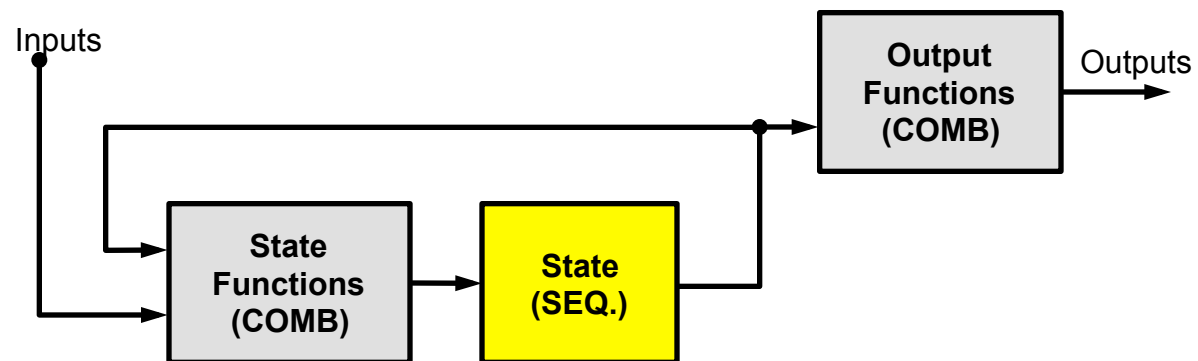- In the Moore model, outputs depend only on the states (not on the inputs)
- Moore finite state machine:
 - $Z = \delta (X, Z)$
 - $Y = \lambda (Z)$
- Structure of a Moore model circuit




Moore Model

- Clock and reset signals do not appear in finite state machines, the association between them and the finite state machine is:
 - In each clock edge there is a transition or state change
 - Reset is used only to establish the initial state
- In Moore machines the outputs change only if there is a state change
 - Outputs are synchronized with the clock signal


Moore Model

 - A FSM can be represented with a State Transition Graph (STG):
 - Each state is represented with a circle
 - Each state transition is represented with an arrow
 - The different input combinations are represented in the arrows
 - In Moore machines, outputs are represented inside each state
- State Transition Graph (Moore):



Mealy Model

 
- In Mealy model the outputs depend both on the inputs and the states (it is the more general case)
- Mealy FSM:
 - $Z = \delta (X, Z)$
 - $Y = \lambda (X, Z)$
- Structure of a Mealy machine associated circuit:



Mealy Model

- **Mealy State Transition Graph:**

 - Each state is represented with a circle
- Each state transition is represented with an arrow
- The different input combinations are represented in the arrows
- En Mealy model, outputs are represented in the arrows (they depend on the state and the inputs)



Mealy Model


- The same as in Moore machines, clock and reset signals are implicit
- In Mealy machines, outputs may change at any moment (a change in the inputs is sufficient):
 - Outputs are **not** synchronized with the clock signal
 - TIP: Although outputs are not synchronized, the circuit is still synchronous (all the flip-flops are synchronized with the same clock signal)

Analysis and Synthesis of Synchronous Sequential Circuits

- **Analysis:** Starting from a circuit, obtain its functionality
 - **Combinational Circuits:**
 - Obtain truth tables of boolean functions of the outputs
 - **Sequential Circuits:**
 - Obtain STG, or state and output functions (δ y λ)
- **Synthesis:** Starting from a functionality, obtain a circuit implementation
 - **Combinational circuits:**
 - Obtain boolean expressions, implement with logic gates, multiplexers, decoders, etc.
 - **Sequential circuits:**
 - Obtain STG and implement state and output functions (δ y λ) with logic gates, multiplexers, dedoders, etc.

Analysis of Synchronous Sequential Circuits

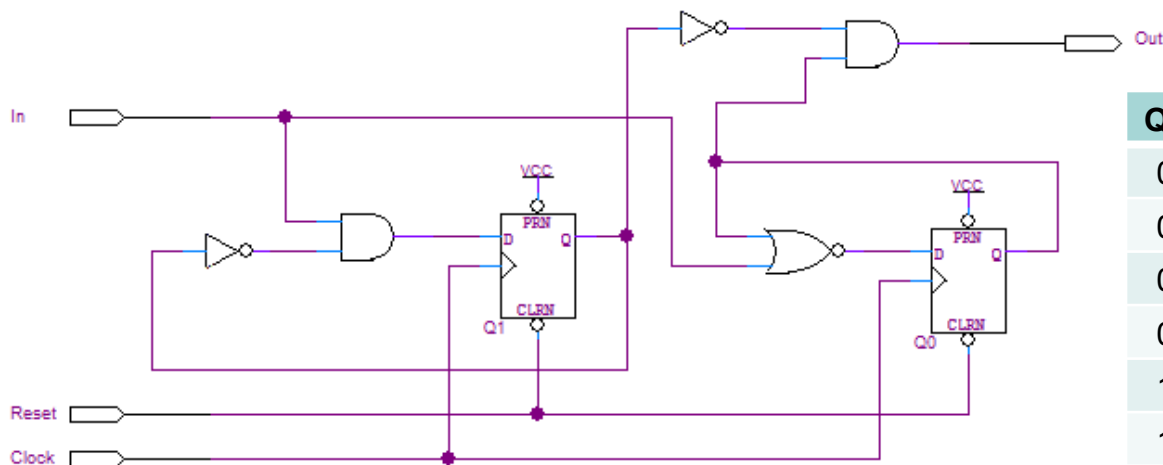- Analysis: Calculate δ y λ , obtain the transitions table, and obtain the STG.
- Example:



Transitions table:

Q1	Q0	In	D1	D0	Q1+	Q0+	Out
0	0	0	0	1	0	1	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	1
0	1	1	1	0	1	0	1
1	0	0	0	1	0	1	0
1	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

$$\delta \Rightarrow \begin{cases} D_0 = \overline{Q_0} + In \\ D_1 = \overline{Q_1} \cdot In \end{cases}$$


$$\lambda \Rightarrow Out = \overline{Q_1} \cdot Q_0$$

Analysis of Synchronous Sequential Circuits


Transitions Table:

Q1	Q0	In	D1	D0	Q1+	Q0+	Out
0	0	0	0	1	0	1	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	1
0	1	1	1	0	1	0	1
1	0	0	0	1	0	1	0
1	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

STG (Mealy):

 

STG (Moore):

 

Synthesis of Synchronous Sequential Circuits

- Starting from the functionality of a sequential circuit, the steps to obtain a circuit implementation are:
 1. Obtain the STG
 2. Encode the states
 3. Obtain the outputs and state transitions tables
 4. Flip-flops excitation table
 5. Obtain the output functions
 6. Obtain the state functions
 7. Implementation
- The difference between Moore y Mealy is in the output funciones

Flip-flop excitation tables

- These tables describe all the possible input combinations that allow to change from state Q to $Q+$

R-S latch

Q	Q+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

J-K flip-flop

Q	Q+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

D flip-flop


Q	Q+	D
0	0	0
0	1	1
1	0	0
1	1	1

T flip-flop

Q	Q+	T
0	0	0
0	1	1
1	0	1
1	1	0

Synthesis of Synchronous Sequential Circuits

 - Problem: Design a synchronous sequential circuit which allows to detect a sequence of three or more 1s in a row through a serial input.
 - The input is read in each clock rising edge.
 - The output is activated if the sequence is detected




- Example of inputs and outputs sequence:
 - X : 0 0 1 1 0 1 1 1 1 0 0 1 1 1
 - Z : 0 0 0 0 0 0 0 1 1 1 0 0 0 0 1

Synthesis of Synchronous Sequential Circuits

- **Example 1: Mealy with D flip-flops:**

1. State Transition Graph:

 


2. State Encoding:

State	Q1	Q0
S0	0	0
S1	0	1
S2	1	1
	1	0

← Unreachable state

Synthesis of Synchronous Sequential Circuits

 - Mealy with D flip-flops:
 3. Transitions table and outputs table (merged together):



In	Q1	Q0	Q1+	Q0+	Out
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	X	X	X
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	X	X	X
1	1	1	1	1	1

Synthesis of Synchronous Sequential Circuits

- Mealy with D flip-flops:

4. Excitation table (D flip-flops):

In	Q1	Q0	Q1+	Q0+	Out	D1	D0
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	X	X	X	X	X
0	1	1	0	0	0	0	0
1	0	0	0	1	0	0	1
1	0	1	1	1	0	1	1
1	1	0	X	X	X	X	X
1	1	1	1	1	1	1	1

5. Output function:

In	Q1 Q0			
	00	01	11	10
0				X
1			1	X

$$Out = Q_1 In$$

6. State functions

In	Q1 Q0			
	00	01	11	10
0				X
1		1	1	X

$$D_1 = Q_0 In$$


In	Q1 Q0			
	00	01	11	10
0				X
1	1	1	1	X

$$D_0 = In$$

Synthesis of Synchronous Sequential Circuits

- Mealy with D flip-flops:

7. Implementation

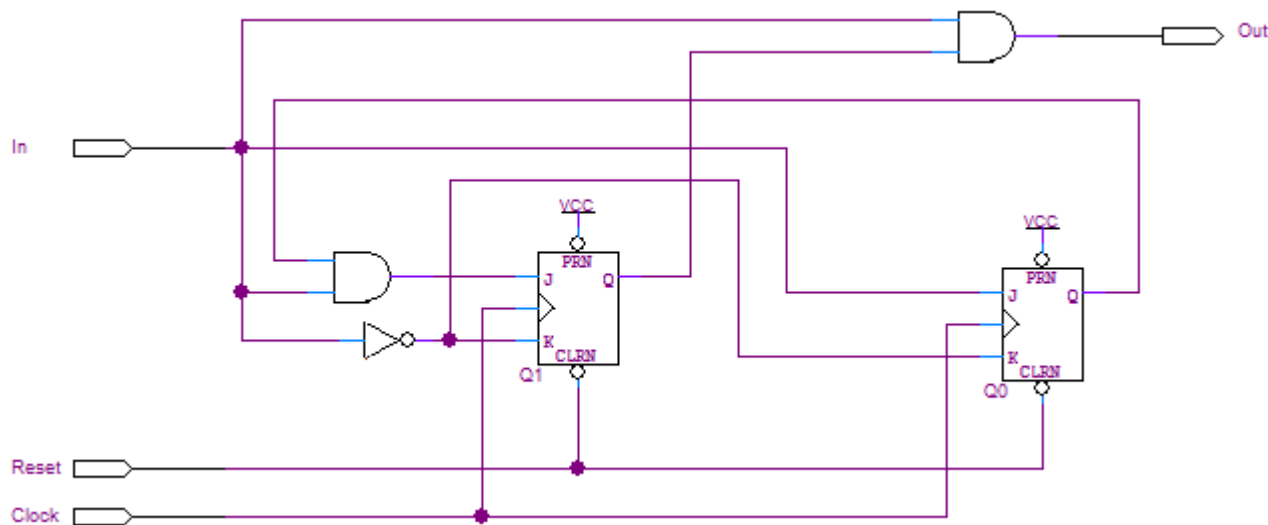

$$Out = Q_1 In$$

$$D_1 = Q_0 In$$

$$D_0 = In$$

Synthesis of Synchronous Sequential Circuits

- **Example 2. Mealy with J-K flip-flops:**





4. Excitation table (J-K flip-flops):

In	Q1	Q0	Q1+	Q0+	Out	J1	K1	J0	K0
0	0	0	0	0	0	0	X	0	X
0	0	1	0	0	0	0	X	X	1
0	1	0	X	X	X	X	X	X	X
0	1	1	0	0	0	X	1	X	1
1	0	0	0	1	0	0	X	1	X
1	0	1	1	1	0	1	X	X	0
1	1	0	X	X	X	X	X	X	X
1	1	1	1	1	1	X	0	X	0

5. Output function:

$$Out = Q_1 In$$


6. State functions:

    

Synthesis of Synchronous Sequential Circuits

- Mealy with J-K flip-flops:

7. Implementation

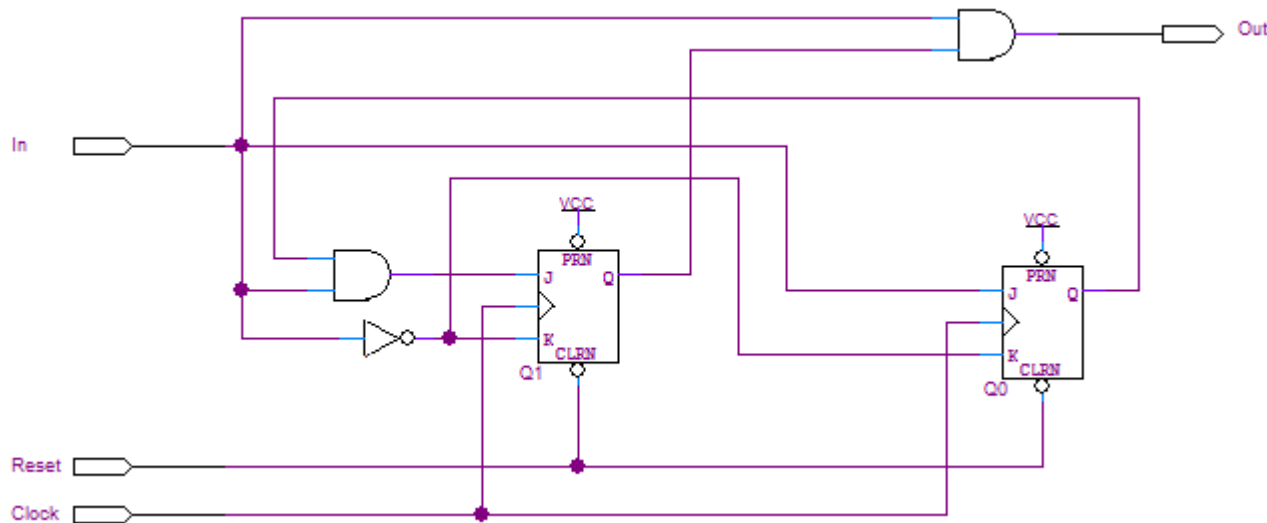

$$\begin{aligned}
 Out &= Q_1 In \\
 J_0 &= In \\
 K_0 &= \overline{In} \\
 J_1 &= Q_0 In \\
 K_1 &= \overline{In}
 \end{aligned}$$

Synthesis of Synchronous Sequential Circuits

- **Example 3.** Mealy with T flip-flops :

4. Excitation table (T flip-flops):

In	Q1	Q0	Q1+	Q0+	Out	T1	T0
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1
0	1	0	X	X	X	X	X
0	1	1	0	0	0	1	1
1	0	0	0	1	0	0	1
1	0	1	1	1	0	1	0
1	1	0	X	X	X	X	X
1	1	1	1	1	1	0	0

5. Output function:

$$Out = Q_1 In$$

6. State functions

		Q1 Q0			
In		00	01	11	10
0				1	X
1			1		X

$$T_1 = Q_1 \bar{In} + \bar{Q}_1 Q_0 In$$


		Q1 Q0			
In		00	01	11	10
0			1	1	X
1		1			X

$$T_0 = \bar{In} Q_0 + In \bar{Q}_0 = In \oplus Q_0$$

Synthesis of Synchronous Sequential Circuits

- Mealy with T flip-flops:

7. Implementation

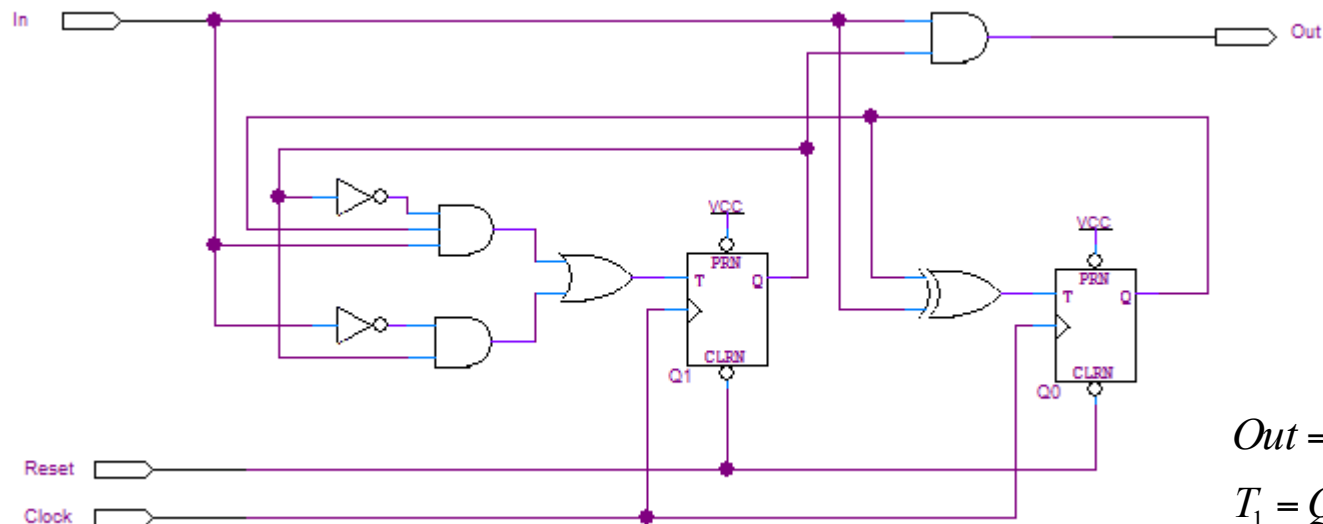

$$Out = Q_1 In$$


$$T_1 = Q_1 \bar{In} + \bar{Q}_1 Q_0 In$$

$$T_0 = \bar{In} Q_0 + In \bar{Q}_0 = In \oplus Q_0$$

Synthesis of Synchronous Sequential Circuits

- **Example 4:** Mealy, with a different state encoding:

1. State Transition Graph:

 

2. State Encoding:

State	Q1	Q0
S0	0	0
S1	0	1
S2	1	0
	1	1





S2 is encoded with a different value

Synthesis of Synchronous Sequential Circuits

- Mealy with D flip-flops (different encoding):

3. Transitions table and outputs table (merged together):

4. :

  

In	Q1	Q0	Q1+	Q0+	Out
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	X	X	X
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	X	X	X

Synthesis of Synchronous Sequential Circuits

- Mealy with D flip-flops :

4. Excitation table (D flip-flops):

In	Q1	Q0	Q1+	Q0+	Out	D1	D0
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	0	0	0	0	0
0	1	1	X	X	X	X	X
1	0	0	0	1	0	0	1
1	0	1	1	0	0	1	0
1	1	0	1	0	1	1	0
1	1	1	X	X	X	X	X

5. Output function:

In	Q1 Q0			
	00	01	11	10
0			X	
1			X	1

$$Out = Q_1 In$$

6. State functions

In	Q1 Q0			
	00	01	11	10
0			X	
1		1	X	1

$$D_1 = Q_0 In + Q_1 In = In(Q_0 + Q_1)$$


In	Q1 Q0			
	00	01	11	10
0			X	
1	1		X	

$$D_0 = \overline{Q_1} \overline{Q_0} In$$

Synthesis of Synchronous Sequential Circuits

- Mealy with D flip-flops (different encoding):

7. Implementación

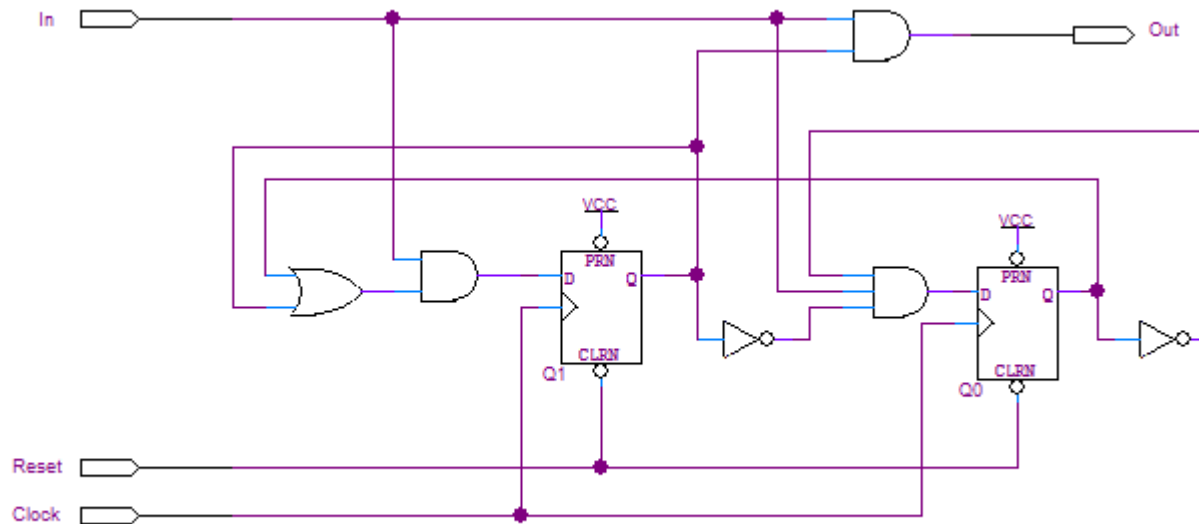


With this different encoding, more logic gates are required

$$\begin{aligned}
 Out &= Q_1 In \\
 D_1 &= In(Q_0 + Q_1) \\
 D_0 &= \overline{Q_1} \overline{Q_0} In
 \end{aligned}$$

Synthesis of Synchronous Sequential Circuits

- **Example 5:** Moore with D flip-flops:

1. State transition graph:


 


2. State encoding:

State	Q1	Q0
S0	0	0
S1	0	1
S2	1	1
S3	1	0

Synthesis of Synchronous Sequential Circuits

  - Moore with D flip-flops:
 3. Transitions table and outputs table:



In	Q1	Q0	Q1+	Q0+
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0


Q1	Q0	Out
0	0	0
0	1	0
1	0	0
1	1	1

Synthesis of Synchronous Sequential Circuits

- Moore with D flip-flops:


4. Excitation table (D flip-flops):

In	Q1	Q0	Q1+	Q0+	D1	D0
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	1	1	1	1
1	1	0	1	0	1	0
1	1	1	1	0	1	0

 

5. Output function:

Q1	Q0	Out
0	0	0
0	1	0
1	0	0
1	1	1

 

$$Out = Q_1 Q_0$$

6. State functions

Q1 Q0

In	00	01	11	10
0				
1		1	1	1

$$D_1 = Q_0 In + Q_1 In = (Q_0 + Q_1) In$$

Q1 Q0


In	00	01	11	10
0				
1	1	1		

$$D_0 = \overline{Q_1} In$$

Synthesis of Synchronous Sequential Circuits

- Moore with D flip-flops:

7. Implementation

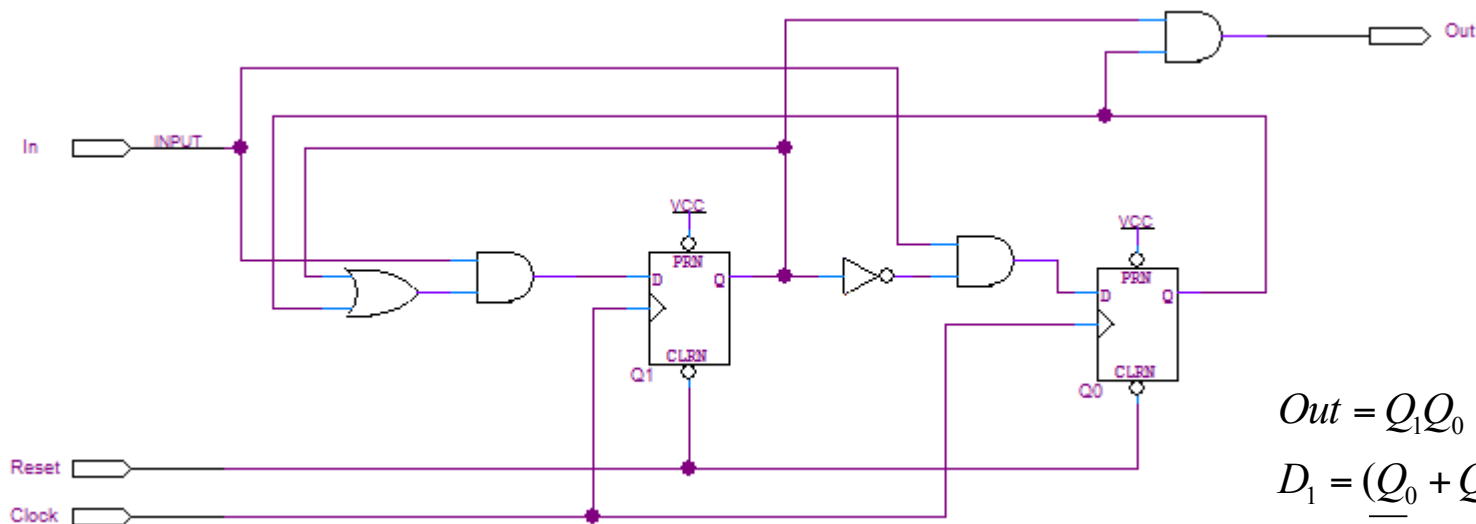

$$Out = Q_1Q_0$$

$$D_1 = (Q_0 + Q_1)In$$

$$D_0 = \overline{Q_1}In$$