





Combinational Circuits

© Luis Entrena, Celia López,
Mario García, Enrique San Millán
Universidad Carlos III de Madrid

Combinational and sequential circuits

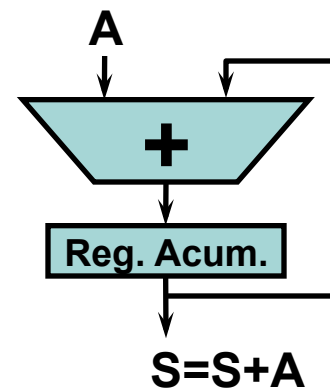 - Combinational:
 - Outputs affected only by inputs
 - Example: adder
- Sequential:
- Outputs affected by inputs and state
 - Example: adder-accumulator




Outline

- Encoders
 - Decoders
 - Multiplexers
 - Demultiplexers
 - Comparators
- Functionality
 - Implementation
 - Asociation
 - Function builders
 - Utilities

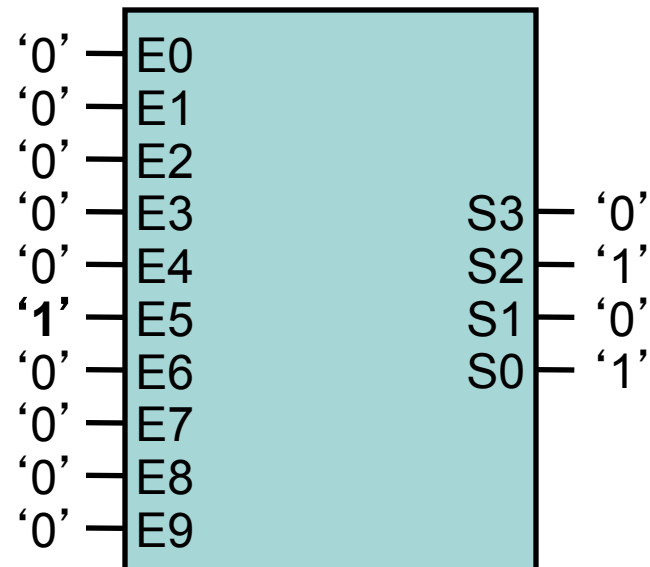1. Encoders

- Definition:
 - A combinational circuit allows to translate and active level of an input into an encoded value
- Example: keypad
 - Inputs: digits 0-9
 - Outputs: 4-bit binary code



E5 active => S="0101" (=5)

No priority encoders

- Restrictions
 - Only one input can be active
 - Several active inputs may lead to erroneous output

- Logic functions

- $S_3 = E_8 + E_9$
- $S_2 = E_4 + E_5 + E_6 + E_7$
- $S_1 = E_2 + E_3 + E_6 + E_7$
- $S_0 = E_1 + E_3 + E_5 + E_7 + E_9$

- Problems:


- E1 and E4 active lead to 5 code
- No active inputs lead to 0 code, same as E₀ active

Active input	S ₃ S ₂ S ₁ S ₀
E ₀	0000
E ₁	0001
E ₂	0010
E ₃	0011
E ₄	0100
E ₅	0101
E ₆	0110
E ₇	0111
E ₈	1000
E ₉	1001

 Example:

no priority 4:2 encoder

- M:N \Rightarrow ‘M’ inputs, ‘N’ outputs
- EO: “Enable Output”
 - Used to distinguish the no active inputs and E0 active input cases.
 - Used to chain several encoders
- Not considered cases
 - Any multiple activation
 - Don’t care output values



E ₃	E ₂	E ₁	E ₀	S ₁	S ₀	EO
0	0	0	1	0	0	0
0	0	1	0	0	1	0
0	1	0	0	1	0	0
1	0	0	0	1	1	0
0	0	0	0	0	0	1
Others				X	X	X

Example: no priority 4:2 encoder

E ₃	E ₂	E ₁	E ₀	S ₁	S ₀	EO
0	0	0	1	0	0	0
0	0	1	0	0	1	0
0	1	0	0	1	0	0
1	0	0	0	1	1	0
0	0	0	0	0	0	1
Others				X	X	X

E ₁ E ₀ E ₃ E ₂	00	01	11	10
00	0	0	X	0
01	1	X	X	X
11	X	X	X	X
10	1	X	X	X

$$S_1 = E_2 + E_3$$

E ₁ E ₀ E ₃ E ₂	00	01	11	10
00	1	0	X	0
01	0	X	X	X
11	X	X	X	X
10	0	X	X	X

$$EO = \overline{E_3} \overline{E_2} \overline{E_1} \overline{E_0}$$

E ₁ E ₀ E ₃ E ₂	00	01	11	10
00	0	0	X	1
01	0	X	X	X
11	X	X	X	X
10	1	X	X	X

$$S_0 = E_1 + E_3$$


Priority Encoders

- Characteristics
 - Prioritize multiple input activation
 - Priority:
 - To the most significant bit (MSB): priority is given to the MSB
E1 and E5 active, result is 5
 - To the least significant bit (LSB): priority is given to the LSB
E1 and E5 active, result is 1

Example:

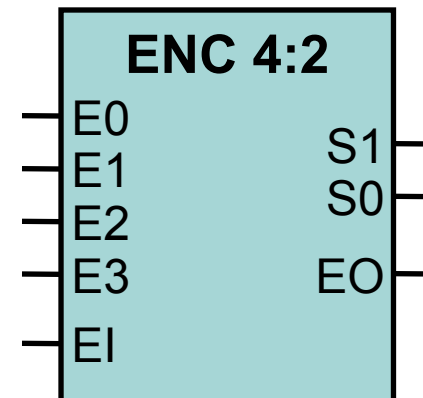4:2 MSB priority encoder

- M:N \Rightarrow ‘M’ inputs, ‘N’ outputs
- EO: “Enable Output”
- EI ó E: “Enable Input” o “Enable”
 - Enables the circuit:
 - ‘0’ (disabled): outputs are tied to ‘0’
 - ‘1’ (enabled): normal operation
 - EI and OE are used together to chain encoders.



EI	E3	E2	E1	E0	S1	S0	EO
0	X	X	X	X	0	0	0
1	0	0	0	0	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	X	0	1	0
1	0	1	X	X	1	0	0
1	1	X	X	X	1	1	0

Example: 4:2 MSB priority encoder

EI	E3	E2	E1	E0	S1	S0	EO
0	X	X	X	X	0	0	0
1	0	0	0	0	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	X	0	1	0
1	0	1	X	X	1	0	0
1	1	X	X	X	1	1	0

- Reminder

- 'X' output \Rightarrow 'X' in table
- 'X' input \Rightarrow several cases

E1E0	00	01	11	10	
E3E2	00	0	0	0	0
01	1	1	1	1	
11	1	1	1	1	
10	1	1	1	1	

$$S_1 = EI(E_2 + E_3)$$

E1E0	00	01	11	10	
E3E2	00	0	0	1	1
01	0	0	0	0	
11	1	1	1	1	
10	1	1	1	1	


$$S_0 = EI(\overline{E_1 E_2} + E_3)$$

E1E0	00	01	11	10	
E3E2	00	1	0	0	0
01	0	0	0	0	
11	0	0	0	0	
10	0	0	0	0	

$$EO = EI(\overline{E_3 E_2 E_1 E_0})$$

Encoder chains: ENC 8:3 using two ENC 4:2

 - EI and EO are chained
- When upper ENC is active (EI= '1') and it has no active inputs, it enables lower ENC (EO= '1').




Encoder utility

- Elevator sensors
 - Encode each sensor to the floor number
 - No priority needed. The elevator can activate only one sensor.
- Keypad
 - Encodes the value of the pressed key
 - Priority is required. Several keys may be pressed at the same time.

 2. Decoders


- Definition:
 - Converts an encoded value, activating the output that corresponds to the converted value
 - Function opposite to encoders



E	E ₁	E ₀	S ₃	S ₂	S ₁	S ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Decoders

 - Logic functions:
 - Each output is a minterm



E ₁	E ₀	S ₃	S ₂	S ₁	S ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$S_0 = \overline{E_1} \overline{E_0}$$


$$S_1 = \overline{E_1} E_0$$

$$S_2 = E_1 \overline{E_0}$$

$$S_3 = E_1 E_0$$

Decoders

 - Low-level output decoders:
 - Each output is a maxterm



E1	E0	S3	S2	S1	S0
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

$$S_0 = E_1 + E_0$$


$$S_1 = E_1 + \overline{E_0}$$

$$S_2 = \overline{E_1} + E_0$$

$$S_3 = \overline{E_1} + \overline{E_0}$$


Decoder association

 - DEC 3:8 with two DEC 2:4
 - Just one decoder is active, depending on E2 value
 - The inverter behaves as a DEC 1:2
 - Doesn't have an Enable input




Decoder association

 - DEC 4:16 with DEC 2:4
 - Just one decoder (on the right) is active, depending on E2 value
 - Left decoder behaves like a DEC1:2
 - There is a Global Enable. If E= '0' , no decoders are active and all outputs are null




Decoder association

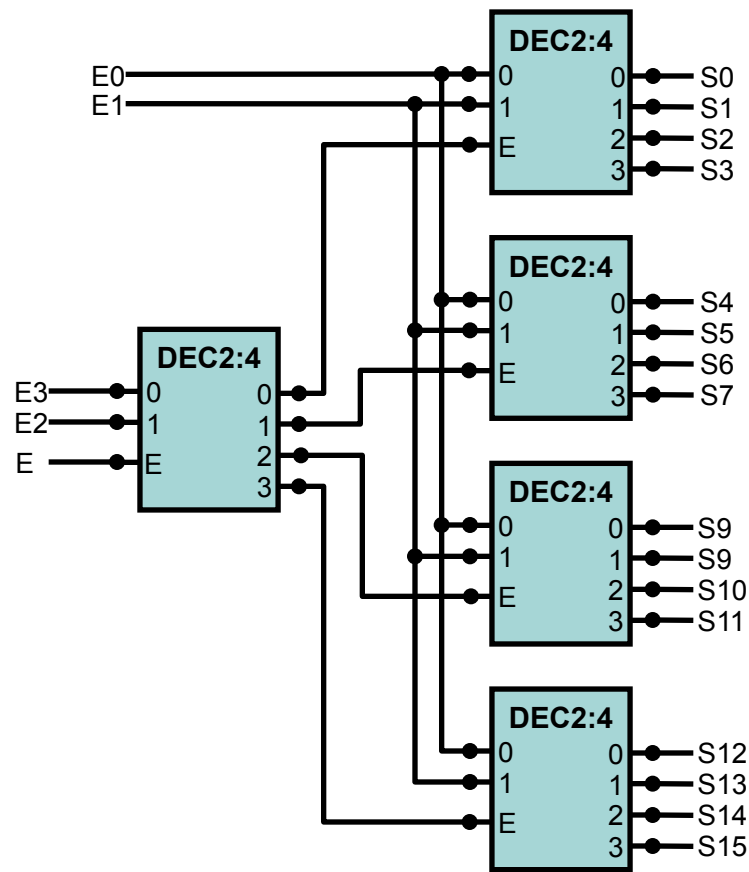- DEC4:16 with DEC2:4
 - Just one decoder (on the right) is active, depending on E2 and E3 values



Logic function implementation using decoders

 - Logic functions can be implemented using a decoder and an OR gate
- DEC outputs are minterms. Outputs with '1' value in truth table are Ored
- Dual case is built with a low-level output DEC and an AND gate



$$S_0 = \bar{a}\bar{b}$$


$$S_1 = \bar{a}b$$

$$S_2 = a\bar{b}$$

$$S_3 = ab$$


m	a	b	f
0	0	0	0
1	0	1	1
2	1	0	0
3	1	1	1

$$f = \bar{a}b + ab = S_1 + S_3$$

 

BCD-decimal decoder

 
- Decodes a BCD encoded decimal digit.
10 outputs (0-9)
- Behaviour is undefined if input is not decimal




BCD-7segment decoder

- Decodes a BCD encoded decimal digit to the LEDs of a 7-segment display

7-seg display

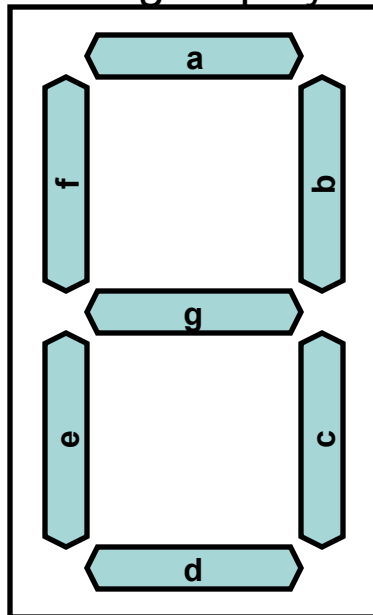

E3	E2	E1	E0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
Others				X	X	X	X	X	X	X


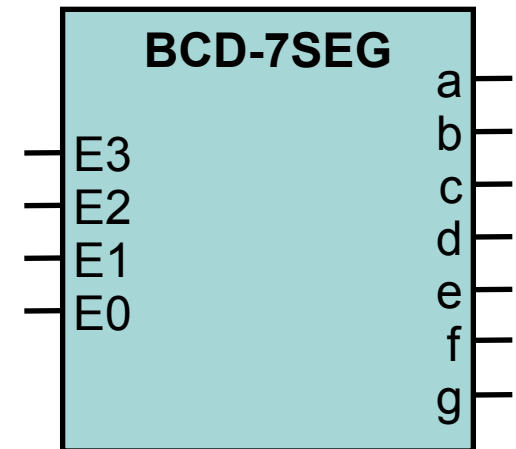


Utility of decoders

- Microprocessors:
 - Instruction decoder
 - I/O port address, memory address.

  
3. Multiplexers

- Definition:
 - Combinational circuit that selects one input according to a control signal and copies its value to the output
 - Named by the number of data inputs: MUX2, MUX4, ...
 - $N = \text{data inputs}$, $n = \text{control inputs} \Rightarrow 2^n = N$



Multiplexers


- Logic function

 

C1	C0	S
0	0	E0
0	1	E1
1	0	E2
1	1	E3


$$S = \overline{C_1} \overline{C_0} E_0 + \overline{C_1} C_0 E_1 + C_1 \overline{C_0} E_2 + C_1 C_0 E_3$$

- Implementation with gates

 

Multiplexers


- Logic function

 

C1	C0	S
0	0	E0
0	1	E1
1	0	E2
1	1	E3


$$S = \overline{C_1} \overline{C_0} E_0 + \overline{C_1} C_0 E_1 + C_1 \overline{C_0} E_2 + C_1 C_0 E_3$$

- Implementation with a decoder

 

Multiplexer association


- MUX8 with MUX4 and MUX2

 

- Right MUX2 selects between upper and lower MUX4 depending on the most significant control bit (C_2)
- C and E bits must be assigned according to their weight

Multiplexer association

- MUX8 with MUX4

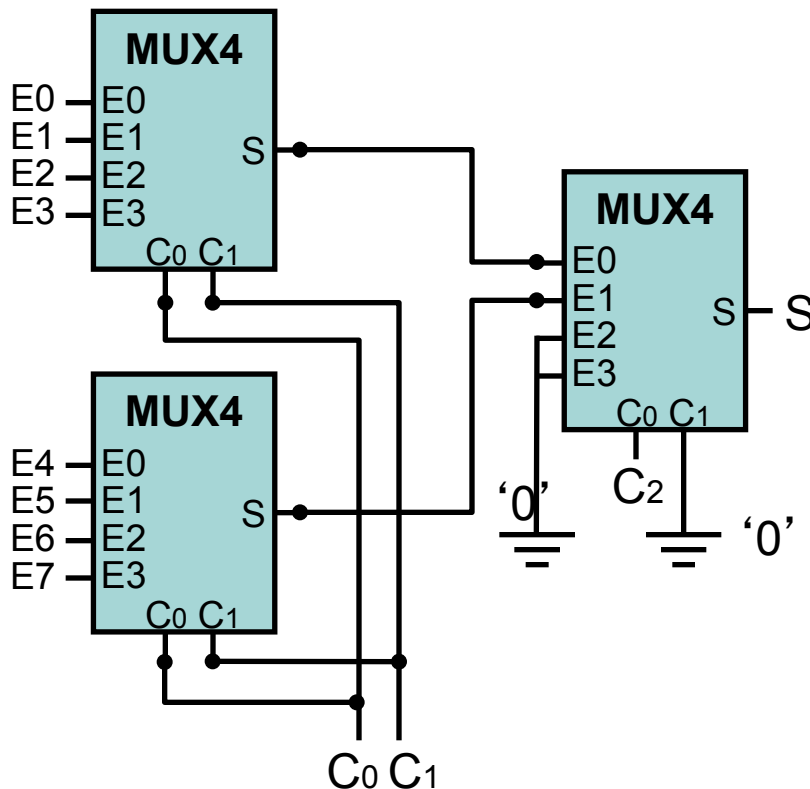


- Right MUX4 behaves as a MUX2
- Remember: circuit inputs MUST have a value, while outputs may be left unconnected

Logic function implementation using multiplexers

- Using a MUX with as many control inputs as function variables
 - Function variables are connected to MUX control inputs, weigh sorted
 - Values in the truth table are assigned to MUX data inputs


a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Logic function implementation using multiplexers



- Using a MUX with less control inputs than function variables
 - Group truth table by least significant variables
 - Most significant variables are connected to MUX control inputs, weight sorted
 - Values in the truth table are assigned to MUX data inputs

a	b	c	f	f(c)
0	0	0	0	0
0	0	1	0	
0	1	0	1	/C
0	1	1	0	
1	0	0	0	C
1	0	1	1	
1	1	0	1	1
1	1	1	1	

 

 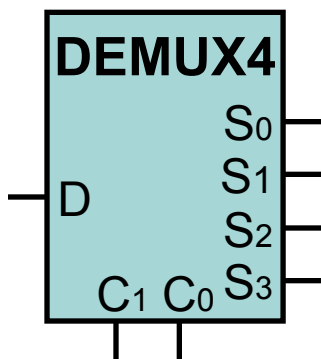4. Demultiplexers


- Definition: combinational circuit that copies the input to one of the outputs, depending on the values of the control signals
- Opposite multiplexers behaviour
- Equivalent to decoders, if DEMUX control (C_i) are DEC data (E_i) and DEMUX data (D) is DEC enable (E)



D	C ₁	C ₀	S ₃	S ₂	S ₁	S ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


Utility of multiplexers and demultiplexers

- Multiplexed serial transmission

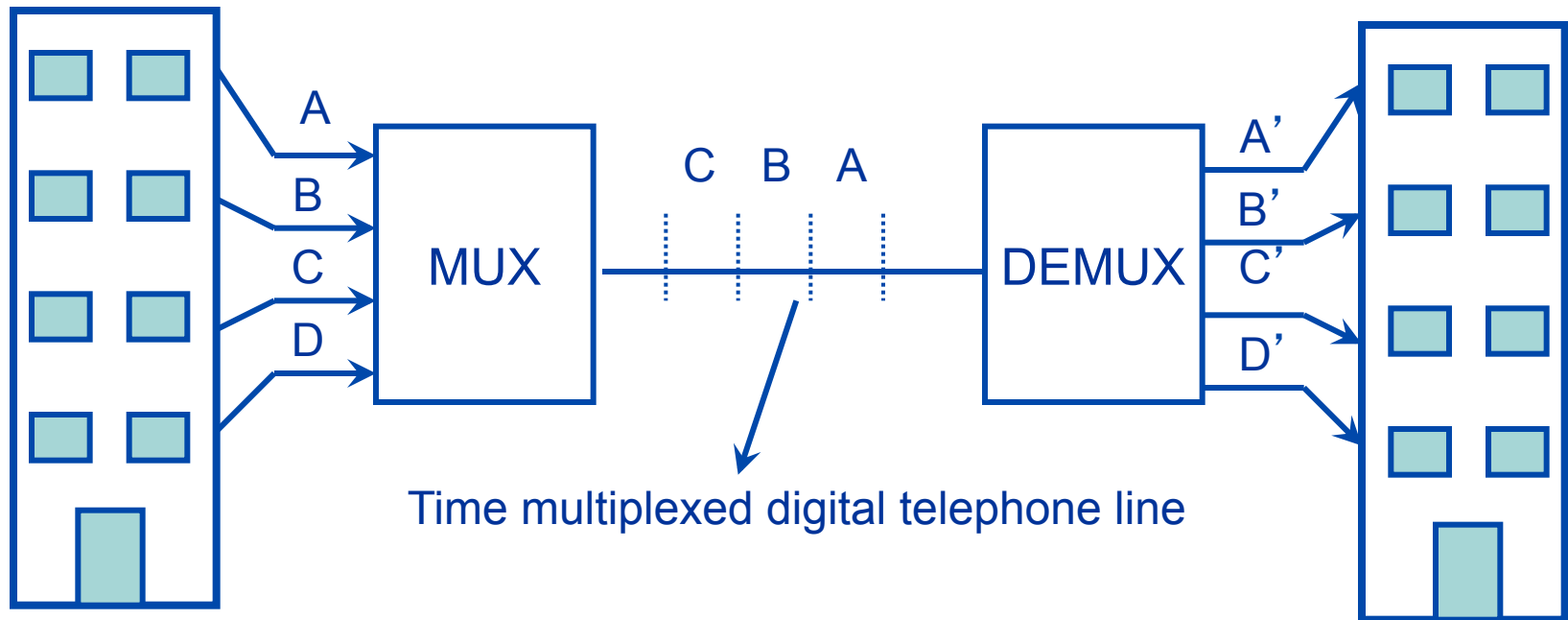

 5. Comparators

- Definition: combinational circuit that determines if a number is greater than, equal to or lower than other
- N-bit data



1-bit comparator

a	b	a=b	a>b	a<b
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

$$f_{a=b} = \overline{a \oplus b}$$

$$f_{a>b} = a\bar{b}$$

$$f_{a<b} = \bar{a}b$$

Comparators

- 3-bit comparator

$$f_{a=b} = \overline{(a_2 \oplus b_2)} \cdot \overline{(a_1 \oplus b_1)} \cdot \overline{(a_0 \oplus b_0)}$$

a2=b2 a1=b1 a0=b0

$$f_{a>b} = a_2 \overline{b_2} +$$

a2>b2

$$+ \overline{(a_2 \oplus b_2)} \cdot a_1 \overline{b_1} +$$

a2=b2 and a1>b1

$$+ \overline{(a_2 \oplus b_2)} \cdot \overline{(a_1 \oplus b_1)} \cdot a_0 \overline{b_0}$$

a2=b2, a1=b1 and a0>b0

$$f_{a<b} = \overline{a_2} b_2 +$$


a2<b2

$$+ \overline{(a_2 \oplus b_2)} \cdot \overline{a_1} b_1 +$$

a2=b2 and a1<b1

$$+ \overline{(a_2 \oplus b_2)} \cdot \overline{(a_1 \oplus b_1)} \cdot \overline{a_0} b_0$$

a2=b2, a1=b1 and a0<b0

 

- It can be generalized
- High gate use (XOR)

Bibliografía

- “Circuitos y Sistemas Digitales”. J. E. García Sánchez, D. G. Tomás, M. Martínez Iniesta. Ed. Tebar-Flores
- “Electrónica Digital”, L. Cuesta, E. Gil, F. Remiro, McGraw-Hill
- “Electric circuits fundamentals”, T.L Floyd, Prentice-Hall