



TEST OF INTEGRATED CIRCUITS

Authors:

Enrique San Millán

Mario García

Celia López

Luis Entrena

Almudena Lindoso

Marta Portela

Design for test

- Goal: increase the controllability and the observability of the circuit internal nodes.
- In general
 - The number of inputs and outputs increases
 - Worse performance (more area and slower)
- Applications:
 - Sequential logic vs. Combinational logic
 - Control logic vs. Data path
 - Asynchronous designs vs. Synchronous designs

Design for test

■ DFT techniques

■ Ad-hoc

- Not general solutions
- Lower cost
- More common in PCB designs, but also used in VLSI designs


■ Structured

- They provide a design methodology for the testability problem
- ATPG tasks and fault simulation with acceptable costs (sequential circuits)


Design for test: soluciones ad-hoc

■ Nodes with low testability (test points)

■ Increasing controllability

 

■ Increasing observability

 


- They should be pins with low activity
- Never critical pins: clock, reset, chipselect, etc.

Design for test: ad-hoc solutions

Sequential circuits

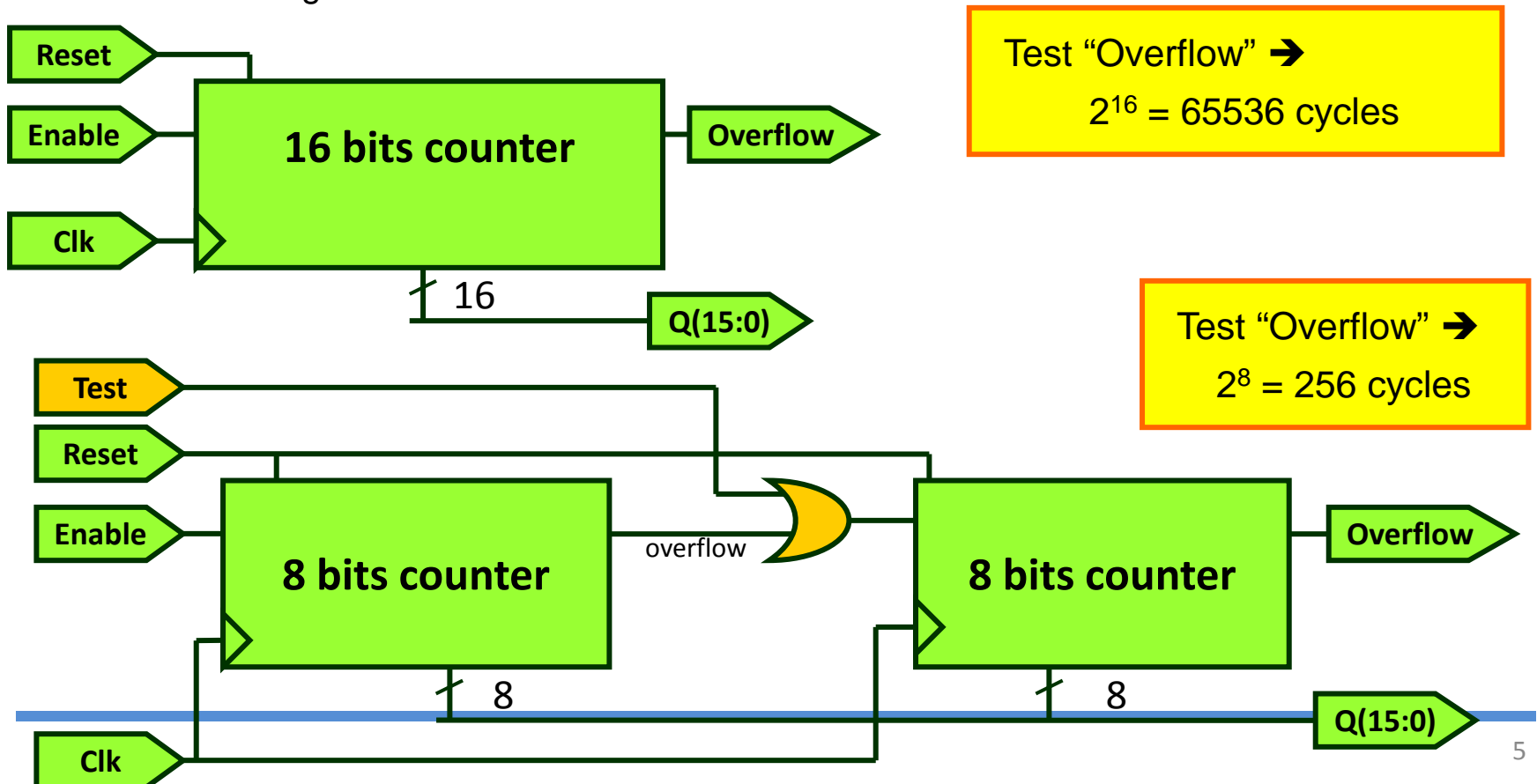- Initialization + synchronous logic + avoid redundant logic
- Partitioning counters




Design for test: structured techniques


- Valid for synchronous circuits with only one clock edge
- Translate the problem of testing a sequential circuit into a problem of testing a combinationa circuit
- Affect the performance (area and maximum operating frequency)
- Two operation modes: TEST and NORMAL
- There are CAD tools that automatically insert those test structures, and automatically generate the test vectors
- The most common are:
 - Scan-Path
 - Boundary Scan
 - Built-In Self-Test

Design for test: Scan-Path

Flip-flops

 

Scan-path

 


Normal mode

Test mode



TDI

TDO


Design for test: Scan-Path

 


s-a-0 on H	
A	→ 1 - 0
B	→ 1 - 0
C	→ 1 - 0
D	→ 0 - 1
E	→ 1 - 0

 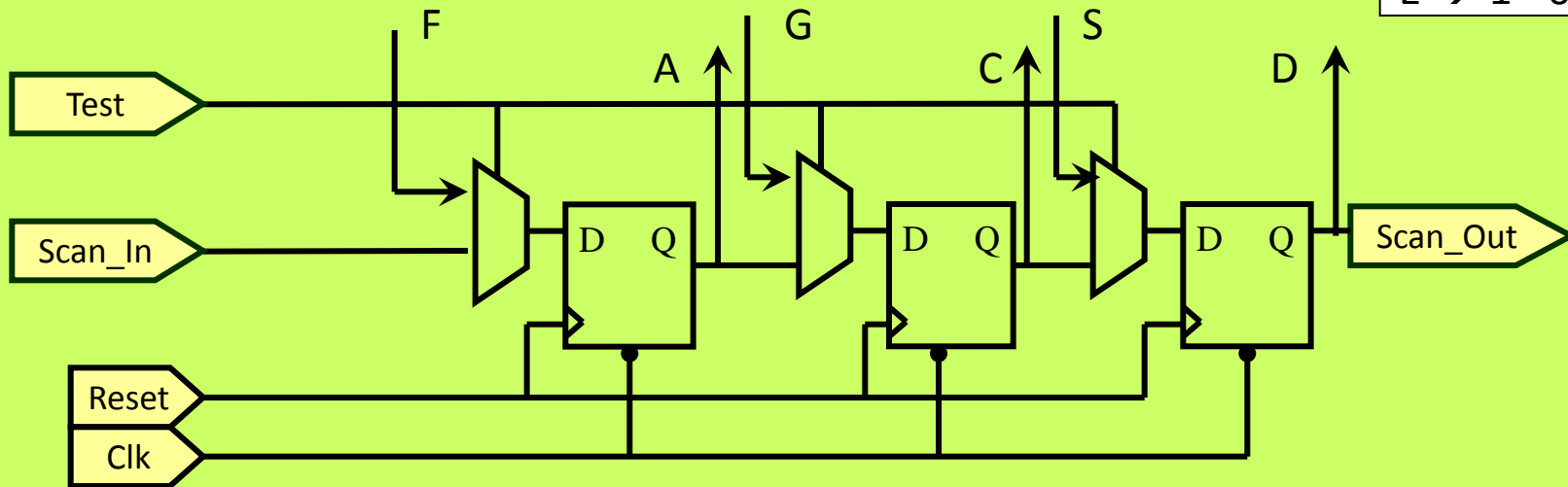

Design for test: Scan-Path

 

s-a-0 on H	
A	→ 1 - 0
B	→ 1 - 0
C	→ 1 - 0
D	→ 0 - 1
E	→ 1 - 0

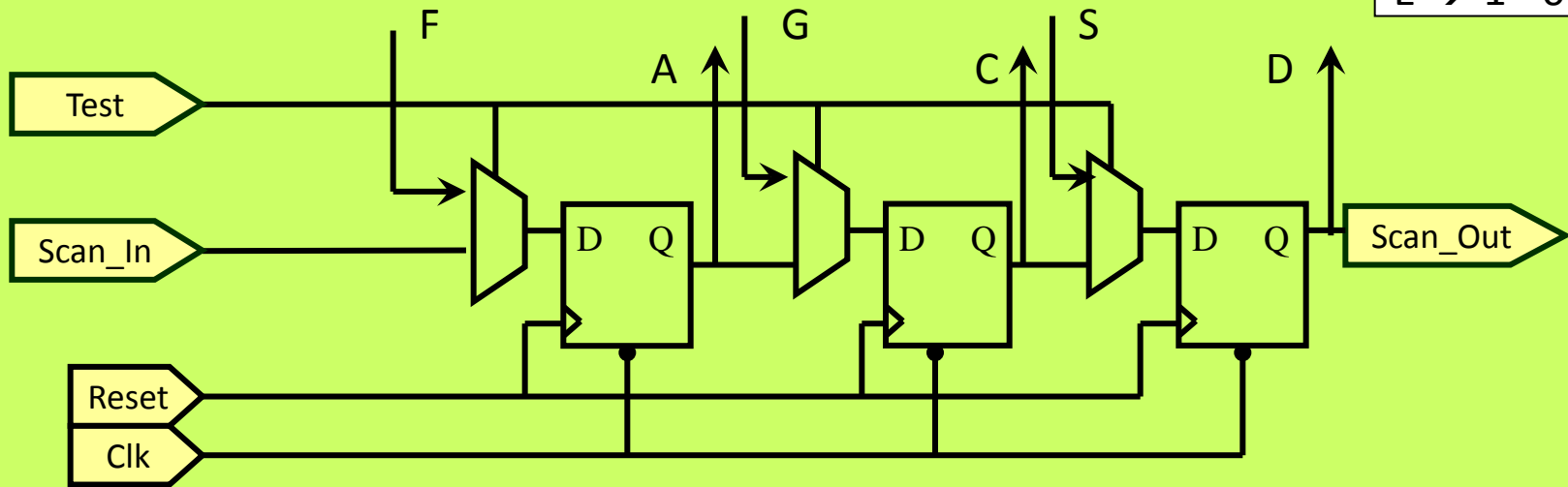

Number of cycles without Scan Path?