

UNIVERSIDAD CARLOS III DE MADRID



MODULE 1 EXAM

Integrated Circuits and Microelectronics

Authors: Mario García, Marta Portela, Enrique San Millán,
Almudena Lindoso, Celia López, Luis Entrena

INTEGRATED CIRCUITS AND MICROELECTRONICS EXAM

Question 1 (30 min, 3 pts)

Given the following VHDL description:

```
1  entity question is
2    port (Clk:          in std_logic;
3          Reset:       in std_logic;
4          Enable:      in std_logic;
5          Up_down:     in std_logic;
6          Count:       out std_logic_vector(3 downto 0));
7  end question;
8
9  architecture a of question is
10   signal sCount: std_logic_vector(3 downto 0);
11   signal a,b: std_logic;
12  begin
13   process(...)
14   begin
15     if Reset = '1' then
16       sCount <= "0000";
17       a <= '0';
18     elsif clk'event and clk = '1' then
19       if Enable = '1' then
20         if Up_down = '1' then
21           if sCount = "1001" then
22             sCount <= "0000";
23             a <='1';
24           else
25             sCount <= sCount + '1';
26             a <='0';
27           end if;
28         else
29           if sCount = "0000" then
30             sCount = "1001";
31             a <='1';
32           else
33             sCount = sCount - '1';
34             a <='0';
35           end if;
36         end if;
37       end if;
38     end process;
39
40     Count <= sCount;
41
42   process(...)
43   begin
44     if sCount = "0111" then
45       b <='1';
46     else
47       b <='0';
48     end if;
49   end process;
50
51 end a;
```

- Fill in the sensitivity lists of the processes with the correct signals.
- Draw the circuit that is going to be synthesized from this VHDL code.
- Modify the code to obtain the same circuit with generic size, with the following specifications:
 - Count is a n-bit signal
 - The last possible count value of the counter is "100...0001" (starts and ends with '1', all zeros in the middle)
 - b is activated when the count value is "0000....0011" (ends with two ones and the rest are zeros)

Note: For c) it is not necessary to rewrite all the code. Write only those lines with some changes, indicating the line number.

Problem 1 (1h 15 min, 7 pts)

We want to design an infrared receiver according to the RC5 protocol from Philips. RC5 code consists in sending 14-bits words, see Figure 1. The first two bits are start bits and they must be '1'. Next bit corresponds to a control bit and it is inverted each time that a new code is transmitted. This allows the receiver to distinguish if a button has been pressed in a remote control once or twice. The following 5 bits in the frame are used to identify the destination system (TV, video, etc.). The last 6 bits identify the command to be run.

 


Figure 1. Format for an RC5 frame

Bits are transmitted by using a Manchester code, that is, every logical value is indicated with an edge, as Figure 2 shows.



Figure 2. Manchester code

Every bit lasts 1.778 ms and therefore a frame lasts 24.892 ms. The system clock works at 50MHz. Design a circuit capable of decoding a RC5 frame. The circuit interface is described in the following paragraph:

- Inputs:
 - Clk: clock signal
 - Reset: asynchronous initialization signal, active at high level.
 - Sin: 1bit signal generated by an infrared detector from the signal transmitted by the remote control.
- Output:
 - TV: active at high level only when the received command is addressed to a system with addr = 0.
 - Cmd: 6 bits. This output must show the last pressed command after it has been decoded.
 - Error: active at high level when there is a fault in the transmission when start bits have not been received correctly or when communication has been interrupted (signal edges are not received any more during a frame transmission).

A counter module is available and it can be used as a component in the system design. Its entity is described with the following code:

INTEGRATED CIRCUITS AND MICROELECTRONICS EXAM

```
Entity counter is
Generic( n: integer );
Port(
  Clk    : in std_logic;--clock signal
  Reset  : in std_logic;-- asynchronous initialization signal, active at high level
  Ena    : in std_logic;--enable
  Clr    : in std_logic; --synchronous initialization signal, active at high level
  Count: out integer range 0 to 2**n-1);
End counter;
```

Answer the following questions:

- a) In order to sample each bit, an edge detector module is needed. It should be capable of detecting edges that occur in the middle of a bit transmission and avoiding those that may appear on the boundary between two bits transmissions. Design the hardware needed to detect edges in the input *Sin*, only when an enable signal is active ($EnaEdge = 1$). This hardware must generate a one cycle pulse (*Edge*) whenever an edge is detected (either rising or falling, if $EnaEdge = 1$), and a signal for indicating the bit value (*ReadBit*) that depends on the type of edge ('1' for rising and '0' for falling, as shown in Figure 2).
- b) Since the bits are transmitted by serial, a shift register is required to store the frame bits. Design a shift register with an input *ReadBit* and an enable signal (*EnaReg*) to control when you load a new bit.
- c) Specify how many counters you consider necessary and write down its/their instance/s. Explain its/their function.
- d) Design a finite state machine that controls the different elements of the circuit and generate the necessary outputs.
- e) Draw a diagram block at RT (Register Transfer) level of the circuit indicating the necessary interconnections.
- f) Describe the complete circuit with VHDL. You can indicate with comments where is included the code developed in the previous steps.
- g) Describe a VHDL test bench to verify the proper operation of the design. Perform self-checks for at least the following cases:
 - a. When an error is produced due to a fault in the start bits. Simulation should not be stopped in this case.
 - b. When an error is detected by an interruption in the transmission. In this cases, simulation must be halted.

Clear and optimal VHDL descriptions will be good considered.