

UNIVERSIDAD CARLOS III DE MADRID



# **Analog integrated circuits design exercises**

## ***Integrated Circuits and Microelectronics***

Luis Entrena

Celia López

Marta Portela

Almudena Lindoso

Mario García

Enrique San Millán

**Exercise 1**

The figure shows the physical scheme of an amplifier stage.

- a) Draw the transistor scheme and indicate the aspect ratio  $W/L$  for each transistor.
- b) Calculate the drain current through each transistor
- c) Obtain  $V_o/V_i$  the amplifier gain

Data:

$$k_n = \mu_n C_{ox} = 120 \mu A/V^2$$



$$k_p = \mu_p C_{ox} = 50 \mu A/V^2$$

$$\lambda_n = \lambda_p = 0.1 V^{-1}$$

$$|V_{tn}| = |V_{tp}| = 1 V$$

$$V_{dd} = 5 V$$

$$V_{ss} = 0 V$$

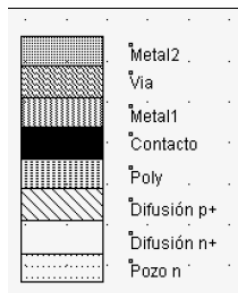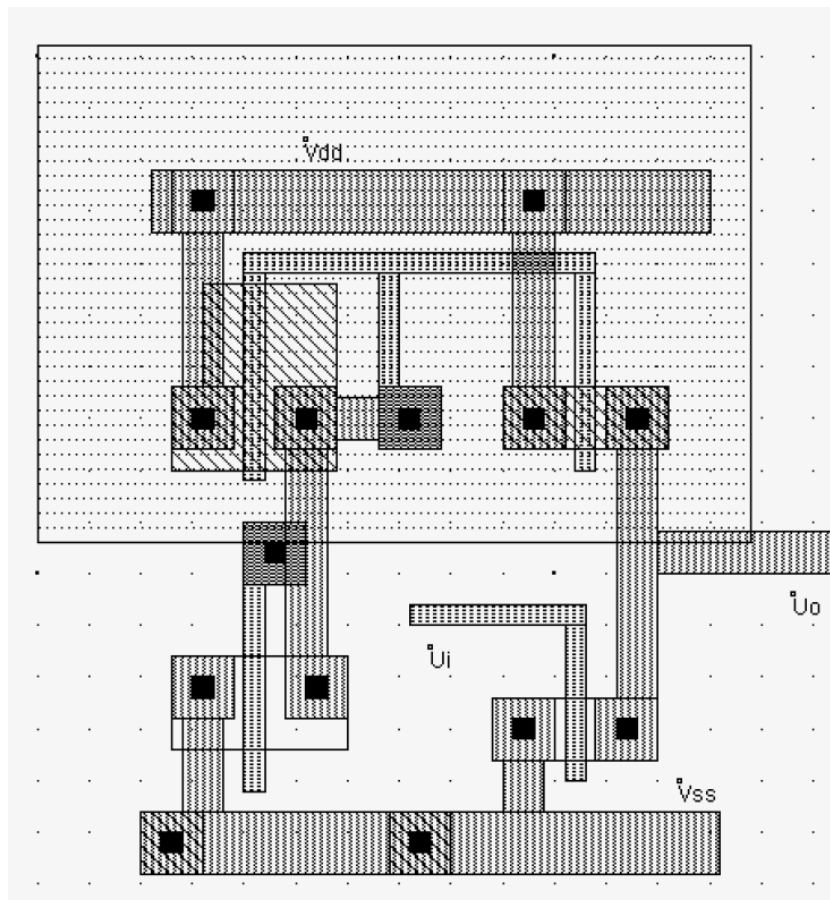

**Exercise 2**

The figure shows the physical scheme of an amplifier of two stages.

- Draw the transistor scheme and indicate the aspect ratio  $W/L$  for each transistor.
- Calculate the drain current through each transistor and the current supplied by the source at  $a$
- Obtain  $V_o/V_i$  the amplifier gain


Data:

$$k_n = \mu_n C_{ox} = 50 \mu A/V^2$$

$$k_p = \mu_p C_{ox} = 20 \mu A/V^2$$

$$\lambda_n = \lambda_p = 1/30 V^{-1}$$

$$|V_{tn}| = |V_{tp}| = 1V$$

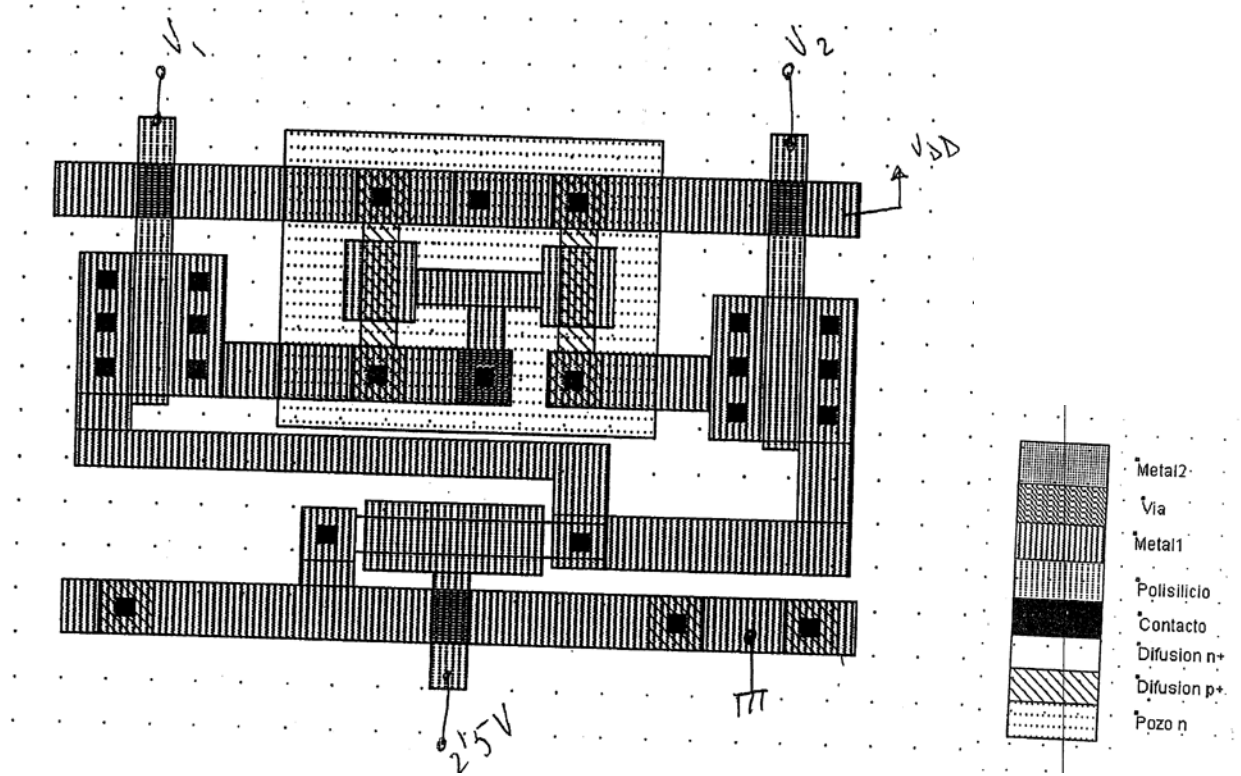

### Exercise 3

The figure shows the physical scheme of an analog circuit.

- Draw the transistor scheme and indicate the aspect ratio  $W/L$  for each transistor.
- Which is the purpose of so many contacts around the circuit?
- Obtain the voltage at A and the current through each transistor

Data:

$$k_n = \mu_n C_{ox} = 120 \mu A/V^2$$


$$k_p = \mu_p C_{ox} = 50 \mu A/V^2$$

$$\lambda_n = \lambda_p = 0.1 V^{-1}$$

$$|V_{tn}| = |V_{tp}| = 1V$$

$$V_{dd}=5V \quad V_{ss}=0V$$

# Integrated Circuits and Microelectronics

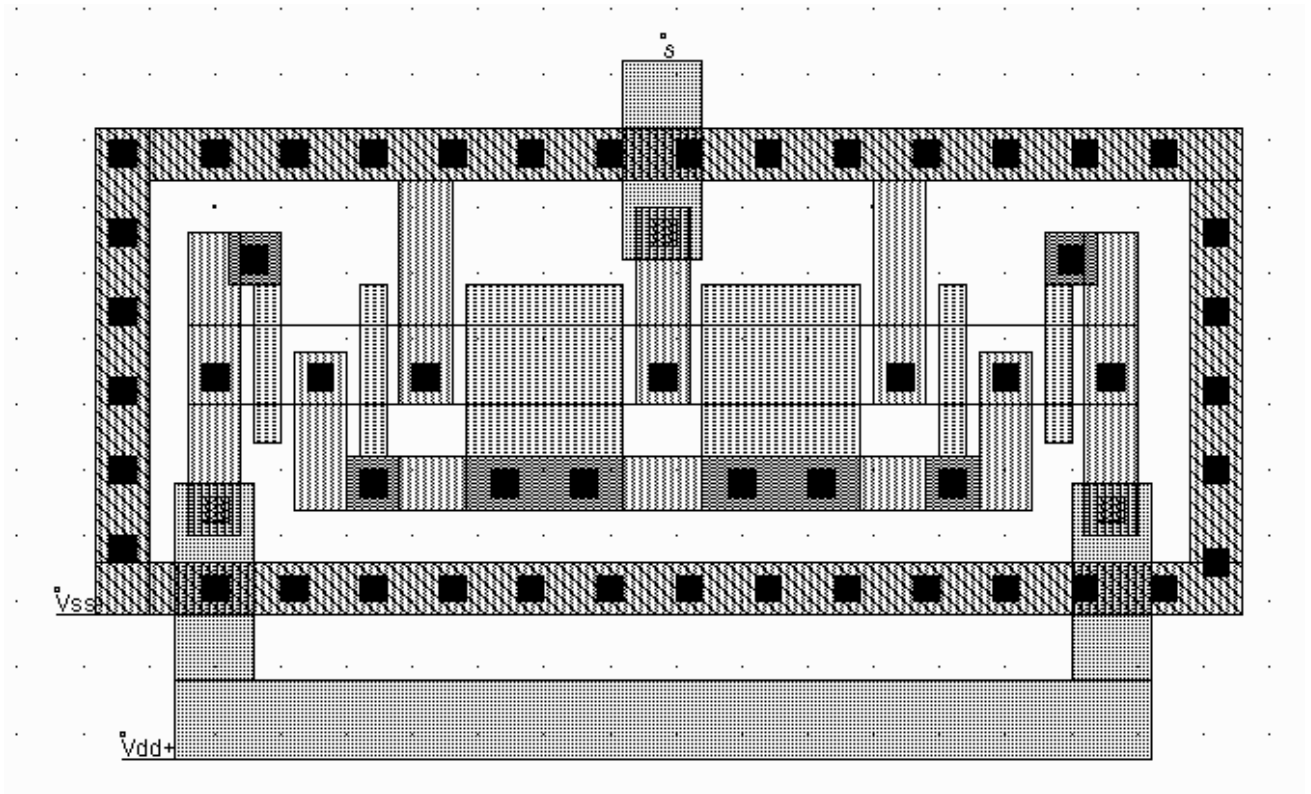

	Metal2
	Via
	Metal1
	Contacto
	Poly
	Difusión p+
	Difusión n+
	Pozo n