

UNIVERSIDAD CARLOS III DE MADRID



ICs Test Exercises

Integrated Circuits and Microelectronics

Enrique San Millán

Mario García

Luis Entrena


Celia López

Almudena Lindoso

Marta Portela

Problem 1

For the circuit in the figure:

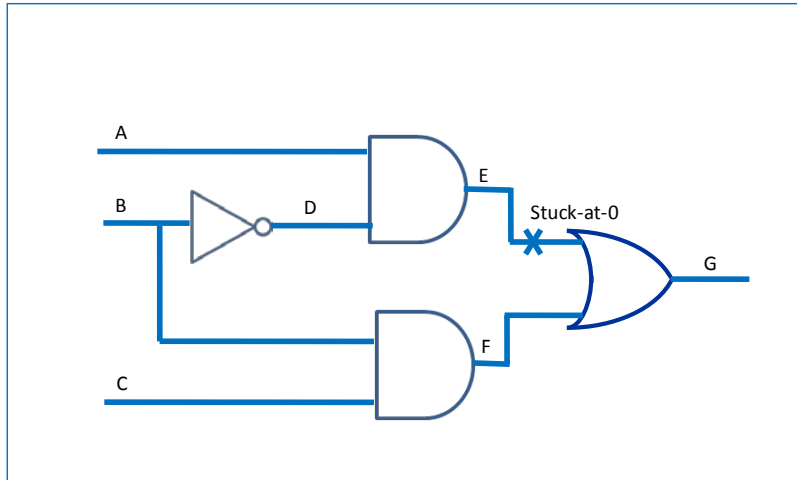


- Find a test vector that detects that E is stuck-at-0.
- What is the test coverage given by this test vector?
- Add more vectors (the least possible number) so that the maximum possible coverage is achieved. How many vectors are needed, and which is the coverage for them?
- Are there any untestable faults? Describe possible solutions to increase the coverage in those circuits with untestable faults.

Consider that all the lines connected to B are a single line when it comes to fault insertion.

Problem 2

For the circuit in the figure:

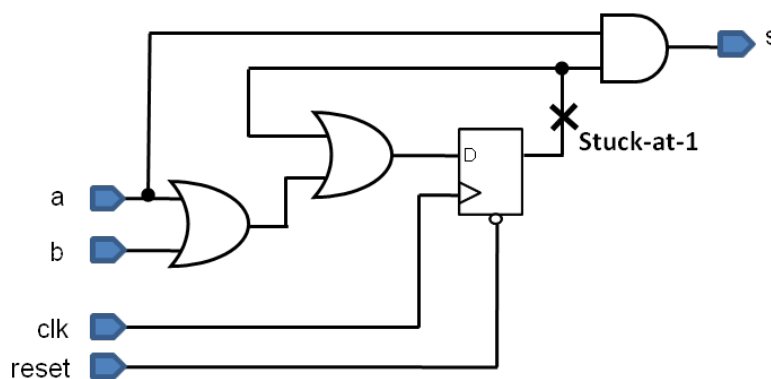

- Specify all the necessary conditions for detecting the stuck-at-1 fault pointing out in the figure (by observing the output S)
- Represent in a chronogram the required conditions.