

UNIVERSIDAD CARLOS III DE MADRID



Layout Exercises

Integrated Circuits and Microelectronics

Mario García

Marta Portela

Almudena Lindoso

Enrique San Millán

Luis Entrena

Celia López


Exercise 1

Answer the following questions regarding the layout shown in the figure:

- a) Obtain the corresponding transistor level scheme.
- b) Represent with logic gates the circuit. Point out which set of transistors corresponds to each logic gate.
- c) Draw the cross section of the layout through the line MN.
- d) Let $y = a + b$ (logic OR). Design y by only using pass transistor logic. Describe the transistor scheme and draw the corresponding layout.

INTEGRATED CIRCUITS AND MICROELECTRONICS

5 λ mda
2.00 μ m

 

Exercise 2

Consider the layout circuit in Fig. 1.

- a) Obtain the associated transistors level circuit.
- b) Represent using logic gates the circuit, pointing out which part corresponds to each part.
- c) Draw the transverse section of the layout for the line XY.

INTEGRATED CIRCUITS AND MICROELECTRONICS

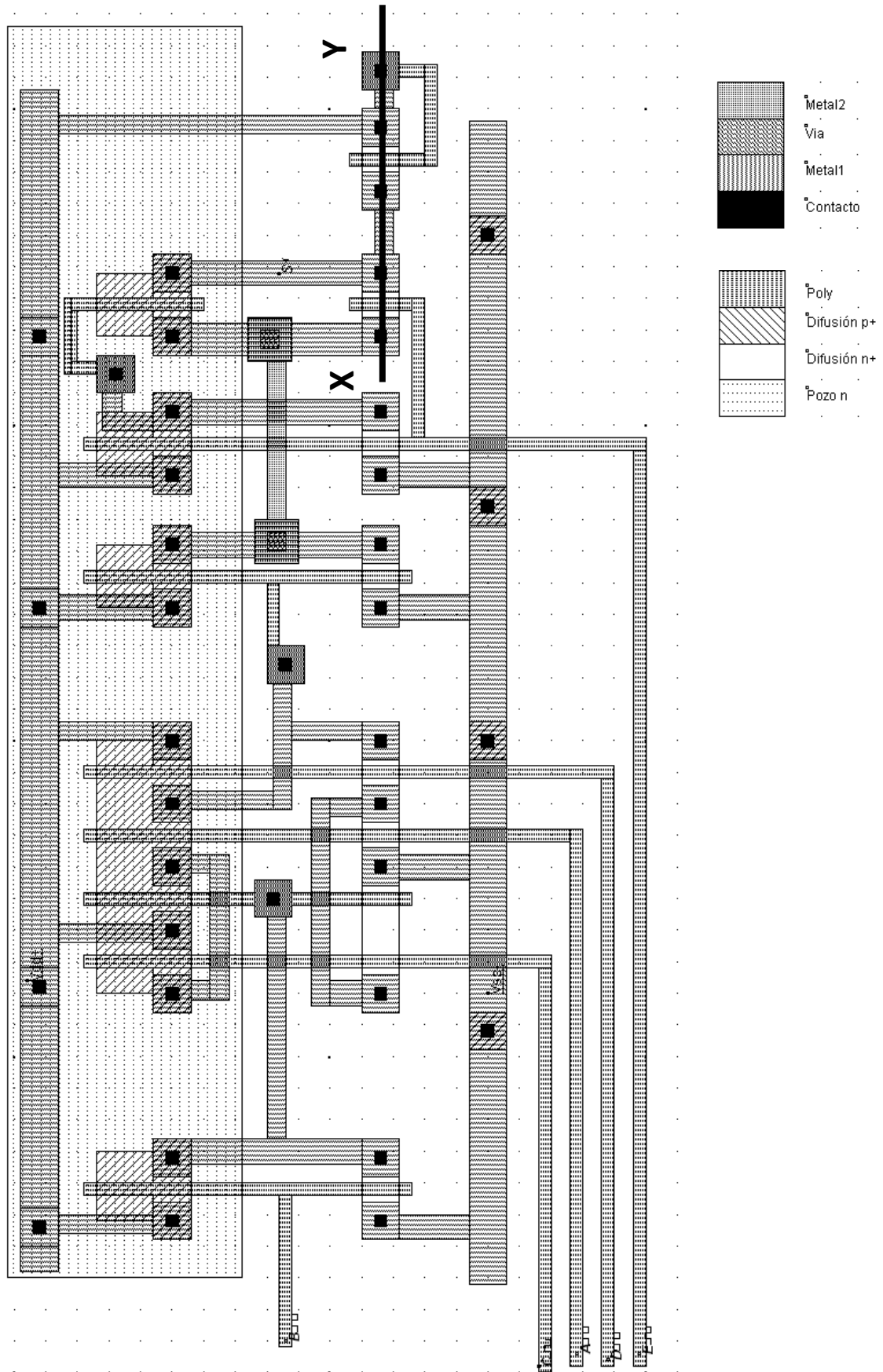


Fig. 1