

# Electrical Power Engineering Fundamentals

Departamento de Ingeniería Eléctrica. Universidad Carlos III de Madrid

Module 1. Basic Concepts. Week 2

**Exercise 1.** In the following circuit:

- Find  $U_{AB}$  and  $U_X$  when  $I_g = 2$  A.
- Find  $U_{BA}$  and  $U_X$  when  $I_g = 1$  A

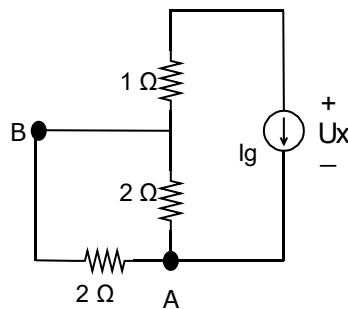


Figure 1. DC circuit 1

**Solution:** a)  $U_{AB} = 2V$ ;  $U_X = -4V$       b)  $U_{BA} = -1V$ ;  $U_X = -2V$

**Exercise 2.** In the following circuit:

- Find  $I_1$  and  $I_T$  when  $U_g = 2$  V
- Find  $U_1$  and  $U_2$  when  $U_g = -1$  V

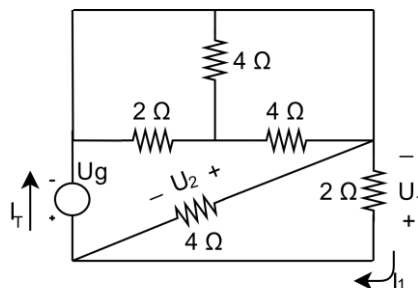


Figure 2. DC circuit 2

**Solution:** a)  $I_1 = -1A$ ;  $I_T = -1.5A$       b)  $U_1 = -1V$ ;  $U_2 = 1V$

**Exercise 3.** Using resistor association techniques and real source equivalences simplify the circuit below to a real voltage source:

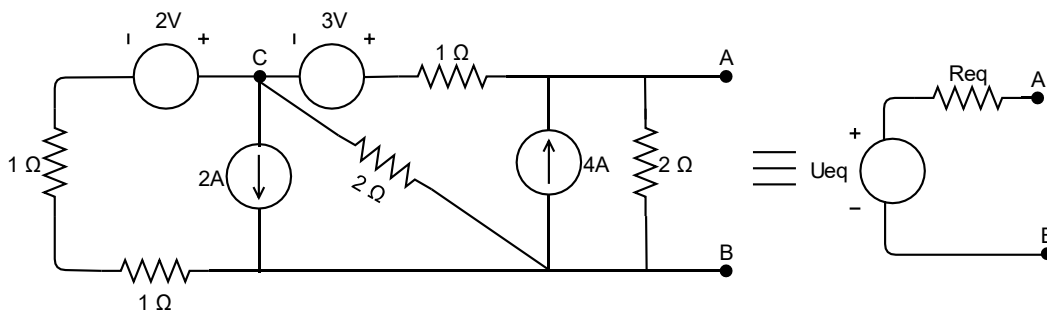


Figure 3. DC circuit 3

**Solution:**  $U_{eq} = 5V$ ;  $R_{eq} = 1 \Omega$

**Exercise 4.** In the circuit below:

- Find  $U_{BC}$  and  $IR_1$
- Find the power generated by each power source.
- Check the power balance

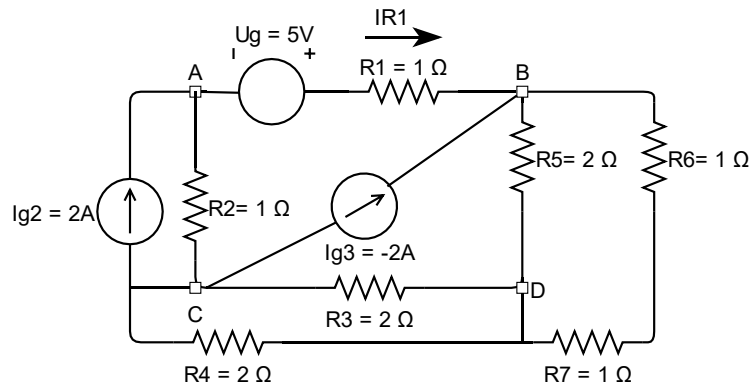


Figure 4. DC circuit 4

**Solution:** a)  $U_{BC} = 1.5V$ ;  $IR_1 = 2.75A$       b)  $P_{U_g} = 13.75W$ ;  $P_{I_{g2}} = -1.5W$ ;  $P_{I_{g3}} = -3W$ ;      c)  $P_{generated\_sources} = P_{consumed\_resistors} = 9.25W$

**Exercise 5.** In the circuit below, calculate the power consumed by the resistors  $P_{R1}$ ,  $P_{R2}$ ,  $P_{R3}$ , and  $P_{R4}$  and the power generated by the sources  $P_{U_g}$  and  $P_{I_g}$ .

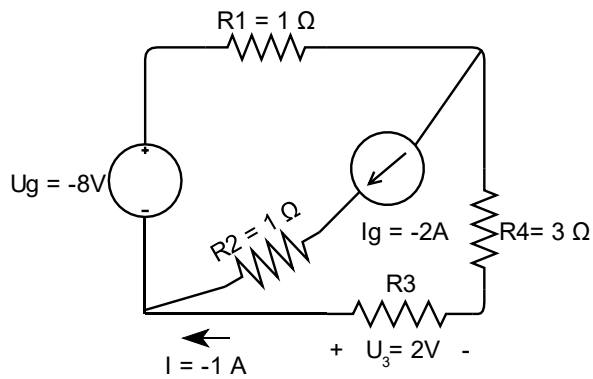


Figure 5. DC circuit 5

**Solution:**  $P_{R1} = 9W$ ;  $P_{R2} = 4W$ ;  $P_{R3} = 2W$ ;  $P_{R4} = 3W$ ;  $P_{U_g} = 24W$ ;  $P_{I_g} = -6W$