

Electrical Power Engineering Fundamentals

Departamento de Ingeniería Eléctrica. Universidad Carlos III de Madrid

Module 2. Analysis of DC Circuits. Week 3

Exercise 1. In the following circuit:

- Find the current i and the voltage U_x using the mesh current method and/or the node-voltage method
- Calculate the power generated by sources and check the power balance.

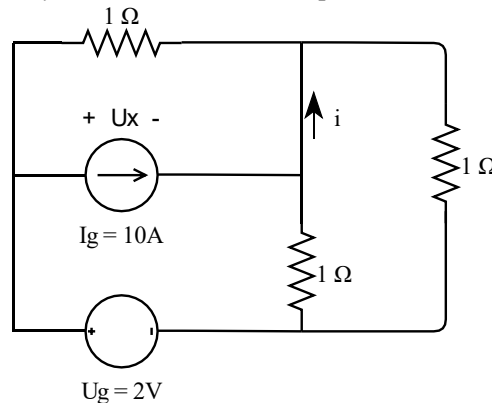


Figure 1 DC circuit 1

Exercise 2. In the following circuit:

- Find the current i and the voltage U_x using the mesh current method and/or the node-voltage method
- Calculate the power generated by sources and check the power balance.

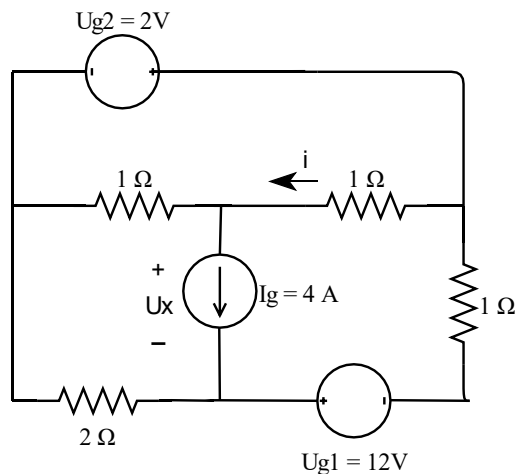


Figure 2 DC circuit 2

Exercise 3. In the following circuit:

- Find the currents i_1 and i_2 and the voltages U_{x1} and U_{x2} using the mesh current method and/or the node-voltage method.
- Calculate the power generated by sources and check the power balance.

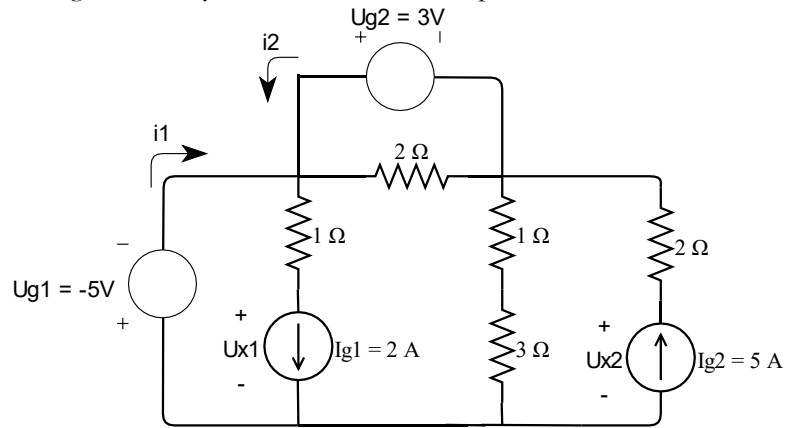


Figure 3. DC circuit 3

Exercise 4. In the circuit below:

- Find the currents i_1 and i_2 and the voltages U_{x1} and U_{x2} using the mesh current method and/or the node-voltage method.
- Calculate the power generated by sources and check the power balance.

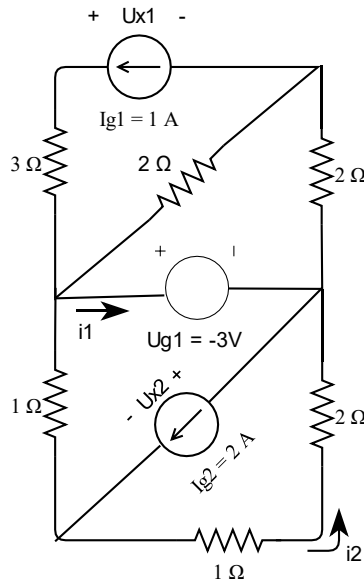


Figure 4. DC circuit 4