

# Electrical Power Engineering Fundamentals

Departamento de Ingeniería Eléctrica. Universidad Carlos III de Madrid

Module 4. Three-phase AC Systems. Week 11

**Exercise 1.** The following circuit shows a balanced three-phase load connected to an ideal balanced three-phase voltage source. (A, B, C) is a direct sequence. Find the values R and X from the load, knowing the following measures:  $W1 = 63094\text{W}$ ;  $W2 = 16906\text{W}$ ;  $V = 400\text{ V}$

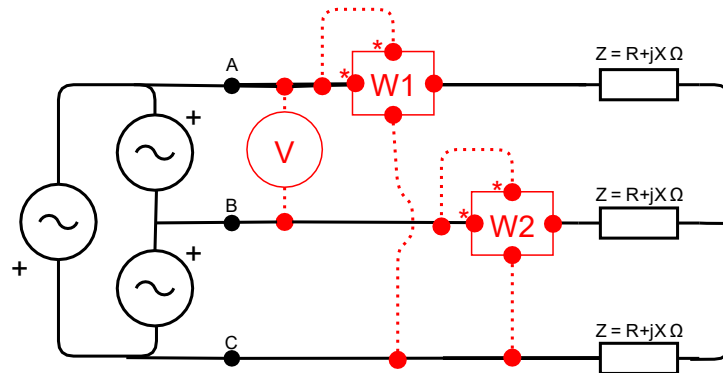


Figure 1 Three-phase AC system 1

**Solution:**  $R=1$ ;  $X=1$

**Exercise 2.** The following circuit shows 2 balanced three-phase loads connected to an ideal balanced three-phase voltage source. (A, B, C) is a direct sequence. The following measures are known:  $W1 = 6154.7\text{ W}$ ;  $W2 = 3845.3\text{W}$ ; and  $V = 400\text{V}$ . The frequency is  $f=50\text{Hz}$ .

- Find the value of the impedance  $Z1$ .
- Find the power consumed by the load 2.
- In the circuit, we want to connect a balanced three-phase capacitor bank in parallel to minimize the current measured by the ammeter. Find the value of the phase-connected capacitor at  $\Delta$  and Y connections.

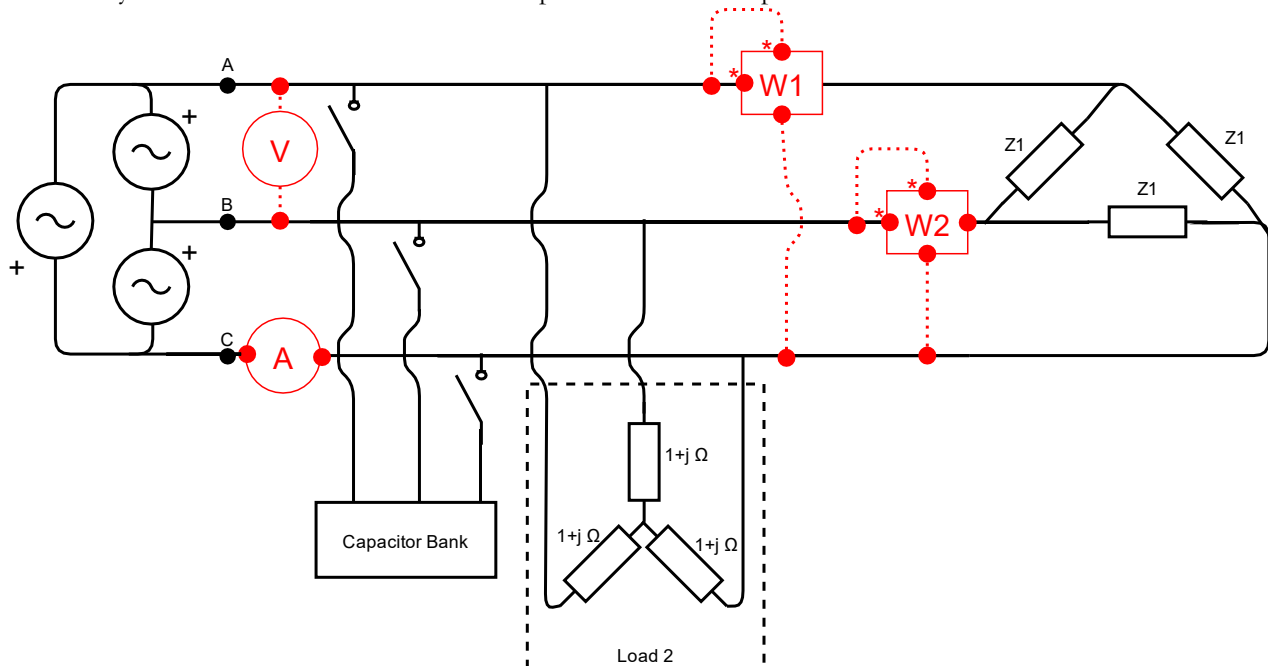


Figure 2. Three-phase AC system 2

**Solution:** a)  $Z1 = 41.4 + 16.55j\ \Omega$ ;  $S_{12} = 80000 + 80000j\ \text{VA}$ ; c)  $C^Y = 1.67\ \text{mF}$ ;  $C^\Delta = 0.557\ \text{mF}$

**Exercise 3.** The following circuit shows a balanced three-phase AC system. (A, B, C) is a direct sequence. The following measures are known:  $W1 = 12309.4 \text{ W}$ ;  $W2 = 7690.6\text{W}$ ; and  $V1 = 400\text{V}$ .

- Find the value of the impedance  $Z_L$ .
- Find the current measured by the ammeter A and voltage measured by the voltmeter V2.

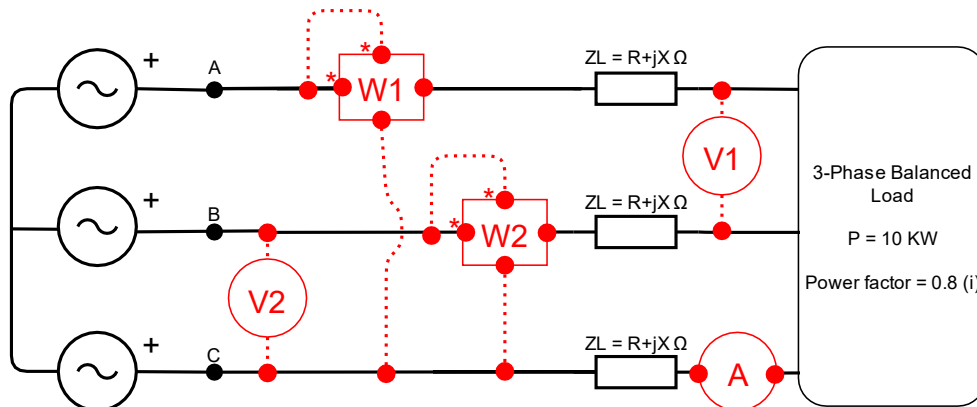


Figure 3. Three-phase AC system 3

**Solution:** a)  $Z_L = 10.24 + 0.512j \Omega$ ; b)  $A = 18.04 \text{ A}$ ;  $V2 = 689.4\text{V}$