

Electrical Power Engineering Fundamentals

Departamento de Ingeniería Eléctrica. Universidad Carlos III de Madrid

Module 4. Three-phase AC Systems. Week 11

Exercise 1. The following circuit shows a balanced three-phase load connected to an ideal balanced three-phase voltage source. (A, B, C) is a direct sequence. Find the values R and X from the load, knowing the following measures: $W1 = 63094\text{W}$; $W2 = 16906\text{W}$; $V = 400\text{ V}$

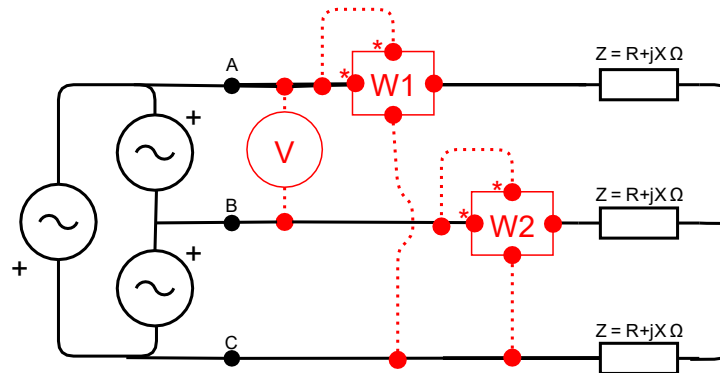


Figure 1 Three-phase AC system 1

Exercise 2. The following circuit shows 2 balanced three-phase loads connected to an ideal balanced three-phase voltage source. (A, B, C) is a direct sequence. The following measures are known: $W1 = 6154.7\text{ W}$; $W2 = 3845.3\text{W}$; and $V = 400\text{V}$. The frequency is $f=50\text{Hz}$.

- Find the value of the impedance $Z1$.
- Find the power consumed by the load 2.
- In the circuit, we want to connect a balanced three-phase capacitor bank in parallel to minimize the current measured by the ammeter. Find the value of the phase-connected capacitor at Δ and Y connections.

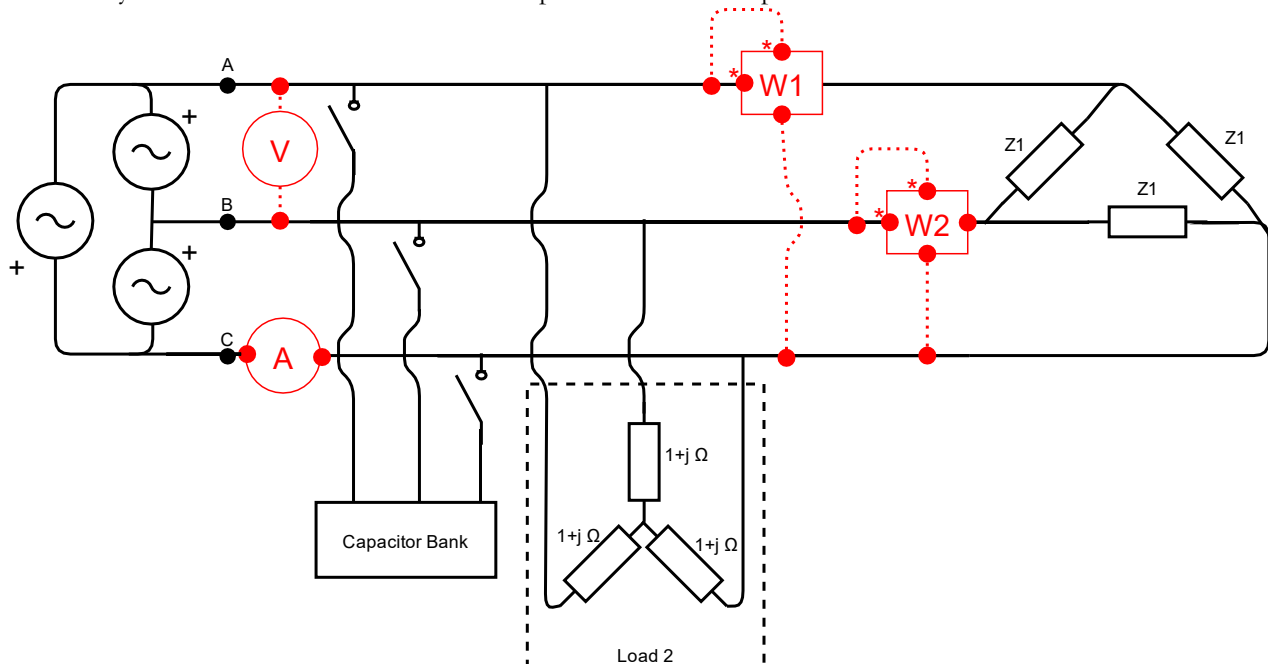


Figure 2. Three-phase AC system 2

Exercise 3. The following circuit shows a balanced three-phase AC system. (A, B, C) is a direct sequence. The following measures are known: $W1 = 12309.4 \text{ W}$; $W2 = 7690.6 \text{ W}$; and $V1 = 400 \text{ V}$.

- Find the value of the impedance Z_L .
- Find the current measured by the ammeter A and voltage measured by the voltmeter V2.

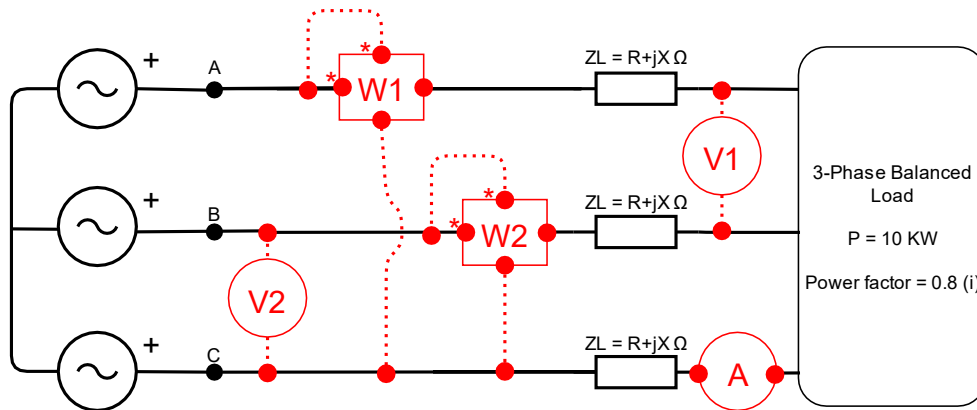


Figure 3. Three-phase AC system 3