

Electrical Power Engineering Fundamentals

Departamento de Ingeniería Eléctrica. Universidad Carlos III de Madrid

Module 1. Basic Concepts. Week 2

Exercise 1. In the following circuit:

- Find U_{AB} and U_X when $I_g = 2$ A.
- Find U_{BA} and U_X when $I_g = 1$ A.

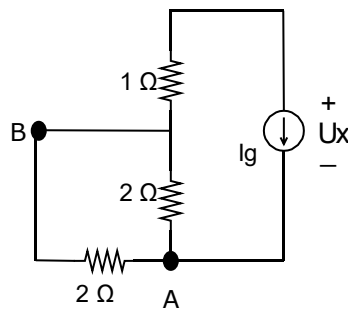


Figure 1. DC circuit 1

Exercise 2. In the following circuit:

- Find I_1 and I_T when $U_g = 2$ V
- Find U_1 and U_2 when $U_g = -1$ V

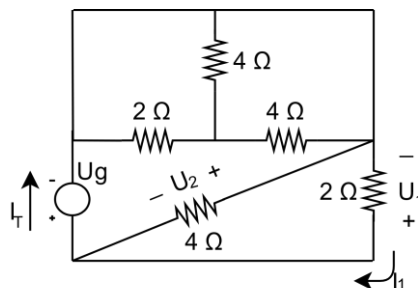


Figure 2. DC circuit 2

Exercise 3. Using resistor association techniques and real source equivalences simplify the circuit below to a real voltage source:

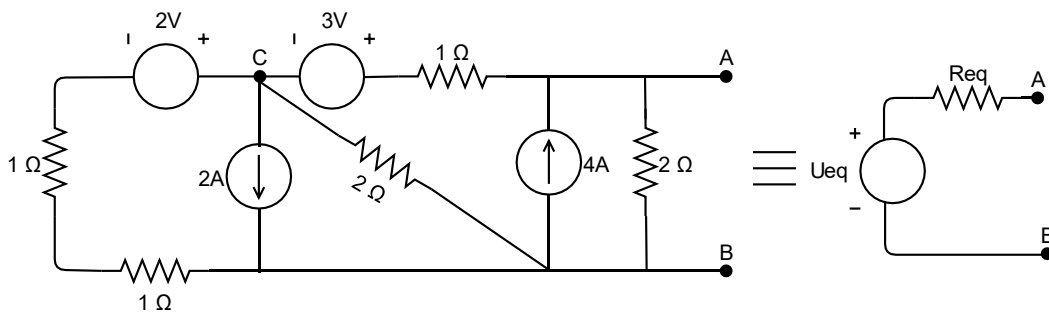


Figure 3. DC circuit 3

Exercise 4. In the circuit below:

- Find U_{BC} and IR_1
- Find the power generated by each power source.
- Check the power balance

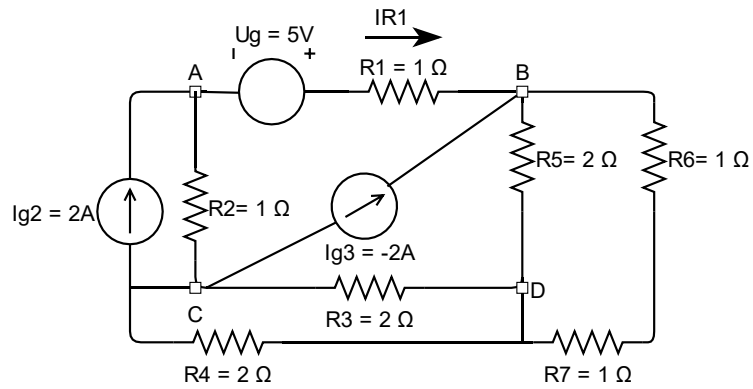


Figure 4. DC circuit 4

Exercise 5. In the circuit below, calculate the power consumed by the resistors P_{R1} , P_{R2} , P_{R3} , and P_{R4} and the power generated by the sources P_{U_g} and P_{I_g} .

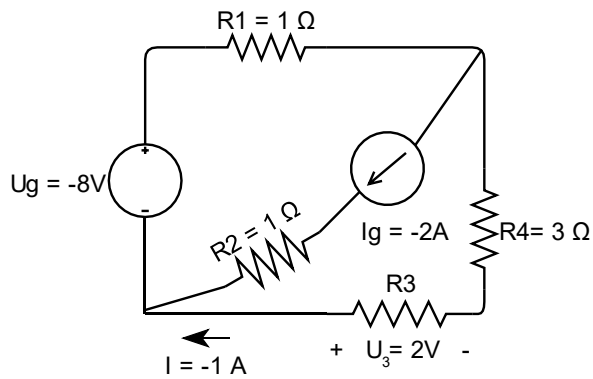


Figure 5. DC circuit 5