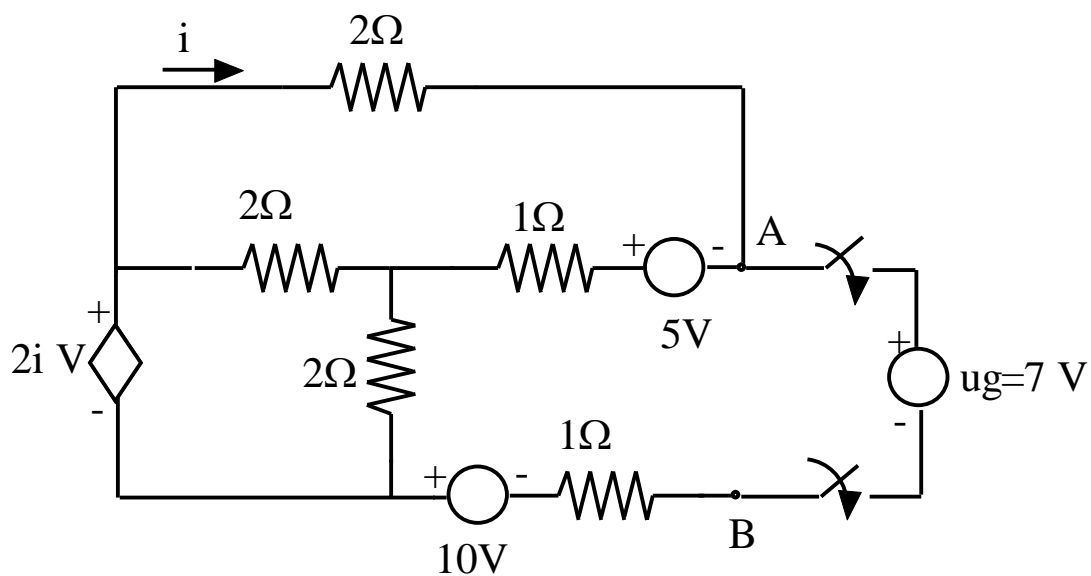




## Electrical Power Engineering Fundamentals First Partial Exam (1<sup>st</sup> March 2018)

- 1) Calculate the Thevenin equivalent of the circuit from terminals A B considering that the switches are open.
- 2) Use the obtained result to calculate the current, voltage and power of the source  $u_g$  when the switches are closed. Indicate if the source absorbs or generates power.



## Solution

### Part 1

To obtain Thevenin voltage we calculate the voltage drop between A and B. Using mesh analysis:

$$2i_1 + 2(i_1 - i_2) + i_1 - 5 = 0$$

$$2(i_2 - i_1) + 2i_2 - 2i_1 = 0$$

$$i_1 = i_2$$

Solving the system:

$$i_1 = 5/3 \text{ A}$$

$$i_2 = 5/3 \text{ A}$$

Then:

$$u_{AB} = u_{th} = -5 + 5/3 + 10/3 + 10 = 10 \text{ V}$$

In order to calculate the Thevenin Resistance we place a short circuit between A and B and calculate the current flowing from A to B. Using mesh analysis again:

$$2i_1 + 1(i_1 - i_3) + 2(i_1 - i_2) - 5 = 0$$

$$2(i_2 - i_1) + 2(i_2 - i_3) - 2i_1 = 0$$

$$2(i_3 - i_2) + 1(i_3 - i_1) + 5 + 1i_3 - 10 = 0$$

$$i_1 = i_2$$

Solving the system:

$$i_1 = 8.33 \text{ A}$$

$$i_2 = 13.33 \text{ A}$$

$$i_3 = 10 \text{ A} = i_{cc}$$

Then:

$$R_{th} = u_{th} / i_{cc} = 10 / 10 = 1 \Omega$$

### Part 2

We connect the source of 7V to the Thevenin equivalent and analyse the circuit:

$$i = (u_{th} - u_g) / R_{th} = (10 - 7) / 1 = 3 \text{ A}$$

$$u_g = 7 \text{ V}$$

$p_g = u \cdot i = 7 \cdot 3 = 21 \text{ W}$  Absorbed: Because the current flowing through  $u_g$  goes from + to –