



Electrical Power Engineering Fundamentals First Partial Exam (1st March 2018)

1) Calculate the Thevenin equivalent of the circuit from terminals A B considering that the switches are open.

2) Use the obtained result to calculate the current, voltage and power of the source u_g when the switches are closed. Indicate if the source absorbs or generates power.

