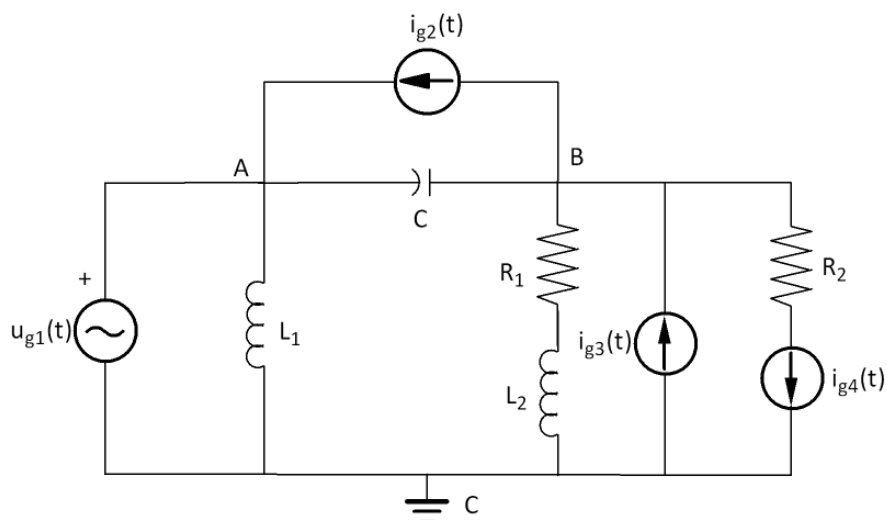


Electrical Power Engineering Fundamentals

Second partial exam, April 12th 2018

- Solve the following circuit in the frequency domain using **nodal analysis** and obtain the phasors current at each branch.



$$R_1=3 \Omega; R_2=1 \Omega; L_1=0.01 \text{ H}; L_2=0.02 \text{ H}; C=0.01 \text{ F}$$


$$u_{g1}(t) = \sqrt{2} \cdot 100 \cos(100t) \text{ V}$$

$$i_{g2}(t) = \sqrt{2} \cdot 10 \cos(100t + 90) \text{ A}$$

$$i_{g3}(t) = \sqrt{2} \cdot 5 \cos(100t) \text{ A}$$


$$i_{g4}(t) = \sqrt{2} \cdot 3 \cos(100t + 90) \text{ V}$$

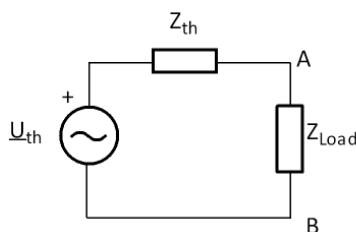- Calculate the power balance of the circuit
- Calculate the Thevenin equivalent of the circuit at terminals AB.
- We connect an impedance $Z_{load} = R + jX \Omega$ at terminals AB as shown in the figure. Calculate the value of Z_{load} knowing that the complex power generated by the Thevenin source in this situation is $S=50+150j$.



SOLUTION

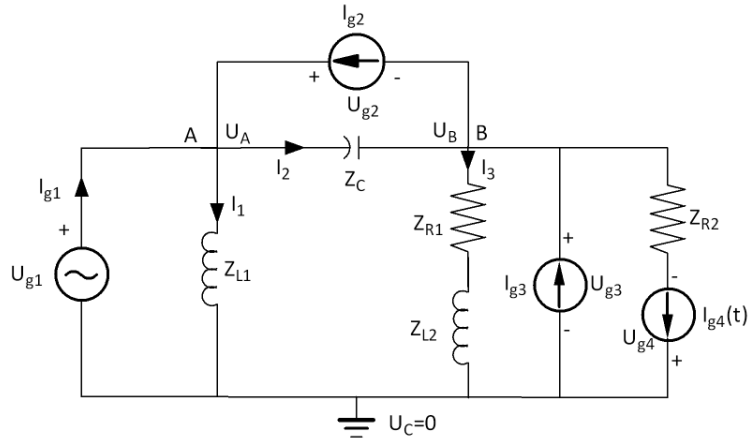a) We move to the frequency domain ($\omega = 100\text{rad/s}$), obtaining the impedances of the passive elements and the phasors that represent the different currents and voltages.



Impedances:

$$Z_{R1} = 3\Omega \quad Z_{R2} = 1\Omega \quad Z_{L1} = j\Omega \quad Z_{L2} = 2j\Omega \quad Z_C = -j\Omega$$

Phasors:

$$\underline{U}_{g1} = 100V \quad \underline{I}_{g2} = 10jA \quad \underline{I}_{g3} = 5A \quad \underline{I}_{g4} = 3jA$$

Nodal equations for nodes A and B:

Node A:

$$\underline{U}_A = \underline{U}_{g1}$$

$$\frac{\underline{U}_B - \underline{U}_A}{Z_C} + \frac{\underline{U}_B}{Z_R + Z_{L2}} + \underline{I}_{g2} - \underline{I}_{g3} + \underline{I}_{g4} = 0$$

Solving the equations we find the nodal voltages:

$$\underline{U}_A = 100V$$

$$\underline{U}_B = 97.2 + 20.6jV = 99.36_{11.96^\circ}A$$

Now we calculate the currents that flow through the different branches:

$$\underline{I}_1 = \frac{\underline{U}_A}{Z_{L1}} = -100jA$$

$$\underline{I}_2 = \frac{\underline{U}_A - \underline{U}_B}{Z_C} = 20.6 + 2.8jA = 20.79_{7.74^\circ}A$$

$$\underline{I}_3 = \frac{\underline{U}_B}{Z_{R1} + Z_{L2}} = 25.6 - 10.2jA = 27.56_{-21.72^\circ}A$$

$$\underline{I}_{g1} = \underline{I}_1 + \underline{I}_2 - \underline{I}_{g2} = 20.6 - 107.2j = 109.16_{-79.12^\circ}A$$

b) Power balance

Active and reactive power of pasive elements

$$P_{loads} = Z_{R1} \cdot I_3^2 + Z_{R2} \cdot I_{g4}^2 = 2287.2W$$

$$Q_{loads} = X_{L1} \cdot I_1^2 + X_{L2} \cdot I_3^2 - |X_C| \cdot I_2^2 = 11087VAr$$

$$S_{loads} = 2287.2 + j11087VA$$

Complex power of sources:

$$S_{U_{g1}} = \underline{U}_{g1} \cdot \underline{I}_{g1}^* = 2060 + 10720jVA$$

$$S_{I_{g2}} = (\underline{U}_A - \underline{U}_B) \cdot \underline{I}_{g2}^* = -206 - 28jVA$$

$$S_{I_{g3}} = \underline{U}_{g1} \cdot \underline{I}_{g1}^* = 486 + 103jVA$$

$$S_{I_{g4}} = (-\underline{U}_B - (Z_{R2} \cdot \underline{I}_{g4})) \cdot \underline{I}_{g4}^* = -52.8 + 291.6jVA$$


$$S_{generators} = S_{U_{g1}} + S_{I_{g2}} + S_{I_{g3}} + S_{I_{g4}} = 2287.2 + 11087jVA$$

$$S_{generators} = S_{loads}$$

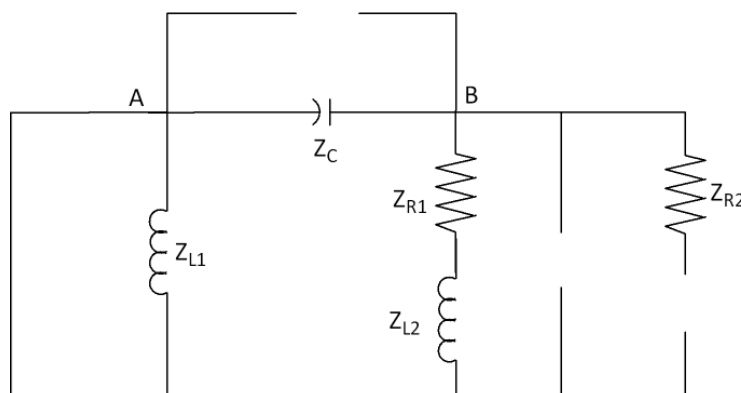c) Thevenin equivalent

$$\underline{U}_{th} = \underline{U}_{AB} = \underline{U}_A - \underline{U}_B = 2.8 - 20.6jV = 20.7894_{-82.2597^\circ}$$


We can obtain Thevenin impedance pasivizing the circuit and finding the equivalent impedance of the resulting net from terminals AB:



The equivalent impedance is:

$$Z_{th} = Z_C \parallel (Z_{R1} + Z_{L2}) = \frac{Z_C \cdot (Z_{R1} + Z_{L2})}{Z_C + Z_{R1} + Z_{L2}} = 0.3 - 1.1j \Omega = 1.14_{-74.74^\circ} \Omega$$

d) The resulting equivalent is:

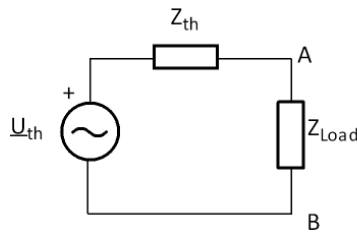

The current supplied by the Thevenin source when the impedance is connected is

$$\underline{I}^* = \frac{S_{gth}}{\underline{U}_{th}} = \frac{50 + 150j}{2.8 - 20.6j} = -6.82 - 3.35j A$$

$$\underline{I} = -6.82 + 3.35j A$$

Voltage drop at Zload

$$\underline{U}_{Zload} = \underline{U}_{th} - \underline{I} \cdot Z_{th} = 8.54 - 27.10j V$$

Then:

$$Z_{load} = \frac{\underline{U}_{Zload}}{\underline{I}} = 0.56 + 3.69j \Omega$$