

Electrical Power Engineering Fundamentals

AC CIRCUITS (15th November 2019)

In the circuit below:


$$u_1(t) = \sqrt{2} \cdot 1,25 \cdot \cos(100t) V$$

$$u_2(t) = \sqrt{2} \cdot 10 \cdot \cos(100t) V$$

$$i_3(t) = \sqrt{2} \cdot 8 \cdot \cos(100t - 90) A$$

$$R1 = 0.25 \Omega; R2 = 1 \Omega, L1 = 2.5 mH; L2 = 5 mH; C1 = 0.05 F; C2 = 0.01 F$$


- Write the nodal equations for nodes A, B and C taking D as reference node. Express the equations as a matrix system. Solve the system and calculate the nodal voltages in phasor form
- Calculate the complex power supplied by the voltage source $ug1$
- Calculate the Thevenin's equivalent of the circuit at terminals C D including all the elements of the circuit in the equivalent. Draw the equivalent
- Calculate the complex power absorbed by an impedance $Z_{load}=3+7j$ connected between terminals C D.

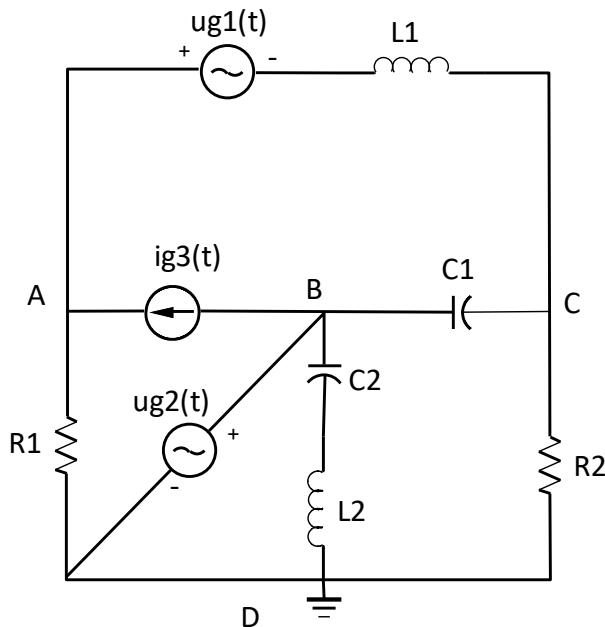

Solution


We transform the circuit into the frequency domain using the equations for the impedances:

$$ZR=R; ZL=j\omega L; ZC=-j/\omega C$$

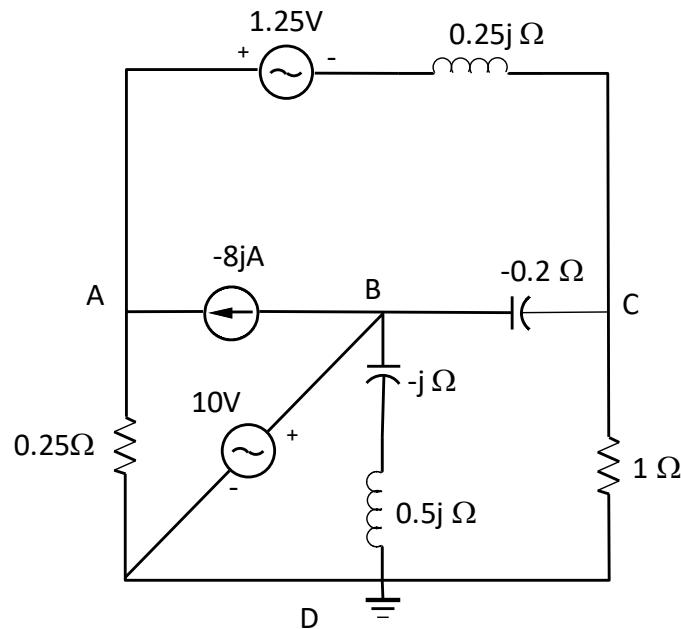

We can transform the real voltage source into a real current source to facilitate the analysis of the system with nodal method
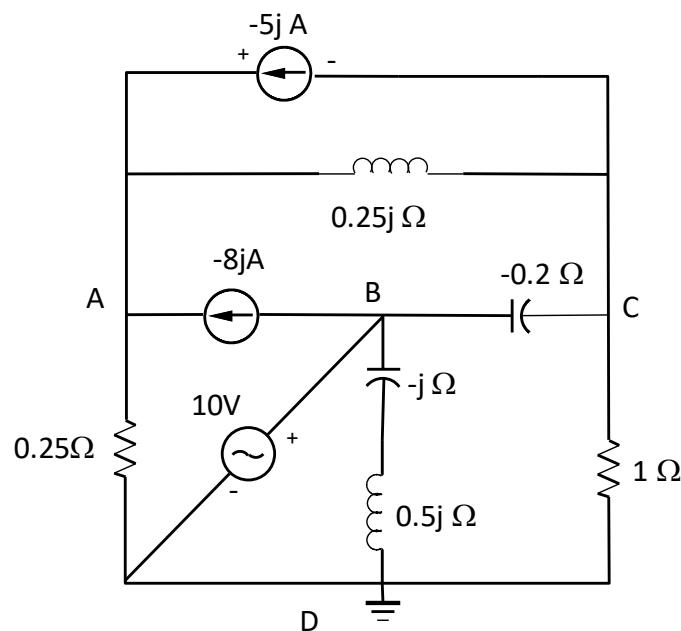
$$Ig1 = \frac{Ug1}{ZI1} = -5j \text{ A}$$



Nodal equations in matrix form

$$\begin{pmatrix} \frac{1}{R1} + \frac{1}{ZL1} & 0 & -\frac{1}{ZL1} \\ 0 & 1 & 0 \\ -\frac{1}{ZL1} & -\frac{1}{ZC1} & \frac{1}{ZL1} + \frac{1}{ZC1} + \frac{1}{ZR2} \end{pmatrix} \begin{pmatrix} U1 \\ U2 \\ U3 \end{pmatrix} = \begin{pmatrix} Ig1 + Ig3 \\ Ug2 \\ -Ig1 \end{pmatrix}$$

$$\begin{pmatrix} 4 - 4j & 0 & 4j \\ 0 & 1 & 0 \\ 4j & -5j & 1 + 1j \end{pmatrix} \begin{pmatrix} U1 \\ U2 \\ U3 \end{pmatrix} = \begin{pmatrix} -13j \\ 10 \\ 5j \end{pmatrix}$$

Solving

$$\underline{U_A} = 9.7083 - 0.5417i = 9.7234 \angle -3.1934^\circ$$

$$\underline{U_B} = 10V$$

$$\underline{U_C} = 7.0000 + 9.1667i = 11.5338 \angle 52.6333^\circ$$

b)

$$\underline{U_{I1}} = (\underline{U_C} - \underline{U_A}) + \underline{U_{g1}}$$

$$\underline{U_{I1}} = -1.4583 + 9.7083i = 9.8173 \angle 98.54^\circ A$$

$$I_{ca} = \underline{U_{I1}} / Z_{I1}$$

$$I_{ca} = 38.8333 + 5.8333i = 39.269 \angle 8.5428A$$

$$S_{g1} = S_{g1} * I_{ca}^*$$

$$S_{g1} = 48.5417 - 7.2917i$$

c) Thevenin's voltage

$$U_{th} = \underline{U_C} = 11.5338 \angle 52.6333^\circ V$$

$$U_{th} = U_D = 7.0000 + 9.1667i = 11.5338 \angle 52.6333^\circ$$

% Impedance with short circuit current

