

# Electrical power engineering fundamentals

Partial exam. 25th November 2020

**Instructions** Solve the problems using the methods indicated in the problem statements and write a summary of your results in this paper. Only the solutions obtained with these methods will be graded.


Name.....

## AC circuits

Given that the values of the parameters are  $R = 4$ ,  $L = 0.1H$ ,  $C = 25mF$

$$u_{g1}(t) = \sqrt{2} \cdot 13 \cdot \cos 10tV$$
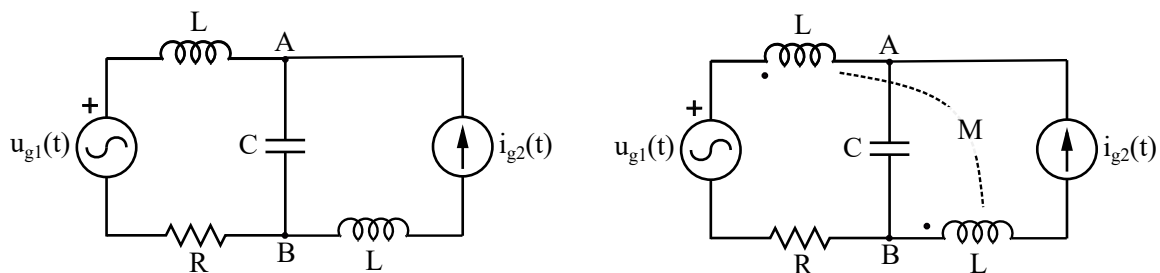
$$i_{g2}(t) = \sqrt{2} \cdot 2 \cdot \cos(10t + 90)A$$




a) Find the Thevenin equivalent in the circuit of the figure on the left between A and B **including all the elements of the circuit in it**. Draw the equivalent indicating the obtained values for the parameters. (6 points)

b) Recalculate the Thevenin equivalent if the two inductors of the circuit are coupled as in the figure on the right given that  $M = 0.5H$ . (4 points)

## DC circuits

In the DC circuit of the figure:

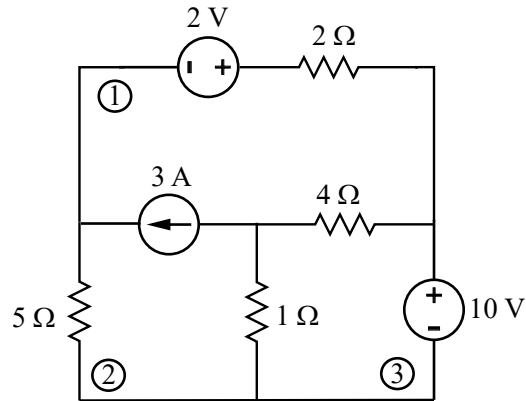

- Write the equations for the **mesh current method** for the circuit in the figure. (Label the mesh currents with the names provided in the figure and take the mesh currents in clockwise direction). (2.5 points)
- Write the mesh equations in matrix form. (2 points)
- Solve the equations and provide the values in the circuit figure indicating their value and direction (2.5 points)
- Do a power balance of the circuit and write the total power delivered by sources and the total power absorbed by resistors (3 points)