

Electrical power engineering fundamentals


Partial exam. 25th November 2020

Instructions Solve the problems using the methods indicated in the problem statements and write a summary of your results in this paper. Only the solutions obtained with these methods will be graded.

Name.....

DC Circuits

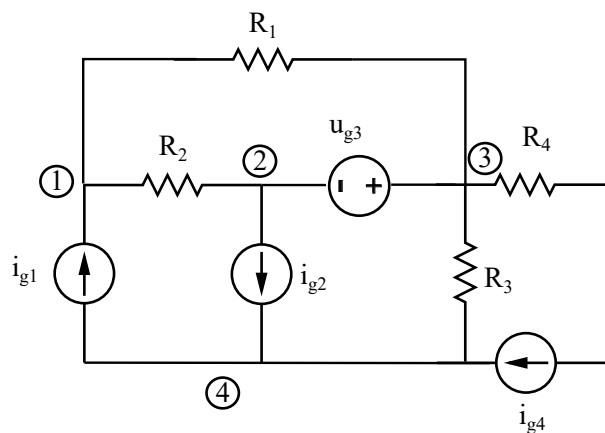Given that the values of the parameters are $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, $R_4 = 4\Omega$, $i_{g1} = 1A$, $i_{g2} = 2A$, $u_{g3} = 3V$, $i_{g4} = 4A$



- Apply nodal analysis to solve the circuit taking 4 as reference node. Write the nodal equations and solve them to find the node voltages (5 points)
- Calculate the power delivered by i_{g4} (2 points)
- Calculate the Thevenin equivalent between nodes 1 and 2 including all the elements of the circuit in the equivalent. Draw the equivalent indicating the values of the parameters (3 points)

Solution

a) Nodal equations:

$$-i_{g1} + \frac{u_1 - u_3}{R_1} + \frac{u_1 - u_2}{R_2} = 0$$

$$\frac{u_2 - u_1}{R_2} + i_{g2} + i_x = 0$$

$$\frac{u_3 - u_1}{R_1} - i_x + i_{g4} + \frac{u_3}{R_3} = 0$$

$$u_3 - u_2 = u_{g3}$$

$$u_1 = -15.33V \quad u_2 = -18V \quad u_3 = -15V \quad i_x = -0.67A$$

b) Power delivered by i_{g4}

$$u_{g4} = -u_3 + u_{R4} = 15 + 16 = 31V$$

$$p_{g4} = u_{g4} \cdot i_{g4} = 31 \cdot 4 = 124W$$

c) Thevenin equivalent:

$$u_{th} = u_1 - u_2 = -15.33 - (-18) = 2.67V$$


$$R_{th} = R_1 || R_2 = 0.67\Omega$$

AC circuits

Given that the values of the parameters are $R_1 = 2$, $R_2 = 3$, $L = 0.2H$, $C = 50mF$

$$u_{g1}(t) = \sqrt{2} \cdot 80 \cdot \cos 10tV$$
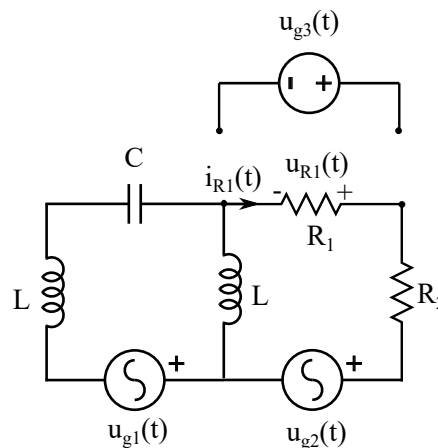
$$u_{g2}(t) = \sqrt{2} \cdot 50 \cdot \cos(10t + 90)V$$



a) Solve the circuit using mesh analysis and calculate the branch currents of the circuit. Write the equations in matrix form and the phasors mesh currents below. (4 points)

b) Do a power balance of the circuit. Write a summary of your results (3 points)

c) If the DC source u_{g3} is connected between the terminals of R_1 . Calculate $u_{R1}(t)$ and $i_{R1}(t)$ with the polarities specified in the circuit. $u_{g3}(t) = 18V$. (3 points)

Solution

a) Circuit in the frequency domain $\omega = 10\text{rad/s}$

$$Z_{R1} = 2\Omega \quad Z_{R2} = 3\Omega \quad Z_L = 2j\Omega \quad Z_C = -2j\Omega \quad \underline{U}_{g1} = 80V \quad \underline{U}_{g2} = 50jA$$

Mesh equations:

$$\begin{pmatrix} Z_L + Z_C + Z_L & -Z_L \\ -Z_L & Z_L + Z_{R1} + Z_{R2} \end{pmatrix} \cdot \begin{pmatrix} \underline{I}_1 \\ \underline{I}_2 \end{pmatrix} = \begin{pmatrix} -\underline{U}_{g1} \\ -\underline{U}_{g2} \end{pmatrix}$$

$$\underline{I}_1 = -16 + 30j = 34\angle 118.07A \quad \underline{I}_2 = -16 - 10j = 18.87\angle -148A$$

b) Power of loads

$$P_{R1} = Z_{R1} \cdot I_2^2 = 712W$$

$$P_{R2} = Z_{R2} \cdot I_2^2 = 1068W$$

$$Q_L = X_L \cdot I_1^2 + X_L \cdot |\underline{I}_1 - \underline{I}_2|^2 = 2312 + 3200 = 5512\text{var}$$

$$Q_C = X_C \cdot I_1^2 = -2312\text{var}$$

$$S_{loads} = P_{R1} + P_{R2} + j \cdot (Q_L + Q_C) = 1780 + 3200jVA$$

Sources:

$$S_{g1} = \underline{U}_{g1} \cdot (-\underline{I}_{g1})^* = 1280 + 2400jVA$$

$$S_{g2} = \underline{U}_{g2} \cdot (-\underline{I}_{g2})^* = 500 + 800jVA$$

$$S_{sources} = S_{g1} + S_{g2} = 1780 + 3200jVA$$

c) As u_{g3} is a DC source we should use superposition principle to analyse the response of the circuit to the sources of different frequencies.

First we turn off the source u_{g3} that becomes a short circuit. Then:

$$u'_{R1} = 0 \quad i'_{R1} = 0$$

Then we turn off sources u_{g1} and u_{g2} and calculate the response of the circuit to u_{g3}

$$u''_{R1} = u_{g3} = 18V \quad i''_{R1} = -u_{R1}/R1 = -9A$$

Response of the three sources acting simultaneously:

$$u_{R1}(t) = u'_{R1} + u''_{R1} = 18V \quad i_{R1}(t) = i'_{R1} + i''_{R1} = -9A$$