


ELECTRICAL POWER ENGINEERING FUNDAMENTALS

FINAL EXAM. ORDINARY CALL (January 10th, 2020)

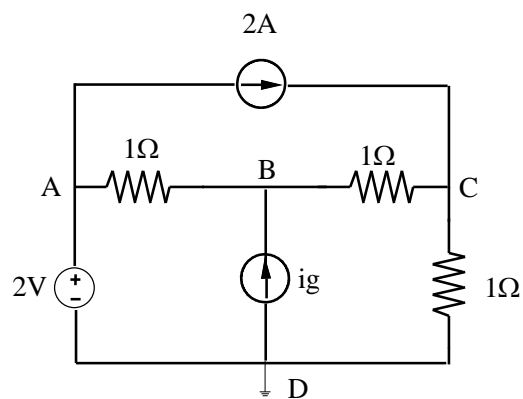Exercise 1

For the circuit below:

- Write the equations for the mesh analysis
- Knowing that the power delivered by the voltage source is 0, calculate i_g
- Calculate the Thevenin's equivalent of the circuit between B and D including all the elements of the circuit in it except the current source i_g .



Solution

- Mesh equations:

$$\text{Mesh 1: } i_1 = 2A$$

$$\text{Mesh 2: } -2 + (i_2 - i_1) + u_x = 0$$

$$\text{Mesh 3: } -u_x + (i_3 - i_1) + i_3 = 0$$

$$\text{Additional equation: } i_3 - i_2 = i_g$$

- Since the voltage source does not supply power $i_2 = 0$. Then the mesh equations can be simplified to:

$$i_1 = 2A$$

$$-2 - i_1 + u_x = 0$$

$$-u_x + 2i_3 - i_1 = 0$$

$$i_3 = i_g$$

Summing equations 2 and 3:

$$-2 - i_1 + 2i_3 - i_1 = 0 \Rightarrow 2i_3 - 6 = 0 \Rightarrow i_3 = i_g = 3A$$

d) We need to remove the source i_g from the circuit to calculate Thevenin's equivalent.

$u_{th} = u_{BD}$ in the resulting circuit.

Applying mesh analysis:

$$i_1 = 2A$$

$$2(i_2 - i_1) + i_2 - 2 = 0$$

Solving

$$3i_2 - 2i_1 - 2 = 0 \Rightarrow i_2 = 2A;$$

The current flowing from A to C is 0; $u_{th} = u_{BD} = u_{CD} = 2V$

To calculate R_{th} we passivize the circuit and calculate $R_{th} = R_{eq_{CD}} = (1+1) \parallel 1 = 2/3 \Omega$

Exercise 2

In the circuit below:

$$u_1(t) = \sqrt{2} \cdot 10 \cdot \cos(100t) \text{ V}$$

$$u_2(t) = \sqrt{2} \cdot 5 \cdot \cos(100t + 90) \text{ V}$$


$$i_3(t) = \sqrt{2} \cdot 10 \cdot \cos(100t + 30) \text{ A}$$

$$R = 5 \Omega; L = 5 \text{ mH}; C = 5 \text{ mF}$$

- Apply nodal analysis to find the nodal voltages $u_A(t)$ and $u_B(t)$
- Do a power balance of the circuit
- We want to add a current source to the circuit, connected between terminals A and B, so that the voltage drop across the resistor R (+ up – down) becomes:


$$u_R(t) = 25 + \sqrt{2} \cdot 7 \cdot \cos(100t - 48) \text{ A}$$

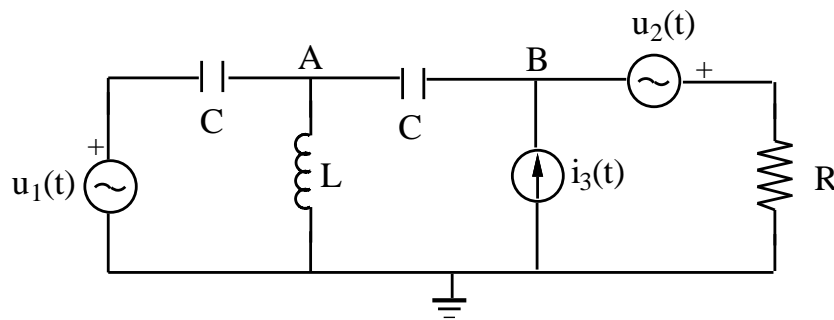Determine the instantaneous value and the polarity of the source.



Solution

- Circuit in the frequency domain:

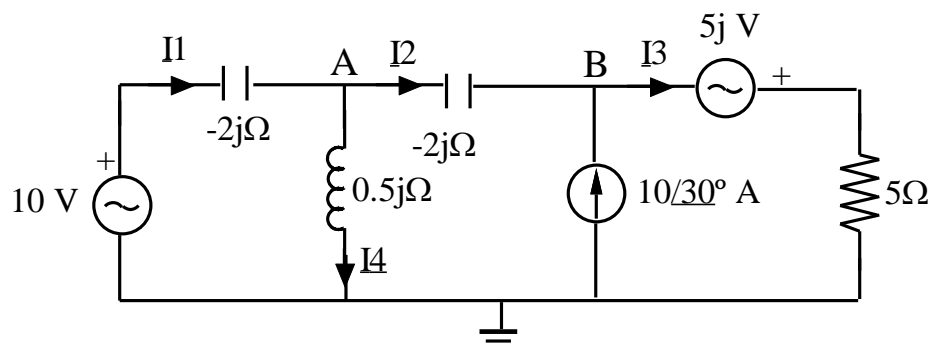

Nodal equations:

(To obtain the equations we could redraw the voltage sources as current sources or find the voltage drop across the impedances that are in series with them)

$$\frac{U_A - 10}{-2j} + \frac{U_A}{0.5j} + \frac{U_A - U_B}{-2j} = 0$$

$$\frac{U_B + 5j}{5} - 10/30 + \frac{U_B - U_A}{-2j} = 0$$

$$\begin{pmatrix} \frac{1}{-2j} + \frac{1}{-2j} + \frac{1}{0.5j} & \frac{1}{2j} \\ \frac{1}{2j} & \frac{1}{-2j} + \frac{1}{5} \end{pmatrix} \begin{pmatrix} U_A \\ U_B \end{pmatrix} = \begin{pmatrix} 5j \\ 10/30 - j \end{pmatrix}$$

Solving:

$$\underline{U}_A = -7.371 + 5.14j = 8.9869 / 145.10^\circ \text{ V}$$

$$\underline{U}_B = 4.74 - 10.28j = 11.32 / -65.24^\circ \text{ V}$$

a) Power balance

Branch currents:

$$\underline{I}_1 = (10 - \underline{U}_A) / (-2j) = 2.57 + 8.68j = 9.06 / 73.51^\circ \text{ A}$$

$$\underline{I}_2 = (\underline{U}_A - \underline{U}_B) / (-2j) = -7.7119 - 6.0565j = 9.81 / -141.86^\circ \text{ A}$$

$$\underline{I}_3 = (\underline{U}_B + 5j) / 5 = 0.95 - 1.06j = 1.41 / -48.09^\circ \text{ A}$$

$$\underline{I}_4 = \underline{U}_A / 0.5j = 10.28 + 14.74j = 17.97 / 55.10^\circ \text{ A}$$

Power absorbed by the passive elements

$$P_R = R \cdot I_3^2 = 10.08 \text{ W}$$

$$Q_L = X_L \cdot I_4^2 = 161.53 \text{ var}$$

$$Q_C = X_C \cdot I_2^2 + X_C \cdot I_1^2 = -356.40 \text{ var}$$

Spower generated by the sources:

$$S_{g1} = \underline{U}_{g1} \cdot \underline{I}_1^* = 25.71 - 86.86j \text{ VA}$$

$$S_{g2} = \underline{U}_{g2} \cdot \underline{I}_3^* = -5.28 + 4.74j \text{ VA}$$

$$S_{g3} = \underline{U}_B \cdot \underline{I}_2^* = -10.35 - 112.76j \text{ VA}$$

Power balance:

$$S_{Tg} = S_{g1} + S_{g2} + S_{g3} = 10.08 - 194.87j \text{ VA} = S_{\text{abs passive}}$$

d) Applying the superposition principle we find that in order to obtain

$$u_R(t) = 25 + \sqrt{2} \cdot 7 \cdot \cos(100t - 48^\circ) \text{ A}$$


We should connect a DC current source of 5A with polarity arrow to the right.

Exercise 3

The following diagram represents a three-phase system which supplies energy to two three-phase loads. Load 1 is Y connected and Load 2 is Δ connected. The impedance per phase of each load is indicated in the diagram. The loads are connected to a generator by means of a distribution line with impedance $Z_{DL} = 3 + j \Omega$.


The phasor line voltage at the load end of the system has a constant value $\underline{U}_{a'b'} = 380 \angle 30^\circ \text{ V}$.

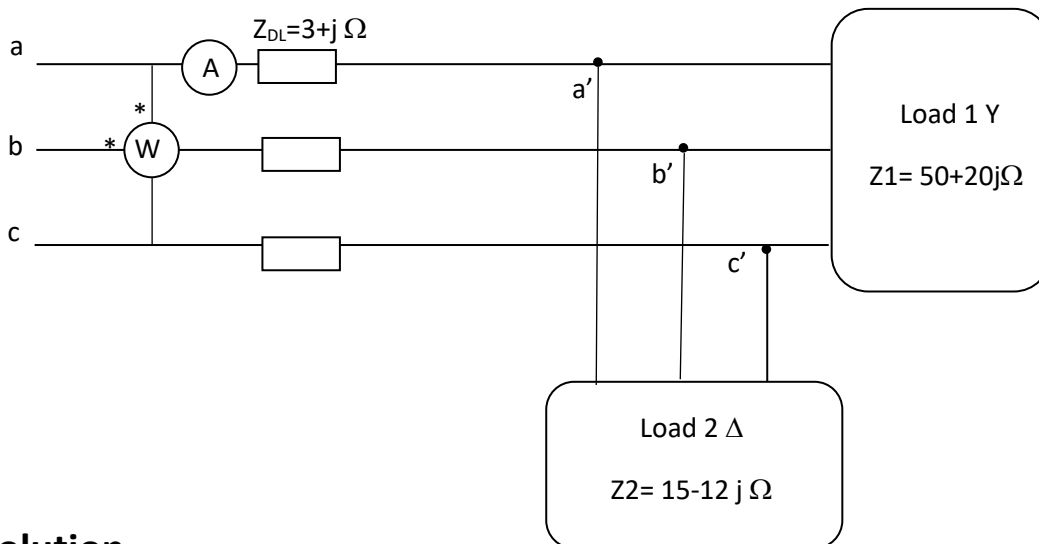- Draw the one-phase equivalent of the system.
- Determine the measure of the ammeter
- Determine the modulus of the line voltage at the generator
- Calculate the active and reactive power absorbed by load 1 and load 2, the power factor of each load and the power factor of the set formed by the two loads.
- Calculate the measure of the wattmeter



Solution

- One phase equivalent

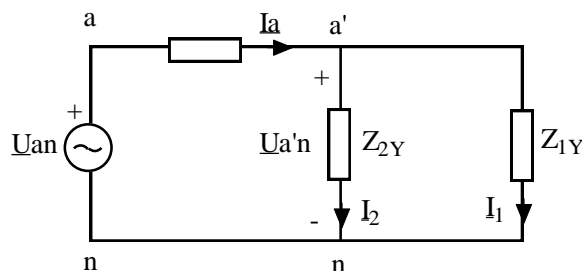

$$Z_{2Y} = 3 - 4j \Omega$$

$$U_{a'n} = 380 / \sqrt{3} = 219.39 \angle 0^\circ \text{ V}$$

- b) To calculate the line current we can associate the two impedances in parallel
 $Z_{eq} = (Z_{1Y} \cdot Z_{2Y}) / (Z_{1Y} + Z_{2Y}) = 5.0442 - 3.2856j = 6.01 \angle -33.05 \Omega$

$$I_a = U_{a'n} / Z_{eq} = 30.54 + 19.89j = 36.44 \angle 33.07 \text{ A}$$

The ammeter measures 36.44 A

Alternatively we could calculate the current flowing through each impedance and sum them to get the total line current:

$$I_1 = U_{a'n} / Z_{1Y} = 4.07 \angle -21.80 \text{ A}$$

$$I_2 = U_{a'n} / Z_{2Y} = 34.26 \angle 38.66 \text{ A}$$

$$I_a = I_1 + I_2 = 36.44 \angle 33.07 \text{ A}$$

- c) $U_{an} = U_{a'n} + (Z_{DL} \cdot I_a) = 291.12 + 90.21j \text{ V} = 304.76 \angle 17.22 \text{ V}$

$$U_L = \sqrt{3} \cdot 304.76 = 527.88 \text{ V}$$

- d) $P_1 = 3 \cdot R_1 \cdot |I_1|^2 = 2484.73 \text{ W}$
 $Q_1 = 3 \cdot X_1 \cdot |I_1|^2 = 993.89 \text{ var}$
 $\text{pf}_1 = 0.93 \text{ ind}$

(The pf can be calculated with the power triangle, the impedance triangle or the phase shift between the current and voltage)

$$I_{2ph} = I_2 / \sqrt{3} = 19.78 \text{ A}$$

$$P_2 = 3 \cdot R_2 \cdot |I_{2ph}|^2 = 17606.2 \text{ W}$$

$$Q_2 = 3 \cdot X_2 \cdot |I_{2ph}|^2 = -14084 \text{ var}$$

$$\text{Pf}_2 = 0.78 \text{ cap}$$

The pf load 1+load 2 can be calculated with the total power, the equivalent impedance or the angle between I_a and $U_{a'n}$

$$\text{pf load 1 and load 2} = 0.84 \text{ cap}$$

- e) The Wattmeter is measuring the reactive power of the system divided by $\sqrt{3}$

$$W = I_b \cdot U_{ac} \cdot \cos(\angle U_{ab} \angle I_c) = I_L \cdot U_L \cdot \cos(90^\circ - \phi) = I_L \cdot U_L \cdot \sin(\phi) = Q_T / \sqrt{3} =$$

$$= (Q_1 + Q_2 + Q_{DL}) / \sqrt{3} = -9107.43 / \sqrt{3} = -5249.67 \text{ W}$$

$$Q_{DL} = 3 \cdot X_{DL} \cdot I_a^2 = 3983.62 \text{ var}$$

Alternatively:

$$\phi = \angle U_{an} - \angle I_a = 17.22^\circ - 33.07^\circ = -15.85^\circ$$

$$W = 527.88 \cdot 36.44 \cdot \cos(90^\circ + 15.85^\circ) = -5253.72 \text{ W}$$