


ELECTRICAL POWER ENGINEERING FUNDAMENTALS

FINAL EXAM. ORDINARY CALL (January 10th, 2020)

Exercise 1

For the circuit below:

- Write the equations for the mesh analysis
- Knowing that the power delivered by the voltage source is 0, calculate i_g
- Calculate the Thevenin's equivalent of the circuit between B and D including all the elements of the circuit in it except the current source i_g .

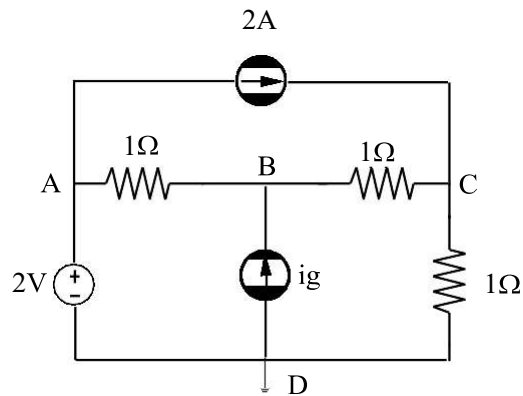

Exercise 2

In the circuit below:

$$u_1(t) = \sqrt{2} \cdot 10 \cdot \cos(100t) \text{ V}$$

$$u_2(t) = \sqrt{2} \cdot 5 \cdot \cos(100t + 90) \text{ V}$$

$$i_3(t) = \sqrt{2} \cdot 10 \cdot \cos(100t + 30) \text{ A}$$

$$R = 5 \Omega; L = 5 \text{ mH}; C = 5 \text{ mF}$$


- Apply nodal analysis to find the nodal voltages $u_A(t)$ and $u_B(t)$



- b) Do a power balance of the circuit
- c) We want to add a current source to the circuit, connected between terminals A and B, so that the voltage drop across the resistor R (+ up – down) becomes:

$$u_R(t) = 25 + \sqrt{2} \cdot 7 \cdot \cos(100t - 48) \text{ A}$$

Determine the instantaneous value and the polarity of the source.

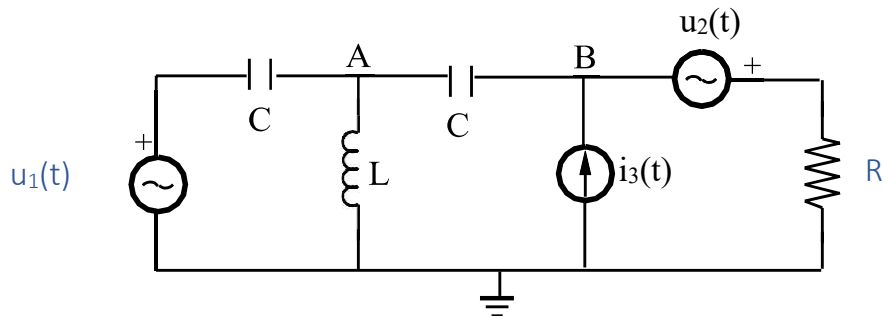

Exercise 3

The following diagram represents a three-phase system which supplies energy to two three-phase loads. Load 1 is Y connected and Load 2 is Δ connected. The impedance per phase of each load is indicated in the diagram. The loads are connected to a generator by means of a distribution line with impedance $Z_{DL} = 3 + j \Omega$.

The phasor line voltage at the load end of the system has a constant value $\underline{U}_{a'b'} = 380 \angle 30^\circ \text{ V}$.

- a) Draw the one-phase equivalent of the system.
- b) Determine the measure of the ammeter
- c) Determine the modulus of the line voltage at the generator
- d) Calculate the active and reactive power absorbed by load 1 and load 2, the power factor of each load and the power factor of the set formed by the two loads.

e) Calculate the measure of the wattmeter

