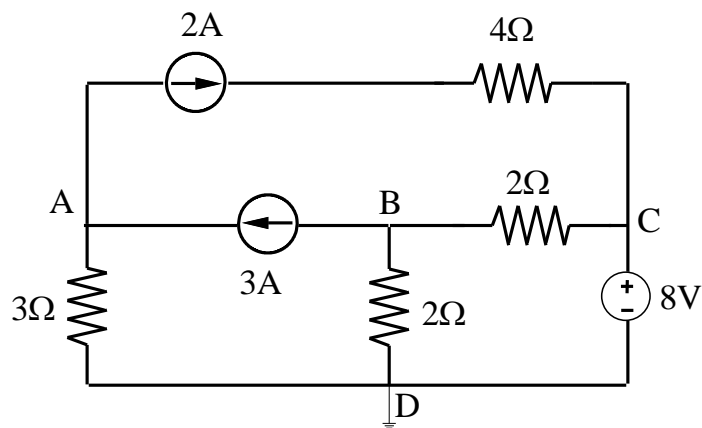


Electrical Power Engineering Fundamentals

DC Exam (18th October 2019)

- Solve the circuit below using mesh analysis and provide a circuit diagram showing the value and direction of the currents that flow through each branch
- Calculate the power balance of the circuit
- Calculate Thevenin's equivalent of the circuit between terminals BD **including all the elements of the circuit in the equivalent**
- Using the results of part c calculate the resistor that connected between B and D extracts the maximum amount of power from the circuit and calculate the power absorbed by the resistor.



Mesh equations:

$$\text{Mesh 1: } i_1 = 2A$$

$$\text{Mesh 2: } u_x + 2 \cdot (i_2 - i_3) + 3 \cdot i_2 = 0$$

$$\text{Mesh 3: } 2 \cdot (i_3 - i_1) + 8 + 2 \cdot (i_3 - i_2) = 0$$

$$\text{Ad eq: } i_1 - i_2 = 3$$

$$\text{Solving } i_1 = 2A; i_2 = -1A; i_3 = -3/2 A; u_x = 2V$$

Branch currents:

$$i_{AC} = 2A$$

$$i_{BA} = 3A$$

$$i_{AD} = 1A$$

$$i_{CB} = 7/2 A$$

$$i_{DC} = 3/2 A$$

$$\text{b) } P_R = \sum R \cdot i^2 = 44W$$

$$p_{8V} = 8 \cdot 3/2 = 12 \text{ W DELIVERED}$$

$$p_{3A} = 3 \cdot 2 = 6 \text{ W DELIVERED}$$

$$p_{2A} = u_x \cdot 2 = 13 \cdot 2 = 26 \text{ W DELIVERED}$$

To calculate u_x we apply 2KL to mesh 1:

$$-u_x + 4 \cdot 2 + 2 \cdot 7/2 - u_x = 0$$

$$u_x = 13V$$

$$p_g = p_{8V} + p_{3A} + p_{2A} = 44W = p_R$$

$$\text{c) } u_{th} = u_B - u_D = 2 \cdot 1/2 = 1V$$

Passivizing the circuit we find that: $R_{th} = 2 \parallel 2 = 1 \Omega$

Alternative: Place a short-circuit between B and D and calculate $i_{sc} = 1A$

$$R_{th} = u_{th} / i_{sc} = 1 \Omega$$

d) The R that absorbs maximum power is $R = R_{th} = 1 \Omega$

Connecting R to the Thevenin's equivalent:

$$i = u_{th} / (R + R_{th}) = 1/2 A$$

$$P = R \cdot i^2 = 1/4 W$$