

Electrical Power Engineering Fundamentals

Third partial exam (16th December 2019)

Note: Please read the questions carefully. All the information you need is written below. No questions will be answered related with the exam solution

Two balanced three phase loads are connected in parallel:


Load 1: Y connected, $S_1= 3000 \text{ VA}$, $\text{pf}_1= 0.4 \text{ ind}$

Load 2: Δ connected $S_2= 1500 \text{ VA}$, $\text{pf}_2= 0.8 \text{ cap}$

The loads are connected to a three-phase generator by means of a transmission line with impedance $3+9j \Omega$. The magnitude of the line voltage at the load end of the line ($A'B'C'$) is 400 V. The system is positive sequence and the frequency is 50 Hz.

Considering $U_{a'n'}$ as phase origin calculate:

- Phasors line current I_{aT} , I_{a1} , I_{a2} (1.5 pt)
- Impedance per phase of load 1 and load 2. (1.5 pt)
- Draw the one phase equivalent of the system (1 pt)
- Phasor U_{BC} and modulus of the voltage drop across the transmission line (1.5 pt)
- Explain how could the **reactive power of the two loads** be measured with one Wattmeter. Draw a diagram of the system indicating the point of the circuit where you need to connect the Wattmeter and the connections of it. Demonstrate your answer with a phasor diagram. Calculate the reading of the Wattmeter (1.5 pt)
- Calculate the active power absorbed in the transmission line and the complex power delivered by the generator(1.5 pt)
- Explain what element or elements should be added to the system and where should they be connected to minimize the complex power absorbed by the transmission line. Calculate the complex power absorbed by the line in that case (The line voltage at $A'B'C'$ remains constant) (1.5 pt)

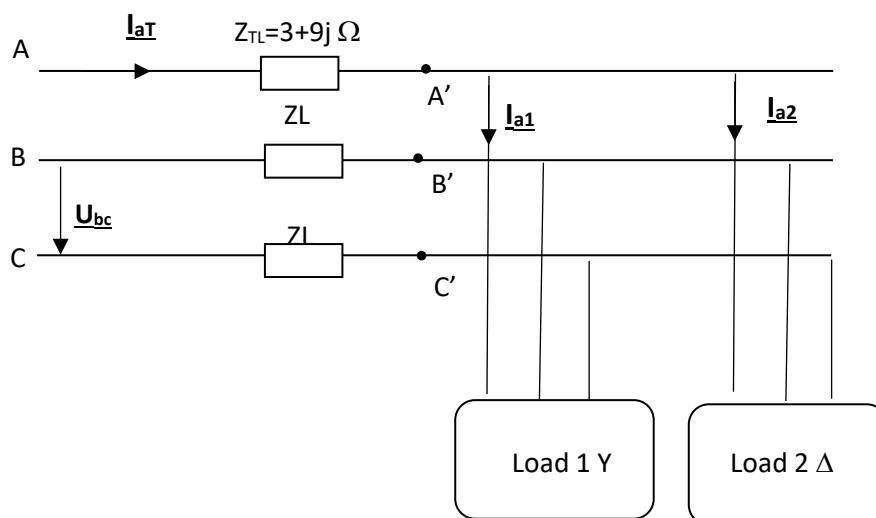

SOLUTION

a) Load 1

$$I_{a1} = S_1 / \sqrt{3} \cdot U_L = 3000 / 400 \cdot \sqrt{3} = 4.33 \text{ A}$$

$$\underline{I_{a1}} = 4.33 / \underline{-\arccos 0.4} = 4.33 / \underline{-66.42} \text{ A}$$

Load 2

$$I_{a2} = S_2 / \sqrt{3} \cdot U_L = 1500 / 400 \cdot \sqrt{3} = 2.165 \text{ A}$$

$$\underline{I_{a2}} = 2.165 / \underline{\arccos 0.8} = 2.165 / \underline{36.87} \text{ A}$$

$$\underline{I_{aT}} = \underline{I_{a1}} + \underline{I_{a2}} = 3.46 - 2.67j = 4.37 / \underline{37.65} \text{ A}$$

b) $Z_{1Y} = \underline{U_{A'N'}} / \underline{I_{a1}} = 21.33 + j 48.88 = 52.85 / \underline{66.42} \Omega$

$$Z_{2Y} = \underline{U_{A'N'}} / \underline{I_{a2}} = 83.32 - 64.11j = 106.72 / \underline{-36.92} \Omega$$

$$Z_{2\Delta} = 3 \cdot Z_{2Y} = 255.95 - 192.33j = 320.16 / \underline{-36.92} \Omega$$

c) The one-phase equivalent includes the Z_{2Y} in parallel with Z_{1Y}

d) $\underline{U_{AN}} = Z_{TL} \cdot \underline{I_{aT}} + \underline{U_{A'N'}} = 266.36 / \underline{4.98} \text{ V}$

$$\underline{U_{BC}} = \sqrt{3} \cdot 266.36 / \underline{4.98 + 30 - 120} \text{ V}$$

Voltage drop across the line

$$\underline{U_{AA'}} = Z_{TL} \cdot \underline{I_{aT}} = 41.46 / \underline{33.94} \text{ V} \Rightarrow \text{Voltage drop} = 41.46 \text{ V}$$

e) The wattmeter should be connected before the two loads, at $A'B'C'$ measuring the current flowing through line and the voltage drop between B' and C' . In this situation the Wattmeter measures:

$$W = U_L \cdot I_{aT} \cdot \cos(90^\circ - \varphi) = U_L \cdot I_{aT} \cdot \sin(\varphi) = (Q_1 + Q_2) / \sqrt{3}$$

$$Q_1 = S_1 \cdot \sin(\varphi_1) = 2791.5 \text{ var}$$

$$Q_2 = -S_2 \cdot \sin(\varphi_2) = -900 \text{ var}$$

$$W = 1849.5 / \sqrt{3} = 1067.8 \text{ W}$$

f) $P_{TL} = 3 \cdot R_{TL} \cdot I_{aT}^2 = 171.90 \text{ W}$

$$(Q_{TL} = 3 \cdot X_{TL} \cdot I_{aT}^2 = 515.71 \text{ W}$$

$$S_g = 3 \cdot \underline{U_{AN}} \cdot \underline{I_{aT}}^* = 2569.1 + 2365.5j = 3492.3 / \underline{42.64} \text{ VA}$$

g) We have to compensate the reactive power of load 1 and load 2 so the total line current drops and the losses in the transmission line drop too. To do so we connect a battery of capacitors in Δ before the loads, in A', B', C'.

$$Q_C = -(Q_1 + Q_2) = -1849.5$$

$$Q_{C\Delta} = -3 \cdot \omega \cdot C_{\Delta} \cdot U_L^2$$

$$C_{\Delta} = -Q_{C\Delta} / 3 \cdot \omega \cdot U_L^2 = 1849.5 / 3 \cdot 2 \cdot \pi \cdot 400^2 = 1.23 \cdot 10^{-5} \text{ F}$$

$$I_L' = P' / \sqrt{3} \cdot U_L = 2400 / \sqrt{3} \cdot 400 = 3.46 \text{ A}$$

$$P' = P = S_1 \cdot \text{pf}_1 + S_2 \cdot \text{pf}_2 = 1200 + 1200 = 2400 \text{ W}$$

$$P_{TL}' = 3 \cdot R_{TL} \cdot I_L'^2 = 107.99 \text{ W}$$

$$Q_{TL}' = 3 \cdot X_L \cdot I_L'^2 = 323.98 \text{ var}$$

$$S_{TL}' = 107.99 + j 323.98 \text{ VA}$$