

Unit 3. Analog CMOS fundamental circuits


System-on-Chip and efficient electronic circuit integration techniques

Carlos III University of Madrid, Spain
Electronics Technology Department

- 1. Current sinks/sources**
- 2. Current mirrors**
- 3. Examples of current mirrors**
- 4. Switches and active resistors**
- 5. References of currents and voltages**


1. Current sinks/sources

➤ Current sink

 

Simple designs

➤ Current source

 


$r_{out} = \frac{1}{\lambda I_D} \rightarrow$ channel modulation




Reducing v_{min} (current sink) and increasing V_{max} are required

1. Current sinks/sources

- How to increase the output resistance?

 


$$r_{out} \approx g_m r_{ds} R$$

 

$$r_{out} \approx g_{m2} r_{ds2} r_{ds1}$$

2. Current mirrors

- Basic structure:

 

$$i_{out} = \frac{W/L|_{M2}}{W/L|_{M1}} I_{in} \quad r_{out} = r_{ds2}$$

- A current mirror takes the current from one branch (I_{in}) and copies it into the other one (i_{out}) considering the size ratio between M_1 and M_2 .

- Error sources in the ratio i_{out}/I_{in} :

- Channel modulation:

$$\frac{i_{out}}{I_{in}} = \frac{W/L|_{M2}}{W/L|_{M1}} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

Different V_{DS} will suppose different current ratio

- Short channel devices → higher error.

Solution? → Increasing r_{out} .

2. Current mirrors

- Error sources in the ratio i_{out}/I_{in} :
 - V_T variation:
 - Two devices placed close in layout → maximum V_T variation of 10 mV.
 - Oxide gradients may suppose variations in the μC_{ox} product.

$$\frac{i_{out}}{I_{in}} = \frac{W/L|_{M2}}{W/L|_{M1}} \cdot \left(\frac{V_{GS} - V_{th2}}{V_{GS} - V_{th1}} \right)^2$$


Error term

- The higher the current I_{in} the lower the error.
- Aspect ratio between the devices in layout:
 - For W and $L > 10 \mu m$ → error negligible.
 - Symmetric designs interleaving devices minimize differences in the aspect ratio.

 
2. Current mirrors

➤ How to increase the output resistance?


- Current mirror with cascode: $r_{out} = r_{ds2} + r_{ds4} + g_{m4}r_{ds4}r_{ds2}$



 
minimum V_{out} to have no dependence between i_{out} and V_{out}



 - Current mirror with cascode and higher V_{out} variation possible:



 
minimum V_{out} to have no dependence between i_{out} and V_{out}



 2. Current mirrors


➤ How to increase the output resistance?

- Wilson current mirror: $r_{out} \approx r_{ds3} + r_{ds2} \frac{1 + r_{ds3}g_{m3} + g_{m1}r_{ds1}g_{m3}r_{ds3}}{1 + g_{m2}r_{ds2}}$



$$r_{M2} = \frac{r_{ds2}}{1 + g_{m2}r_{ds2}}$$

 
- Degenerated current mirror: $r_{out} \approx g_{m2}r_{ds2}R_o$




Higher output swing because we have one single device at the output stage.

2. Current mirrors

- Regulated current mirror:

 

 
$$r_{out} \approx g_{m1}g_{m3}r_{ds1}r_{ds2}r_{ds3}$$



$$r_{out} \approx g_{m3}(1 + A)r_{ds3}r_{ds2}$$

 2. Current mirrors

- Degenerated current mirror: $r_{out} \approx g_{m2}r_{ds2}R_o$




Higher output swing because we have one single device at the output stage.

Tips for current mirror design:


- Increasing output resistance r_{out} .
- The higher the current the less error due to V_T .
- The bigger the devices the less error due to aspect ratio.
- Longer $L \rightarrow$ less error due to channel modulation.
- To minimize the error due to $V_T \rightarrow$ multiple W/L aspect ratios.
- Symmetric layout designs.

3. Examples of current mirrors

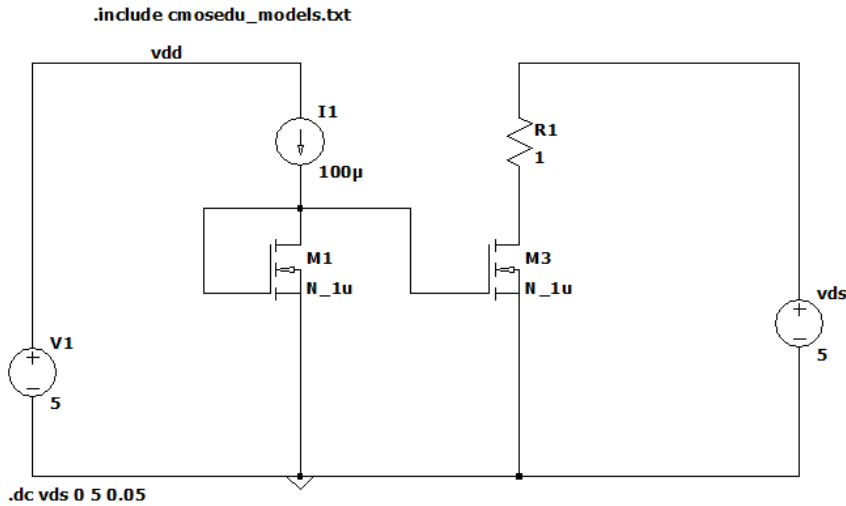


$$V_{GS} = 1.42 \text{ V}, V_T = 0.8 \text{ V}$$

 
$$V_{\min} = V_{ON} = 1.42 - 0.8 = 0.62 \text{ V}$$




3. Examples of current mirrors

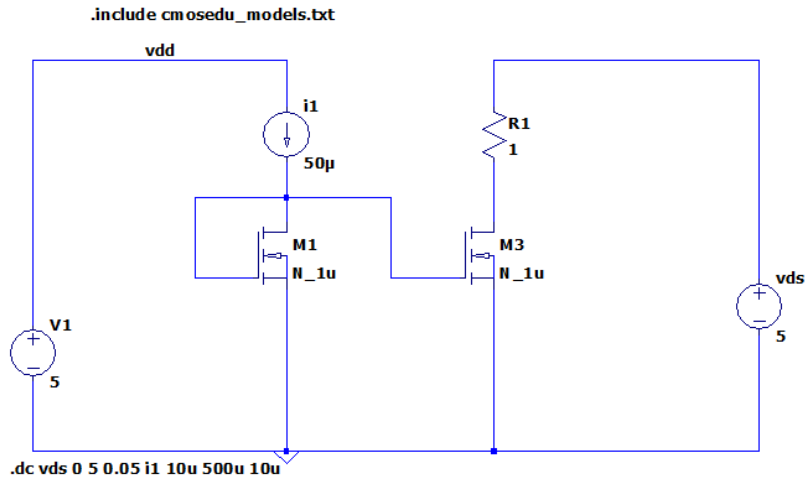

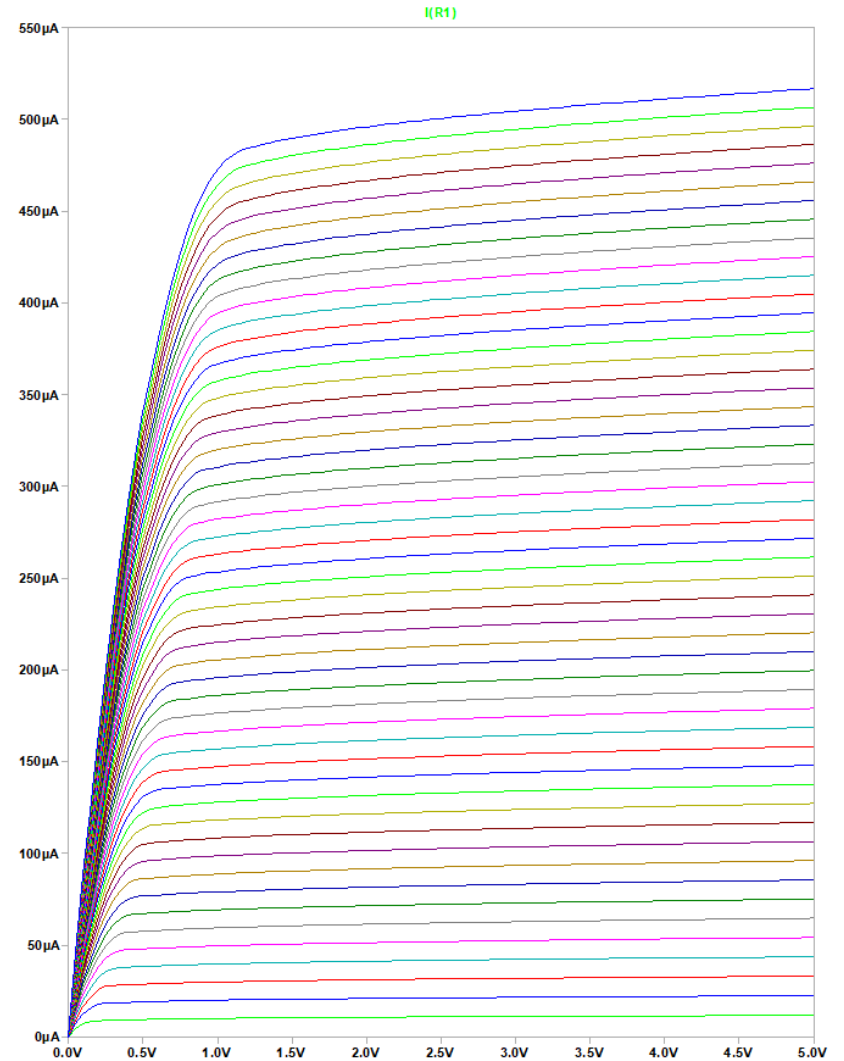The lower the current the lower the required V_{ON}




3. Examples of current mirrors

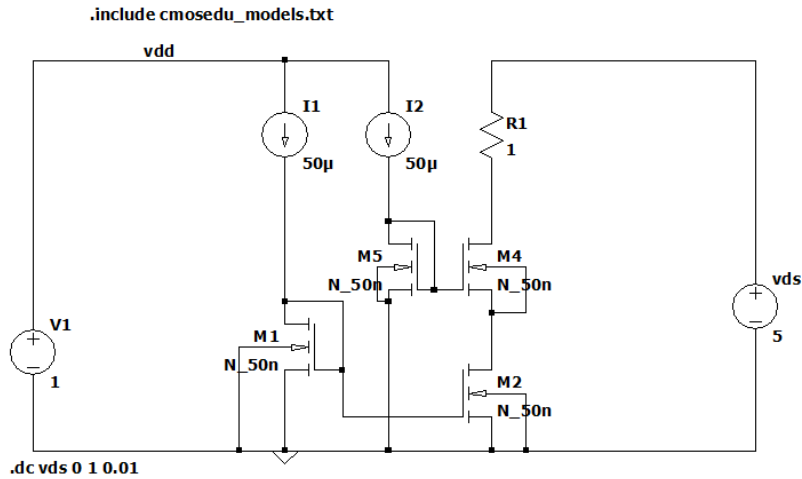


$$V_{GS} = 0.4 \text{ V}, V_T = 0.28 \text{ V}$$
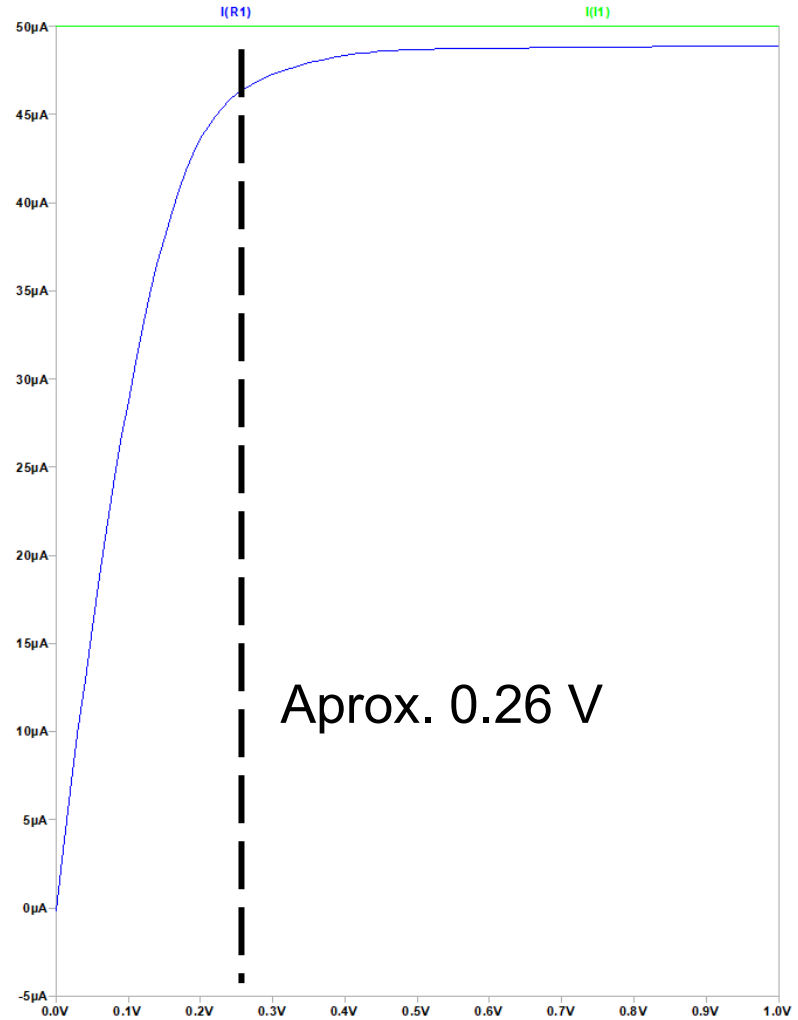
$$V_{\min} = 2 * V_{ON} = 0.24 \text{ V}$$




3. Examples of current mirrors

Plot $I_s(m1)$ and $I_s(m2)$

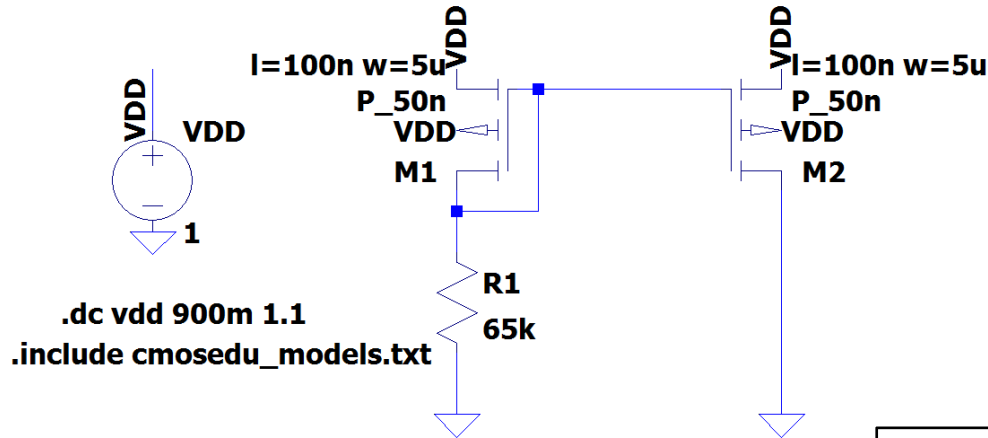


Error current due to channel modulation

 


3. Examples of current mirrors

$$I_{ref} = 20 \mu A$$

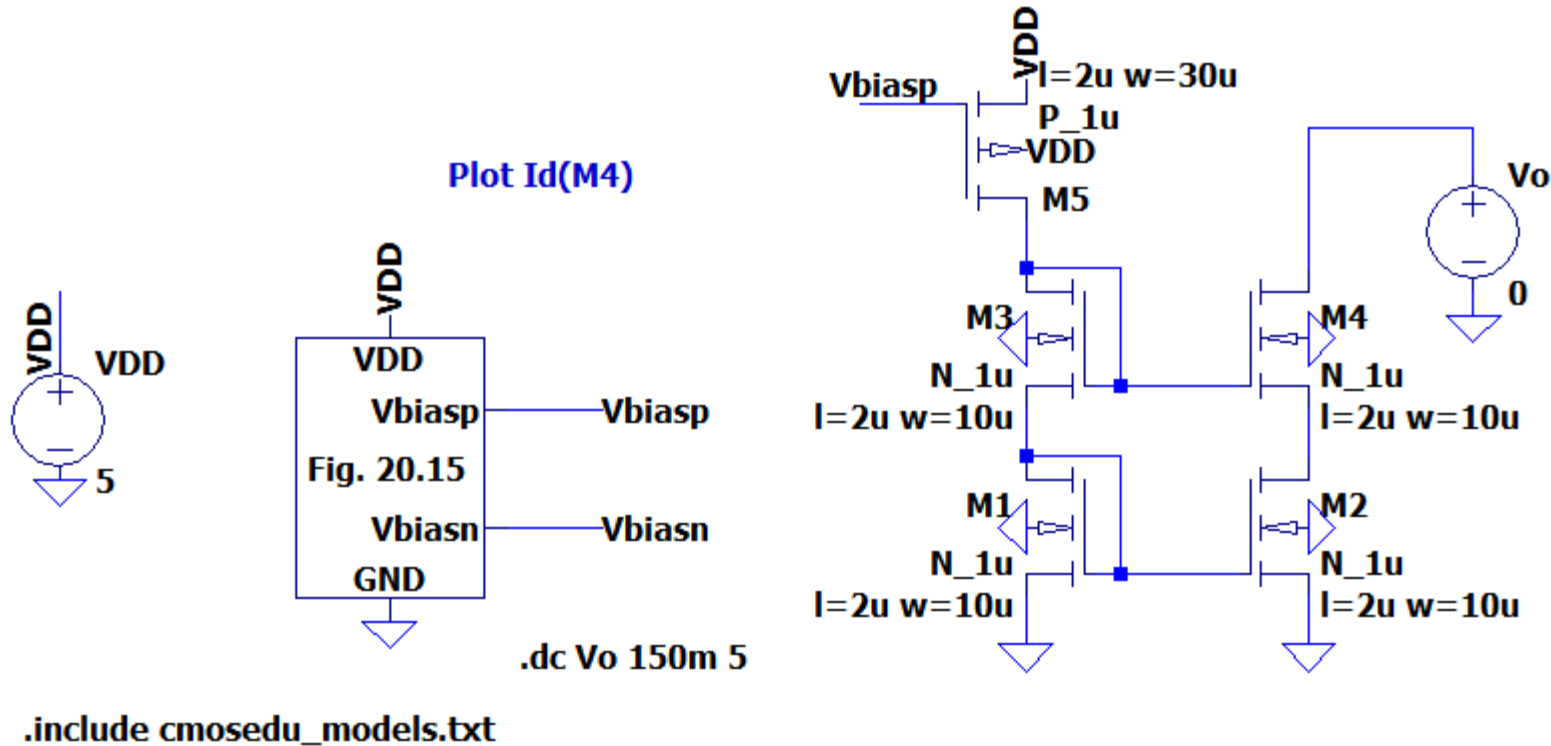

All transistors have the same size, and therefore the same V_T and $V_{DS,sat} \rightarrow V_{GSi} = V_{DS,sat} + V_T$
 $V_{G3} = V_{G4} = V_{GS3} + V_{GS1} = 2V_{DS,sat} + 2V_T \rightarrow V_{DS2} = V_{G4} - V_{GS4} = V_{DS,sat} + V_T$ (V_T more than needed!!!)
 The minimum V_o to set M4 in sat is: $V_{o,min} = V_{DS2} + V_{DS,sat} = 2V_{DS,sat} + V_T = 1.3V$

3. Examples of current mirrors

 


We need a minimum voltage of 1.3V!

3. Examples of current mirrors




$I_{ref} = 10 \mu A$

All transistors are equally sized

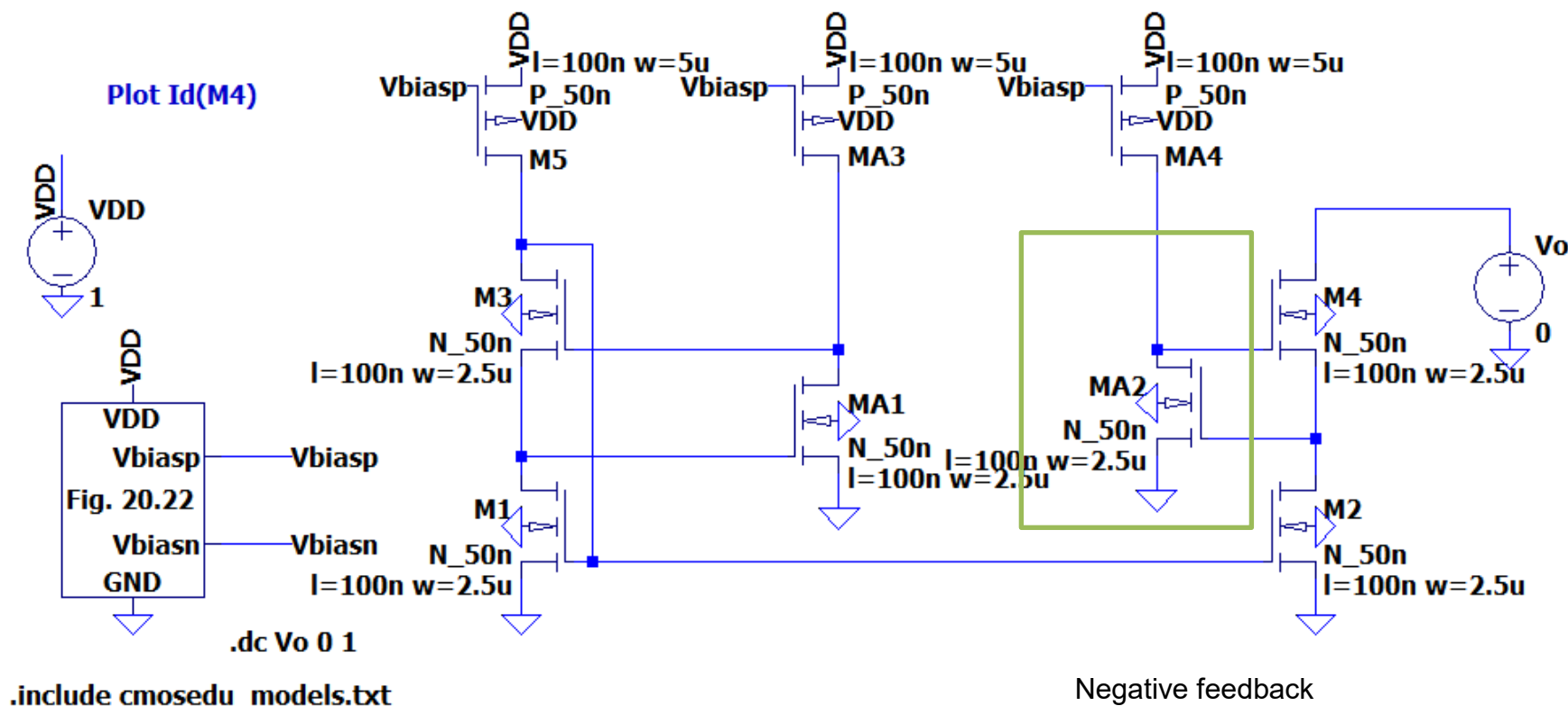


3. Examples of current mirrors

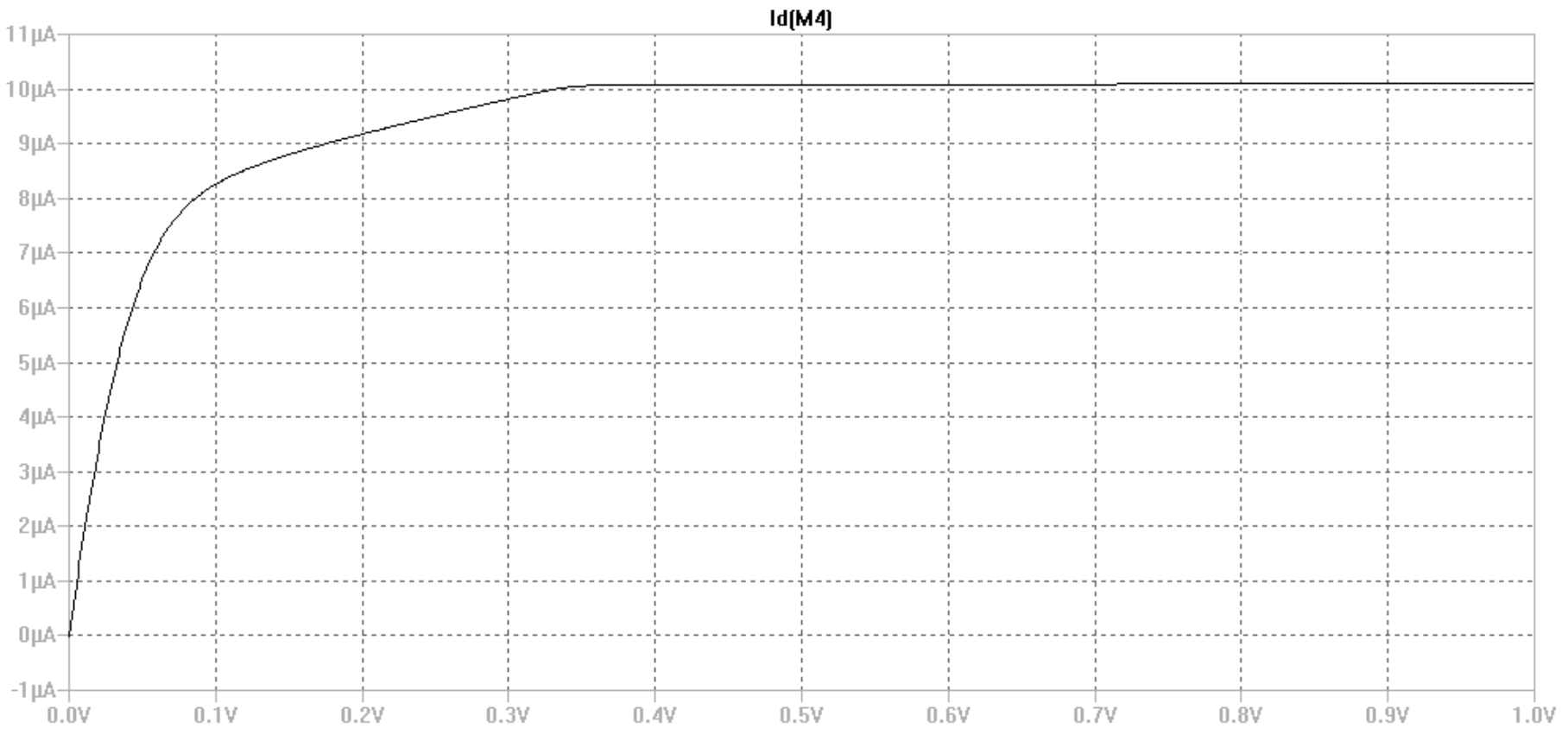

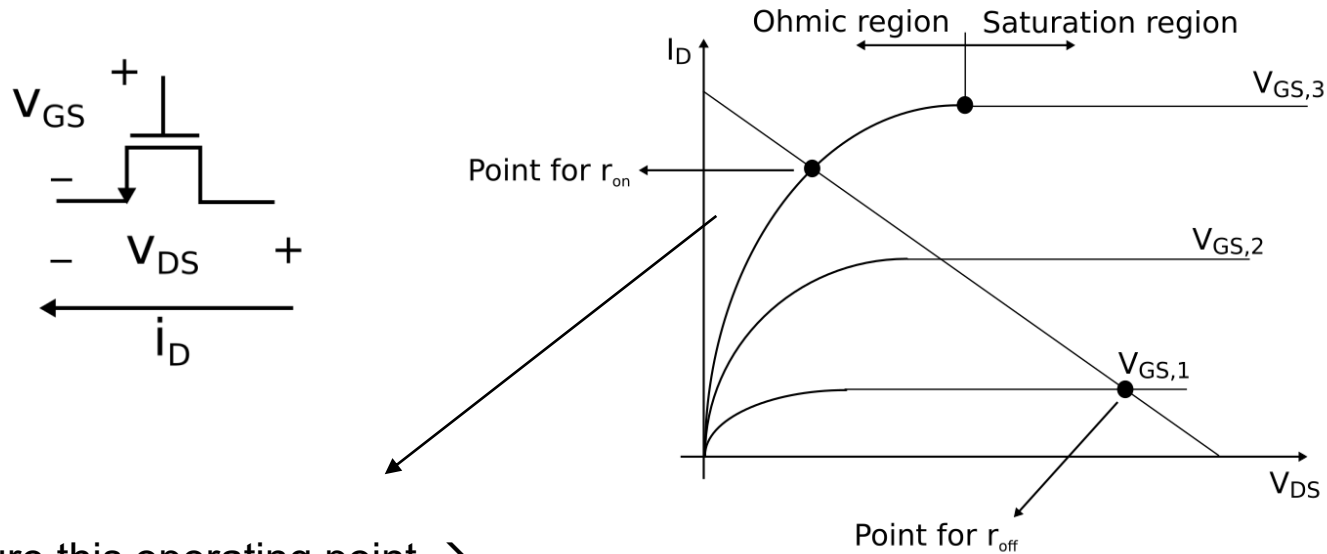4. Switches and active resistors

- MOS devices can be used to implement switches




To ensure this operating point →
 $|V_{GS}| \gg |V_{DS}|$

$$i_D = C_{ox} \mu_n \frac{W}{L} \left(V_{GS} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS} \rightarrow r_{ON} = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{C_{ox} \mu_n \frac{W}{L} (V_{GS} - V_{th} - V_{DS})}$$

Variable R_{ON}

 
4. Switches and active resistors

- Enhanced version to increase analog dynamic range:





$$r_{ON,N} = \frac{1}{C_{ox}\mu_n \frac{W}{L_N} (V_{DD} - V_{th,n} - V_{IN})}$$
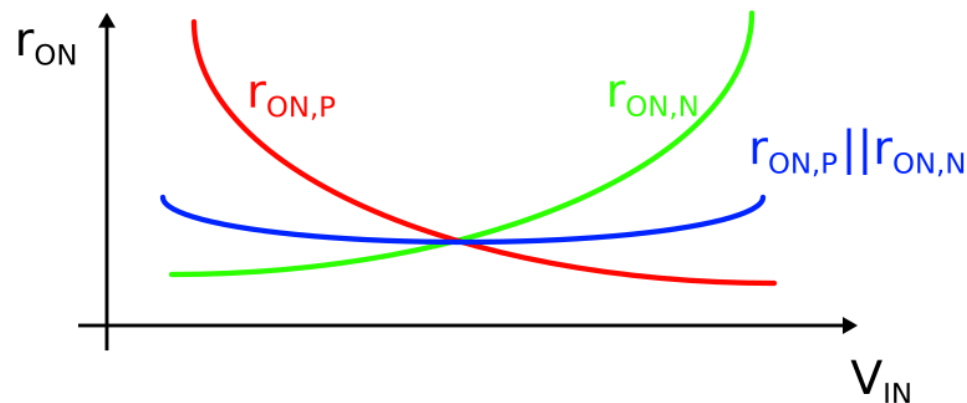
$$r_{ON,P} = \frac{1}{C_{ox}\mu_p \frac{W}{L_P} (V_{IN} - V_{th,p})}$$




  4. Switches and active resistors

- Active resistor: connecting the gate to the drain:



 
$$R_{eq} = \frac{1}{g_m + g_{mb} + 1/r_o} \approx \frac{1}{g_m}$$



Non-linearity is mitigated by restricting V_{DS} variations.

 5. Reference of currents and voltages

- Independent of power supply and temperature.




This voltage strongly depends on $V_{DD} \rightarrow$ not a good reference.

- How to improve it? \rightarrow We may use the pn junction of a BJT device:


$$V_{REF} \approx \frac{kT}{q} \ln \frac{V_{DD}}{RI_S}$$

V_{DD} sensitivity less than one.

 

 5. Reference of currents and voltages

- Power-supply independent current reference:



Bibliography

- Allen, P. E., & Holberg, D. R. (2002). CMOS analog circuit design. New York: Oxford University Press.
- R. Jacob Baker. 2010. CMOS Circuit Design, Layout, and Simulation (3rd. ed.). Wiley-IEEE Press.

Simulations are performed through software LTSPice, provided courtesy of Analog Devices and authored by Mike Engelhardt.

Spice models of transistors come from <http://cmosedu.com/>, website maintained by R. Jacob Baker.