


Unit 5. Operational amplifiers (opamps) and OTAs

System-on-Chip and efficient electronic circuit integration techniques


Carlos III University of Madrid, Spain
Electronics Technology Department

- 1. Basic concepts**
- 2. Compensation techniques**
- 3. Two-stage architecture design**
- 4. Cascode structures**
- 5. Symmetric CMOS OTA**
- 6. Output stages**
- 7. CMFB circuits**
- 8. Examples**


1. Basic concepts

 

 Very large $G \rightarrow$ gain fixed when negative feedback \rightarrow stability?




 
If R_{out} must be small, we need an output stage (buffer) \rightarrow output voltage \rightarrow opamp (classic definition of an operational amplifier)



If R_{out} must be high, we do not need an output stage (unbuffered) \rightarrow output current \rightarrow OTA (operational transconductance amplifier), they only feed capacitive loads or very high resistances

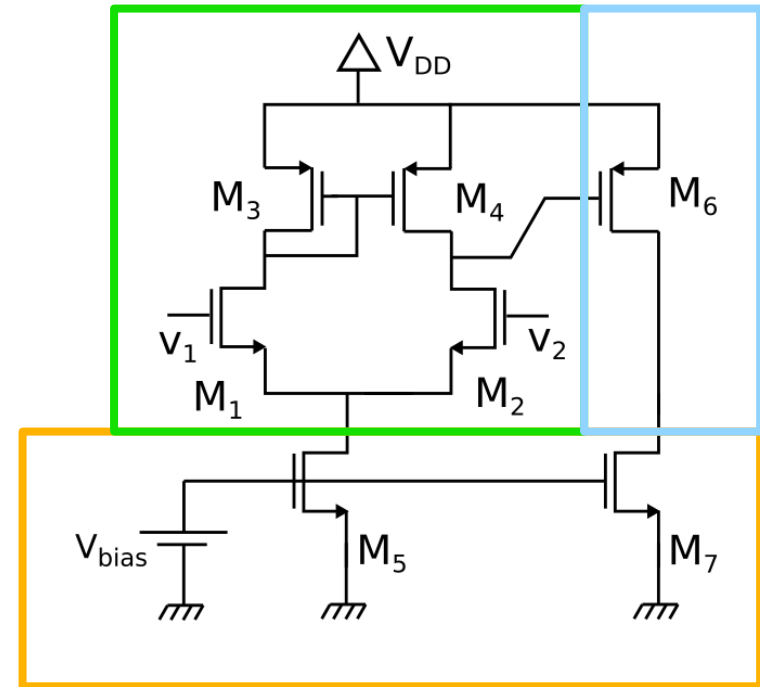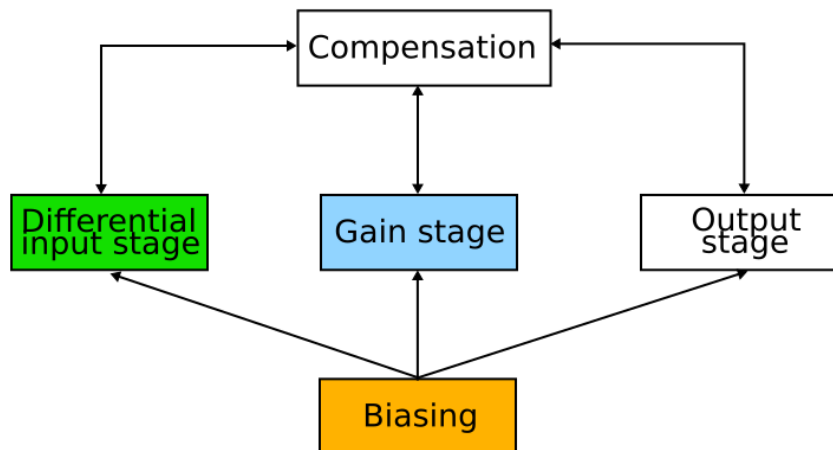1. Basic concepts

- Most of the opamps make use of two or more stages to have enough gain, especially with deep-submicron processes.
- General scheme:



1. Basic concepts

- Requirements for opamp design:

1. Constraints due to the process selected:

- ☐ Process specifications (V_{th} , intrinsic gain, C_{ox} , ...).
- ☐ Nominal voltage supply.
- ☐ Maximum current.
- ☐ Temperature range.

2. Design requirements:

- ☐ Gain.
- ☐ GBW.
- ☐ Maximum power.
- ☐ SR.
- ☐ ICMR.
- ☐ CMRR.
- ☐ PSRR.
- ☐ Output swing.
- ☐ Output resistance.
- ☐ Noise.

Architecture optimization



Idea conception

- Design steps:
 1. Select suitable architecture.
 2. Select compensation technique to be implemented.
 3. Architecture desing: devices' size and bias conditions.
 4. Validation and tuning through simulations


$$PSRR = 20 \log_{10} \frac{\Delta V_{DD} A_V}{\Delta V_{out}}$$

1. Basic concepts

- Opamp stability:

  


$$\frac{A_V(s)}{1 + A_V(s)F(s)}$$

 

To avoid ringing at the output a phase margin higher than 45° is required (**preferably 60°**)

 
2. Compensation techniques

- General structure of a two-stage opamp:




$$p_1 = \frac{-1}{R_1 C_1} \quad p_2 = \frac{-1}{R_2 C_2}$$

 The open-loop frequency response of a negative-feedback loop using an uncompensated opamp and a feedback factor of $F(s)=1$.



2. Compensation techniques

- Miller compensation:

 

$$p'_1 = \frac{-1}{g_{m2}R_1R_2C_c} < p_1 \longrightarrow \text{First pole is shifted to a lower frequency. DC gain remains.}$$

$$p'_2 \approx \frac{-g_{m2}}{C_2} > p_2 \longrightarrow \text{Second pole is shifted to a higher frequency. Phase margin increases.}$$

$$C_2, C_c \gg C_1 \quad z_1 \approx \frac{g_{m2}}{C_c} \longrightarrow \text{A positive extra zero is added. Phase margin may be degraded.}$$


$$GBW \approx g_{m1}/C_c$$

Recipe: If $z_1 = 10 \cdot GBW$:

- $P_2 = 1.2 \cdot GBW \rightarrow MF = 45^\circ$
- $P_2 = 2.2 \cdot GBW \rightarrow MF = 60^\circ$
 $\rightarrow C_c = 0.22 \cdot C_2$

 2. Compensation techniques



- Miller compensation: now we have a **positive zero** that might limit **GBW** → it can be compensated with a resistor.




With the resistor we can control the zero frequency. Two options:

1. Remove the zero → $R_z = 1/g_{m2}$.
2. Make the zero frequency equal to the second pole frequency → $R_z = \frac{C_C + C_2}{C_C} \frac{1}{g_{m2}}$.

- Another way?

  


 If R_2 is decreased the second pole frequency will increase.




2. Compensation techniques

- Feedforward compensation:

 


 A negative extra zero is added \rightarrow positive phase shift \rightarrow phase margin is improved



Compensation technique used in common-drain configurations $\rightarrow C_C$ is designed to be a short-circuit at high frequencies.

3. Two-stage architecture design

 

Some tips:

- Gain defined by gm_1 , gm_2 , gm_6 and bias currents.
- GBW defined by I_5 , gm_1 and gm_2 .
- Slew-rate defined by I_5 .

4. Cascode structures


- Two-stage opamp might have either limited gain or bandwidth. Additionally, PSRR is low
→ cascode-based configurations.
 1. Cascode structure in the first stage.
 2. Cascode structure in the second stage.
 3. Folded-cascode structure.
- Two-stage opamp → how to increase the gain?
 1. Increase the number of stages → higher instability.
 2. Increase g_m in the first or in the second stage.
 3. Increase r_{out} in the first or in the second stage.

The third option is more energy efficient because the bias currents are decreased.

- Cascode structures → especially suitable for capacitive loads.

4. Cascode structures

1. Cascode structure in the first stage.

 


$$A_v = g_{m1} r_{out}$$

$$r_{out} \approx (g_{m4} r_{o4} r_{o2}) \parallel (g_{m6} r_{o6} r_{o8})$$

$$p_1 \approx \frac{1}{r_{out} C_L} \quad GBW = \frac{g_{m1}}{C_L}$$

4. Cascode structures

 1. Cascode structure in the first stage with enhanced r_{out} .




$$A_v = g_{m1} r_{out}$$

$$r_{out} \approx (A g_{m4} r_{o4} r_{o2}) \parallel (A g_{m6} r_{o6} r_{o8})$$

The gain stage can be implemented with a simple common-source configuration

4. Cascode structures

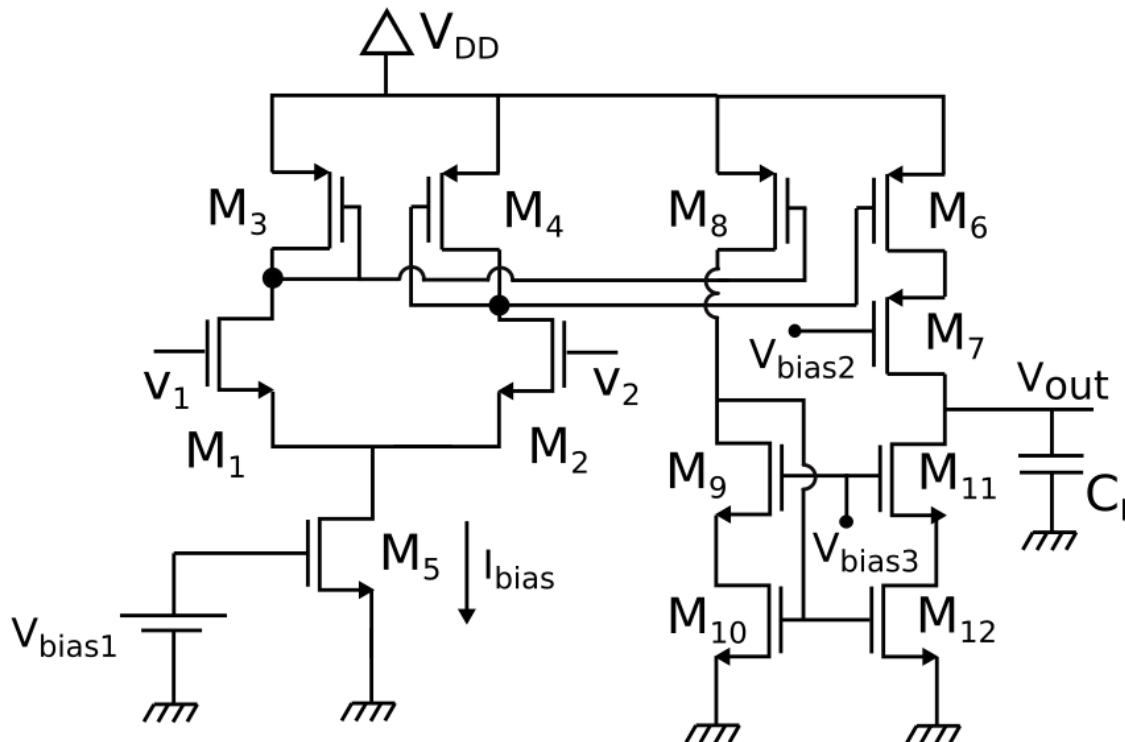2. Cascode structure in the second stage.



$$A_v = g_{m1} k r_{out}$$

$$k = g_{m8}/g_{m3} = g_{m6}/g_{m4}$$



$$r_{out} \approx (g_{m11} r_{o11} r_{o12}) ||$$

$$|| (g_{m7} r_{o7} r_{o6})$$

The pole of the first stage is located at high frequencies.

4. Cascode structures

3. Folded-cascode structure.

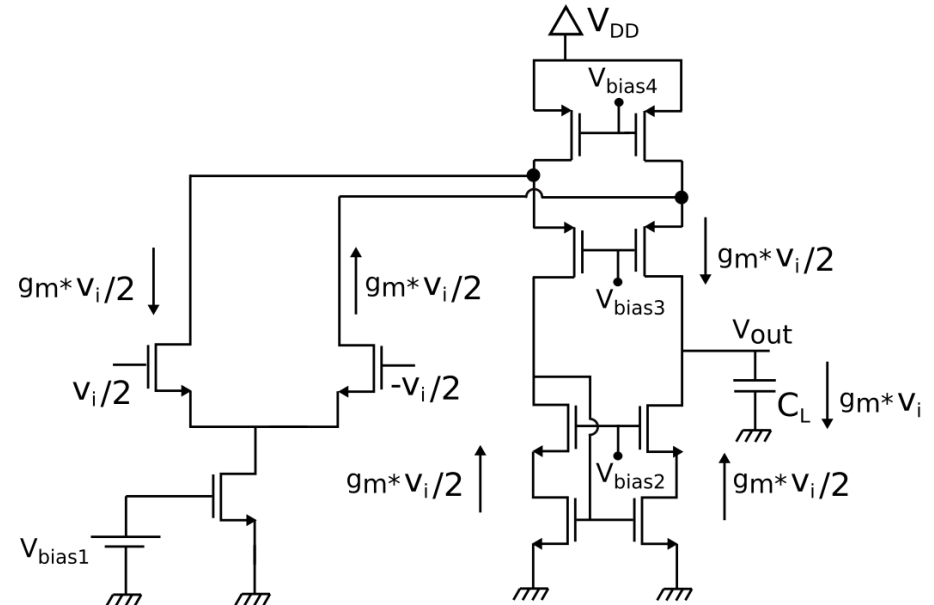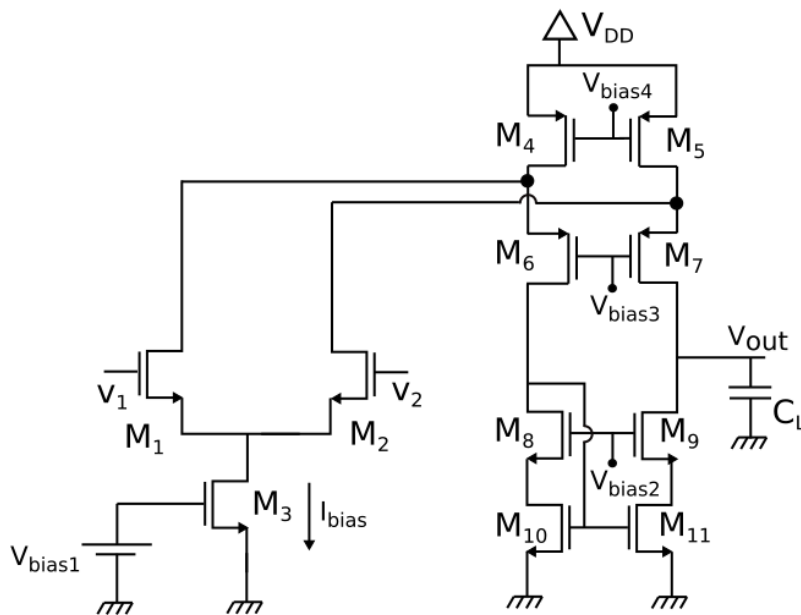

In practice, making all the PMOS and NMOS equal, respectively

$$r_{out} \approx (g_{m9}r_{o9}r_{o11}) || (g_{m7}r_{o7}(r_{o5} || r_{o2}))$$

$$A_v = g_{m1}r_{out} \longrightarrow \text{Maximum achievable gain} \longrightarrow A_v \approx \frac{3}{4} g_{m1}r_{out}$$

Self-compensated \rightarrow suitable for high frequency

High ICMR

[illegible]


$$\text{BW} = \frac{1}{2\pi R_{\text{out}} C_L} \quad \text{GBW} = \frac{\mathbf{B}g_{m1}}{2\pi C_L}$$

- Improved gain due to current amplification **B**.
- For wide-band performance \rightarrow high-speed current amplifiers with large overdrive voltage ($V_{GS}-V_{th}$) and small L.

17

 6. Output stages

- All the structures seen till now have a very high output resistance (in the range of dozens of kΩs) → they only feed moderate capacitive loads and high resistances.
- If we need to feed either high capacitive loads (dozens of pFs) or low resistances (100 Ω) → we need a low output resistance → output stage required.
- Conventional source follower:





Source follower

$$A_v = \frac{g_{m1} + g_{m2}}{g_{m1} + g_{m2} + r_{o1} + r_{o2}} \approx 1$$

$$r_{out} \approx \frac{1}{g_{m1} + g_{m2}}$$

AB class → lower power consumption

7. CMFB circuits

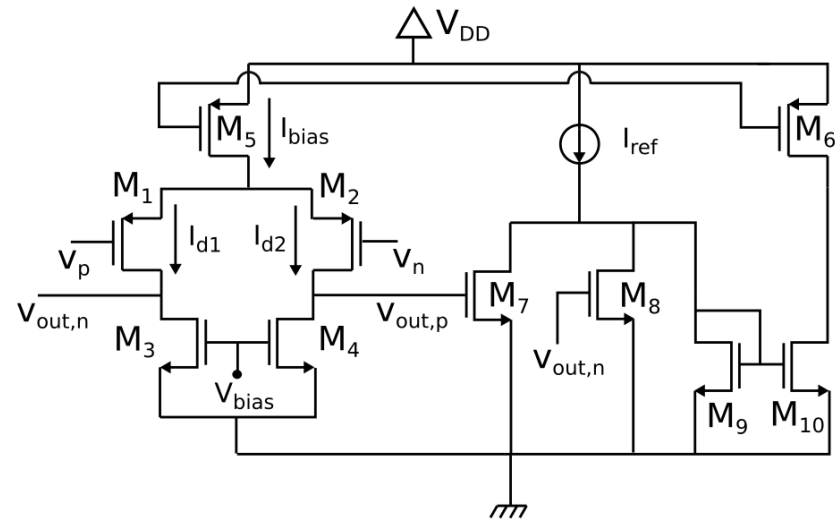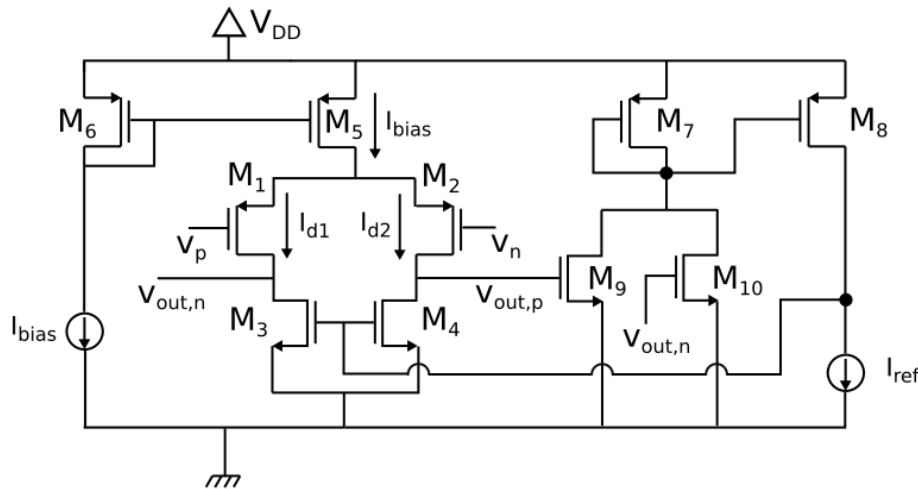


Three tasks:

1. Measure the output voltages.
2. Cancel out the differential signals.
3. Close the CMFB loop.

- CMFB circuit → **unitary gain**.
- It measures the output signal and removes differential component.
- Close-loop feedback → stability issues.
- **CMFB's bandwidth > opamp's bandwidth**.
- It should consume less power than the opamp itself.

8. Examples


- Folded cascode OTA (1 μm):

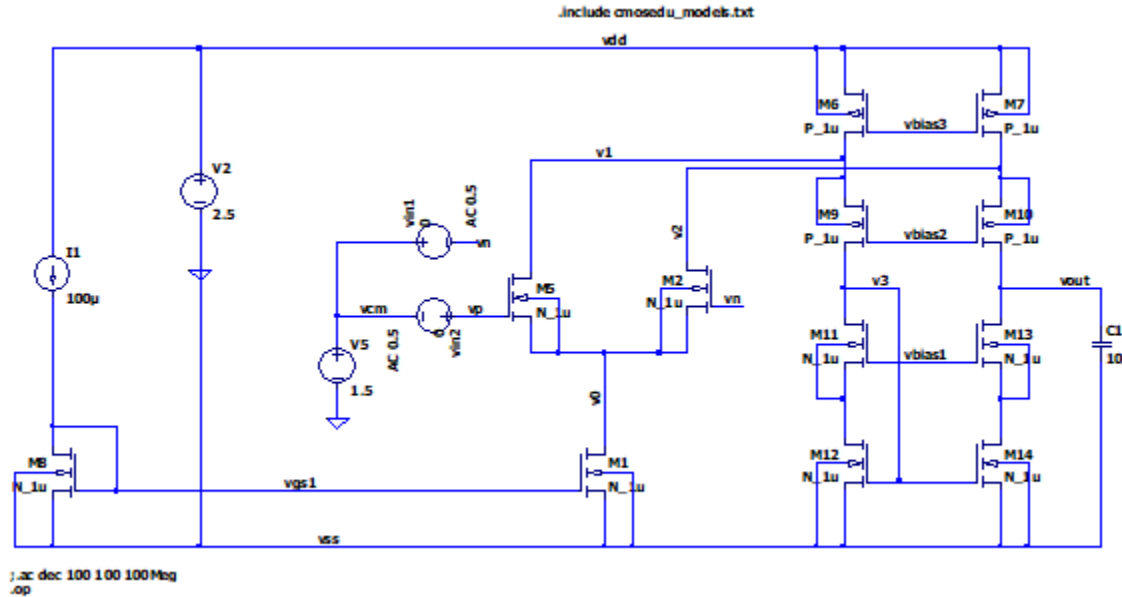

```

--- Operating Point ---
V(v2):      2.22352      voltage
V(vn):      1.5         voltage
V(v0):      0.610514    voltage
V(v1):      2.22352    voltage
V(vp):      1.5         voltage
V(vdd):     2.5         voltage
V(vcm):     1.5         voltage
V(vgs1):    1.38518     voltage
V(vbias3):  1.35        voltage
V(vbias2):  1.11        voltage
V(v3):      1.0617      voltage
V(vout):    1.0617      voltage
V(vbias1):  1.3         voltage
V(n001):    0.240131    voltage
V(n002):    0.240131    voltage



```

 

Self-compensated

8. Examples

- Folded cascode OTA (1 μm):

 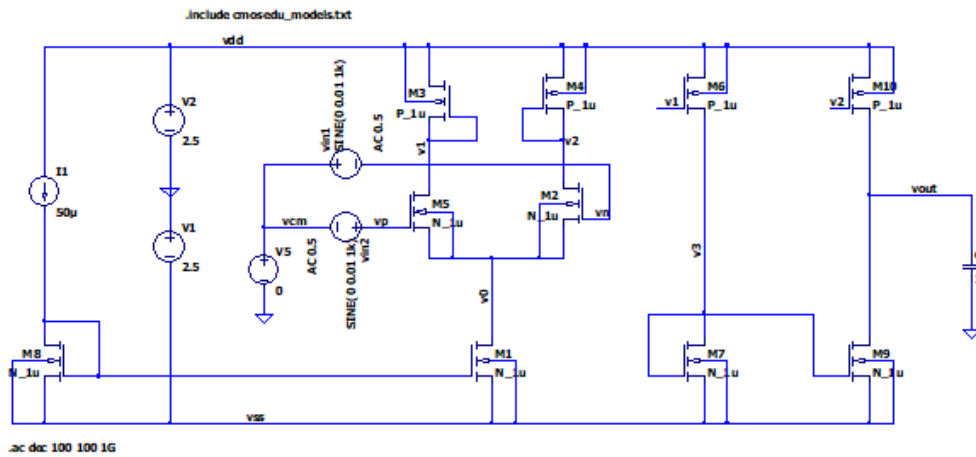


8. Examples

- Simple common-source single-ended amplifier (50 nm):

Name:	m1	m2	md
Model:	n_50n	p_50n	p_50n
Id:	1.54e-04	-1.54e-04	-1.50e-04
Vgs:	5.00e-01	-3.31e-01	-3.31e-01
Vds:	5.20e-01	-4.80e-01	-3.31e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00
Vth:	3.62e-01	-2.48e-01	-2.48e-01
Vdsat:	1.41e-01	-1.14e-01	-1.14e-01
Gm:	1.41e-03	1.97e-03	1.93e-03
Gds:	5.34e-05	2.50e-05	2.93e-05
Gmb:	4.20e-04	6.32e-04	6.17e-04
Cbd:	4.36e-15	8.79e-14	9.10e-14
Cbs:	5.00e-15	1.00e-13	1.00e-13

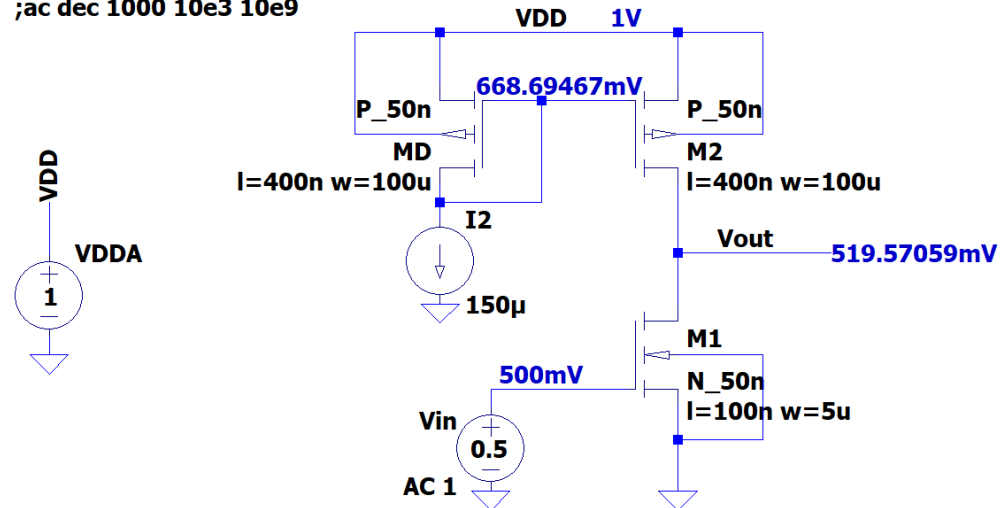
```
.include cmosedu_models.txt
.op dec 1000 10e3 10e9
;ac dec 1000 10e3 10e9
```



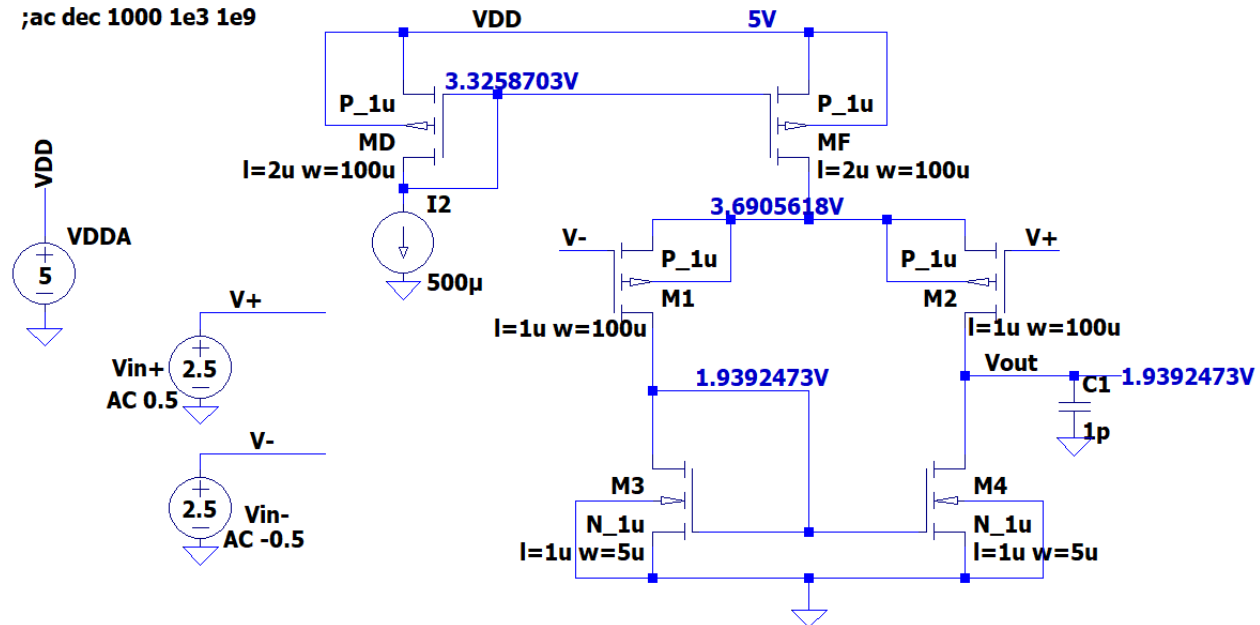8. Examples

- Differential pair (1 μm):


```
.include cmosedu_models.txt
.op dec 1000 1e3 1e9
;ac dec 1000 1e3 1e9
```



Name:	m3	m4	m2	m1	mf
Model:	n_1u	n_1u	p_1u	p_1u	p_1u
Id:	2.48e-04	2.48e-04	-2.48e-04	-2.48e-04	-4.95e-04
Vgs:	1.94e+00	1.94e+00	-1.19e+00	-1.19e+00	-1.67e+00
Vds:	1.94e+00	1.94e+00	-1.75e+00	-1.75e+00	-1.31e+00
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	8.42e-01	8.42e-01	-8.92e-01	-8.92e-01	-9.29e-01
Vdsat:	6.63e-01	6.63e-01	-2.80e-01	-2.80e-01	-6.27e-01
Gm:	3.08e-04	3.08e-04	1.27e-03	1.27e-03	1.09e-03
Gds:	6.79e-05	6.79e-05	3.49e-05	3.49e-05	3.09e-05

8. Examples

- Simple folded-cascode (1 μm):

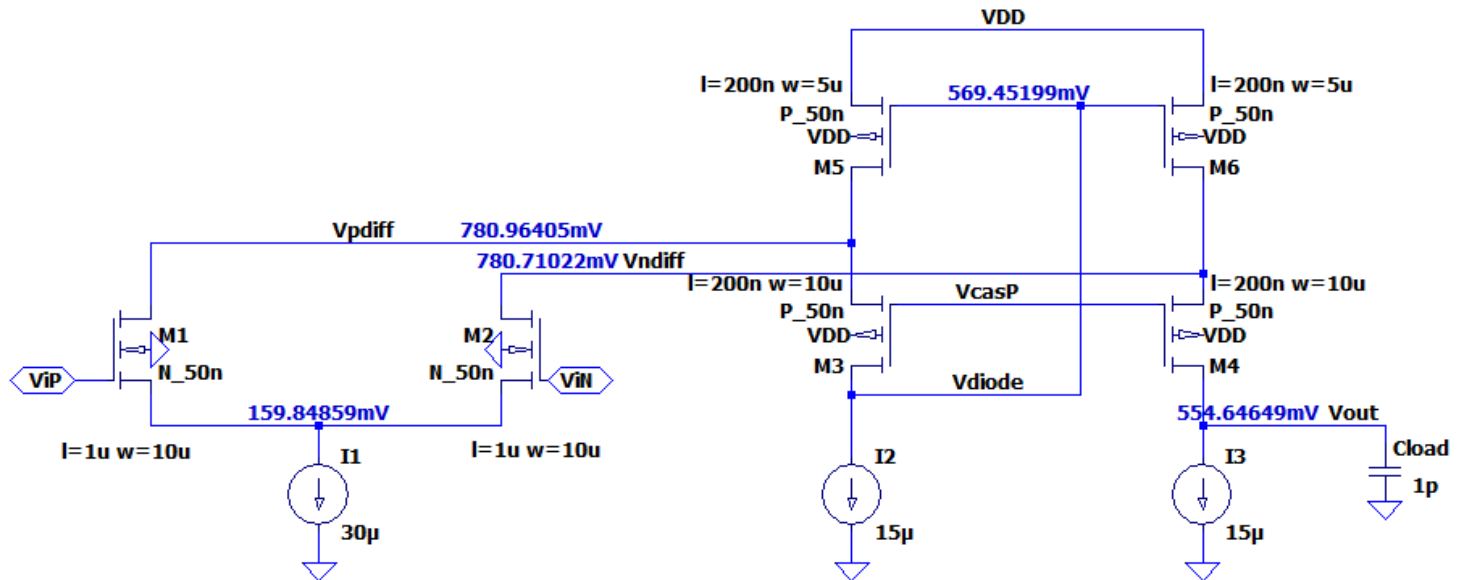

Name:	m3	m4	m5	m6	m2
Model:	p_50n	p_50n	p_50n	p_50n	n_50n
Id:	-1.50e-05	-1.50e-05	-3.00e-05	-3.00e-05	1.50e-05
Vgs:	-3.81e-01	-3.81e-01	-4.31e-01	-4.31e-01	3.40e-01
Vds:	-2.12e-01	-2.26e-01	-2.19e-01	-2.19e-01	6.21e-01
Vbs:	2.19e-01	2.19e-01	0.00e+00	0.00e+00	-1.60e-01
Vth:	-3.32e-01	-3.32e-01	-2.78e-01	-2.78e-01	2.72e-01
Vdsat:	-9.95e-02	-9.93e-02	-1.64e-01	-1.64e-01	9.36e-02
Gm:	2.26e-04	2.26e-04	2.68e-04	2.68e-04	1.98e-04
Gds:	5.73e-06	5.19e-06	1.76e-05	1.75e-05	4.82e-06

Bibliography

- Allen, P. E., & Holberg, D. R. (2002). CMOS analog circuit design. New York: Oxford University Press.
- R. Jacob Baker. 2010. CMOS Circuit Design, Layout, and Simulation (3rd. ed.). Wiley-IEEE Press.

Simulations are performed through software LTSPice, provided courtesy of Analog Devices and authored by Mike Engelhardt.

Spice models of transistors come from <http://cmosedu.com/>, website maintained by R. Jacob Baker.