

Unit 8. Robust SoC design and circuit reliability

System-on-Chip and efficient electronic circuit integration techniques


Carlos III University of Madrid, Spain
Electronics Technology Department

- 1. PVT variations**
- 2. Voltage and frequency control in digital circuits**
- 3. What is the effect on analog/mixed-signal circuits?**

1. PVT variations

- When manufacturing a chip process variations (static) modify the performance of different samples, even in the wafer.
- But not only process variations, voltage supply and temperature can vary (dynamic), and the threshold voltage can vary over time (aging).
- In sub.micron technologies, it is assumed that active devices and resistors can vary ~ 20%, and capacitors ~ 10%, so an **overall 30%** has to be tolerated by the SoC, with minimum performance loss.
- Observation, control, and tuning circuitry is needed... but with an optimized AREA and POWER.

• Prediction of them?

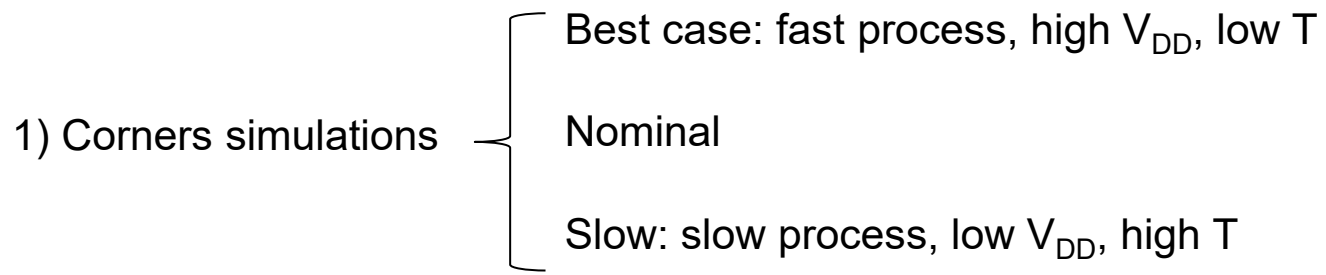

2) MonteCarlo simulations All components are randomly varied
 Statistical analysis

• We can not design for the worst case → too pessimistic, we need:


Digital:

- Error detection and correction circuits**
- Dynamic voltage and frequency scaling**


Analog and Mixed-Signal:

Calibration

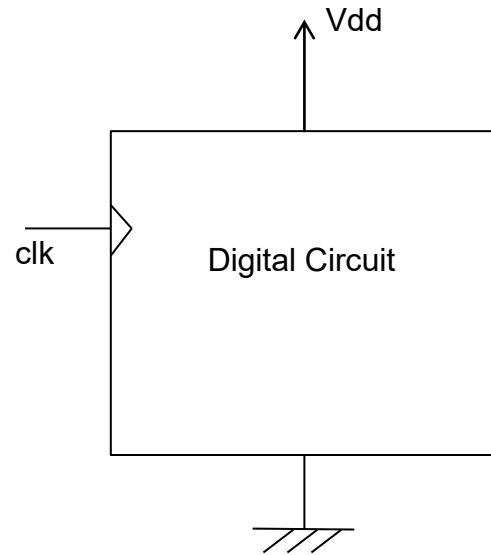2. Voltage and frequency control in digital circuits



 PVT detection: Clock is measured with a TDC(Time-to-Digital Converter), and used as a hint of the deviation from the nominal circuit.



This is too simple!

We need to regulate Clock (PLL, DDS), and V_{DD} (LDO, DC-DC)

Digital Circuits has a set of “Design rules” to make the circuit “technology independent” and therefore, they are scalable and more robust than analog and mixed-signal circuits. Example: Clock tree distribution design rules.

However, performance can be improved if accurate regulation is done for V_{DD} and Clock. In very deep sub-micron technologies, like 28nm, mismatches between masks design (in the lay-out) and implemented circuit are large, and circuit robustness decreases.

Some references: P. Franco, et al. VLSI Test Symp., 1994, M . Nicolaidis, VLSI Test Symp., 1999., D. Ernst, et al., MICRO, 2003.

3. What is the effect on analog/mixed-signal circuits?

We need calibration:

Calibration techniques

- Trimming and/or tuning of currents, voltages, laser trimming, etc.
- Elements selection (resistors, capacitors, current cells), programming coefficients, delays, etc
 - Background calibration: they operate continuously while the circuit is in normal operation
 - Foreground Calibration: they need a calibration phase, at start-up, or periodically (interrupting normal circuit operation)

- Based on statistical properties / test based
- Direct deviation observation / Indirect deviation estimation

3. What is the effect on analog/mixed-signal circuits?

Some specific cases: filters and D/A s

Switched Capacitors Filters:

- Mismatch can be reduced by design (large transistors)

Continuous time Filters:

- Time constant tuning/trimming is needed
- background calibration techniques are common


Switched current D/As:

- Mismatch can be reduced by design (large transistors)
- In Sigma Delta ADCs accuracy of D/As has to be much larger than their resolution → calibration is needed

3. What is the effect on analog/mixed-signal circuits?

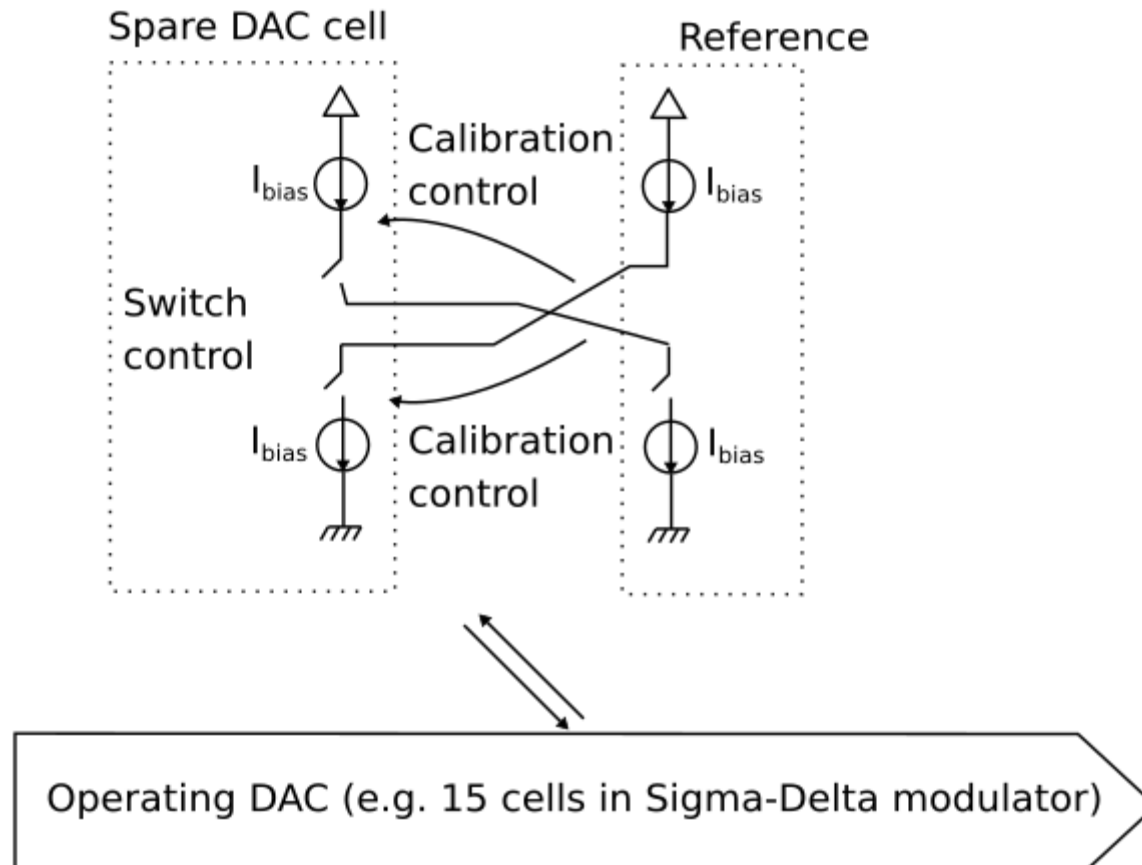
Example of a Switched-current 4-bit D/A (background calib)

- There is a spare cell that replaces another one in the DAC.




3. What is the effect on analog/mixed-signal circuits?

Self-calibration circuit:

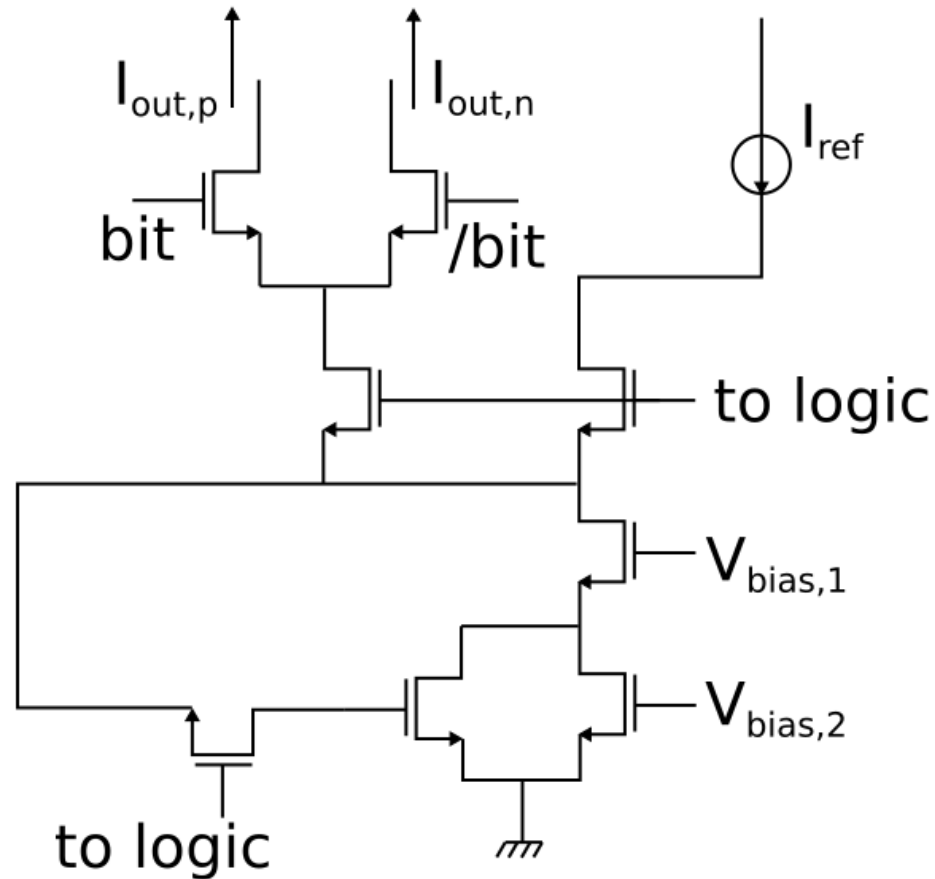

3. What is the effect on analog/mixed-signal circuits?

Dynamic Element Matching:

 

We can change the selection of the cells, to average the error in the time domain

The target is that every cell is used with the same probability

| | | DAC elements | | | |
|------|------|--------------|---|---|---|
| Time | Data | 1 | 2 | 3 | 4 |
| 1 | 1 | █ | | | |
| 2 | 2 | █ | █ | | |
| 3 | 4 | █ | █ | █ | █ |
| 4 | 3 | █ | █ | █ | |
| 5 | 1 | █ | | | |


Selection with thermometer code

| | | DAC elements | | | |
|------|------|--------------|---|---|---|
| Time | Data | 1 | 2 | 3 | 4 |
| 1 | 1 | █ | | | |
| 2 | 2 | | █ | █ | |
| 3 | 4 | █ | █ | █ | █ |
| 4 | 3 | █ | █ | | █ |
| 5 | 1 | | | █ | |

Selection with DEM

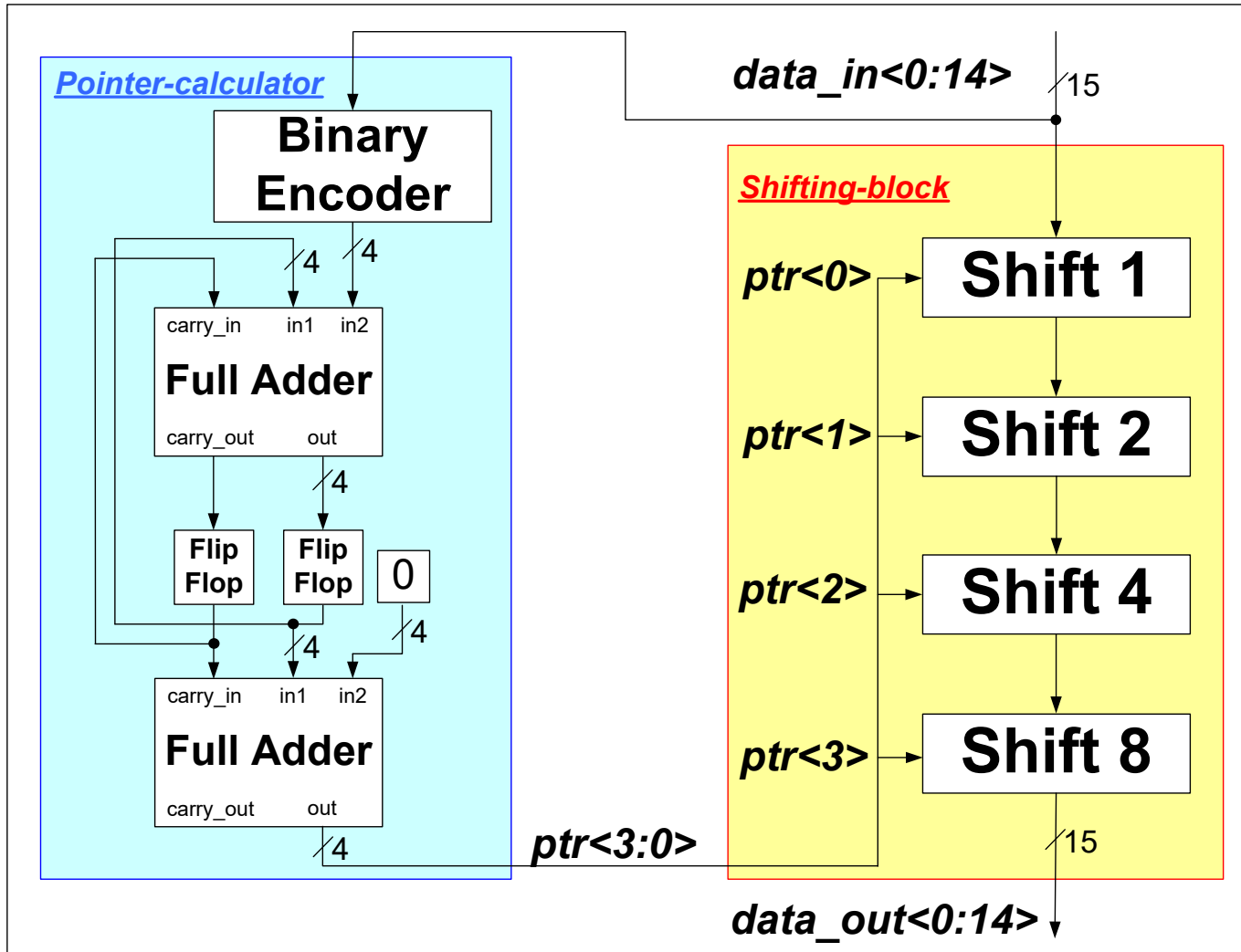3. What is the effect on analog/mixed-signal circuits?


Dynamic Element Matching: implementation example, the barrel shifter



We have a pointer to indicate the last used cell

 3. What is the effect on analog/mixed-signal circuits?

Dynamic Element Matching: simulation of mismatch error shaping



It is zero in average

- Crop, Joseph A., "Methods to improve the reliability and resiliency of near/sub-threshold digital circuits" Ph.D dissertation 2014, Oregon State University; <http://ir.library.oregonstate.edu/xmlui/handle/1957/48935?show=full>
- R. Jevtić et al., "Per-Core DVFS With Switched-Capacitor Converters for Energy Efficiency in Manycore Processors," in IEEE Transactions on Very Large Scale Integration (VLSI) Systems, vol. 23, no. 4, pp. 723-730, April 2015.
- Analog Circuit Design: Smart Data Converters, Filters on Chip, Multimode Transmitters, Ed. Arthur van Roermund, Herman Casier, Michiel Steyaert, Springer, 2010