


Unit 4,5: EXERCISES

Ex1. Design a single-stage amplifier that accomplishes with the next requirements:

V_{DD}	5 V
P (max)	1 mW
A_v	-50 V/V
V_{out(max)}	4 V
V_{out(min)}	1.5 V
SR	10 V/us
C_L	10 pF

Data: $\mu_n C_{ox} = 120 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 40 \mu\text{A}/\text{V}^2$, $\lambda_p = \lambda_n = 0.04 \text{ V}^{-1}$, $|V_{thp}| = |V_{thn}| = 0.7 \text{ V}$, $\lambda_n = 0.04 \text{ V}^{-1}$, $L_{min} = 1 \mu\text{m}$

 Let's try a single-ended cascode configuration like:



- 1) Estimation of I_D due to SR:

$$SR = \frac{I_D}{C_L} \rightarrow I_{D,min} = 100 \mu\text{A}$$

- 2) Omitting power consumption of M4 and M5 → Estimation of $I_{D,max}$ for power requirement:

$$P = V_{DD} I_D \rightarrow I_{D,max} = 200 \mu\text{A}$$

$$100 \mu\text{A} \leq I_D \leq 200 \mu\text{A}$$

- 3) Selection of I_D : intermediate value → $I_D = I_{bias} = 150 \mu\text{A}$
- 4) $V_{out,max}$ requirement:

$$V_{out,max} = V_{DD} - V_{SD3,sat} = V_{DD} - \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} \rightarrow V_{SD3,sat} = 1 \text{ V}$$


$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 V_{SD,sat}^2$$

$$\left(\frac{W}{L}\right)_3 = 7.5 \rightarrow \left(\frac{W}{L}\right)_4 = 7.5$$

 5) $V_{out,min}$ requirement:

$$V_{out,min} = V_{DS1,sat} + V_{DS2,sat}$$

From the small signal model, we may assume that:



$$A_V = \frac{v_{out}}{v_{in}} \approx -g_{m1}r_{o3} \rightarrow \text{Estimation of } (\frac{W}{L})_1$$

$\left(\frac{W}{L}\right)_1 \approx 2 \rightarrow \text{highly dependent of channel modulation effect.}$

$$V_{DS1,sat} = \sqrt{\frac{I_D}{\frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} = 1.11 V$$

$$V_{DS2,sat} = 0.4 V$$

$$\left(\frac{W}{L}\right)_3 = 15.6$$

6) $\left(\frac{W}{L}\right)_5$ estimation:


$$V_{DS2,sat} = V_{GS2} - V_{th,n} \rightarrow V_{D2} = V_{G2} - V_{th,n}$$

$$V_{G2} = \sqrt{\frac{I_D}{\frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{DS1,sat} + V_{th,n} = 2.31 V$$

$$V_{G2} = V_{G5}$$

$$\left(\frac{W}{L}\right)_5 \approx 1$$

Ex2. Given the following amplifier:

 

Provide a proper size for the each of the devices such as the following requirements are accomplished:

V _{DD}	2.5 V
P (max)	1 mW
A _v	100 V/V
SR	10 V/us
C _L	5 pF
BW	100 kHz
ICMR	Between -1.5 V and 2 V

Data: $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\lambda_p = 0.05 \text{ V}^{-1}$, $\lambda_n = 0.04 \text{ V}^{-1}$, $|V_{thp}| = |V_{thn}| = 0.7 \text{ V}$, $\lambda_n = 0.04 \text{ V}^{-1}$, $L_{min} = 1 \mu\text{m}$

1) Estimation of I_D due to SR:

$$SR = \frac{I_D}{C_L} \rightarrow I_{D,min} = 50 \mu\text{A}$$

2) Estimation of $I_{D,max}$ for power requirement:

$$P = 2V_{DD}I_D \rightarrow I_{D,max} = 200 \mu\text{A}$$

3) BW requirement \rightarrow when SR defines BW $\rightarrow BW = \frac{1}{2\pi R_{out}C_L} \geq 100 \text{ kHz}$

$$R_{out} = r_{o4} || r_{o2} = \frac{1}{(\lambda_p + \lambda_n)I_D} \leq 318 \text{ k}\Omega \rightarrow I_D \geq 35 \mu\text{A} \rightarrow I_{bias} \geq 2I_D \\ = 70 \mu\text{A}$$

$$70 \mu\text{A} \leq I_{bias} \leq 200 \mu\text{A}$$

Design choice: $I_{bias} = 100 \mu\text{A}$

4) ICMR, max requirement:

Two paths to establish the requirement:

$$V_{ICMR,max} = V_{DD} - V_{SG3} - V_{SD,sat1} + V_{GS1} \rightarrow V_{ICMR,max} = V_{DD} - V_{SG3} + V_{THN}$$

$$V_{ICMR,max} = V_{DD} - V_{SD,sat4} + V_{THN}$$

$$V_{SG3} > V_{SD4,sat}$$

$$V_{ICMR,max} = V_{DD} - V_{SG3} + V_{THN} = 2\text{ V} \rightarrow V_{SG3} = 1.2\text{ V} \rightarrow \left(\frac{W}{L}\right)_3 = 8$$

$$\text{Current mirror} \rightarrow \left(\frac{W}{L}\right)_4 = 8$$

5) ICMR, min requirement:


$$V_{ICMR,min} = V_{GS1} + V_{DS5,sat} - V_{DD}$$

M5 is the device needed to implement a simple current source.

6) Gain requirement:

$$\begin{aligned} |A_V| &= \frac{v_{out}}{v_{in}} \approx g_{m1} R_{out} \\ R_{out} &= 222\text{ k}\Omega \\ g_{m1} &= \sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{bias}} = 450\text{ }\mu\text{A/V} \\ \left(\frac{W}{L}\right)_1 &= \left(\frac{W}{L}\right)_2 = 18.4 \end{aligned}$$

Ex3. Given the following amplifier:

 


Data: $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\lambda_p = 0.05 \text{ V}^{-1}$, $\lambda_n = 0.04 \text{ V}^{-1}$, $|V_{thp}| = |V_{thn}| = 0.7 \text{ V}$, $L_{min} = 1 \mu\text{m}$, $(W/L)_1 = 2/1$, $(W/L)_2 = (W/L)_3 = (W/L)_4 = 1/1$.

Find the value of V_{in} such that the current in M1 equals 110 μA . Compute the small-signal gain and the output resistance.

1) Estimation of V_{IN} to $I_{D1} = 110 \mu\text{A}$:

$$V_{IN} = V_{THN} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} = 1.7 \text{ V}.$$


2) Small-signal model:

 

$$A_V = \frac{v_{out}}{v_{in}} \approx -\frac{g_{m1}}{g_{m2}}$$

$$g_{m1} = 220 \mu\frac{A}{V} \quad g_{m2} = 31.6 \mu\frac{A}{V} \rightarrow A_V = -7 \text{ V/V}$$


3) For output resistance:

 

$$R_{out} = \frac{V_x}{i_x} \approx \frac{1}{g_{m2}} = 31.6 \text{ k}\Omega$$

Similar to common-source configuration.

Ex4. Given the following amplifier:

 

Data: $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\lambda_p = 0.05 \text{ V}^{-1}$, $\lambda_n = 0.04 \text{ V}^{-1}$, $|V_{thp}| = |V_{thn}| = 0.7 \text{ V}$, $L_{min} = 1 \mu\text{m}$, $(W/L)_1 = 5/1$, $(W/L)_2 = 1/1$.

Answer the following questions:


a) What is the value of V_{GG} to make I_D equal to $100 \mu\text{A}$?

$$V_{GG} = V_{THN} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} = 2.61 \text{ V}$$

b) What is the DC value of V_{in} ?

$$V_{in} = V_{DD} - V_{THP} - \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1}} = 3.03 \text{ V}$$

c) Small-signal gain?

 


$$A_V = \frac{v_{out}}{v_{in}} \approx -\frac{g_{m1}}{1/r_{o1} + 1/r_{o2}} = -17.56 \text{ V/V}$$

d) What is the BW if $C_{GD1}=C_{GD2}=5 \text{ fF}$, $C_{BD1}=C_{BD2}=30 \text{ fF}$ and $C_L=500 \text{ fF}$?

Mainly due to C_L :

$$\text{BW} = \frac{1/r_{o1} + 1/r_{o2}}{2\pi C_L} = 5.72 \text{ MHz}$$

Ex5. Given the following circuits:

 

Assume that the bias current is the same for all the cases.

Looking at the circuits:

- Circuit 1:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-g_{m1}}{g_{m2}+1/r_{o1}+1/r_{o2}} \quad R_{out} = \frac{v_x}{i_x} \approx \frac{1}{g_{m2}+1/r_{o1}+1/r_{o2}}$$

- Circuit 2:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-g_{m2}}{g_{m1}+1/r_{o1}+1/r_{o2}} \quad R_{out} = \frac{v_x}{i_x} \approx \frac{1}{g_{m1}+1/r_{o1}+1/r_{o2}}$$

- Circuit 3:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-g_{m1}}{g_{m2}+1/r_{o1}+1/r_{o2}} \quad R_{out} = \frac{v_x}{i_x} \approx \frac{1}{g_{m2}+1/r_{o1}+1/r_{o2}}$$

- Circuit 4:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-g_{m2}}{g_{m1}+1/r_{o1}+1/r_{o2}} \quad R_{out} = \frac{v_x}{i_x} \approx \frac{1}{g_{m1}+1/r_{o1}+1/r_{o2}}$$

- Circuit 5:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-g_{m1}}{1/r_{o1}+1/r_{o2}} \quad R_{out} = \frac{v_x}{i_x} \approx \frac{1}{1/r_{o1}+1/r_{o2}}$$

- Circuit 6:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-g_{m2}}{1/r_{o1}+1/r_{o2}} \quad R_{out} = \frac{v_x}{i_x} \approx \frac{1}{1/r_{o1}+1/r_{o2}}$$

For the same configuration, the one implemented with NMOS devices will have higher gain due to the higher mobility of negative charges.

- a) In which one we may expect the highest small-signal gain?

Circuit 5.

- b) In which one we may expect the lowest small-signal gain?

Circuit 4.


- c) In which one we may expect the highest output resistance?

Circuit 5 and circuit 6 (similar value).

 - d) In which one we may expect the lowest output resistance?

Circuit 1 and circuit 4 (similar value).

Ex6. The following circuit is called folded-current-mirror differential amplifier and is a low-power solution for amplification tasks. Assume that all the devices are of $W/L = 100\mu\text{m}/1\mu\text{m}$.



Data: $\mu_n C_{ox} = 120 \mu\text{A/V}^2$, $\mu_p C_{ox} = 40 \mu\text{A/V}^2$, $\lambda_p = 0.05 \text{ V}^{-1}$, $\lambda_n = 0.04 \text{ V}^{-1}$, $|V_{thp}| = |V_{thn}| = 0.8 \text{ V}$, $V_{DD} = 1.5 \text{ V}$.

a) Compute ICMR.

$$V_{ICMR,max} = V_{DD} - V_{SD6,sat} + V_{THN}$$

$$V_{SD6,sat} = \sqrt{\frac{2I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)_6}} = 0.71 \text{ V}$$

$$V_{ICMR,max} = 1.593 \text{ V}$$

$$V_{ICMR,min} = V_{GS1} - V_{SD5,sat}$$


$$V_{SD5,sat} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5}} = 0.41 \text{ V}$$

$$V_{GS1} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{THN} = 1.08 \text{ V}$$

$$V_{ICMR,min} = 1.49 \text{ V}$$

$$ICMR = 1.593 - 1.49 = 0.103 \text{ V}$$

 b) Compute the differential small-signal gain.



$$R_{out} \approx \frac{1}{1/r_{o4} + 1/r_{o2} + 1/r_{o7}}$$

Defining $v_{in} = v_1 - v_2$:

$$A_v = \frac{i_{out} R_{out}}{v_{in}} = g_{m1} R_{out} = 37.7 \text{ V/V} \rightarrow \text{very optimist value!}$$


c) If $C_L = 10 \text{ pF}$, what is the BW of the circuit considering only C_L ?

$$\text{BW} = \frac{1}{2\pi R_{out} C_L} = 144 \text{ kHz}$$

Ex7. Design an opamp with Miller compensation:

V_{DD}	2.5 V
P (max)	2 mW
 A_v 	5000 V/V
SR	10 V/us
C_L	10 pF
GBW	5 MHz
ICMR	Between -1 V and 2 V
Output range	Between -2 V and 2 V
Phase margin	60°

Data: $\mu_n C_{ox} = 120 \text{ } \mu\text{A/V}^2$, $\mu_p C_{ox} = 40 \text{ } \mu\text{A/V}^2$, $\lambda_p=0.02 \text{ V}^{-1}$, $\lambda_n=0.02 \text{ V}^{-1}$, $|V_{thp}|=0.9 \text{ V}$, $|V_{thn}|=0.8 \text{ V}$, $V_{DD} = 1.5 \text{ V}$, $L_{min} = 1 \text{ } \mu\text{m}$.

 

1) For $M_f = 60^\circ \rightarrow C_c > 0.22C_L$

$$C_c > 2.2 \text{ pF} \rightarrow C_c = 3 \text{ pF}$$

2) Two-stage opamps $\rightarrow SR$ usually limited by the first stage:

$$SR = \frac{I_{D5}}{C_c} \rightarrow I_{D5} = 30 \text{ } \mu\text{A}$$

3) ICMR,max requirement:

$$\begin{aligned} V_{ICMR,max} &= V_{DD} - V_{SG3} + V_{THN} \rightarrow V_{SG3} = 1.3 \text{ V} \\ \left(\frac{W}{L}\right)_3 &= \frac{2I_{D3}}{\mu_p C_{ox}(V_{SG3} - |V_{THP}|)^2} \approx 5 \\ \left(\frac{W}{L}\right)_3 &= \left(\frac{W}{L}\right)_4 = 5 \end{aligned}$$

4) GBW requirement:

$$GBW = \frac{g_{m1}}{C_c} \rightarrow g_{m1} = 94.24 \frac{\mu\text{A}}{\text{V}}$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 3$$

5) ICMR,min requirement:

$$V_{GS1} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{THN} = 1.08 V$$

$$V_{DS5,sat} = V_{ICMR,min} - V_{GS1} + V_{DD} = 0.42 V$$

$$\left(\frac{W}{L}\right)_5 = \frac{2I_{D3}}{\mu_n C_{ox} (V_{DS5,sat})^2} = 3$$

6) Gm6:

$$2.2GBW = \frac{g_{m6}}{C_L} \rightarrow g_{m6} = 691 \frac{\mu A}{V}$$

$$g_{m6} > 10g_{m2} \rightarrow g_{m6} = 942.4 \frac{\mu A}{V}$$

$$g_{m6} = 942.4 \frac{\mu A}{V}$$

7) Output voltage requirement:

$$V_{out,max} = V_{DD} - V_{DS6,sat} \rightarrow V_{DS6,sat} = 0.5 V$$

$$\left(\frac{W}{L}\right)_6 = \frac{g_{m6}}{\mu_p C_{ox} V_{DS6,sat}} = 35$$

$$I_{D6} = 175 \mu A \rightarrow I_{D7} = 175 \mu A$$

$$V_{GS5} = \sqrt{\frac{2I_{D5}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5}} + V_{THN} = 1.21 V \rightarrow V_{GS5} = V_{GS7} = 1.21 V$$

$$\left(\frac{W}{L}\right)_7 = \frac{2I_{D7}}{\mu_n C_{ox} (V_{GS7} - |V_{THN}|)^2} \approx 18$$

$$V_{out,min} = V_{DS7,sat}$$

$$V_{DS7,sat} = 1.21 - 0.8 = 0.4 V$$

$$V_{out,min} = -2.5 + 0.4 = -2.1 V < 2 V$$

$$V_{out,min} \rightarrow \text{accomplished}$$

8) Small-signal gain requirement:

$$A_V = \frac{v_{out}}{v_{in}} \approx \frac{-2g_{m1}g_{m6}}{I_{D5}(\lambda_2 + \lambda_4)I_{D7}(\lambda_7 + \lambda_6)} = 21145.66 \frac{V}{V} > 5000 \frac{V}{V}$$

9) Power consumption requirement:

$$P_{diss} = 2I_{D5}V_{DD} + 2I_{D7}V_{DD} = 1.025 \text{ mW} < 2 \text{ mW}$$

10) What about other poles and zeros?

Current mirror pole $\rightarrow f_p \approx \frac{g_{m3}}{2\pi 2C_{GS3}} = \frac{-\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_3 I_{D3}}}{2\pi 2^2/3 W_3 L_3 C_{ox}} = 1.83 \text{ GHz} \rightarrow \text{too high.}$

$$C_{ox} = 2.47 \frac{fF}{\mu m^2}, L_3 = 1 \mu m, W_3 = 5 \mu m$$

Zero $\rightarrow f_z \approx \frac{g_{m6}}{2\pi C_C} = 50 \text{ MHz} > 10.5 \text{ MHz}$


Once we have designed the sizes, we must refine the solution through behavioral simulations \rightarrow

Device	W/L, before simulation	W/L, after simulation
1	3	10 with L = 2um
2	3	10 with L = 2um
3	5	5 with L = 3um
4	5	5 with L = 3um
5	3	3 with L = 2um
6	35	90
7	18	30 with L = 2um

We can compensate the right-half-plane zero with a resistance:

$$R_Z = \frac{C_C + C_L}{C_C} \frac{1}{g_{m6}} = 4600 \Omega \rightarrow \text{MF} = 96^\circ$$

 Ex8. Design a folded-cascode opamp with the following requirements:



Data: $\mu_n C_{ox} = 120 \mu\text{A/V}^2$, $\mu_p C_{ox} = 40 \mu\text{A/V}^2$, $\lambda_p=0.02 \text{ V}^{-1}$, $\lambda_n=0.02 \text{ V}^{-1}$, $|V_{thp}|=0.9 \text{ V}$, $|V_{thn}|=0.8 \text{ V}$, $V_{DD} = 1.5 \text{ V}$, $L_{min} = 1 \mu\text{m}$.

V_{DD}	2.5 V
P (max)	5 mW
A_v	3000 V/V
SR	10 V/us
C_L	10 pF
GBW	10 MHz
ICMR	Between 1.5 V and 2 V
Output range	Between 0.5 V and 2 V

1) SR requirement:

$$SR = \frac{I_{D3}}{C_L} \rightarrow I_{D3} = 100 \mu\text{A}$$

$I_{D5} = I_{D4} \rightarrow$ typically, $I_{D5} = I_{D4}$ between 1.25-2 I_{D3}

$$I_{D5} = I_{D4} = 200 \mu\text{A}$$

For the sake of simplicity, we assume M4=M5=M6=M7 and M8=M9=M10=M11:

2) Output voltage requirement:

$$V_{out,max} = V_{DD} - V_{SD5,sat} - V_{SD7,sat} \rightarrow V_{DS5sat} = V_{DS7sat} = 0.25 \text{ V}$$

$$\left(\frac{W}{L}\right)_5 = \frac{2I_{D5}}{\mu_p C_{ox} (V_{SD5,sat})^2} = 160 = \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_7$$

$$V_{out,min} = V_{DS9,sat} + V_{DS11,sat} \rightarrow V_{DS9sat} = V_{DS11sat} = 0.25 \text{ V}$$

$$I_{D9} = I_{D5} - I_{D2}$$

$$\left(\frac{W}{L}\right)_9 = \frac{2I_{D9}}{\mu_n C_{ox} (V_{DS9,sat})^2} = 40 = \left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_{10} = \left(\frac{W}{L}\right)_{11}$$

3) GBW requirement:

$$GBW = \frac{g_{m1}}{2\pi C_L} \rightarrow g_{m1} = 628.32 \frac{\mu A}{V}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{g_{m1}^2}{2\mu_n C_{ox} I_{D1}} = 33$$

4) ICMR requirement:

$$V_{ICMR,min} = V_{GS1} + V_{DS,sat3}$$

$$V_{GS1} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{THN} = 0.96 \text{ V} \rightarrow V_{DS3,sat} = 0.54 \text{ V}$$

$$\left(\frac{W}{L}\right)_3 = \frac{2I_{D3}}{\mu_n C_{ox} (V_{DS3,sat})^2} = 6$$

$$V_{ICMR,max} = V_{DD} - V_{SD,sat4} + V_{THN} \rightarrow V_{SD,sat4} = 1.3 \text{ V}$$

$$\left(\frac{W}{L}\right)_4 = \frac{2I_{D4}}{\mu_p C_{ox} (V_{SD4,sat})^2} = 6 \ll 160 \rightarrow \left(\frac{W}{L}\right)_4 = 160$$

5) Gain requirement: maximum gain achievable:

$$A_V = \frac{v_{out}}{v_{in}} \approx g_{m1} R_{out}$$

$$R_{out} = [g_{m7} r_{o7} (r_{o5} || r_{o2})] || [g_{m9} r_{o9} r_{o11}]$$

$$A_V = 100000 \frac{V}{V} \gg 3000 \frac{V}{V}$$

6) Power consumption requirement:

$$P_{diss} = 1.25 \text{ mW} < 2 \text{ mW}$$

7) V_{bias} ?

$$V_{bias1} = V_{DD} - V_{SG4} = 1.35 \text{ V}$$

$$V_{bias2} = V_{DD} - V_{SD4,sat} - V_{SG6} = 1.14 \text{ V}$$

$$V_{bias3} = V_{GS8} - V_{DS10,sat} = 1.03 \text{ V}$$

$$V_{bias4} = \sqrt{\frac{2I_{D3}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_3}} + V_{THN} = 1.33 \text{ V}$$

Exercises 3, 4, 5, and 6 adapted from Allen, P. E., & Holberg, D. R. (2011). CMOS analog circuit design. New York: Oxford University Press, USA.