

SIMULATION SESSION 1: AMPLIFIERS

**SYSTEM-ON-CHIP AND EFFICIENT ELECTRONIC CIRCUIT
INTEGRATION TECHNIQUES**

DEPARTAMENTO DE TECNOLOGÍA ELECTRÓNICA

Campus de Leganés

Avenida del Universidad 30

28911 Leganés

INTRODUCTION

In this session we will learn the design process of a Miller opamp. A Miller opamp is a two stage opamp whose frequency response can be approximated by:

$$A_v \left(\frac{s}{z_1} - 1 \right) \frac{1}{\left(\frac{s}{p_1} + 1 \right) \left(\frac{s}{p_2} + 1 \right)}$$

where

$$z_1 = \frac{gm_2}{C_c} \cdot GBW$$

$$p_1 = \frac{A_v}{gm_2}$$

$$p_2 = \frac{gm_2}{C_2}$$

$$GBW = \frac{gm_1}{C_c}$$

gm_1 is the transconductance of the first amplifier (part of diff pair)

gm_2 is the transconductance of the second amplifier.

C_c is the compensation capacitor?

C_2 is the load of the Miller amplifier?

One typical rule of thumb to compute the compensation is to start from a certain transconductance ratio, as $gm_2/gm_1 = 10$. This will push the RHP zero to high frequencies (avoiding lead compensation) and will ensure a small compensation capacitor. If we use that ratio, we can use Matlab to predict typical phase margins (PM):

$z_1 = 10GBW$	
$gm_2 = 10gm_1$	
PM=45°	$p_2 = 1.2GBW$
PM=60°	$p_2 = 2.2GBW$

The design process will consist in the following steps:


- Compute compensation
- Use specs to compute bias and sizes.
- Simulate the circuit and refine sizes.

1. Opamp Specs

Design a Miller opamp for capacitive (or large resistive) loads with the following specifications:

- DC gain > 5000 V/V
- Gain-Bandwidth product > 5MHz, Phase Margin > 60°
- Slew Rate > 10V/μs
- Output swing ±2V, Supply ±2.5V, Input Common Mode Range (ICMR) -1V to 2V.
- Power consumption < 2mW

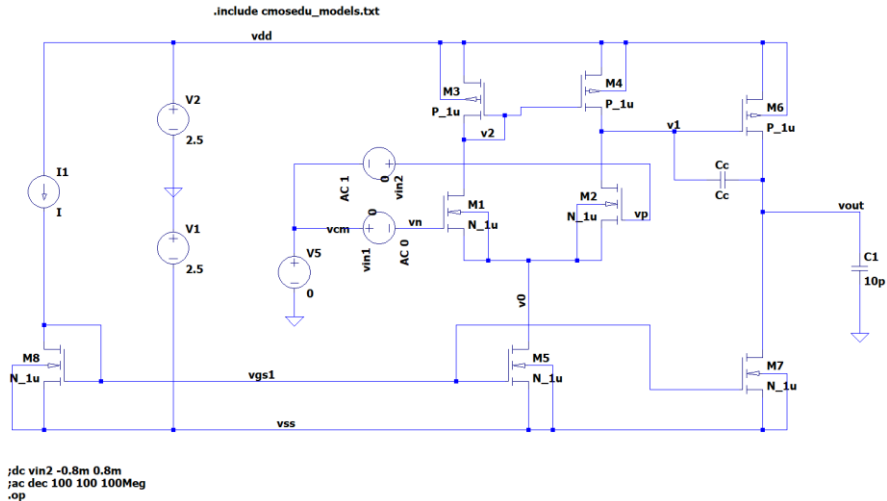Use the following schematic and 1μm technology (available in cmosedu_models.txt)



$$K_P = 40 \mu\text{A/V}, \lambda_P = 0.02\text{V}^{-1}, V_{thp} = -0.9 \text{ V}$$

$$K_N = 120 \mu\text{A/V}, \lambda_n = 0.02\text{V}^{-1}, V_{thn} = 0.8 \text{ V}$$

Useful equations in saturation:

$$I_D = \frac{KN}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{th})^2 = \frac{KN}{2} \left(\frac{W}{L}\right) V_{DSsat}^2$$

$$g_m = \sqrt{2KN \left(\frac{W}{L}\right) I_D} = \frac{2I_D}{V_{GS} - V_{th}}$$

$$r_{ds} = \frac{1}{\lambda I_D}$$

2. Compensation

Compute C_c assuming $z_1 = 10GBW$

3. Reference current

Compute the reference for M1, assuming the amplifier is slewing when maximum current is integrated in C_c .

4. Bias and Sizes

Compute the size of M3, assuming maximum input common mode

Compute g_{m1}

Compute the size of M5, assuming minimum input common mode

Compute g_{m6} for the maximum output swing

Compute the size of M6 and M7

5. **Simulate the amplifier**


Simulate the Bias, check all the transistors in .log

6. **Check all the specs, and prove them by simulation**

Bias is simulated with .op command

Offset and DC gain is simulated with a DC sweep

 AC response can be simulated using the following feedback and the 10pF load



Transient response can be simulated using voltage follower with the 10pF load

