

# **SIMULATION SESSION 2: DELTA-SIGMA ADC**

**SYSTEM-ON-CHIP AND EFFICIENT ELECTRONIC CIRCUIT  
INTEGRATION TECHNIQUES**

**DEPARTAMENTO DE TECNOLOGÍA ELECTRÓNICA**

**Campus de Leganés**

Avenida del Universidad 30

28911 Leganés

## INTRODUCTION

In this session we will use the designed amplifier in a practical circuit. The chosen practical circuit is a First-Order Delta-Sigma Modulator ADC. It is an oversampled noise-shaped modulator composed of an active integrator, a latched comparator and single bit DAC (see Fig. 1).

It is recommended the reading of “The Delta-Sigma Modulator, Razavi, A circuit for all seasons (SSC Magazine)”.

 


Fig. 1 First Order Delta-Sigma Modulator and Decimation Filter Example

## 1. Simulations

 


Fig. 3. Circuit to be simulated (“Ideal\_DSM.asc”)

Vout is the single-bit output of the Oversampled Delta-Sigma Circuit, D[2:0] is the decimated output (Decimation by 8), and DAC\_out is a reconstructed analog version of D[2:0].

All the blocks are ideal.

1. Simulate circuit in Fig. 3.
  - a. Plot Vin and DACOut. How many levels and bits are in the digital output?
  - b. Plot Vint. What is the Slew-Rate of signal Vint?
2. Replace the ideal opamp by the Miller opamp “opamp\_poor\_SR.asc” designed in a similar way as in previous session. Simulate circuit of figure 1 again with the real opamp.
  - a. Plot Vin and DACOut. How many levels and bits are in the digital output? Are they the same as in the ideal opamp simulation?
  - b. Plot Vint. What is the Slew-Rate of signal Vint? Is there any difference with the ideal opamp simulation? Comment the results.
3. Try now “opampmiller\_v50nm\_SR\_100MHz.asc”
4. Introduce offset in the comparator and analyze the influence.